

# Electricity and Magnetism


- Reminder
  - RLC Circuits
  - Resonance
- Today
  - LC circuits / Oscillations
  - Displacement current
  - Maxwell's equations

# AC Circuit

- AC circuit
  - $I(t) = I_0 \sin(\omega t)$
  - $V(t) = V_0 \sin(\omega t + \phi)$
  - Relationship between  $V$  and  $I$  can be characterized by two quantities
    - Impedance  $Z = V_0/I_0$
    - Phase-shift  $\phi$

$\phi/\omega$


# AC Circuit

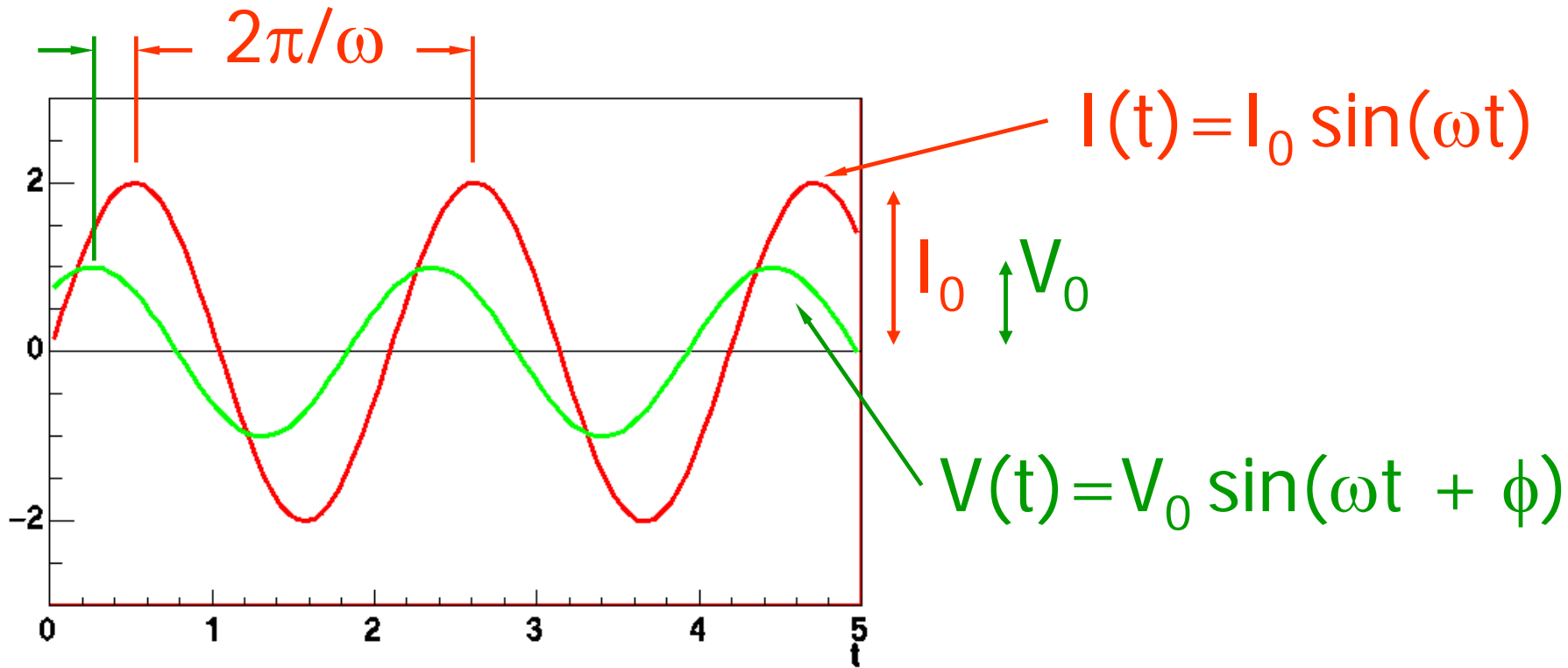

Impedance  $Z = V_0/I_0$

Phase-shift  $\phi$

# First: Look at the components

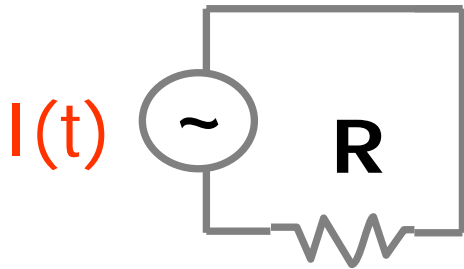


$$V = I R$$

$$Z = R$$

$$\phi = 0$$

$V$  and  $I$  in phase

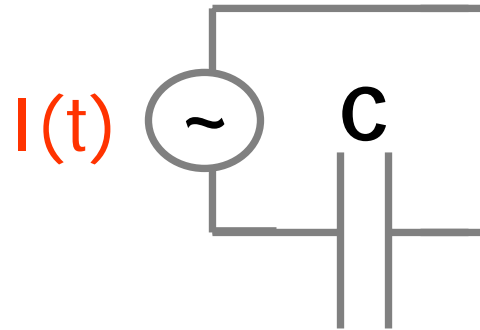


$$V = Q/C = 1/C \int I dt$$

$$Z = 1/(\omega C)$$

$$\phi = -\pi/2$$

$V$  lags  $I$  by  $90^\circ$

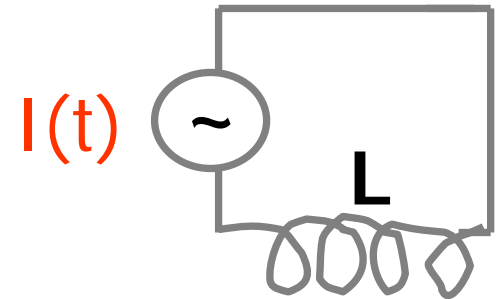


$$V = L dI/dt$$

$$Z = \omega L$$

$$\phi = \pi/2$$

$I$  lags  $V$  by  $90^\circ$

# RLC Circuit

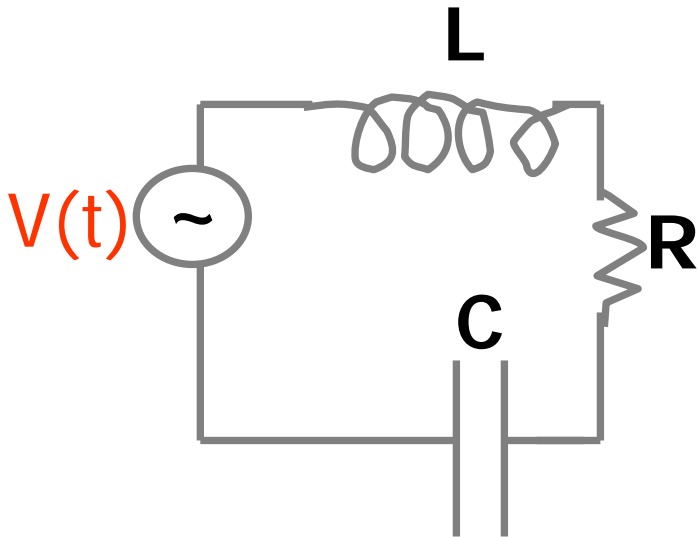

$$V - L \frac{dI}{dt} - IR - Q/C = 0$$

$$L \frac{d^2Q}{dt^2} = -1/C Q - R \frac{dQ}{dt} + V$$



'Inertia'


'Spring'



'Drag'


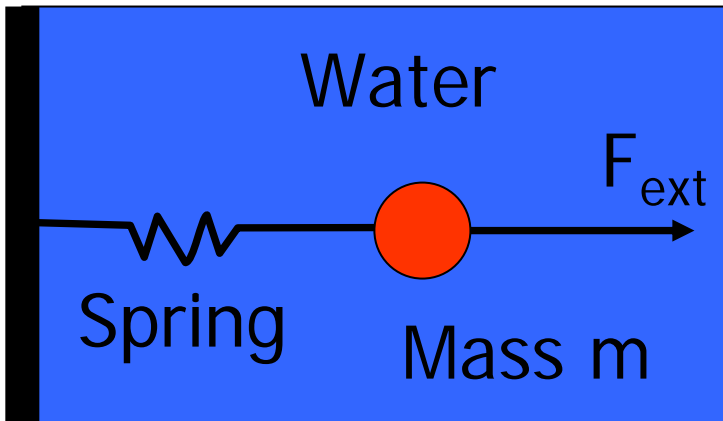
$$m \frac{d^2x}{dt^2} = -k x - f \frac{dx}{dt} + F_{\text{ext}}$$



# RLC Circuit

$$V_0 \sin(\omega t) = I_0 \{ [\omega L - 1/(\omega C)] \cos(\omega t - \phi) + R \sin(\omega t - \phi) \}$$

Solution (requires two tricks):


$$I_0 = V_0 / ([\omega L - 1/(\omega C)]^2 + R^2)^{1/2} = V_0 / Z$$

$$\tan(\phi) = [\omega L - 1/(\omega C)] / R$$


-> For  $\omega L = 1/(\omega C)$ ,  $Z$  is minimal and  $\phi = 0$

i.e.  $\omega_0 = 1/(LC)^{1/2}$  Resonance Frequency

# In-Class Demo (on scope)

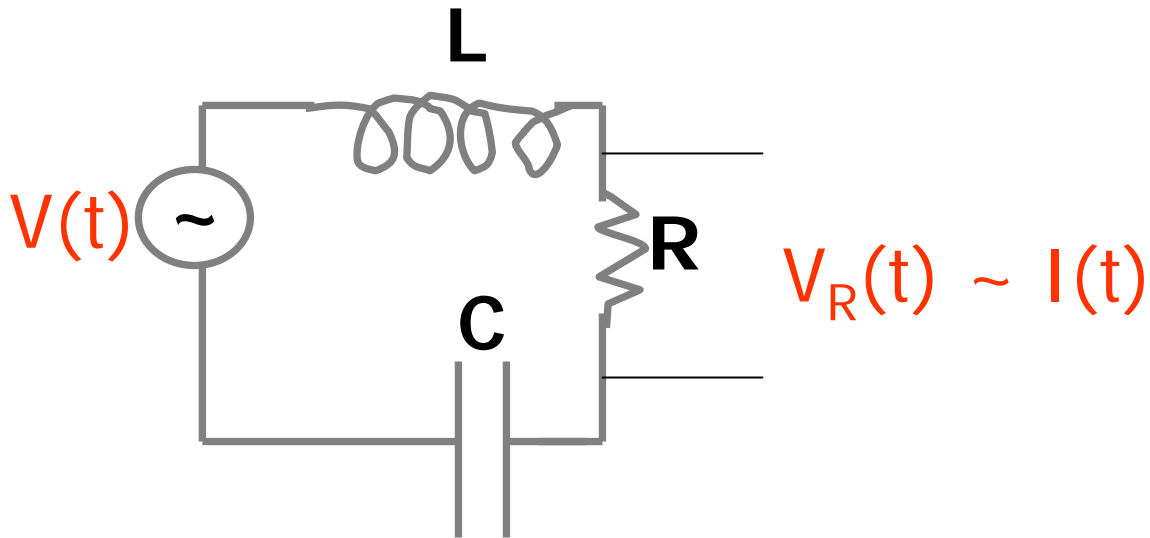

# Resonance

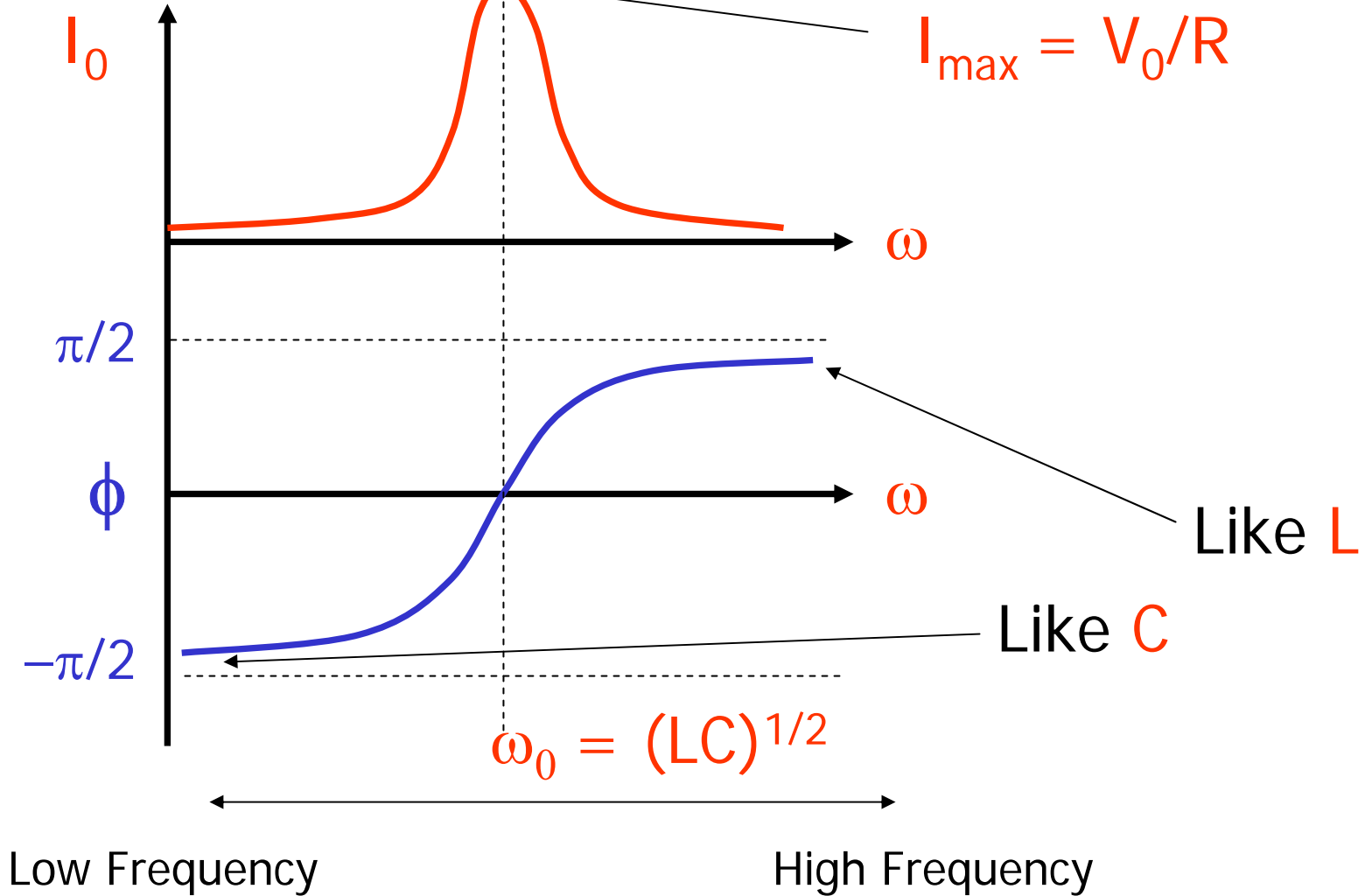


# Resonance

- Practical importance
  - ‘Tuning’ a radio or TV means adjusting the resonance frequency of a circuit to match the frequency of the carrier signal

# LC Circuit

- What happens if we open switch?

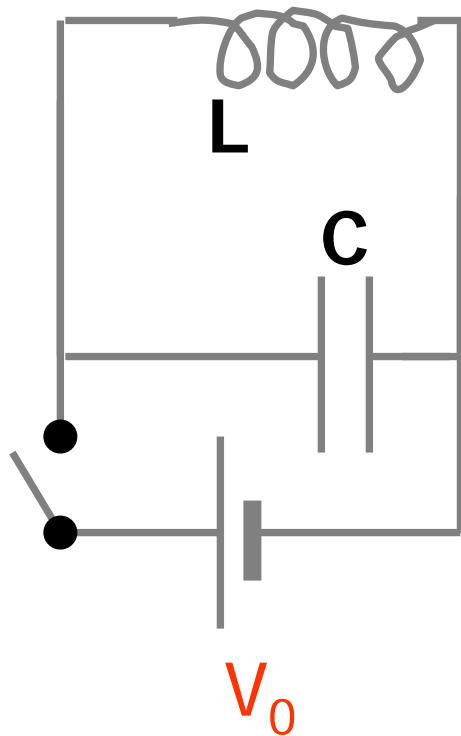

$$-L \frac{dI}{dt} - Q/C = 0$$


$$L \frac{d^2Q}{dt^2} + Q/C = 0$$



$$\frac{d^2x}{dt^2} + \omega_0^2 x = 0$$


Harmonic Oscillator!

# LC Circuit

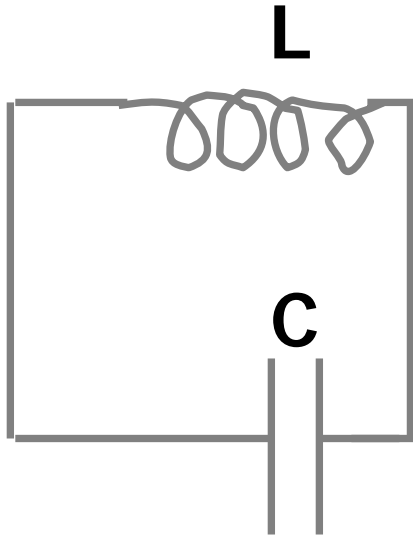

$$d^2Q/dt^2 + 1/(LC) Q = 0$$


$$\omega_0^2 = 1/(LC)$$

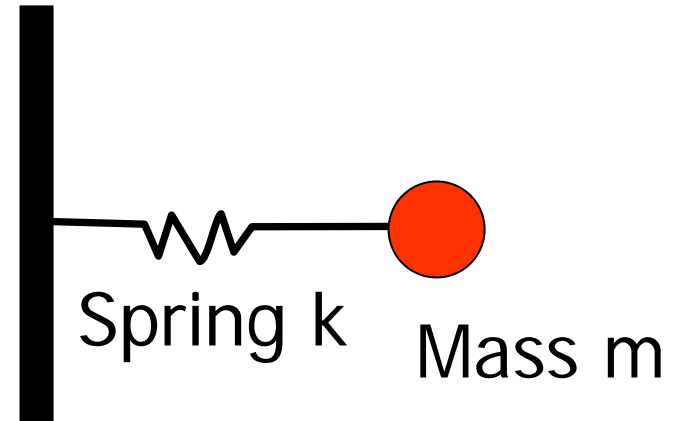

$$d^2x/dt^2 + k/m x = 0$$

$$\omega_0^2 = k/m$$

# LC Circuit

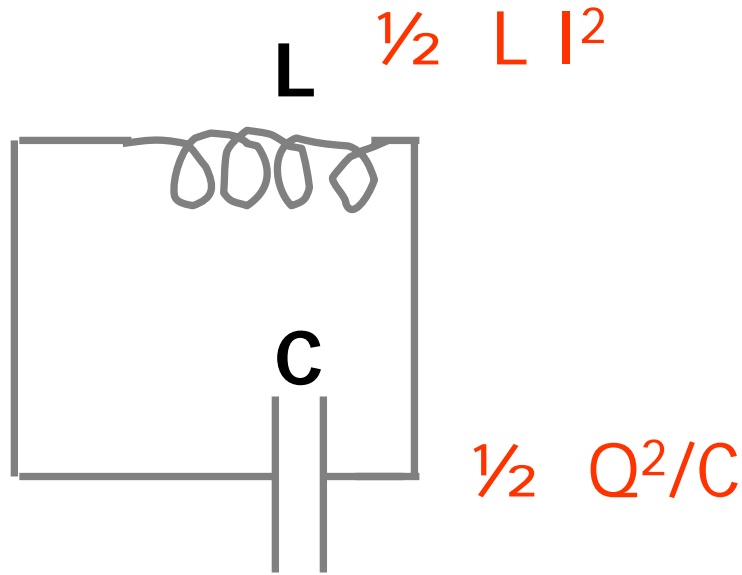


Energy in E-Field



Oscillation

Energy in B-Field

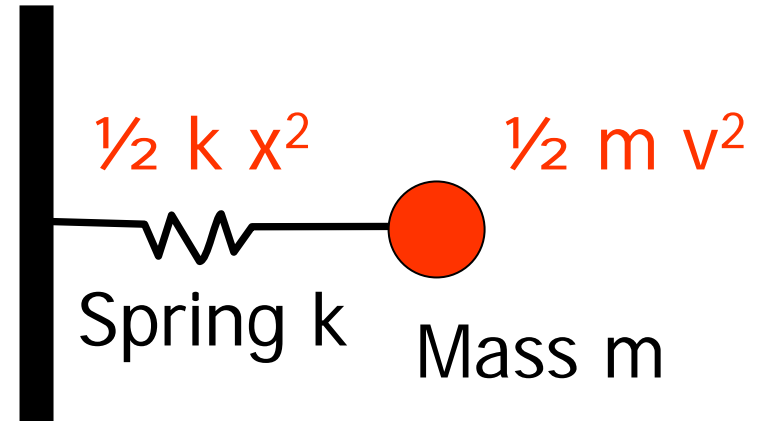

Potential Energy



Oscillation

Kinetic Energy

# Electromagnetic Oscillations

- In an LC circuit, we see oscillations:

Energy in E-Field



Energy in B-Field

- Q: Can we get oscillations without circuit?
- A: Yes!
  - **Electromagnetic Waves**

# Maxwell's Equations (almost)

$$\oint_{A_{closed}} \vec{E} \cdot d\vec{A} = \frac{Q_{encl}}{\epsilon_0}$$

Charges are the source of  
Electric Flux through close surface

$$\xi = \oint_{L_{closed}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

Changing magnetic field creates  
an electric field

$$\oint_{A_{closed}} \vec{B} \cdot d\vec{A} = 0$$



There are no magnetic monopoles

$$\oint_{L_{closed}} \vec{B} \cdot d\vec{l} = \mu_0 I_{encl}$$

Moving charges create magnetic field

- Connection between electric and magnetic phenomena
- But not symmetric
- -> James Clerk Maxwell (~1860)

# The missing piece

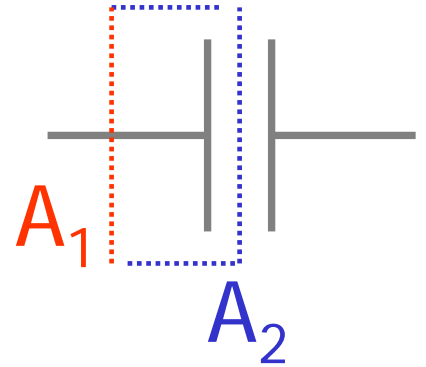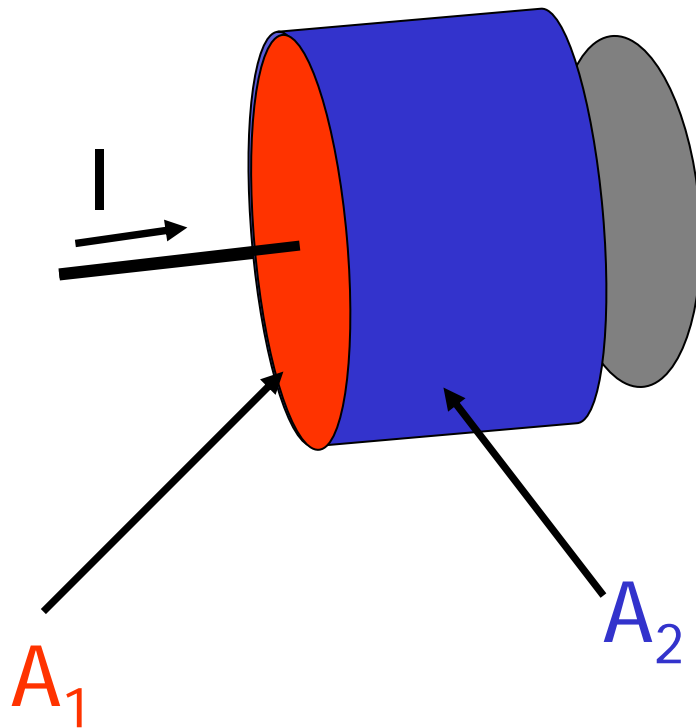


$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 \int_{A_1} \vec{J}_1 d\vec{A}$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 \int_{A_2} \vec{J}_2 d\vec{A} \quad \swarrow = 0!$$
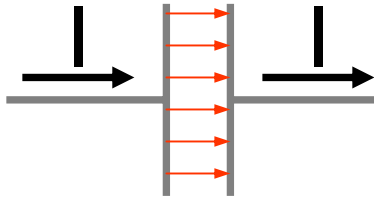
# Displacement Current

- Ampere's Law broken – How can we fix it?



$$Q = C V$$

Displacement Current  $I_D = \epsilon_0 d\Phi_E/dt$

# Maxwell's Equations

$$\oint_{A_{\text{closed}}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$\oint_{L_{\text{closed}}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

$$\oint_{A_{\text{closed}}} \vec{B} \cdot d\vec{A} = 0$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{encl}} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

- Symmetry between E and B
  - although there are no magnetic monopoles
- Basis for radio, TV, electric motors, generators, electric power transmission, electric circuits etc

# Maxwell's Equations

$$\oint_{A_{\text{closed}}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$\oint_{L_{\text{closed}}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

$$\oint_{A_{\text{closed}}} \vec{B} \cdot d\vec{A} = 0$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{encl}} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

1/c<sup>2</sup>

- M.E.'s *predict* electromagnetic waves, moving with speed of light
- Major triumph of science

# Maxwell's Equations

$$\oint_{A_{\text{closed}}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$\oint_{L_{\text{closed}}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

$$\oint_{A_{\text{closed}}} \vec{B} \cdot d\vec{A} = 0$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{encl}} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

1/c<sup>2</sup>

- Symmetry between E and B
  - although there are no magnetic monopoles
- Basis for radio, TV, electric motors, generators, electric power transmission, electric circuits etc