

Small Signal Models of the Bipolar Transistor


6.301 — Spring 2002

Massachusetts Institute of Technology

Michael Perrott

(Courtesy of Michael Perrott. Used with permission.)

General Thevenin Resistance View

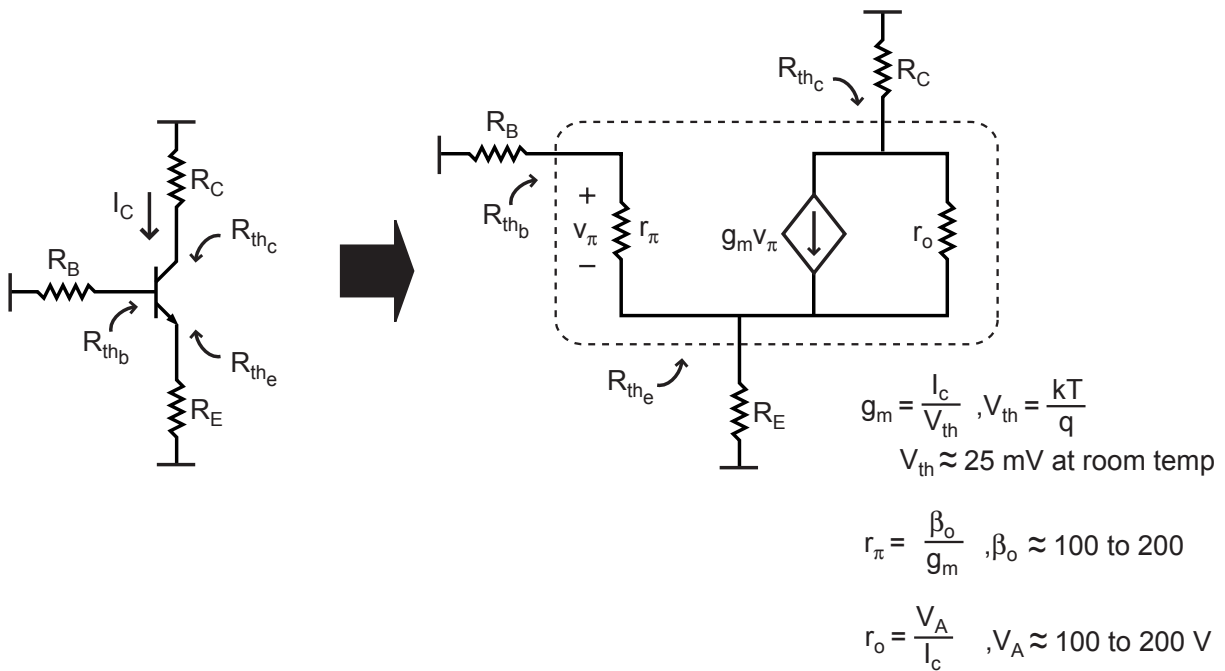

Thevenin resistance at collector:

$$R_{thc} = \frac{(1 + g_m r_o) R_E (r_{\pi} + R_B / (1 + g_m r_o))}{R_E + r_{\pi} + R_B} + r_o$$

$$R_{thc} \approx (1 + g_m (r_{\pi} || R_E)) r_o \quad \text{for } R_B \ll r_{\pi}, R_E$$

Thevenin resistance at base:

$$R_{thb} = r_{\pi} + (\beta_o + 1) R_E \left(\frac{r_o + R_C / (\beta_o + 1)}{r_o + R_C + R_E} \right)$$

$$R_{thb} \approx r_{\pi} + (\beta_o + 1) R_E \quad \text{for } R_C \ll r_o, R_E \ll r_o$$


Thevenin resistance at emitter:

$$R_{the} = \frac{r_{\pi} + R_B}{1 + \beta_o} || \frac{r_o}{1 + R_C / (r_{\pi} + R_B)}$$

$$R_{the} \approx \frac{1}{g_m} + \frac{R_B}{1 + \beta_o} \quad \text{for } \frac{r_o}{1 + R_C / (r_{\pi} + R_B)} \gg \frac{1}{g_m} + \frac{R_B}{1 + \beta_o}$$


Amplifier Configurations

Common Emitter (with degeneration):

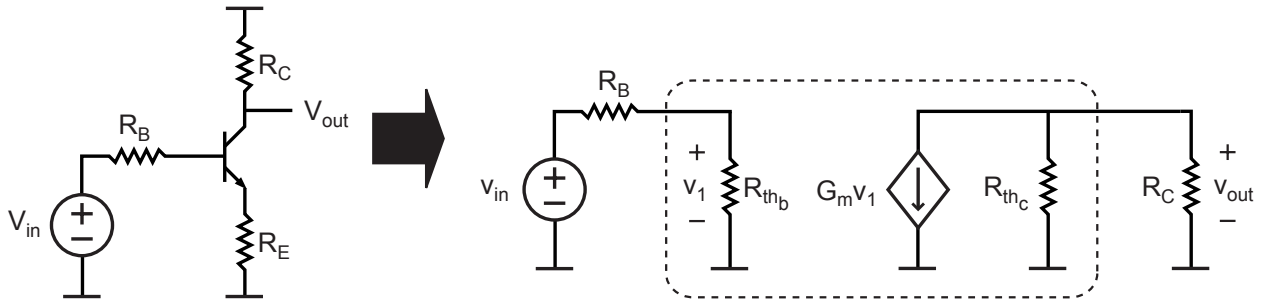


$$G_m = g_m \left(\frac{1 - R_E/(\beta_o r_o)}{1 + g_m R_E (1 + 1/\beta_o + 1/(g_m r_o))} \right) \approx \frac{g_m}{1 + g_m R_E} \quad \text{for } R_E \ll r_o, g_m r_o \gg 1$$

Emitter Follower:

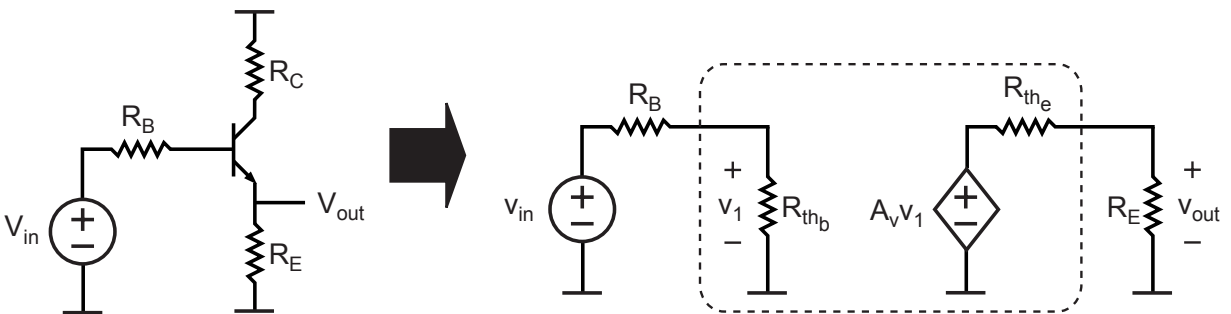

$$A_v = \frac{1}{1 + (1 + R_C)/(r_\pi + \beta_o r_o)} \approx 1$$

Common Base:

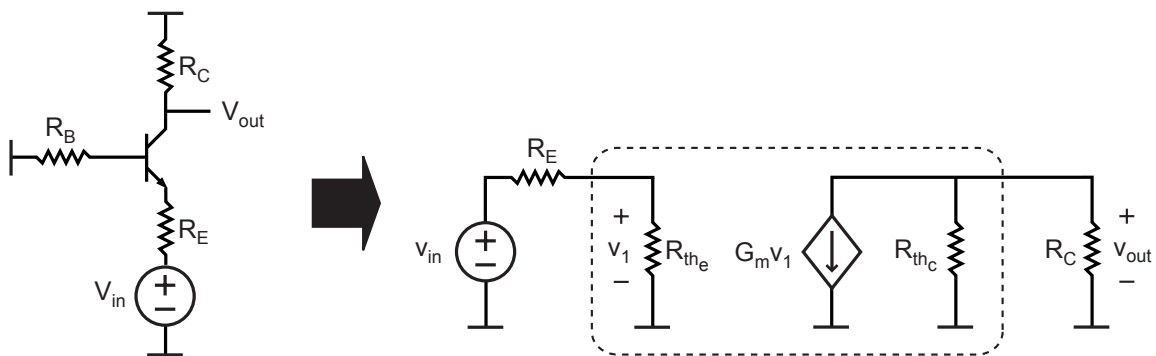

$$G_m = - \left(g_m \left(\frac{r_\pi}{R_B + r_\pi} \right) + \frac{1}{r_o} \right) \approx -g_m \quad \text{for } R_B \ll r_\pi, r_o \gg 1/g_m$$