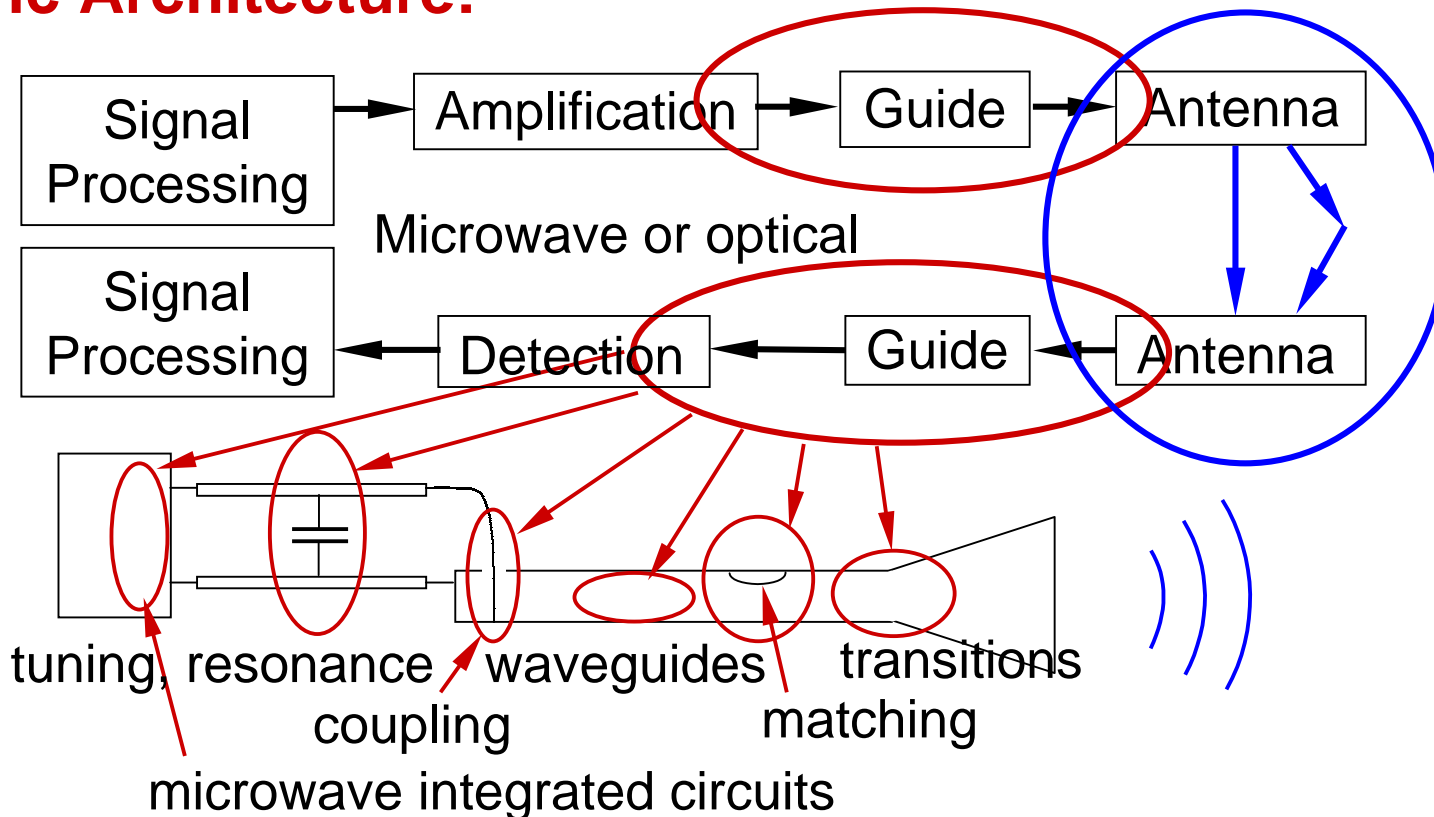


MICROWAVE COMMUNICATIONS AND RADAR

Generic Architecture:



Communications, bi-static radar—separately located systems

Radar, lidar, data recording—co-located systems


Passive sensing—uses receiver side only

Systems fail at the weakest link, therefore understand all parts

MICROWAVE CIRCUITS

Printed Circuits Exhibit R,L,C Behavior:


Equivalent TEM line circuit:

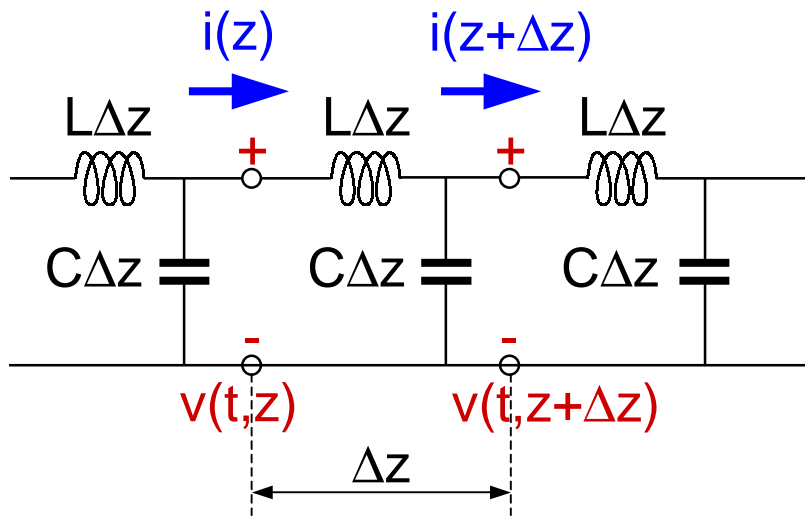

Let $v(z, t) = \text{Re} \{ \underline{V}(z) e^{j\omega t} \}$:

$$\frac{d\underline{V}(z)}{dz} = -j\omega L \underline{I}(z)$$
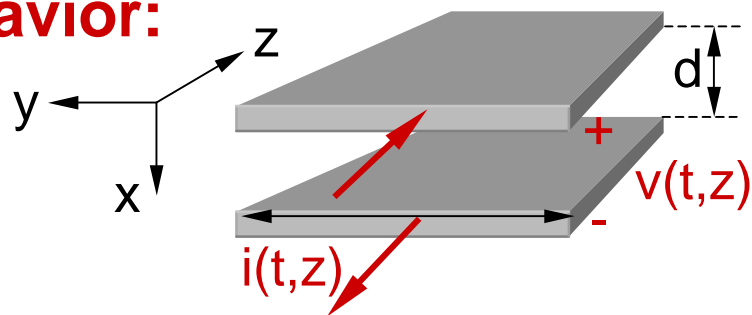
$$\frac{d\underline{I}(z)}{dz} = -j\omega C \underline{V}(z) \Rightarrow$$



“TEM” $\Rightarrow \bar{\mathbf{E}} \cdot \hat{\mathbf{z}} = \bar{\mathbf{H}} \cdot \hat{\mathbf{z}} = 0$

Difference Equations

$$v(z + \Delta z) - v(z) = -L\Delta z \frac{di(z)}{dt}$$

$$i(z + \Delta z) - i(z) = -C \Delta z \frac{dv(z)}{dt}$$

Limit as $\Delta z \rightarrow 0$:

$$\frac{dv}{dz} = -L \frac{di}{dt}$$

$$\frac{di}{dz} = -C \frac{dv}{dt}$$

Wave Equation

$$\frac{d^2 \underline{V}(z)}{dz^2} + \omega^2 LC \underline{V}(z) = 0$$

TEM SINUSOIDAL STEADY STATE EQUATIONS

Wave Equation: $d^2\underline{V}(z)/dz^2 + \omega^2LC\underline{V}(z) = 0$

Voltage Solution: $\underline{V}(z) = \underline{V}_+e^{-jkz} + \underline{V}_-e^{jkz}$

Test solution: $[(-jk)^2\underline{V}_+e^{-jkz} + (jk)^2\underline{V}_-e^{jkz}] + \omega^2LC[\underline{V}_+e^{-jkz} + \underline{V}_-e^{jkz}] = 0$

Passes test iff: $k^2 = \omega^2LC$

Current $\underline{I}(z)$:

Since: $\partial\underline{V}(z)/\partial z = -j\omega L \underline{I}(z)$

Therefore
$$\begin{aligned}\underline{I}(z) &= (1/j\omega L)jk(\underline{V}_+e^{-jkz} - \underline{V}_-e^{jkz}) \\ &= Y_o(\underline{V}_+e^{-jkz} - \underline{V}_-e^{jkz})\end{aligned}$$

[Characteristic admittance $Y_o = k/\omega L = \omega(LC)^{0.5}/\omega L = (C/L)^{0.5} = 1/Z_o$]

Transmission Line Equations:

$$\begin{aligned}\underline{V}(z) &= \underline{V}_+e^{-jkz} + \underline{V}_-e^{jkz} \\ \underline{I}(z) &= Y_o(\underline{V}_+e^{-jkz} - \underline{V}_-e^{jkz})\end{aligned}$$


COMPLEX LINE IMPEDANCE $\underline{Z}(z)$

Impedance:

$$\underline{Z}(z) = \underline{V}(z) / \underline{I}(z) = R(z) + jX(z)$$

Resistance

Reactance

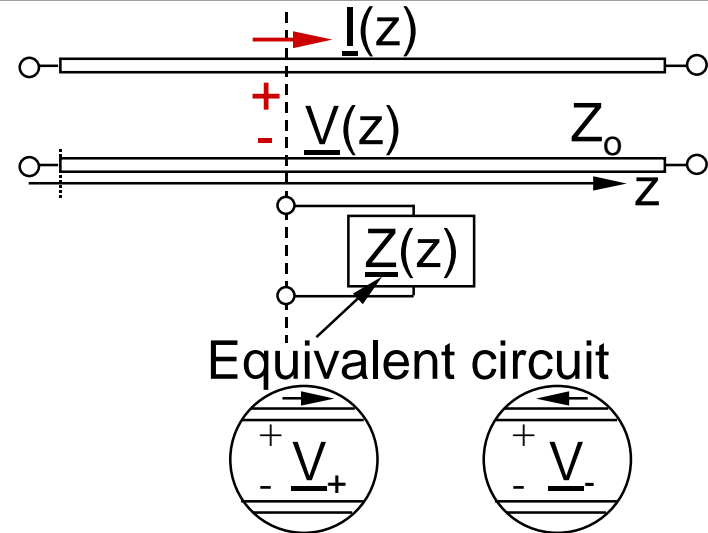

$$\underline{Z}(z) = \underline{V}(z) / \underline{I}(z) = \frac{Z_0 (\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz})}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}} = Z_0 \frac{1 + \underline{\Gamma}(z)}{1 - \underline{\Gamma}(z)}$$

Complex Reflection Coefficient $\underline{\Gamma}(z)$:

$$\underline{\Gamma}(z) = \underline{V}_- e^{+jkz} / \underline{V}_+ e^{-jkz} = \underline{\Gamma}_L e^{2jkz} \quad \text{where } \underline{\Gamma}_L = \underline{\Gamma}(z=0) = \underline{V}_- / \underline{V}_+$$

Examples: $\underline{\Gamma} = 0 \Rightarrow \underline{Z}(z) = Z_0$ $\underline{\Gamma} = +1 \Rightarrow \underline{Z} = \infty$ $\underline{\Gamma} = -1 \Rightarrow \underline{Z} = 0$

GENERAL EXPRESSIONS FOR $Z(z)$

Complex Reflection Coefficient $\Gamma(z)$:

Since
$$\underline{Z}(z)/Z_0 = [1 + \Gamma(z)]/[1 - \Gamma(z)] = \underline{Z}_n(z)$$

Therefore:
$$\Gamma(z) = [\underline{Z}(z) - Z_0]/[\underline{Z}(z) + Z_0] = [\underline{Z}_n(z) - 1]/[\underline{Z}_n(z) + 1]$$

$\underline{Z}(z)$ as a Function of Z_L , Z_0 , k , and z :

Substituting:
$$\Gamma_L(z) = [\underline{Z}_L - Z_0]/[\underline{Z}_L + Z_0]$$

Into:
$$\underline{Z}(z) = \underline{V}(z)/\underline{I}(z) = Z_0 \frac{\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}}$$
$$= Z_0 \left[\frac{(e^{-jkz} + \Gamma_L e^{+jkz})}{(e^{-jkz} - \Gamma_L e^{+jkz})} \right]$$

Yields:
$$\underline{Z}(z) = Z_0 \frac{(\underline{Z}_L + Z_0) e^{-jkz} + (\underline{Z}_L - Z_0) e^{jkz}}{(\underline{Z}_L + Z_0) e^{-jkz} - (\underline{Z}_L - Z_0) e^{jkz}}$$
$$= Z_0 \frac{\underline{Z}_L \cos kz - jZ_0 \sin kz}{-j\underline{Z}_L \sin kz + Z_0 \cos kz}$$


Therefore:
$$\underline{Z}(z) = Z_0 \frac{\underline{Z}_L - jZ_0 \tan kz}{Z_0 - j\underline{Z}_L \tan kz}$$

EXAMPLES OF Z(z) TRANSFORMATIONS

Transformation Equation:

$$\underline{Z}(z) = Z_0 \frac{Z_L - jZ_0 \tan kz}{Z_0 - jZ_L \tan kz}$$

Example—Open Circuit, $Z_L = \infty$:

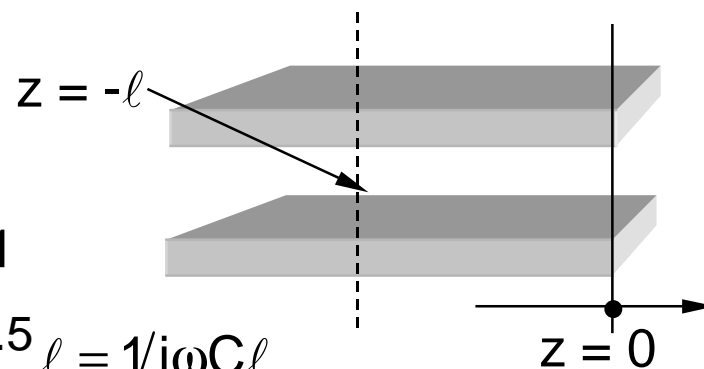


$$\underline{Z}(-l) = -jZ_0 \cot kl = -jZ_0 / kl \text{ for } kl \ll 1$$

$$= -j(L/C)^{0.5} / \omega(LC)^{0.5} l = 1/j\omega \underbrace{C l}_{C_0}$$

C_0 (capacitor)

$$= 0 \text{ when } z = -\lambda/4, -3\lambda/4, \dots$$
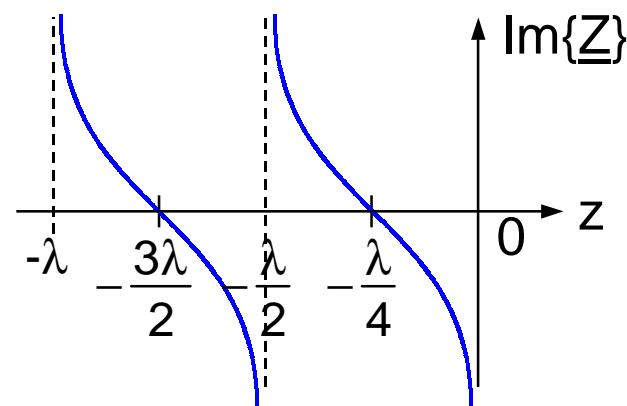
$$= \infty \text{ when } z = 0, -\lambda/2, \dots$$



In general: $-j\infty < \underline{Z}(-l) < +j\infty$


(ANY capacitance or inductance at a SINGLE frequency)

MORE EXAMPLES OF Z(z) TRANSFORMATIONS

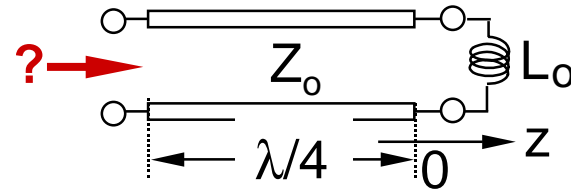Example—Inductive Load, $Z_L = j\omega L_o$ for $z = -\lambda/4$:

Recall:

$$\underline{Z}(z) = Z_o \frac{\underline{Z}_L - jZ_o \tan kz}{Z_o - j\underline{Z}_L \tan kz}$$




Since: $kz = -kl = (2\pi/\lambda)/(\lambda/4) = -\pi/2$, and $\tan(-kl) = -\infty$

Therefore: $\underline{Z}(z) = Z_o^2 / \underline{Z}_L = (L/C)/(j\omega L_o) = 1/(j\omega C L_o/L) = 1/j\omega C_o$

Note: $\underline{Z}(z) = 1/j\omega L_o$ if $l = \lambda/2, \lambda, \dots$ ($\tan - (2\pi/\lambda)\lambda = 0$)

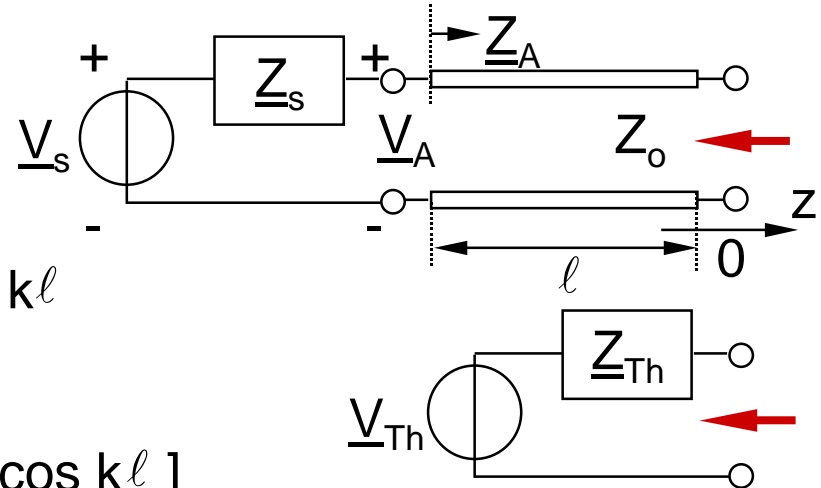Example—Transformation of Source Impedances:

$$\underline{Z}_{Th} = Z_o \frac{\underline{Z}_s + jZ_o \tan kl}{Z_o - j\underline{Z}_s \tan kl}$$




$\underline{V}_A = \underline{V}_s \underline{Z}_A / (\underline{Z}_s + \underline{Z}_A)$ where $\underline{Z}_A = jZ_o \cot kl$

$$= \underline{V}_+ (e^{jk l} + e^{-jk l}) = 2\underline{V}_+ \cos kl$$

Therefore: $\underline{V}_{Th} = 2\underline{V}_+ = \underline{V}_s \underline{Z}_A / [(\underline{Z}_s + \underline{Z}_A) \cos kl]$

ALTERNATE APPROACH TO FINDING $Z(z)$

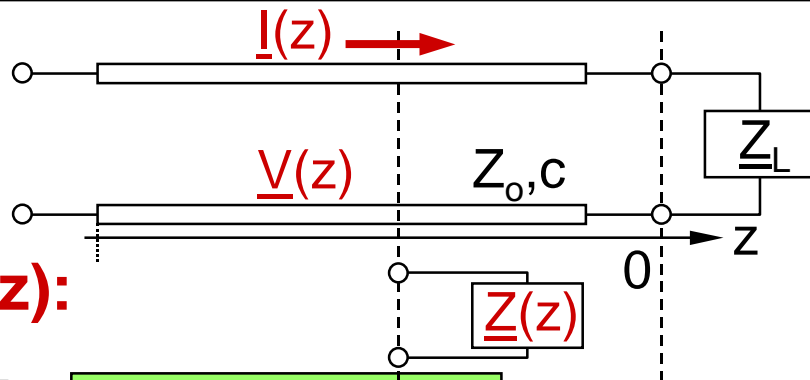

Complex Reflection Coefficient $\Gamma(z)$:

$$1) \quad Z(z) = \underline{V}(z)/\underline{I}(z) = Z_0 \frac{\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)} = \underline{Z}(z)$$

$$2) \quad \Gamma(z) = \underline{V}_- e^{+jkz} / \underline{V}_+ e^{-jkz} = \Gamma_L e^{2jkz} = \Gamma(z) \quad \text{where} \quad \Gamma_L = \Gamma(z=0) = \underline{V}_- / \underline{V}_+$$

$$3) \quad \Gamma_L = [\underline{Z}_L - Z_0] / [\underline{Z}_L + Z_0]$$

Γ -Plane Solution Method:

$$\underline{Z}_L \Leftrightarrow \Gamma_L \Leftrightarrow \Gamma(z) \Leftrightarrow \underline{Z}(z)$$

(3) (2) (1)

Recall: $\underline{Z}_n = \underline{Z}/Z_0$

