

RESONATORS

Impedance [$v(t) = R_e\{\underline{V}e^{j\omega t}\}$]:


$v = RI$	\rightarrow	$\underline{V} = R\underline{I}$	\rightarrow	$\underline{Z} = R$
$v = L di/dt$	\rightarrow	$\underline{V} = j\omega L\underline{I}$	\rightarrow	$\underline{Z} = j\omega L$
$i = C dv/dt$	\rightarrow	$\underline{I} = j\omega C\underline{V}$	\rightarrow	$\underline{Z} = 1/j\omega C$

Series RLC Resonance:

$$\underline{V}(\omega) = \underline{I}(\omega)[R + j\omega L + (j\omega C)^{-1}]$$

$$= \min \text{ if } j\omega L = -1/j\omega C$$

$$\omega_o = (LC)^{-0.5}$$

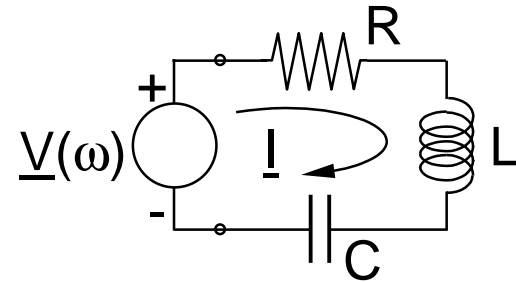


$$Q = \omega_o W_T / P_{\text{diss}} \cong \omega_o / \Delta\omega \cong \omega_o L / R$$

where:

$$W_T = L |I|^2 / 4 + C |V|^2 / 4 = L |I|^2 / 2 [J] \text{ at } \omega_o$$

$$P_{\text{diss}} = |I|^2 R / 2 [W]$$

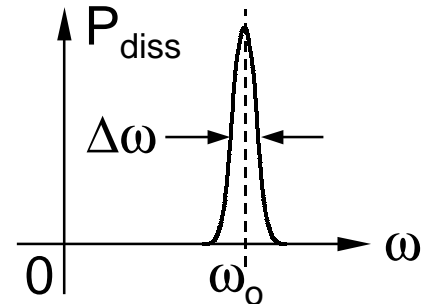


Parallel RLC Resonance:

$$\underline{I}(\omega) = \underline{V}(\omega)[G + j\omega C + (j\omega L)^{-1}]$$

$$= \min \text{ if } j\omega C = -1/j\omega L, \text{ i.e. if}$$

$$Q = \omega_o C / G$$

$$\omega_o = (LC)^{-0.5}$$

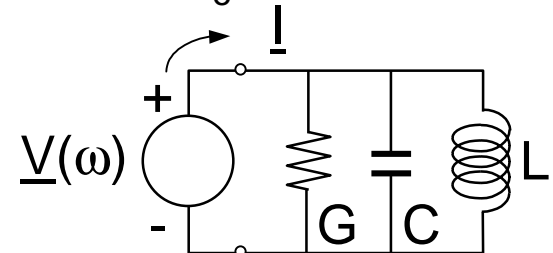


COUPLING TO RESONATORS

RLC Resonators:

To maximize power dissipated in R:

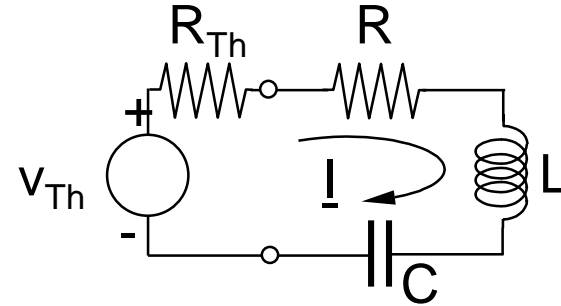Set $R = R_{Th}$ at $\omega = \omega_o = (LC)^{-0.5}$



Proof that $R = R_{Th}$ for Maximum Power Dissipation:

$$P_{diss} = i^2 R = [v_{Th} / (R + R_{Th})]^2 R$$


Set $\partial P_{diss} / \partial R = 0$ to maximize P_{diss}

$$\partial P_{diss} / \partial R = v_{Th}^2 [(R + R_{Th})^{-2} - 2R(R + R_{Th})^{-3}] = 0, \text{ so}$$

$$R + R_{Th} = 2R \Rightarrow \boxed{R = R_{Th} \text{ for maximum } P_{diss}}$$

“matched load”

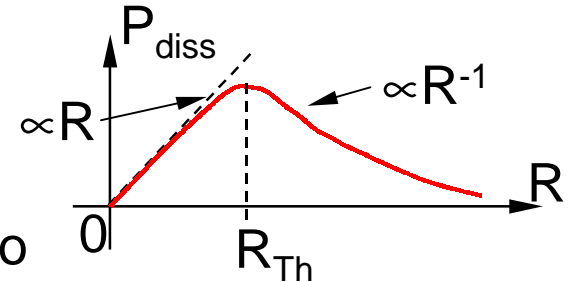Conversely, resonator loses power fastest if $R_L = R (v_{Th} = 0)$




Resonator Internal Q_I , External Q_E , and Loaded Q_L :

$$Q = \omega_o W_T P_{diss} \Rightarrow Q_I = \omega_o L / P_{dissI}, \quad Q_E = \omega_o L / P_{dissE}, \quad Q_L = \omega_o L / P_{dissL}$$

Therefore: $Q_L^{-1} = Q_I^{-1} + Q_E^{-1}$ and $\boxed{Q_I = Q_E \text{ for maximum } P_{diss}}$

TEM RESONATORS

Voltages and Currents:

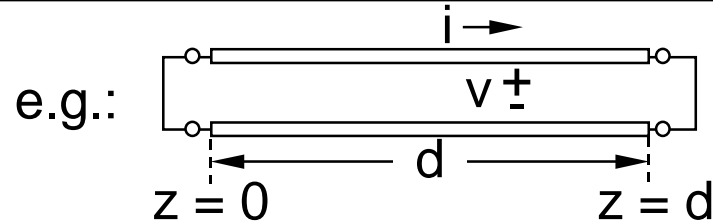

$$v(t,z) = V_+ \cos(\omega t - kz) + V_- \cos(\omega t + kz) = 0 \text{ at } z = 0, d$$

$$\text{Boundary conditions} \Rightarrow V_- = -V_+$$

$$v(t,z) = V_+ [\cos(\omega t - kz) - \cos(\omega t + kz)] = 2V_+ \sin \omega t \sin kz$$

$$\text{where } \cos \alpha - \cos \beta = -2 \sin[(\alpha + \beta)/2] \sin[(\alpha - \beta)/2]$$



$$i(t,z) = (V_+/Z_0) [\cos(\omega t - kz) + \cos(\omega t + kz)] = 2(V_+/Z_0) \cos \omega t \cos kz$$

Resonant Frequencies ω_n :

$$k_n d = \omega_n d/c = n\pi, \quad n = 0, 1, 2, \dots$$

$$\omega_n = n\pi c/d$$

$$n\lambda_n/2 = d$$

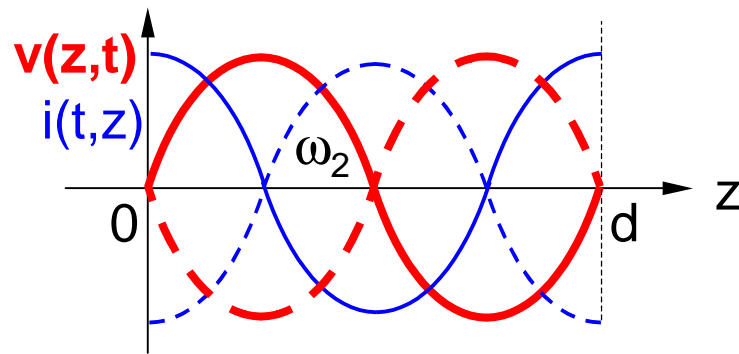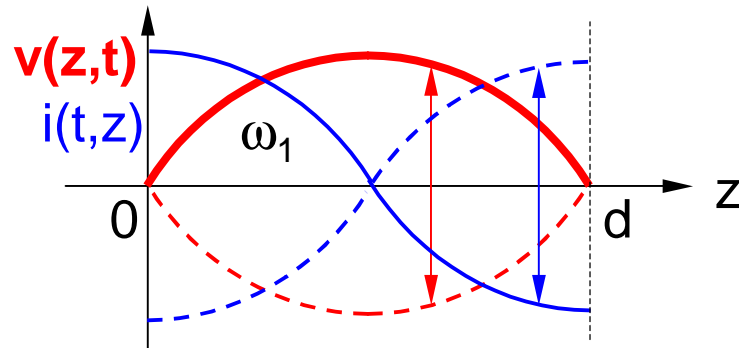

DC Resonance ($\omega = 0$):

Current flows in loop,
Voltages are zero

$$w_e = 0, w_m \neq 0 \text{ [J]}$$

MORE TEM RESONANCES

Open-Circuit Resonator:

$$n\lambda_n/2 = d, \quad n = 0, 1, 2, \dots \Rightarrow \lambda_n = 2d/n$$


$$\omega_n = n\pi c/d$$

$$\lambda_0 = \infty \quad \rightarrow \quad \omega_0 = 0$$

$$\lambda_1 = 2d \quad \rightarrow \quad \omega_1 = \pi c/d$$

$$\lambda_2 = d \quad \rightarrow \quad \omega_2 = 2\pi c/d$$
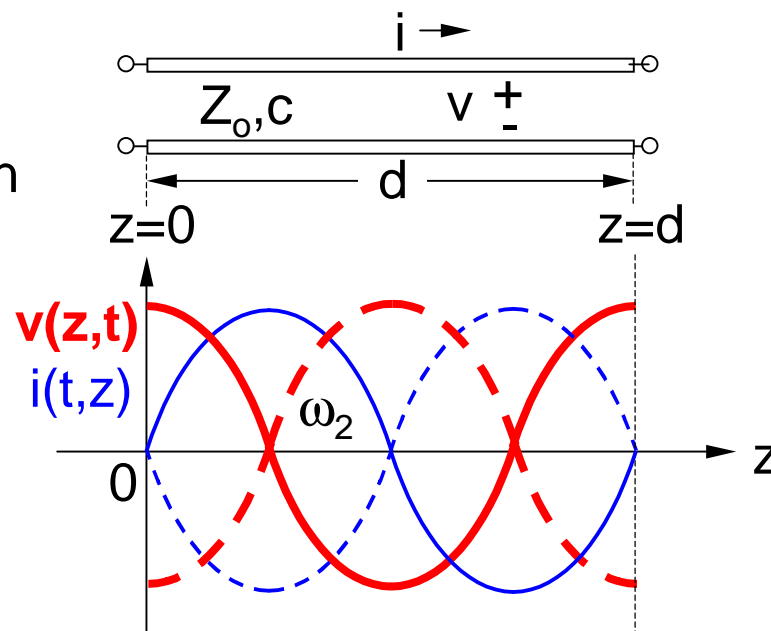
$$\lambda_3 = 3d/2 \quad \rightarrow \quad \omega_3 = 3\pi c/d$$



Quarter-Wave Resonator:

$$n\lambda_n/2 - \lambda_n/4 = d = (n - 0.5)\lambda_n/2$$


$$\Rightarrow \lambda_n = 2d/(n - 0.5)$$

$$\lambda_1 = 4d$$

$$\lambda_2 = 4d/3$$

$$\lambda_3 = 4d/5$$

$$\lambda_4 = 4d/7$$

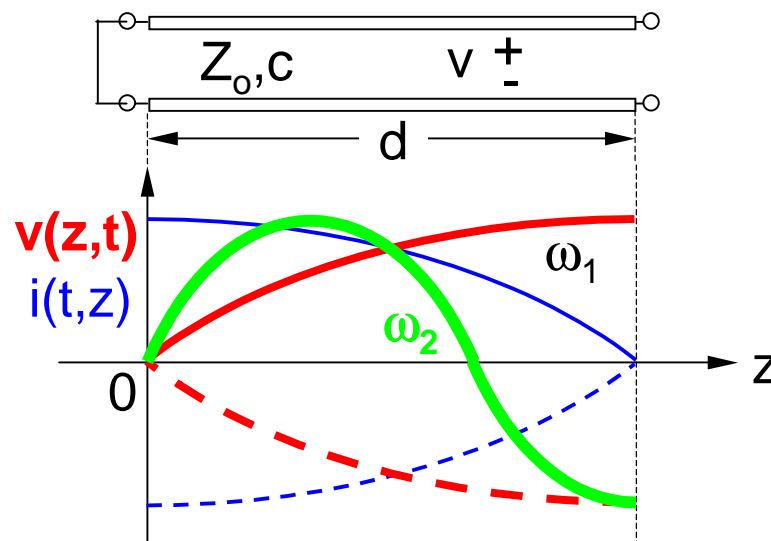

ENERGY IN TEM RESONATORS


Electric Energy Density W_e :

$$v(t,z) = V_o \sin \omega_n t \sin k_n z$$

$$w_e(t,z) = Cv^2/2$$

$$= CV_o^2 (\sin^2 \omega_n t)(\sin^2 k_n z)/2$$
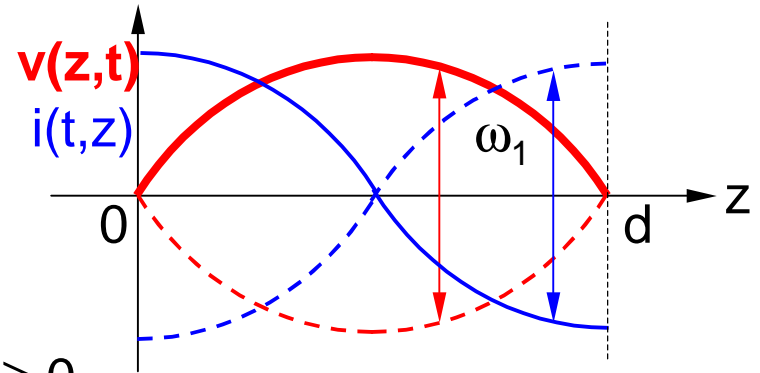
$$= CV_o^2 (1 - \cos 2\omega_n t)(1 - \cos 2k_n z)/8 \geq 0$$




Magnetic Energy Density W_m :

$$i(t,z) = (V_o/Z_o) \cos \omega_n t \cos k_n z$$

$$w_m(t,z) = Li^2/2$$

$$= L(V_o/Z_o)^2 (\cos^2 \omega_n t)(\cos^2 k_n z)/2$$
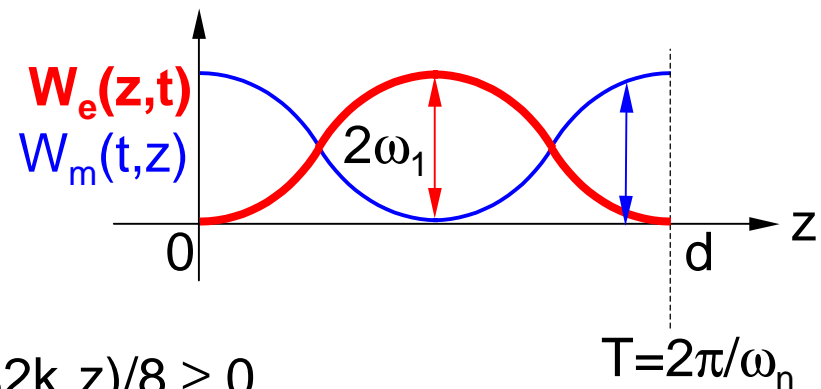
$$= L(V_o/Z_o)^2 (1 + \cos 2\omega_n t)(1 + \cos 2k_n z)/8 \geq 0$$



Electric and Magnetic Energies w_e and w_m :

$$w_e(t) = CV_o^2 (1 - \cos 2\omega_n t) d/8,$$

$$\langle w_e \rangle = CV_o^2 d/8$$

$$w_m(t) = L(V_o/Z_o)^2 (1 - \cos 2\omega_n t) d/8,$$

$$\langle w_m \rangle = L(V_o/Z_o)^2 d/8$$

$$\langle w_e \rangle = \langle w_m \rangle \text{ because } C = L/Z_o^2 \quad [Z_o = (L/C)^{0.5}]$$

LOSSES IN TEM RESONATORS

Distributed Losses:


$$P_{\text{diss}}(t, z) = i^2 R + v^2 G \text{ [watts/m]}$$

$$P_d = \int_0^d \langle P_{\text{diss}} \rangle dz$$

$$= \int_0^d (V_o/Z_o)^2 \langle \cos^2 \omega_n t \rangle (\cos^2 k_n z) R dz$$

$$+ \int_0^d V_o^2 \langle \sin^2 \omega t \rangle (\sin^2 k_n z) G dz \text{ (for short-circuited TEM)}$$
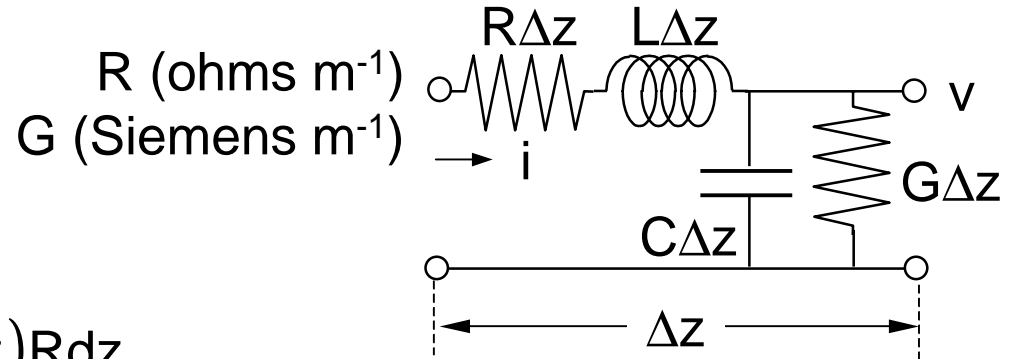
$$= R d (V_o/Z_o)^2 / 4 + G d V_o^2 / 4 \text{ [watts]}$$




Example of Q Calculation (n = 1):

$$Q_l = Q_L = \omega_o w_T / P_d = \pi c C Z_o^2 / R d = \pi (LC)^{-0.5} C (L/C) / R d = \pi Z_o / R d$$

$$\omega_o (n = 1) = \pi c / d$$

$$w_T = 2 \langle w_e \rangle = C V_o^2 d / 4$$

$$P_d = R d (V_o / Z_o)^2 / 4$$

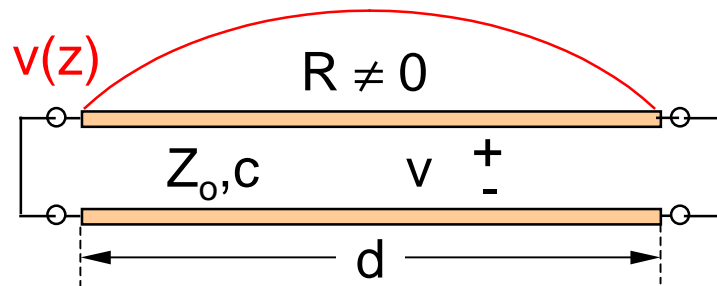


LUMPED LOSSES IN TEM RESONATORS

Lumped Losses **a** :

$$i = V_o/Z_o \cos \omega t$$

e.g. shorted TEM line, length d :

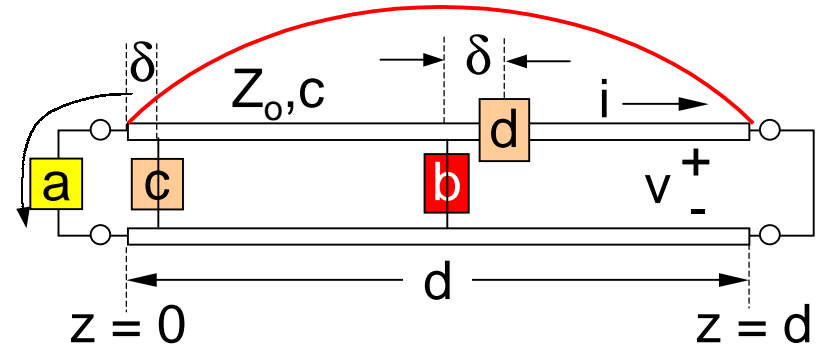

Perturbation technique: calculate losses using unperturbed v or i

Requires: $\Delta v \ll v_o$ or $\Delta i \ll i_o$; $\Gamma \cong \Gamma_o$

Examples: $G_{z=0} = (Z_n - 1)/(Z_n + 1) \cong G_{0(z=0)} = -1$, if $Z_{an} = R_a/Z_o \ll 1$

$G_{(z=d/2)} \cong G_o = 0$, if $Z_{bn} = R_b/Z_o \gg 1$

$R_c \gg |Z_{left}(z = \delta)| = |-jZ_o \sin k\delta|$ is perturbation

Note: $R_c = Z_o \gg Z_o \sin k\delta$ if $2\pi\delta/\lambda \ll 1$

$R_d \ll |-jZ_o/\sin k\delta|$ is perturbation, so is $R_d=Z_o$ if $2\pi\delta \ll \lambda$

Loss Computation Examples:


$P_d \cong \langle i_{z=0}^2 \rangle R_a$ for resistor "a" (use unperturbed $i_{z=0}$)

$P_d \cong \langle v_{z=d/2}^2 \rangle / R_b$ for resistor "b" (use unperturbed $v_{z=d/2}$)

$P_d \cong \langle (V_o \sin kd \sin \omega t)^2 \rangle / R_c$ for "c" (uses unperturbed v)

COUPLED TEM RESONATORS

Example, Q Computation (n = 1):

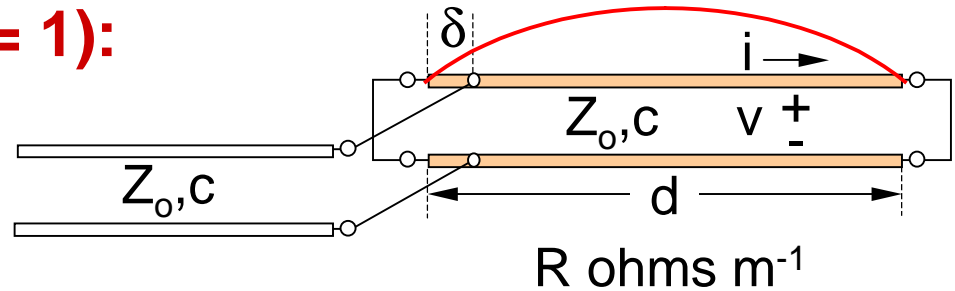

$$\omega_o (n = 1) = \pi c/d$$

$$w_T = 2 \langle w_e \rangle = CV_o^2 d/4$$

$$P_{\text{dext}} \cong \langle (V_o \sin k\delta \sin \omega t)^2 \rangle / Z_o$$

$$Q_I = \omega_o w_T / P_{\text{dInternal}} = \pi Z_o / Rd \quad (\text{see L18-6})$$

$$Q_E = \omega_o w_T / P_{\text{dExternal}}$$

$$= (\pi c/d) (CV_o^2 d/4) Z_o / \langle (V_o \sin k\delta \sin \omega t)^2 \rangle$$

$$\cong \pi c C Z_o \lambda^2 / (2\pi\delta)^2 = \pi (LC)^{-0.5} C (L/C)^{0.5} (2d)^2 / (2\pi\delta)^2$$

$$= (d/\delta)^2 / \pi$$

Example, Coupling to TEM Resonator:

$$Q_I = Q_E = 2Q_L \text{ for perfect coupling at resonance (matched load)}$$

$$\Rightarrow \pi Z_o / Rd \cong (d/\delta)^2 / \pi \rightarrow \text{Set } \delta \cong (d^3 R / Z_o \pi^2)^{0.5} \text{ [m]}$$

$$\Delta\omega = \omega_o / Q_L = \omega_o / 2Q_I = (\pi c/d) / (2\pi Z_o / Rd) = cR / 2Z_o \text{ [rs}^{-1}\text{]}$$

$$\text{Imperfect coupling if } Q_E \neq Q_I; \quad Q_E / Q_I = R / R_{\text{Th}} \Rightarrow G \text{ at } \omega_o$$