

**Massachusetts Institute of Technology**  
**Department of Physics**  
**Physics 8.022 - Fall 2002**

**Assignment #5**  
**Current, Resistance, Ohm's Law**  
**EMF, Circuits, Kirchhoff's Rules, RC Circuits**

**Reading** *Purcell* Chapter 4.

**Problem Set #5**

Work on **all** problems. Not all problems receive equal points. Total points for this set is 100.

- **(20 points) [1]** Current Flow Between Cylindrical Plates.

The space in between two cylindrical copper plates of radius  $a$  and  $b$  ( $b > a$ ) is filled with a material of conductivity  $\sigma$ . The length of the plates is  $L$ . The two plates are kept at constant potential  $V_a$  and  $V_b$  ( $V_a > V_b$ ). Express all your answers in terms of  $V_a, V_b, a, b$  and  $L$ .

- Find the resistance of this configuration.
  - Find the current density  $\vec{J}$  in the space between the two cylinders.
  - Find the electric field  $\vec{E}$  in the space between the two cylinders.
- **(20 points) [2]** Snell's Law for Electric Currents.  
An infinite medium has two regions I and II each with conductivity  $\sigma_1$  and  $\sigma_2$  separated by a plane interface. In region I a uniform current density  $\vec{J}_1$  flows up to the interface at an angle  $\theta_1$ .
    - Find the magnitude and angle of the current density  $\vec{J}_2$  in region II.
    - Find the charge density  $\sigma$  on the interface.
  - **(15 points) [3]** *Purcell* Problem 4.21 (p.165): Resistive Network.
  - **(15 points) [4]** *Purcell* Problem 4.25 (p.165): Discharging Capacitor.
  - **(15 points) [5]** *Purcell* Problem 4.32 (p.168): Infinite Resistor Chain..
  - **(15 points) [6]** *Purcell* Problem 4.33 (p.168): Kirchhoff's Law and Minimum Power Requirement.