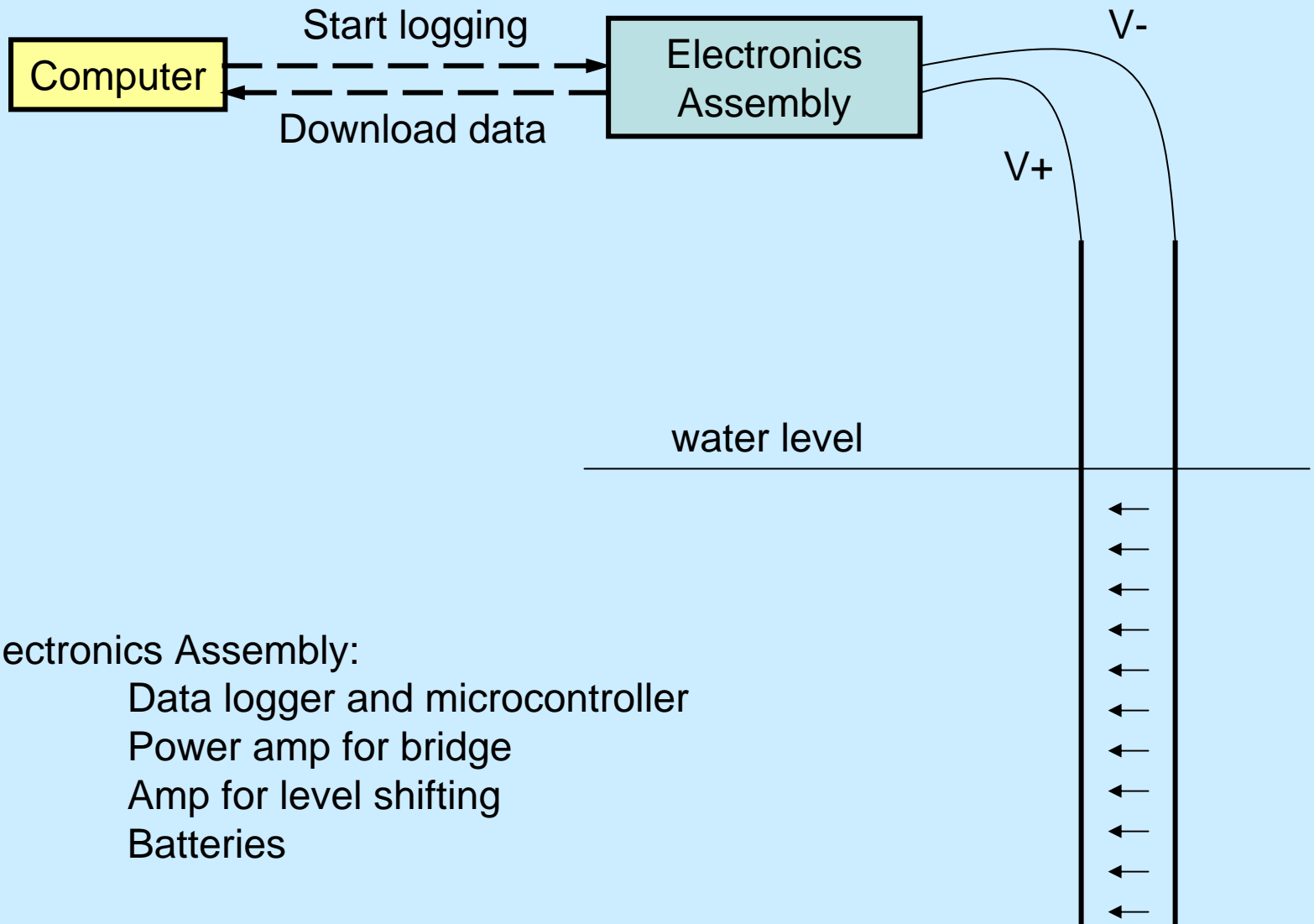


Building a Resistive Wave Probe




Electronics Assembly:

- Data logger and microcontroller
- Power amp for bridge
- Amp for level shifting
- Batteries

Resistance $R = \text{Volts loss per Ampere driven through the "device"}$

R is not a property of bulk material!

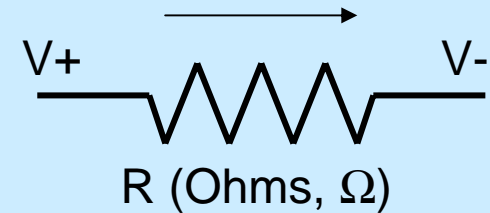$\text{Conductance} = 1 / \text{Resistance}$



Conductivity of seawater: $K \sim 4 \text{ S/m}$, where

$1 \text{ S} = 1 \text{ Siemen} = 1 \text{ Ampere per Volt}$:

One Volt across opposing plates of area 1 m^2 drives one Ampere


1 S/m means one Volt drives one Ampere, when the distance between electrodes is one meter

Conductivity is a property of bulk material!

$\text{Resistivity} = 1 / \text{Conductivity}$

Equivalent resistance through seawater:

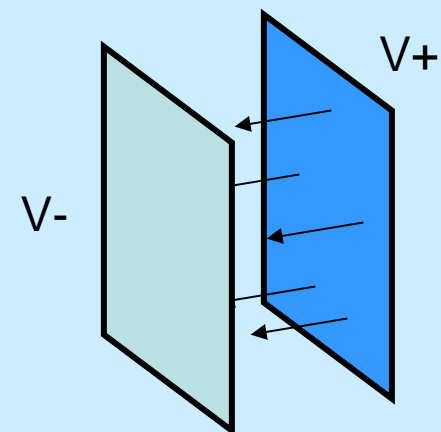$R = \text{distance} / [\text{area} \times K]$



Your Wave Probe

d = wire diameter


z = immersion depth

D = separation distance


Two wires of immersed surface area πdz :

Then **$R = D / [\pi d z K]$**

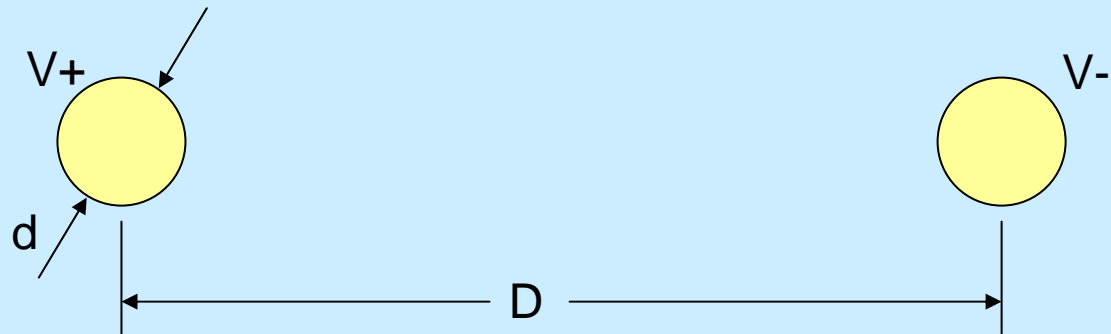
$$\sim 0.10\text{m} / [\pi \times 0.001\text{m} \times 1\text{m} \times 4\text{S/m}] = 8\Omega$$




Voltage Divider

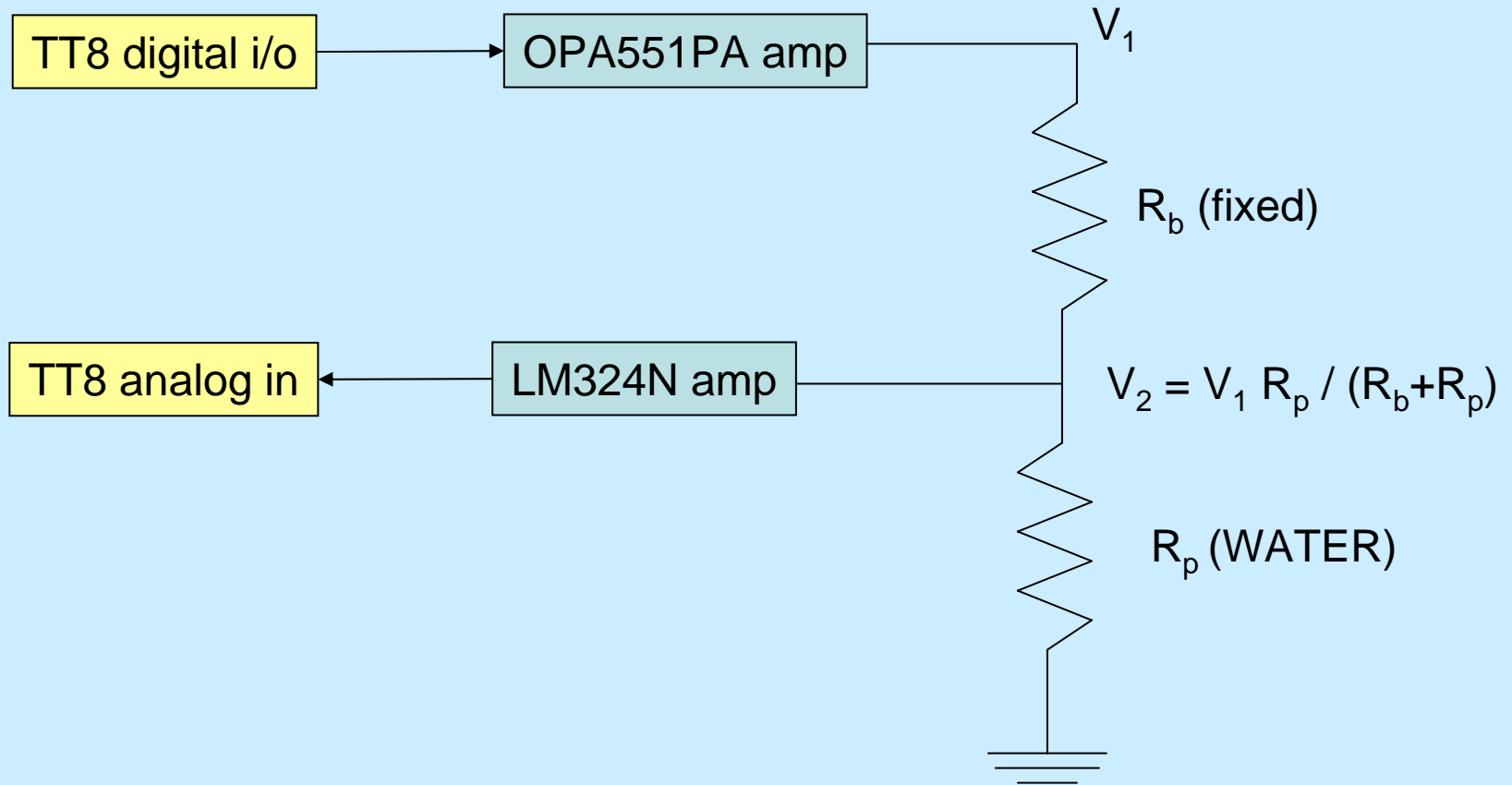

Wave Probe Electronics Schematic

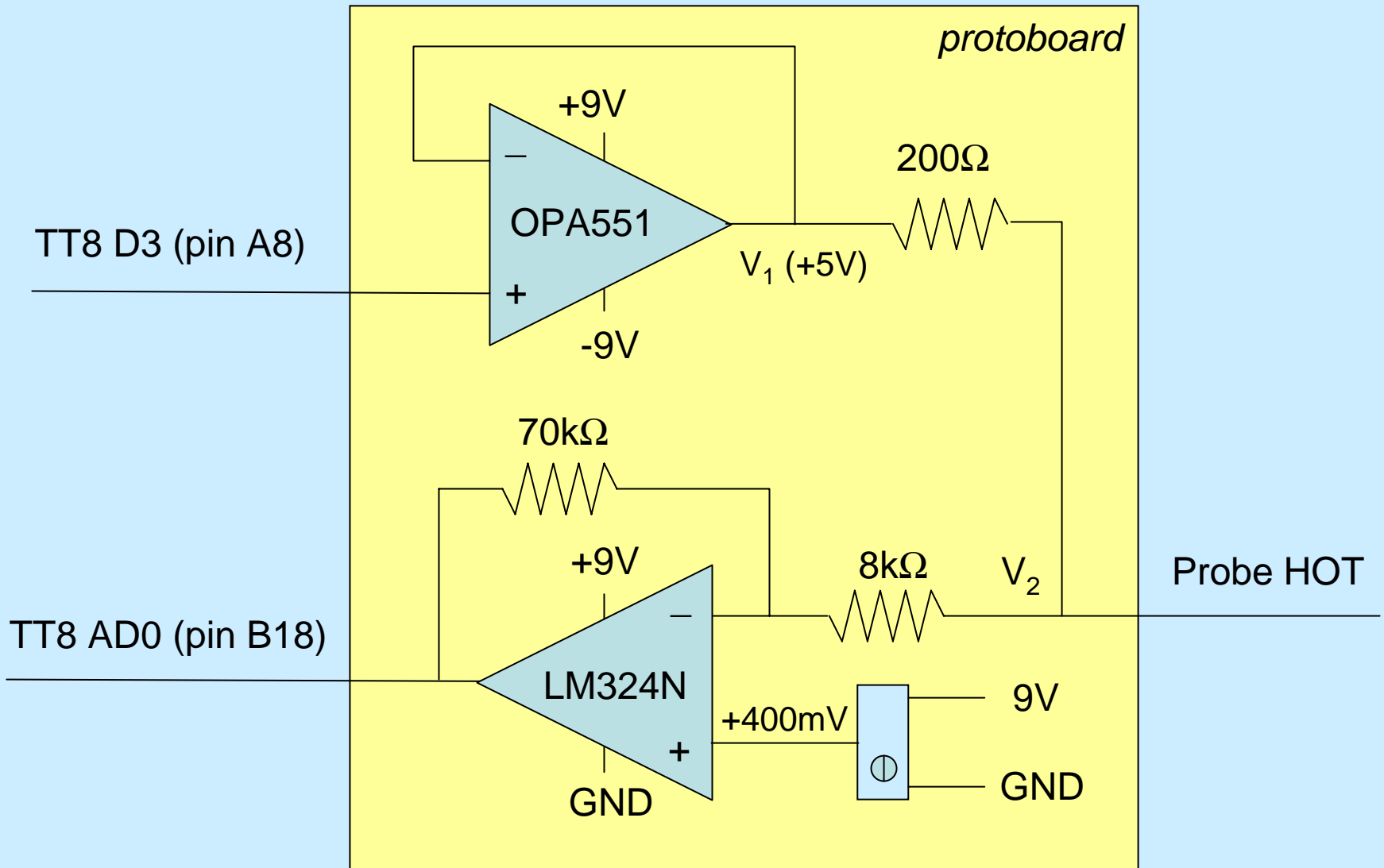

Check the Math!

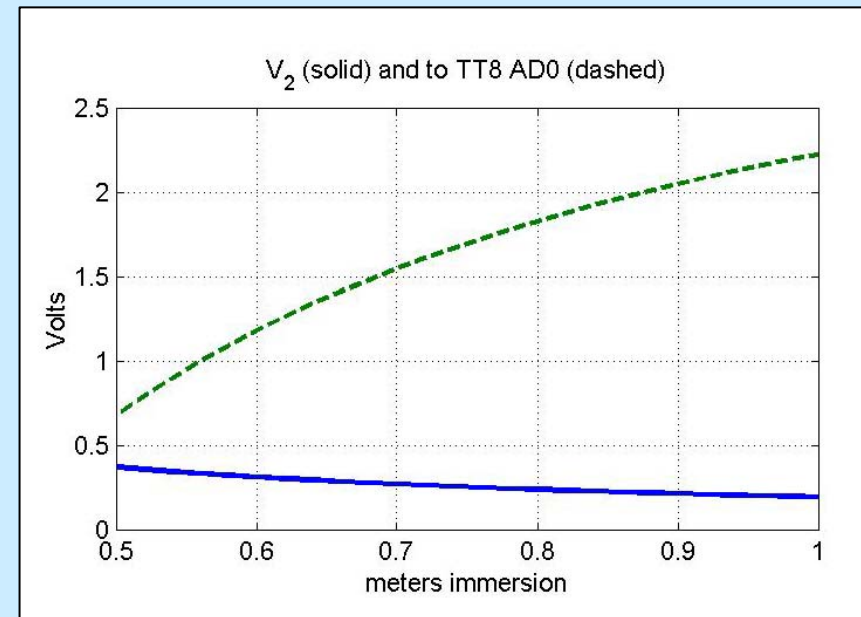


- Output of OPA551 is zero (bridge not energized) or five Volts (energized).
- The voltage divider splits the fixed 200 Ω with about 10 Ω in the water, so $V_2 \sim 250\text{mV}$.
- The TT8 AD0 sees about:
$$(70\text{k}\Omega + 8\text{k}\Omega) / 8\text{k}\Omega * 400\text{mV} - 70\text{k}\Omega / 8\text{k}\Omega * V_2$$
$$\sim 3.9\text{V} - 8.8 V_2$$
$$\sim 1.7\text{V} \quad \text{if } V_2 = 250\text{mV} \quad \text{OK}$$

Guidelines to Building

- Run the TT8 with a 12V battery – always double check polarity!
RED IS POSITIVE
- You'll run the program sclogger, the output will always be written to output.dat. Use `ren output.dat myfile.dat` to rename the file.
- Tie the analog and digital grounds of the TT8 to the protoboard.
- Tie the middle of the two 9V cells to ground; the batteries supply +9V and -9V.
- Start by building up the OPA551; confirm that V_1 is zero when input is zero, and V_1 is 5V when input is 5V.
- When the circuit is complete, use a resistor of around 10Ω in place of the probe to check the LM324N output. It should be about +1.5V to +2V.
- When you can log the test circuit output using *sclogger*, you're ready to go in the water!
- When you calibrate, the curve should have the form $V = k_1 + k_2 / z$
- TT8 can read 0 to +4095mV, in units of one millivolt


Hooking up the amps

OAP551
High Voltage
High Current

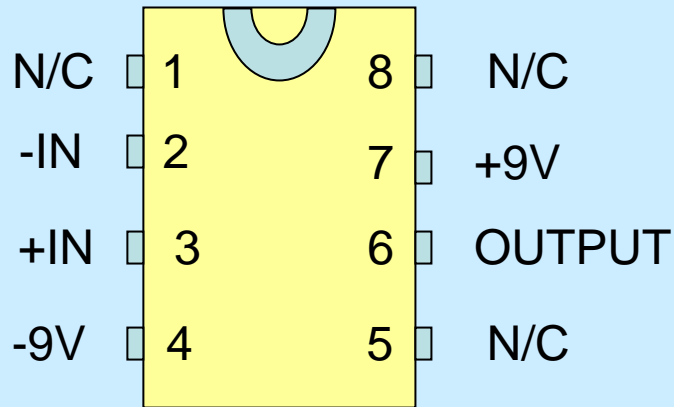

8-DIP (dual in-line pin)

LM324N
Low-Power
Quad

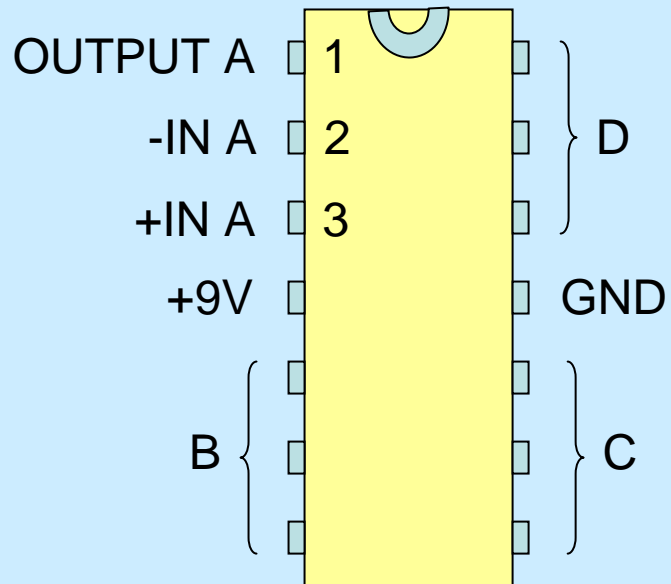

14-DIP