

---

2.003 Spring 2003  
Quiz 2 - Sample problem Set 2 Solutions

Problem A - RLC circuit analysis

1.

$$\frac{V_o}{V_i} = \frac{1}{LCs^2 + RCs + 1}$$

2.

$$\omega_n = 2 * \pi * 5000 = 31,400 \text{ r/s} = \frac{1}{\sqrt{LC}}$$


$$L = \frac{1}{\omega_n^2 C} = 0.001 \text{ H} = 1 \text{ mH}$$


$$\frac{R}{L} = 2\zeta\omega_n = 2 * 0.707 * 31,400$$

$$R = 44.4 \Omega$$

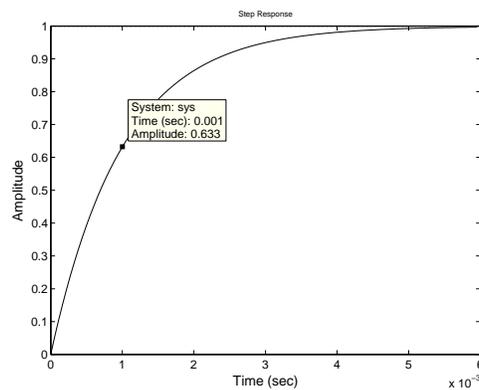3. There are no zeros, poles at roots of

$$s^2 + \frac{1000}{0.001}s + \frac{1}{1e-6 * 1e-3} = 0$$
$$s_1 \approx -1e6$$
$$s_2 \approx -1e3 \text{ dominant pole}$$
$$x_{ss} = 1$$



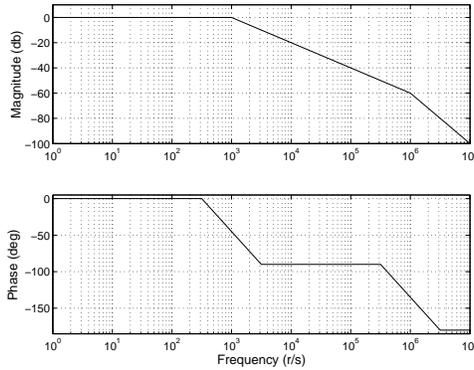

4.

5.  $s = -1e3 = s_2$

6.

$$\text{For circuit with R\&C in } \parallel \quad \frac{v_o}{v_i} = \frac{R_2}{R_2LCs^2 + (R_1R_2C + L)s + R_1 + R_2}$$

$$\text{For circuit with R\&C in series} \quad \frac{v_o}{v_i} = \frac{R_2Cs + 1}{LCs^2 + (R_1 + R_2)Cs + 1}$$

### Problem B

1.

$$T(s) = \frac{K}{s^2 + 20s + K}$$

$$\omega_n = \sqrt{K}$$

$$2\zeta\omega_n = 2\sqrt{K} = 20$$

$$K = 100$$

2.

$$\frac{V_{out}}{V_1} = \frac{(s+3)(6s+1)}{(s+3)(6s+1) + (8s+7)}$$

$$\frac{V_{out}}{V_2} = \frac{(6s+1)}{(s+3)(6s+1) + (8s+7)}$$

3. Solve using superposition

$$V_{out}(6s^2 + 27s + 10) = V_1(6s^2 + 19s + 3) + V_2(6s + 1)$$

$$6\ddot{V}_{out} + 27\dot{V}_{out} + 10V_{out} = 6\dot{V}_1 + 19\dot{V}_1 + 3V_1 + 6\dot{V}_2 + V_2$$

---

**Problem C**

The transfer function for this system is

$$\frac{x(s)}{f(s)} = \frac{1}{m_{eq}s^2 + cs + k}$$
$$\omega_n = \sqrt{\frac{k}{m_{eq}}}$$
$$2\zeta\omega_n = \frac{c}{m_{eq}}$$

1. From graph, we measure the following

$$T \approx 1.0s \Rightarrow \omega_d = \frac{2\pi}{T} = 6.28r/s$$
$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$
$$M_p \approx 100 \frac{0.75 - 0.5}{0.5} = 50$$
$$\zeta = \frac{A}{\sqrt{\pi^2 + A^2}} = 0.215$$
$$A = \ln \frac{100}{M_p} = 0.693$$
$$\omega_n = 6.43r/s$$
$$m_{eq} = \frac{\omega_n^2}{k} = 4.8 \approx 5kg$$
$$c = 2\zeta\omega_n m_{eq} = 13.8Ns/m \approx 14Ns/m$$

Alternately, you could determine  $\zeta$  using the log decrement method.

- 2.

$$m_{eq} = m + \frac{I}{r^2}$$
$$I = 0.5 kg m^2$$

**Problem D**

The transfer function for this system is

$$\frac{\omega(s)}{\phi(s)} = \frac{k}{Js^2 + cs + k}$$

Thus  $\omega_n = \sqrt{\frac{k}{J}}$

$$2\zeta\omega_n = \frac{c}{J}$$

1. There are a couple of ways to solve this part of the problem. First, you can read  $\omega_r = 9 r/s$  and  $M_p = 5 dB$  from the bode plot and use the following

---

relationships

$$M_p = \frac{1}{2\zeta\sqrt{1-\zeta^2}}$$
$$\omega_r = \omega_n\sqrt{1-2\zeta^2}$$

to find  $\zeta \approx 0.3$  and  $\omega_n \approx 10$  *r/s*. Or you can read  $\omega_n = 10$  *r/s* directly from the phase plot ( $\theta = -90^\circ$ )

2.  $k = 1500$  *Nm/r*,  $c = 90$  *Nms/r*

3.

$$\omega = 1.1 \text{ r/s } \theta(t) \approx \sin(1.1t + 0)$$
$$\omega = 10 \text{ r/s } \theta(t) \approx 1.58 \sin(10t - \pi/2)$$
$$\omega = 20 \text{ r/s } \theta(t) \approx 0.3 \sin(20t - 2.75)$$