

MIT OpenCourseWare  
<http://ocw.mit.edu>

2.00AJ / 16.00AJ Exploring Sea, Space, & Earth: Fundamentals of Engineering Design  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

# ***Basic* Circuits**

2.00A Lecture

Prof. A. Techet

Image removed due to copyright restrictions.

Please see:


<http://www.art-sci.udel.edu/ghw/phys245/05S/lab/images/schematics.gif>

or [http://commons.wikimedia.org/wiki/File:Circuit\\_elements.png](http://commons.wikimedia.org/wiki/File:Circuit_elements.png)

## Electronic Circuits


- **Resistance:** The property of a component to oppose the flow of electrical current through itself.
- **Capacitance:** The property of a component to oppose any change in voltage across its terminals, by storing and releasing energy in an internal electric field.
- **Inductance:** The property of a component to oppose any change in current through itself, by storing and releasing energy in a magnetic field surrounding itself.

### Resistance

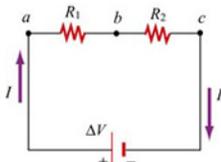

**Resistance in Series:**  
Current is the same everywhere  
 $V_T = I * R_T$ ;  $V_1 = I * R_1$ ;  $V_2 = I * R_2$   
 $V_T = V_1 + V_2 = I * (R_1 + R_2)$

**Resistors in series**

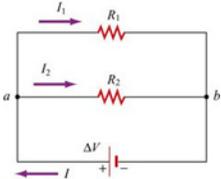

**Resistance in Parallel:**  
Voltage is the same everywhere  
 $I_T = V / R_T$ ;  $I_1 = V / R_1$ ;  $I_2 = V / R_2$   
 $I_T = I_1 + I_2 = V / R_T = V / R_1 + V / R_2$   
 $R_T = 1 / (1/R_1 + 1/R_2) = R_1 R_2 / (R_1 + R_2)$

**Resistors in Parallel**

Courtesy John Belcher, Peter Dourmashkin, and Sen-Ben Liao. Used with permission.

## Capacitance



Capacitors in series

**Capacitance in Series:**  
Voltage is the same everywhere  
 $C_T = 1 / (1/C_1 + 1/C_2) = C_1 C_2 / (C_1 + C_2)$



Capacitors in Parallel

**Capacitance in Parallel:**  
Current is the same everywhere  
 $C_T = C_1 + C_2 + \dots$

# RESISTORS

Images removed due to copyright restrictions.  
 Please see <http://www.art-sci.udel.edu/ghw/phys245/05S/lab/images/penny.jpg> and  
<http://www.art-sci.udel.edu/ghw/phys245/05S/lab/images/dime.jpg>  
 and any table of resistor color codes, such as [http://en.wikipedia.org/wiki/Electronic\\_color\\_code](http://en.wikipedia.org/wiki/Electronic_color_code)

Resistor Decoder Java Applet:  
<http://www.physics.udel.edu/~watson/phys345/decoder/>



# Tools

Figure 3: Tools for Building LED Light Bank

Image removed due to copyright restrictions.  
 Please see <http://www.art-sci.udel.edu/ghw/phys245/05S/lab/images/leads.gif>

# LED Light Bank

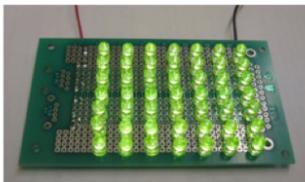


Figure 13: Working LED Light Bank

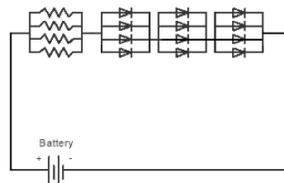


Figure 2: Circuit Diagram for LED Light Bank

Intro to circuit building: <http://www.instructables.com/id/Circuit-Building-101/>

# Light Absorption in the Ocean

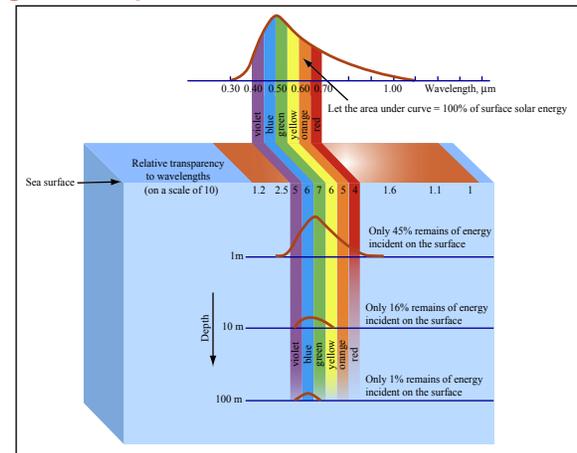


Figure by MIT OpenCourseWare.