

April 18, 2001 - Quiz #2

Name: _____

Recitation: _____

problem	grade
1	
2	
3	
4	
5	
total	

General guidelines (please read carefully before starting):

- Make sure to write your name on the space designated above.
- **Open book:** you can use any material you wish.
- All answers should be given in the space provided. Please do not turn in any extra material. If you need more space, use the back page.
- You have **120 minutes** to complete your quiz.
- Make reasonable approximations and *state them*, i.e. quasi-neutrality, depletion approximation, etc.
- Partial credit will be given for setting up problems without calculations. **NO** credit will be given for answers without reasons.
- Use the symbols utilized in class for the various physical parameters, i.e. μ_n , I_D , E , etc.
- Every numerical answer must have the proper units next to it. Points will be subtracted for answers without units or with wrong units.
- Use $\phi = 0$ at $n_o = p_o = n_i$ as potential reference.
- Use the following fundamental constants and physical parameters for silicon and silicon dioxide at room temperature:

$$\begin{aligned}
 n_i &= 1 \times 10^{10} \text{ cm}^{-3} \\
 kT/q &= 0.025 \text{ V} \\
 q &= 1.60 \times 10^{-19} \text{ C} \\
 \epsilon_s &= 1.05 \times 10^{-12} \text{ F/cm} \\
 \epsilon_{ox} &= 3.45 \times 10^{-13} \text{ F/cm}
 \end{aligned}$$

1. (25 points) You are given a CMOS inverter with the following parameters:

$$\begin{array}{lll} V_{Tn} = 0.5 \text{ V} & t_{ox} = 10 \text{ nm} & \mu_n = 400 \text{ cm}^2/\text{V} \cdot \text{s} \\ V_{Tp} = -1 \text{ V} & \lambda_n = \lambda_p = 0.1 \text{ V}^{-1} & \mu_p = 200 \text{ cm}^2/\text{V} \cdot \text{s} \\ V_{DD} = 5 \text{ V} & L_n = L_p = 1 \text{ } \mu\text{m} & \end{array}$$


(1a) (5 points) Calculate the ratio W_p/W_n so that $V_M = 2.5 \text{ V}$.

(1b) (5 points) We want this inverter to have an average propagation delay $t_p = 1 \text{ ns}$ when driving a $C_L = 1 \text{ pF}$ capacitive load. Calculate W_n and W_p .

(1c) (10 points) Estimate NM_L and NM_H for this inverter.

(1d) (5 points) Sketch and appropriately label the voltage transfer characteristics of this inverter.

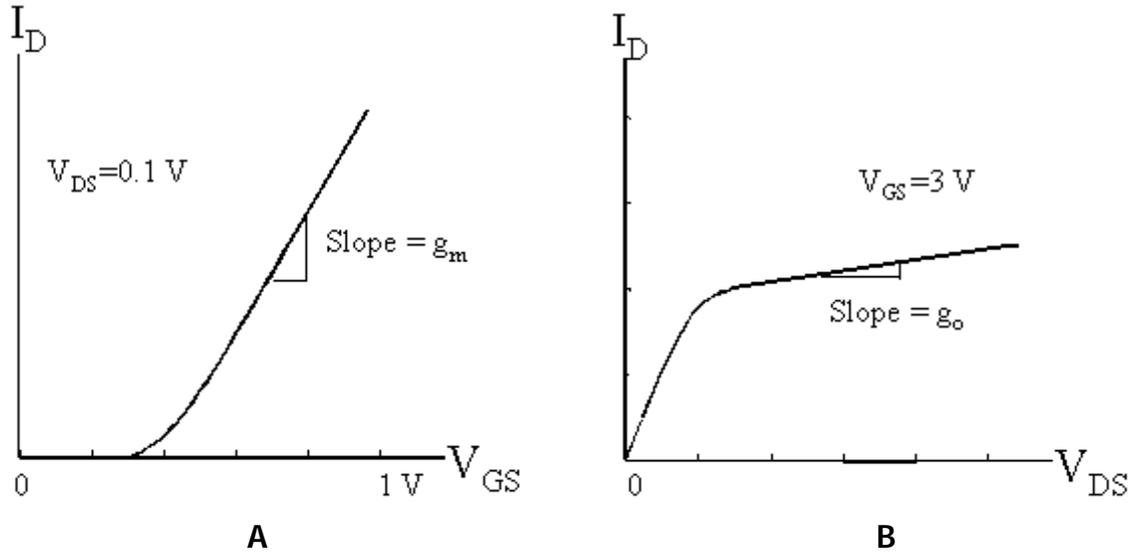2. (20 points) You are given the following I-V characteristics for a n-MOSFET with $t_{ox} = 10 \text{ nm}$, $W = 10 \text{ }\mu\text{m}$, and $L = 1 \text{ }\mu\text{m}$. The gate material is n^+ -doped polysilicon. The body is tied up to the source.



In (A), $g_m = 1.4 \times 10^{-4} \text{ A/V}$. In (B), $g_o = 5.7 \times 10^{-5} \text{ A/V}$.


(2a) (5 points) From (A), estimate the threshold voltage, V_T .

(2b) (5 points) From (A), estimate the electron mobility, μ_n .

(2d) (5 points) Estimate the saturation voltage, V_{DSsat} , and the saturation current, I_{Dsat} , corresponding to the characteristics in (B).

(2e) (5 points) From (B), estimate the length of the channel pinch-off region, ΔL , at $V_{DS} = 4\text{ V}$.

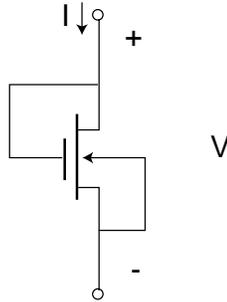
3. (20 points) An n-channel MOSFET is wired up in the form indicated below. This is an enhancement-mode device ($V_T > 0$). Neglect channel length modulation.



(3a) (10 points) In terms of usual MOSFET parameters, derive suitable equations for the I-V characteristics of the resulting two-terminal device. Sketch the I-V characteristics in a linear scale.

(3b) (10 points) Sketch a complete high-frequency small-signal equivalent circuit model for this two-terminal device for situations in which $V > V_T$. Express all small-signal elements in terms of those of the MOSFET, *i.e.*: as a function of g_m , g_o , C_{gs} , C_{gd} , C_{sb} , etc.

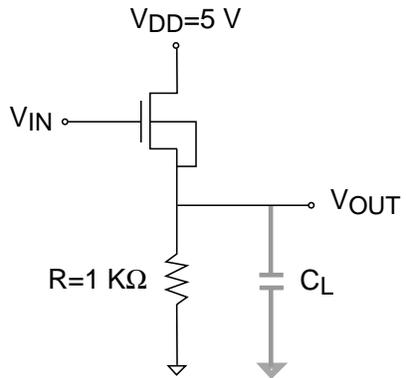4. (15 points) An NMOS inverter with a resistor pull up was miswired and ended up as sketched below.



The parameters of the transistor are: $\mu_n C_{ox} = 50\ \mu\text{A}/\text{V}^2$, $W/L = 5$, and $V_T = 1\text{ V}$. Neglect channel length modulation in this problem.

(4a) (5 points) For $V_{IN} = 0$, in what regime is the transistor biased? How much is V_{OUT} ? (numerical answer expected).

(4b) (10 points) For $V_{IN} = 5\text{ V}$, in what regime is the transistor biased? How much is V_{OUT} ? (you can leave the result in the form of an equation where V_{OUT} is the only unknown).

5. (20 points) In a certain pn junction diode at room temperature at a particular forward bias voltage, the current supported by hole injection into the n-side of the diode is $100 \mu A$.

The quasi-neutral width of the n-side of the diode is $w_n - x_n = 1 \mu m$. The hole diffusion coefficient is $10 \text{ cm}^2/s$. The pn junction area is $10 \mu m^2$.

Make and state suitable approximations.

(5a) (5 points) Estimate the hole concentration at the space-charge region edge of the n quasi-neutral region. (numerical answer expected).

(5b) (5 points) Estimate the velocity at which holes are injected at the edge of the n quasi-neutral region (numerical answer expected).

(5c) (5 points) Estimate the hole flux arriving at the surface of the n quasi-neutral region. (*numerical answer expected*).

(5d) (5 points) Estimate the diffusion capacitance associated with hole storage in the n quasi-neutral region. (*numerical answer expected*).