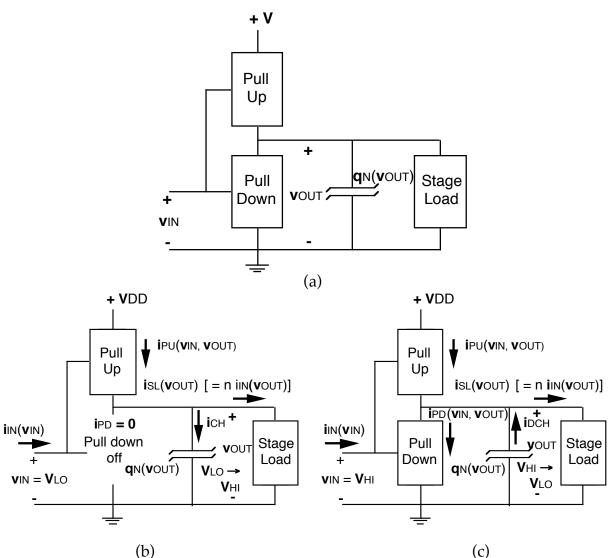
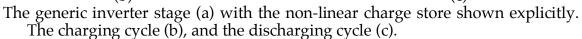

Inverter Switching Transient Analysis





The charge store will in general be a non-linear function of the output voltage; so too are the currents. Thus the differential equations we must solve are

Charging: $dq_N(v_{OUT})/dt = i_{CH}(v_{OUT})$, Discharging: $dq_N(v_{OUT})/dt = i_{DCH}(v_{OUT})$.


and

These are in general very complicated and difficult to solve by any means. If, however, the charge store can be modeled as a linear capacitor, C_L (i.e., $q_N \approx C_L v_{OUT}$), as illustrated below, then we can write,

Charging:
$$dv_{OUT}/dt = i_{CH}(v_{OUT})/C_L$$

Discharging: $dv_{OUT}/dt = i_{DCH}(v_{OUT})/C_L$

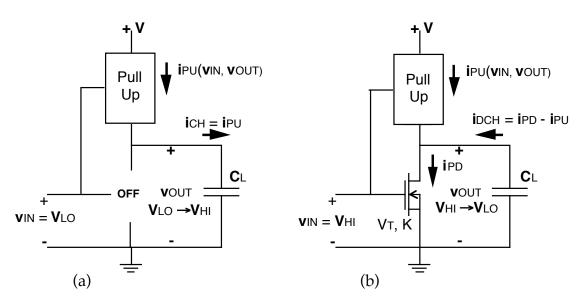These are now differential equations for $v_{OUT}(t)$ that we should at least be able to solve numerically, if we can not do so analytically. They also show us the value of knowing the size and shape of i_{CH} and i_{DCH} . (See Figure 6.14 in the course text, and the discussion accompanying it, for more on this topic).



Charging (a) and discharging (b) cycles with a linear load capacitor and zero static load current. Note that for MOS inverters the <u>static</u> current into the stage load, i_{SL}(v_{OUT}), is zero.

Finally, if the charge store can be modeled as a linear capacitor <u>and</u> the charging and discharging currents can also be approximated as being constant, then

 $\tau_{\text{LO}\rightarrow\text{HI}} \approx C_{\text{L}}(V_{\text{HI}} - V_{\text{LO}}) / I_{\text{CH}},$

and

and

$$\tau_{\rm HI \rightarrow LO} \approx C_{\rm L} (V_{\rm HI} - V_{\rm LO}) / I_{\rm DCH}$$

We will find that we can use such an approximation to advantage when we are analyzing CMOS inverters.

6.012 Microelectronic Devices and Circuits Fall 2009

For information about citing these materials or our Terms of Use, visit: http://ocw.mit.edu/terms.