

**6.012 Electronic Devices and Circuits
Spring 2005**

**May 16, 2005
Final Exam
(200 points)
-OPEN BOOK-**

	<u>Problem</u>
NAME _____	1 _____
RECITATION TIME _____	2 _____
	3 _____
	4 _____
	5 _____
	Total _____


General guidelines (please read carefully before starting):

- Make sure to write your name on the space provided above.
- All answers should be given in the space provided. Please do not turn in any extra material. If you need more space, use the back page.
- You have 180 minutes to complete the quiz.
- Where required, make reasonable approximations and *state them*.
- Partial credit will be given for setting up problems without calculations. NO credit will be given for answers without reasons.
- Use the symbols utilized in class for the various physical parameters, i.e. N_d , n_o , etc.
- Every numerical answer must have the proper units next to it. Points will be subtracted for answers without units or with wrong units.
- Use the following fundamental constants and physical parameters for silicon at room temperature.

$$\begin{aligned}n_i &= 1.0 \times 10^{10} \text{cm}^{-3} \\kT/q &= 0.025 \text{V} \\q &= 1.6 \times 10^{-19} \text{C} \\\epsilon_S &= 1.0 \times 10^{-12} \text{F/cm} \\\epsilon_{OX} &= 3.45 \times 10^{-13} \text{F/cm}\end{aligned}$$

 Problem 1 [40 points]


An ideal n-MOSFET has transconductance, g_m characteristics as shown below:



In addition, C_g is measured to be 0.1725pF at $V_{DS} = 0\text{V}$, $V_{GS} = 3\text{V}$, $V_{BS} = 0\text{V}$.

$W = 10\mu\text{m}$ and $L = 5\mu\text{m}$. Neglect channel length modulation and neglect any overlap capacitances. Assume $N_a = 10^{17}\text{cm}^{-3}$.

 
- a) On the axes below, draw the g_m characteristic for $V_{DS} = 2\text{V}$ and $V_{BS} = 0\text{V}$. Label the various regions of operation and any break-points on the plot.



b) Find the oxide thickness, t_{ox} .

c) Find the electron mobility, μ_n .

 d) On the axes below, sketch I_D vs. V_{GS} for $V_{DS} = 1V$, $V_{BS} = -3.0V$. Label the regions of operation of the device, and the value of I_D at $V_{GS} = 3V$.



e) Another n-MOSFET is now fabricated with the same W , L , and N_a . A new gate dielectric material is used, with dielectric constant $\epsilon_{new} = 2 \cdot \epsilon_{ox}$, and thickness $t_{new} = 2t_{ox}$. The electron mobility for the device with the new gate dielectric is half that of a MOSFET fabricated with silicon dioxide, i.e. $\mu_{new} = 1/2 \mu_n(oxide)$. For each of the following, assume the same bias for each device, and circle one of the choices, giving a brief justification:

i) V_T for the new device, relative to the oxide-dielectric device is:

lower higher the same

ii) g_{msat} for the new MOSFET, relative to the oxide-dielectric device is:

lower higher the same

iii) g_{mb} for the new MOSFET, relative to the oxide-dielectric device is:

lower

higher

the same

iv) C_g for $V_{GS} = 0V$ and $V_{DS} = 0V$ for the new device, relative to the oxide-dielectric device is:


lower

higher

the same

 
Problem 2 [40 Points]

A Bipolar transistor is biased to form a simple current amplifier. We are assuming no loading ($R_S \rightarrow \infty$, $R_L \rightarrow 0$) as shown below:



The minority carrier concentration profiles are shown on a linear scale at the DC operating point.

 $A_e = 10\mu\text{m} \times 10\mu\text{m}$
 $D_n = 10\text{cm}^2/\text{s}$
 $D_p = 5\text{cm}^2/\text{s}$




a) From the information given above, calculate I_{BIAS} .

b) Calculate the DC collector current I_C .

c) Assuming the depletion capacitances, C_{je} and C_{bc} are negligible, find the frequency at which the magnitude of the current gain is unity, $f = f_T$.

 d) From the information given, find β_o and f_{3dB} for the Bode Plot shown below.




e) Given an input signal in the time domain

$$i_s(t) = 1\mu A \left[\cos \left(2\pi \left(\frac{f_T}{10} \right) t \right) \right]$$

calculate the amplitude of the sinusoid at the output.

 Problem 3 [40 Points]

Consider the following amplifier circuit:



Bipolar Device Data

$$I_S = 10^{-15} A$$

$$\beta_o = 100$$

$$|V_A| \rightarrow \infty (r_o \rightarrow \infty)$$

$$C_\pi = 200fF$$

$$C_\mu = 20fF$$

Diode Device Data

$$I_o = 10^{-16} A$$

- a) Determine V_{BIAS} such that $V_{OUT} = 0$ when $V_S = 0V$. Assume the BJT is in the forward active region and ignore base current for this calculation.

b) Sketch an appropriate small signal model to determine the overall low frequency gain including R_L .


c) Calculate the overall low frequency voltage gain using the model you sketched in part (b). State any simplifying assumptions.

d) Sketch a small signal model that includes C_{π} and C_{μ} .

e) Using the Miller Theorem, calculate the Miller capacitance numerical value.

 Problem 4 [40 Points]

You are given a CS amplifier driving a purely capacitive load as shown below with the NMOS and PMOS device data. Assume all transistors are in the saturated region and assume all sources are shorted to the backgate.



Device Data

$$V_{tn} = 0.5V$$

$$V_{tp} = -0.5V$$

$$\mu_n C_{ox} = 50 \mu A/V^2$$

$$\mu_p C_{ox} = 25 \mu A/V^2$$

$$\text{For } W/L = 150/1.5$$

$$C_{gd} = 150fF$$

$$C_{gs} = 350fF$$

Neglect channel length modulation for part a & b.


- a) Calculate the value of I to make the p-channel supply current source for the CS amplifier have a value of $100 \mu A$.

b) Calculate V_{BIAS} such that the NMOS drain current is equal to $I_{SUP} = 100 \mu A$.

c) Calculate the transconductance of the CS amplifier at the operating point set in a & b.

- d) Given that the low frequency voltage gain is -50 , calculate R_{out} and $(\lambda_n + \lambda_p)$. Do not assume any particular λ .

 - e) A two-port model for the CS amplifier with capacitors added is shown below. Using the Miller Theorem and Method of Open Circuit Time Constants, find ω_{3dB} .




f) The width of the p-channel supply current source in the CS amplifier is reduced from $150\mu\text{m}$ to $1.5\mu\text{m}$ and the reference current source value remains I . Estimate the new low frequency voltage gain.

g) Estimate the new ω_{3dB} with the smaller ($1.5\mu\text{m}$) p-channel current source. State assumptions to reduce the amount of work you do for this part.

 Problem 5 [40 Points]

You are given a multistage voltage amplifier shown below. Assume that all devices are in their constant current region (MOS-saturated, BJT-forward active), at the operating point set by V_{BIAS} . Assume all substrates are shorted to their source.




Device Data

$$\begin{aligned}
 V_{Tp} &= -0.5 \\
 \mu_p C_{ox} &= 25 \mu\text{A}/\text{V}^2 \\
 \lambda_p &= 0 \\
 \beta_o &= 100 \\
 V_A &= 10\text{V}
 \end{aligned}$$

- a) Identify the type of stage (e.g. CS, CD) and the numerical value of the supply current sources for stages 1 and 2.

 b) A small signal two-port model of both stages including R_S and R_L is shown below. Calculate R_{in1} , A_{v1} , and R_{out1}



c) Calculate R_{in2} , A_{v2} , and R_{out2} .

d) Given $R_S = 20k\Omega$, adjust the width of the p-channel stage 1 supply current source such that 50% of the voltage enters the amplifier.

e) Given $R_L = 500\Omega$ adjust the width of the p-channel stage 2 supply current source such that 50% of the voltage is transferred to the load.

f) What is the overall voltage gain v_{out}/v_s [assuming the p-channel current sources are sized as in (d) and (e) above]?

MIT OpenCourseWare
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.