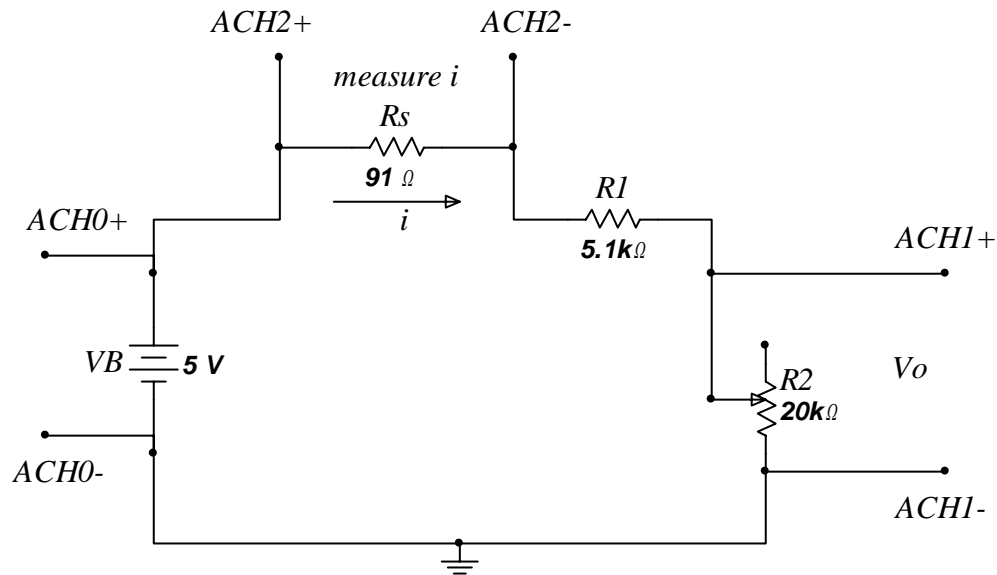


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
22.071/6.071 Introduction to Electronics, Signals and Measurement
Spring 2006

Lab8. Equivalent circuits, Power Transfer

With this exercise we will explore the concept of equivalent circuits and power transfer.

Let's start with the circuit shown below. The terminals labeled $ACH0+$, $ACH0-$, $ACH1+$, etc. are used for performing measurements of the circuit at the corresponding nodes.



In this circuit the resistor R_2 represents the load resistance. R_s is a current sensing resistor and its value is small compared with the other resistors in the circuit. By knowing the value of R_s a simple measurement of the voltage drop across it gives us the amount of current flowing through it.

Before proceeding with the experiment do the following calculations:

1. Derive an expression for R_2 as a function of V_B , V_o , R_1 , and R_s .
2. For $R_s \ll R_1$ and R_2 , derive the expression for the power dissipated in R_2 as a function of the circuit parameters.

Now construct the circuit on your protoboard and make the connections as indicated. For R_2 use your $20\text{k}\Omega$ variable resistor. For R_s use a 91Ω resistor.¹

Download the instrument called “**Power_Transfer_1**” from the class web site. Run it and vary R_2 . Observe the behavior of the circuit.

At what resistance is the power dissipated in R_2 maximized?


In the space below draw the power dissipated in R_2 as a function of R_2 .



Does your experimental result agree with your calculations?

¹ Any other resistance values could be used for R_s and R_3 . But since we have the 91Ω and the $5.1\text{k}\Omega$ in our kit we use these.

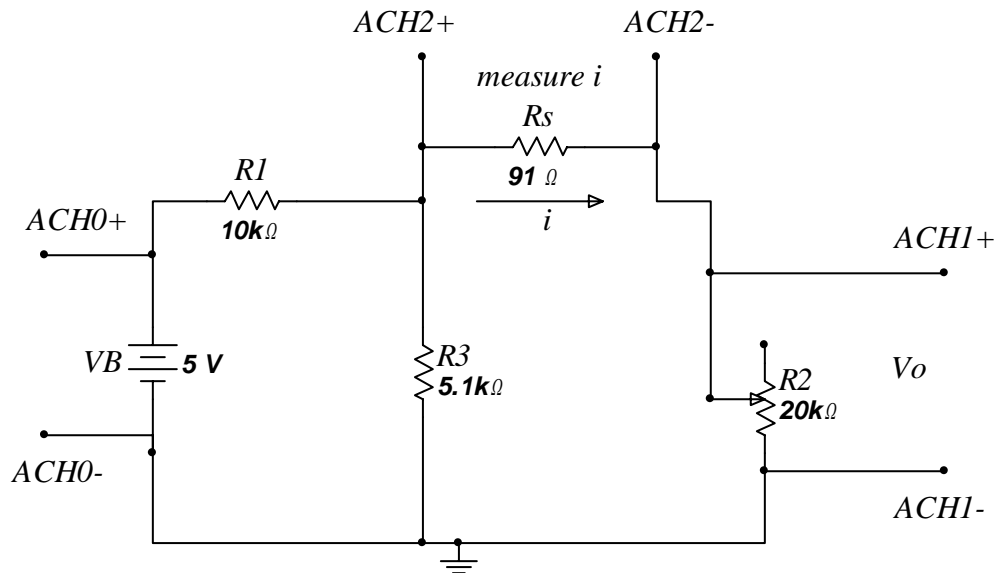Now let's modify the circuit by changing $R1$ to $10k\Omega$ and adding the $5.1k\Omega$ $R3$ resistor as indicated in the schematic below. Again use a 91Ω resistor for R_s .



Before proceeding with the experimentation with this circuit let's analyze it.

1. Determine the Thevenin equivalent circuit seen by resistor $R2$.

2. Calculate the voltage V_o across resistor $R2$ as a function of the circuit parameters.

Download the instrument called “**Power_Transfer_2**” from the class web site. Run it and vary R_2 and observe the behavior of the circuit. (Note: turn the previous instrument **Power_Transfer_1** off before proceeding with this one)

The instrument measures the power dissipated in R_2 and plots it as a function of R_2 . This is accomplished while you are trimming (changing the value) of the variable resistor R_2 .

In the space below redraw the results you are observing from the measurements



At what value of R_2 does the power dissipated in R_2 becomes a maximum in this case?

Do you see how that optimum value is related to R_1 and R_3 ? (We still have $R_s \ll R_1, R_2, \text{ and } R_3$).