

6.071 Review Session
Quiz 1

3/1/2006

Signals:

$$\text{RMS} = \text{Root mean squared} = \sqrt{\langle x^2(t) \rangle}$$

Time domain representation $x(t) \xleftrightarrow{F} \text{Frequency Domain } X(\omega)$

$$\text{Frequency } f = \frac{\omega}{2\pi}$$


$$\text{Period } T = 1/f$$

$$\text{Amplitude } A = \frac{1}{2} \cdot (\text{peak to peak value})$$


Signal Examples:

ex $x(t) = 4 \sin(6\pi t)$
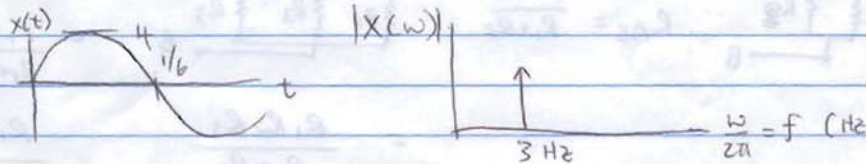
$$\text{RMS} = 4/\sqrt{2}, \quad \omega = 6\pi, \quad f = 3 \text{ Hz}, \quad A = 2+2 = 4$$







ex $|X(\omega)|$:

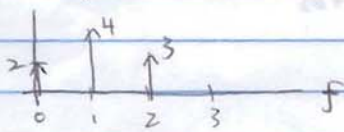


$$x(t) = 2 + 4 \cos(2\pi t) + 3 \cos(4\pi t)$$

$$\text{Nyquist rate} = 2 \times \text{highest frequency} = 4 \text{ Hz}$$

ex:

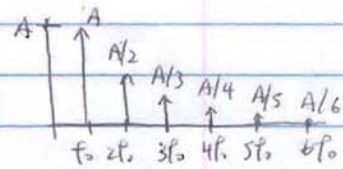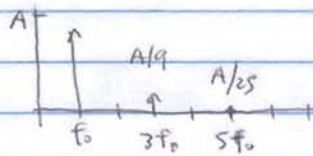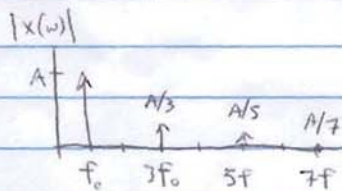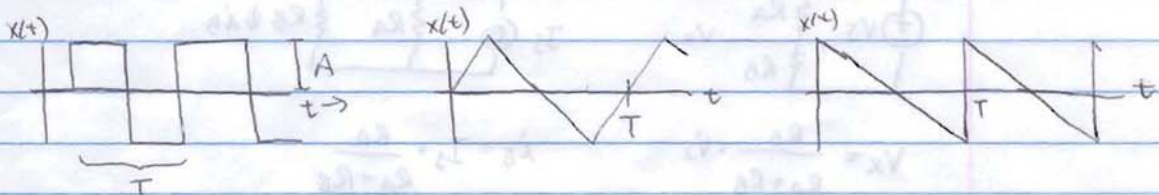

ex:

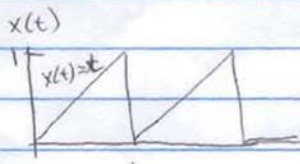

$$\begin{aligned} \text{RMS} &= \sqrt{\text{mean}\{1 \text{ period of } x^2(t)\}} \\ &= \sqrt{\frac{1}{1-0} \int_0^1 t^2 dt} \\ &= \sqrt{1 \cdot \left[\frac{1}{3} t^3 \right]_0^1} = \frac{1}{\sqrt{3}} \end{aligned}$$

Circuits:

$$V = IR$$


parallel + series R's, voltage + current dividers

superposition

ohm's Law, KVL, KCL, Mesh Method, Nodal Analysis, Thevenin, Norton, Power,

wheatstone bridge


ohm's Law: $V = IR$

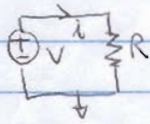


Parallel R's: $\frac{1}{R_{eq}} = \frac{1}{R_A} + \frac{1}{R_B}$

Series R's: $R_{eq} = R_A + R_B$

Parallel & Series:

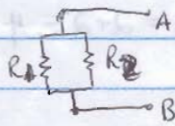

$$R_{AB} = \frac{R_1 R_2}{R_1 + R_2}$$

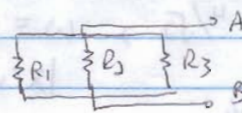


$$R_{AB} = R_1 \parallel R_2 \parallel R_3$$


$$= \frac{R_1 R_2}{R_1 + R_2} \parallel R_3$$

$$= \frac{R_1 R_2 R_3}{R_1 + R_2} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

Voltage + Current Dividers:

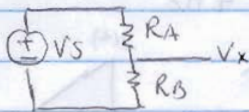

$$V_x = \frac{R_B}{R_A + R_B} V_S$$

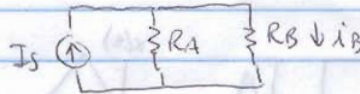


$$i_B = I_S \cdot \frac{R_A}{R_A + R_B}$$

~~Mesh Method~~

KVL: $\sum_{loop} V = 0$ KCL: $\sum_{node} i = 0$


Mesh Method:

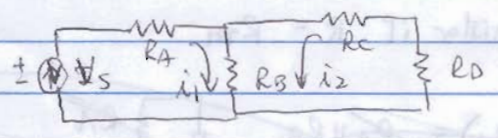

$$V_s - i_1 R_A - (i_1 + i_2) R_B = 0$$

$$(i_1 + i_2) R_B + i_2 R_D + i_2 R_C = 0$$


Nodal Analysis:

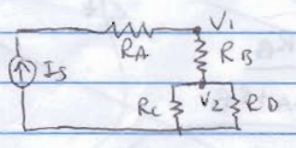

$$\left. \begin{aligned} \frac{V_1 - V_2}{R_B} - I_s &= 0 \\ \frac{V_2 - V_1}{R_B} + \frac{V_2}{R_C \parallel R_D} &= 0 \end{aligned} \right\} \begin{aligned} V_1 - V_2 &= I_s R_B \\ V_1 (R_B \parallel R_D) + V_2 (R_B + R_C \parallel R_D) &= 0 \end{aligned}$$

$$\rightarrow \begin{bmatrix} 1 & -1 \\ -[R_C \parallel R_D] & R_B + R_C \parallel R_D \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_s R_B \\ 0 \end{bmatrix}$$

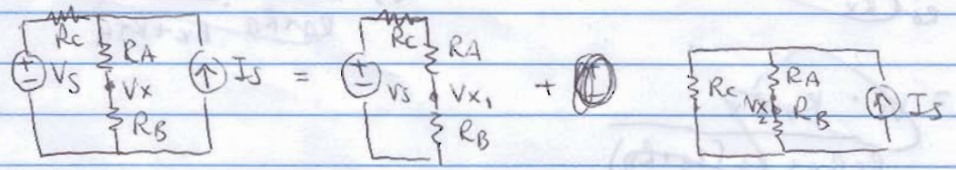Superposition: Analyze Circuit w/ 1 independent source at a time.




$$V_x = V_{x1} + V_{x2}$$

$$V_x = \frac{R_B}{R_A + R_B + R_C} V_s + \frac{R_C}{R_C + R_A + R_B} \cdot R_B \cdot I_s$$

Thevenin / Norton

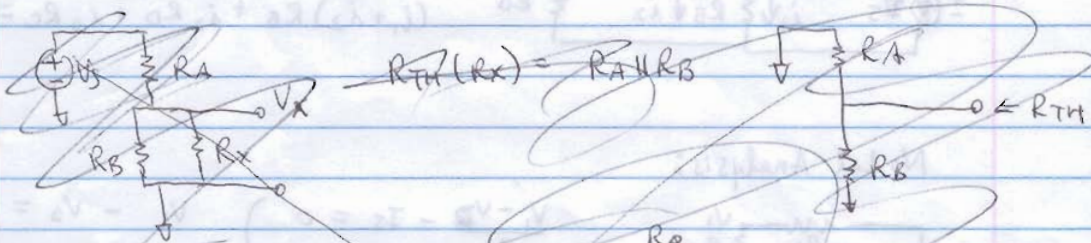- Take out the element between the measured nodes
- For R_{TH} , short all V_s and open all I_s
- $V_{oc} = I_N \cdot R_{TH}$
- Max power through a resistor if $R = R_{TH}$



$$R_{TH}(R_x) = R_A \parallel R_B$$

$$V_{TH}(R_x) = V_s \cdot \frac{R_B}{R_A + R_B}$$

$$V_x = V_s \cdot \frac{R_B \parallel R_x}{R_B \parallel R_x + R_A}$$

$$= V_s \cdot \frac{R_B R_x}{R_B + R_x + R_A}$$


$$\frac{R_B R_x}{R_B + R_x + R_A}$$

$$= V_s \cdot \frac{R_B R_x}{R_B R_x + R_A(R_B + R_x)}$$



$$V_o = V_{oc} \cdot \frac{R_x}{R_x + R_{TH}}$$
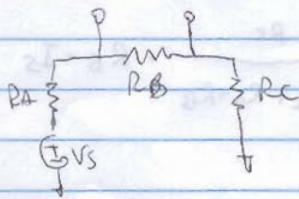
$$= V_s \cdot \frac{R_B}{R_A + R_B} \cdot \frac{R_x}{R_x + R_{TH}}$$



$$V_{oc} = V_s$$

$$R_{TH} = R_A \parallel R_B \parallel R_C$$

$$V_o = \frac{R_B}{R_A + R_B \parallel R_C}$$

