

## I. RLC circuits

- transient behavior intuition
- be able to derive 1st or 2nd order differential equation
- solve differential equations
- Norton, Thevenin, KCL, KVL; stuff from 1st two quizzes

## II. Diodes

- given a diode's forward voltage, reverse breakdown voltage, know its effect on an arbitrary circuit
- from its I-V characteristic derive its effect on any circuit

## III. Transistors

- recognize regions of operation
- figure out bias for given quiescent conditions & vice versa
- sketch  $I_o$

## I: RLC circuits:

- \* Always perform sanity check:  $v(t=0)$  and  $i(t=0)$ ,  $v(t=\infty)$  and  $i(t=\infty)$
- Energy is only dissipated through resistance; L and C just store energy
- Use your intuition; math errors are common!

1st order examples:  $\checkmark$  WHAT DOES THIS CIRCUIT SERVE? (what purpose)

$$V_s = v(t)$$

$$V_s - i_C R - V_L = 0$$

$$V_s - \frac{dV_L}{dt} R - V_L = 0$$

$$\frac{1}{RC} V_s = \underbrace{\frac{dV_L(t)}{dt}}_{\text{response}} + V_L(t) \cdot \frac{1}{RC} \quad \leftarrow \text{1st order diff. eq.}$$

System

to find  $V_L(t)$ :

- ① solve for  $V_{LH}(t)$   
Homogeneous
- ② guess  $V_{LP}(t)$
- ③ fit to initial conditions

2]

① Homogeneous solution: set response to 0

$$\rightarrow \frac{dV_o(t)}{dt} = -\frac{1}{RC} V_o(t)$$

$$\rightarrow \int \frac{dv}{v} = \int -\frac{1}{RC} dt$$

$$\rightarrow \ln v = -\frac{1}{RC} t + C$$

$$\rightarrow V_H = e^{-\frac{1}{RC} t + C} = K \cdot e^{-\frac{t}{RC}}$$

② Given Particular  $V_p = V_p(\infty) = V_s$

$$③ V_o(t) = V_{oH} + V_{op} = K e^{-t/RC} + V_s \quad \text{init condition } V_o(t=0) = 0$$

$$\rightarrow K = -V_s$$

$$\rightarrow V_o(t) = V_s (1 - e^{-t/RC})$$

\* Do transient check now!

Stored in capacitor at  $t = \infty$ ?

$$E = \int_{-\infty}^{\infty} I \cdot V \cdot dt$$


$$i_c(t) = C \frac{dV}{dt} = C \frac{V_s}{RC} e^{-t/RC} = \frac{V_s}{R} e^{-t/RC}$$

$$E = \int_0^{\infty} \frac{V_s}{R} (e^{-t/RC} - e^{-2t/RC}) dt$$

$$= \frac{V_s^2}{R} \left[ -RC e^{-t/RC} + \frac{1}{2} RC e^{-2t/RC} \right]_0^{\infty} = \frac{1}{2} CV_s^2$$

\* What about for other types of inputs? delta, ramp?

2nd order system

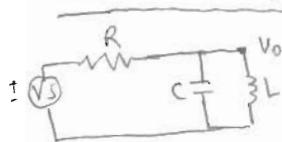

$$KCL: \frac{V_o - V_s}{R} + C \frac{dV_o}{dt} + \int \frac{V_o}{L} dt = 0$$

$$\rightarrow \frac{1}{R} \frac{dV_o}{dt} + C \frac{d^2V_o}{dt^2} + \frac{V_o}{L} = 0$$

$$\rightarrow \frac{d^2V_o}{dt^2} + \frac{1}{RC} \frac{dV_o}{dt} + \frac{V_o}{LC} = 0$$

$$\rightarrow x^2 + bx + c = 0, b = \frac{1}{RC}, c = \frac{1}{LC}$$

$$\rightarrow x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2}$$

graph undamped case: underdamped? check if  $\sqrt{b^2 - 4ac}$  = imaginary


$$V_o(t=0) = 0$$

$$V_o(t=\infty) = 0$$



3)

①

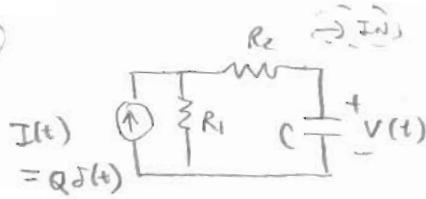

- i) Derive diff. eq. that relates  $V(t)$  to  $I(t)$   
hint: try Thevenin/Norton

$$\rightarrow I_N \quad \boxed{\frac{1}{R_N} \frac{1}{T} V_c} \quad R_N = R_1 + R_2$$

$$I_N = \frac{R_1}{R_1 + R_2} I(t)$$

by KCL:

$$\frac{1}{R_N} V(t) + C \frac{dV(t)}{dt} - I_N(t) = 0$$

- b) find  $V(t)$  for  ~~$t=0^+$~~  &  $t \geq 0$

f

$$\rightarrow \frac{dV}{dt} + \frac{1}{R_N C} V(t) = \frac{1}{C} I_N(t) \quad V(0^+) = 0$$

$$\rightarrow \int_0^{0^+} dV + \frac{1}{R_N C} \int_0^{0^+} V(t) dt = \frac{1}{C} \int_0^{0^+} I_N(t) dt$$

$$\rightarrow V(t) \Big|_{0^-}^{0^+} + 0 = \underbrace{\frac{1}{C} \cdot \frac{R_1}{R_1 + R_2} Q}_{\text{since } V(t) \text{ is finite}} , \quad \int_0^{0^+} V(t) dt = 0$$

$$\rightarrow V(0^+) =$$

$$\boxed{V(0^+) = 0}$$

since  $V(t)$  is finite &  
integral over 0 time = 0.  
we know  $V(t)$  finite since  
 $I(t)$  delivers a finite  
amt of charge.

c)  $\tau = ? \quad \tau = R_N \cdot C$



d)  $v(t) \quad t \geq 0 \quad v(t) \text{ solving eqn}$

$$\boxed{v(t) = \frac{R_1}{R_1 + R_2} \cdot \frac{Q}{C} \cdot e^{-t/\tau}}$$

Diode bridge:


Full wave rectifier.

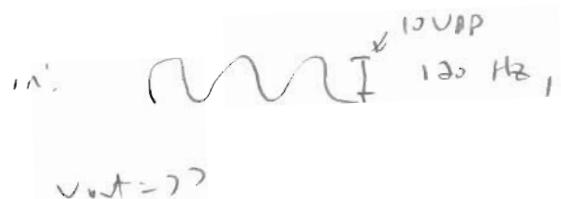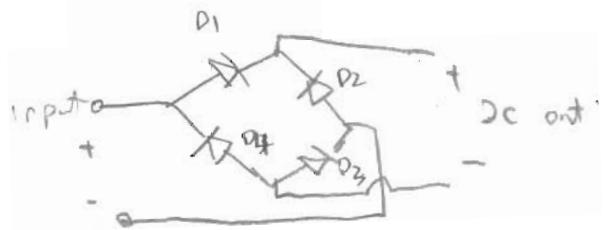$V_{\text{Forward}} = 0.7$  unless specified





$$V_{\text{Forward}} = 0$$



$$V_{\text{in}} > 0$$

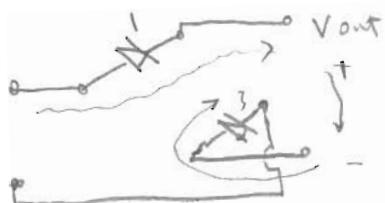

$$V_{\text{in}} < 0$$

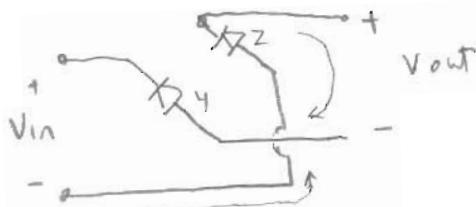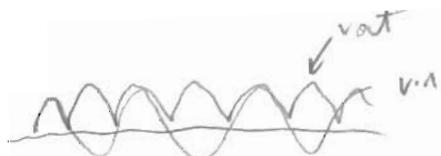


Load Lines:

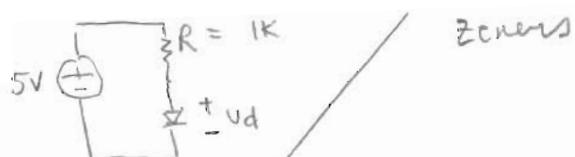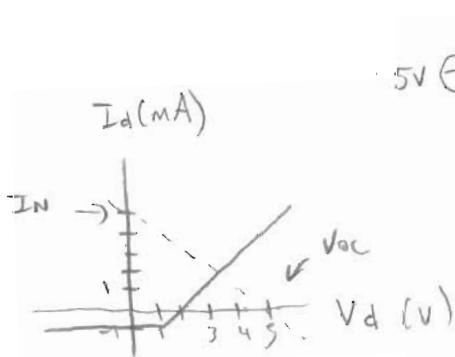


What does the zener do?


#### 4) Transistors:

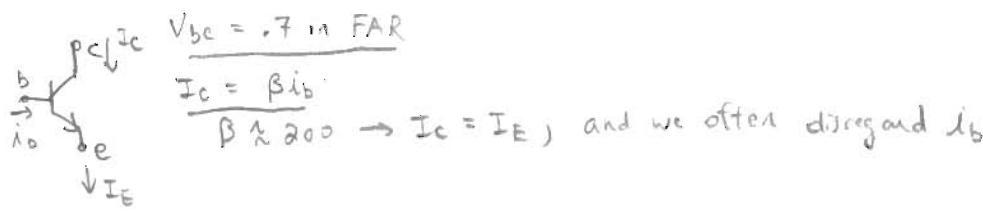

Ex:  $V_o = ?$

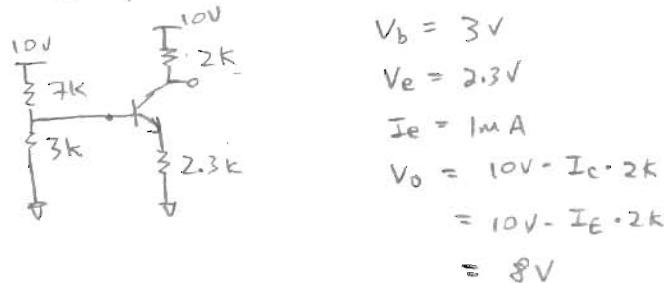

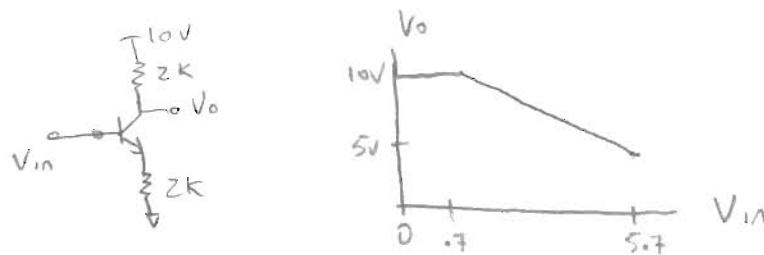Ex: Draw  $V_o$  for  $0 < V_{IN} < 5.7V$



$$V_e = V_{IN} - .7$$

$$I_E = \frac{V_{IN} - .7}{2k}$$

$$V_{OUT} = 10V - 2k \cdot I_E$$

$$= 10V - V_{IN} + .7$$

$$= 10.7 - V_{IN} \quad \text{for } V_{IN} \geq .7V \quad (\text{turn on BJT})$$

Ex: Load Lines

