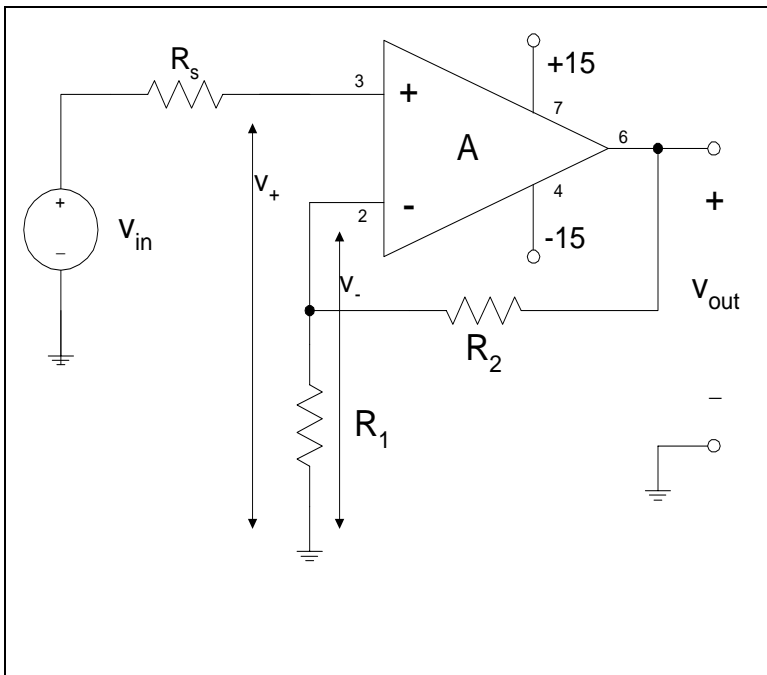


NON-INVERTING AMPLIFIER GAIN DERIVATION with FINITE OPEN LOOP GAIN ANALYSIS

ASSUMPTIONS: INFINITE INPUT IMPEDANCE: $\therefore i_+ = 0; \quad i_- = 0$
 ZERO VOLTAGE DROP BETWEEN INPUTS, and $A = \infty$.
 ZERO AC INPUT CURRENT.

ASSUMPTIONS HOLD FOR $A \gg A_v = 1 + \frac{R_2}{R_1}$



Let $R_s = 0$; Therefore $v_+ = v_{in}$

$$v_- = \frac{R_1}{R_1 + R_2} \times v_{out}; \quad \text{but } v_+ = v_-$$

$$\text{so } v_{in} = \frac{R_1}{R_1 + R_2} \times v_{out};$$

$$\frac{v_{out}}{v_{in}} = \frac{R_1 + R_2}{R_1}$$

$$\text{or } A_v = 1 + \frac{R_2}{R_1}$$

FINITE OPEN-LOOP GAIN ANALYSIS:

$$v_{out} = A v_{id} = A(v_+ - v_-) = A(v_{in} - v_-); \quad v_- = \frac{R_1}{R_1 + R_2} v_{out} = \beta v_{out} \quad \text{where } \beta = \frac{R_1}{R_1 + R_2}.$$

β is called the feedback transfer function and represents the fraction of the output voltage that is fed back from the output to the input. Combining the equations above gives:

$$v_{out} = A[v_{in} - \beta v_{out}]; \quad v_{out} + A\beta v_{out} = Av_{in}; \quad \frac{v_{out}}{v_{in}} = A_v = \frac{A}{1 + A\beta}$$

This gives the classic negative feedback amplifier gain expression. The product $A\beta$ is called the loop gain or loop transmission. For $A\beta \gg 1$, A_v approaches the ideal gain expression found above $[=1/\beta]$. In reality, A is a function whose value decreases with increasing frequency, until, at some point when $A\beta$ is no longer $\gg 1$, the ideal gain equation, a function of only two resistor values, no longer

applies. A_v drops at those high frequencies where the value of A approaches the value of A_v . [Note: $A = A_{vol}$]