

Massachusetts Institute of Technology  
6.101 Analog Electronics Lab  
Spring 2007  
Problem Set 2  
Due Wednesday, February 28, 2007

---

Refer to Chapters 2 and 5 of *Circuit Analysis and Design, 3<sup>rd</sup> Edition*  
by Donald Neamen for text that supports this problem set.  
Remember to use 5% standard resistor values. Assume  $V_T=26\text{mV}$

---

**Problem 1.** Neamen 5.27 (2<sup>nd</sup> ed: 3.16)

**Problem 2.** This problem refers to Figure 1. You are told that  $V_A$  is set so that  $V_{\text{OUT}} = 50\text{mV}$ . If  $v_a = 6\sin(100t)$  mV, then what is  $v_{\text{out}}$ ? What is  $v_{\text{OUT}}$ ?

**Problem 3.** This problem refers to Figure 2.

(a) Choose R so that the transistor is biased with  $I_C = 4\text{mA}$ , assuming  $V_{\text{BE}} = 0.6\text{V}$ , and  $\beta$  is large. Remember to use a standard value.

(b) You get a really bad transistor with  $\beta=10$ . If you use the design from part (a), what will  $I_C$  be, assuming  $V_{\text{BE}} = 0.6\text{V}$ ?

**Problem 4.** Neamen 5.42 (2<sup>nd</sup> ed: 3.32)

**Problem 5.**

(a) It is often the case the DC bias stability is achieved by placing a resistor at the emitter connection of a BJT (for example, this is done in Figure 2 with a 100ohm resistor). However, this resistance drastically decreases the overall gain of Common Emitter circuits. If our input is a small signal AC wave, what can be added to the emitter connection to allow for higher values of gain while not affecting the DC bias stability of the circuit?

(b) What determines the Q-point when doing load line analysis? What factors should be considered when deciding on a Q-point? What are the x and y intercepts of the load line?

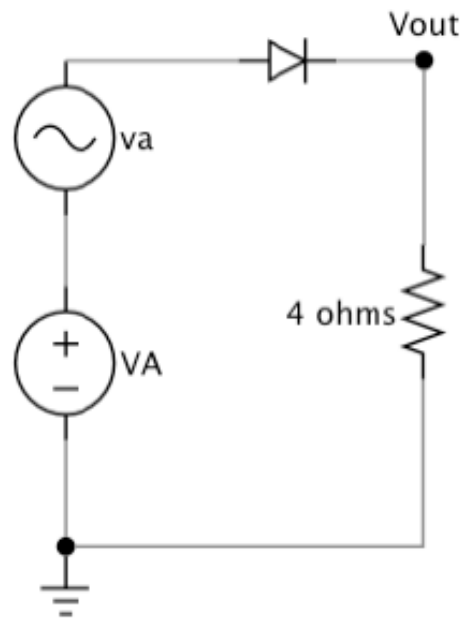


Figure 1: Figure for Problem 2

 


Figure 2: Figure for Problem 3