

6.111 Lecture # 6

VHDL Statements

Concurrent

Signal assignment

Instantiation

When-Else

With-Select-When

Process (used as wrapper for sequential statements)

Sequential (must be inside a process)

Signal assignment

If-Then-Elsif-Else

Case-When

Concurrent Statements

Signal assignment:

```
outc <= ina AND (inb OR inc);
```

Instantiation:

```
h1: halfadd PORT MAP (a => ina, b => inb,  
                      sum => s1, c => s3);    -- named association
```

Or:

```
h1: halfadd PORT MAP (ina, inb, sum, c);    -- positional association
```

With-Select-When (Note: always use OTHERS as there are values other than '0' and '1')
Select conditions must be mutually exclusive and exhaustive

```
WITH inc SELECT
```

```
  outc <= ina WHEN '0',  
    inb WHEN '1',  
    inb WHEN OTHERS;
```

Process Statement

A process is concurrent with other concurrent statements

Multiple processes are possible in an architecture

A process is a wrapper for sequential statements

Sequential statements model combinational or synchronous logic (or both)

Statements within a process are 'executed' sequentially (but use care in interpreting this statement)

Signal assignments can be both sequential and concurrent

'Variables' may be declared within a process (more later)

Signals must be declared outside of the process

Process Syntax:

```
label: PROCESS (sensitivity list)  
    VARIABLE -- declarations  
BEGIN  
    -- sequential statements  
END PROCESS label;
```

Process label and variable declarations are optional:

```
PROCESS (sensitivity list)  
BEGIN  
    -- sequential statements  
END PROCESS;
```

Sensitivity list is there for simulation:

When simulated, the process is executed when something in that list changes

Sensitivity list is not synthesized in actual logic (except for the use of clocks)

Sequential Statements

Signal Assignment

```
outc <= ina AND (inb or inc);
```

If-then-elsif-else

```
IF      inc = '0' THEN outc <= ina;  
ELSIF  inc = '1' THEN outc <= inb;  
          ELSE outc <= inc;  
END IF;
```

Case-When:

```
CASE inc IS  
  WHEN '0'      => outc <= ina;  
  WHEN '1'      => outc <= inb;  
  WHEN OTHERS  => outc <= ind;  
END CASE;
```

There are other sequential statements which we won't use. See the book if you are curious (various LOOP statements, etc.)

Basic Operators

Logical (use ieee.std_logic_1164.all)

AND, OR, NAND, NOR, XOR, XNOR, NOT

Relational (use ieee.std_logic_1164.all)

=, /=, <, >, <=, >=

(note that <= and => have other meanings too)

Arithmetic:

**+, - (* too, but it can't be synthesized)
- is defined for unary arithmetic too**

Concatenation -- defined for strings and signal values

&

Simulation vs. Synthesis

**Synthesis is to produce hardware that does what the statements specify
(processes as well as other concurrent statements)**

**Simulation is used to produce outputs from specified input signals
Concurrent statements are evaluated whenever any input changes
If evaluation of a concurrent statement changes the input to a concurrent
statement, that statement is evaluated**

**Processes: you must list conditions that initiate evaluation of the process
(we use the sensitivity list for this purpose)
All signals in the process are updated when the process finishes
(NOT when each sequential statement is executed)**

Synthesis ignores this sensitivity list

What will synthesis do with this?

```
library ieee;  
use ieee.std_logic_1164.all;  
entity reg is
```



```
  port (  
    a, clk : in std_logic;  
    c      : out std_logic);
```

```
end reg;  
architecture top of reg is  
  signal b : std_logic;  
begin -- top
```

```
  reg2: process (clk)  
  begin -- process  
    if rising_edge(clk) then  
      b <= a;  
      c <= b;  
    end if;  
  end process;
```

```
end top;
```

  Will this generate one or two flip flops?



Well, here is what it did, from the .rpt file:

DESIGN EQUATIONS (16:16:54)

$$c.D = b.Q$$

$$c.C = \text{clk}$$

$$b.D = a$$

$$b.C = \text{clk}$$

Implicit Memory - Latch example

```
library ieee;
use ieee.std_logic_1164.all;
entity reg is
    port (d, g: in std_logic;
          q : out std_logic);
end reg;

architecture top of reg is

begin
    process(d, g)
    begin
        IF g = '1' then q <= d;
            -- notice there is no ELSE
        end IF;
    end process;
end top;
-- this produces  $q = /g * q + d * g$  (mind your g's and q's!)
```

Explicit Memory: Latch (same function, different architecture)

```
library ieee;
use ieee.std_logic_1164.all;
entity reg is
    port (d, g: in std_logic;
          q : out std_logic);
end reg;

architecture top of reg is
    signal s1: std_logic;

begin
    q <= s1;
    s1 <= d when g = '1' else s1;
end top;
```

Explicit Memory: Latch (same function, yet another architecture)
(note this is more verbose than the prior)

```
library ieee;
use ieee.std_logic_1164.all;
entity reg is
    port (d, g: in std_logic;
          q   : out std_logic);
end reg;

architecture top of reg is
    signal s1: std_logic;

begin
    process (s1, d, g)
    begin
        if g = '1' then s1 <= d;
        else s1 <= s1;
        end if;
    end process;
end top;
```

Clocked Register (implicit memory): This is a T-ff

```
library ieee;
use ieee.std_logic_1164.all;
entity clked_t is
    port (t, clk : in std_logic;
          q      : out std_logic);
end clked_t;

architecture top of clked_t is
    signal s1: std_logic;
begin
    q <= s1;
    process (clk, s1)
    begin
        if rising_edge(clk) then
            if t = '1'
                then s1 <= NOT s1;
            end if;
        end if;
    end process;
end top;
-- this produces q.D = t*/q.Q + /t*q.Q
--                and q.C = clk
```

Clocked Register (explicit memory): This is a T-ff

```
library ieee;
use ieee.std_logic_1164.all;
entity clked_t is
    port (t, clk : in std_logic;
          q       : out std_logic);
end clked_t;

architecture top of clked_t is
    signal s1: std_logic;
begin
    q <= s1;
    process (clk, s1)
    begin
        if rising_edge(clk) then
            if t = '1'
                then s1 <= NOT s1;
                else s1 <= s1;
            end if;
        end if;
    end process;
end top;
-- this produces q.D = t*/q.Q + /t*q.Q
--                and q.C = clk
```

Example: build a counter

```
library ieee;
use ieee.std_logic_1164.all;
use work.std_arith.all;
entity ctr is
    generic (width: integer := 4); -- allows to change width easily


port(
    clk: in std_logic;
    n_clr, n_ld, enp, ent: in std_logic;
    data in std_logic_vector (width-1 downto 0);
    cnt out std_logic_vector (width-1 downto 0);
    rco out std_logic);
end ctr;
```

Note we are using generic to define a number which we can easily redefine once we get the thing working. This is the entity for this counter. The architecture comes next.

```
Architecture behavioral of ctr is
signal intcnt, allones: std_logic_vector (width-1 downto 0);
begin
clocked: process (clk)
begin
    if rising_edge(clk) then
        if n_clr = '0' then
            intcnt <= (others => '0');
        elsif n_ld = '0' then
            intcnt <= data;
        elsif (enp = '1') and (ent = '1') then
            intcnt <= intcnt +1;
        end if;
    end if;
end process clocked;
allones <= (others => '1');
zco <= '1' when ((ent = '1') AND (intcnt = allones))
    else '0';
cnt <= intcnt;
end behavioral;
```

Construction of a finite state machine in VHDL

 Binary divide by 5, bitwise. This is a simple FSM for which current state is the running remainder. Output is the bit by bit dividend.



Here is a suitable entity declaration:

```
library ieee;
use ieee.std_logic_1164.all;
use work.std_arith.all;
entity divby5 is port
(
    x, clk : in std_logic;
    y      : out std_logic);
end divby5;
```

```

architecture state_machine if divby5 is
    type StateType is (state0, state1, state2, state3, state4);
    signal p_s, n_s : StateType;
begin
    fsm: process (p_s, x)
    begin
        case p_s is
            when state0 => y <= '0';
                if x = '1' then
                    n_s <= state1;
                else
                    n_s <= state0;
                end if;
            when state1 => y <= '0';
                if x = '1' then
                    n_s <= state3;
                else
                    n_s <= state2;
                end if;
            when state2 =>
                if x = '1' then
                    n_s <= state0;
                    y <= '1';
                else

```

Continued next slide...

```

        n_s <= state4;
        y <= '0';
    end if;
    when state3 => y <= '1';
    if x = '1' then
        n_s <= state2;
    else
        n_s <= state1;
    end if;
    when state4 => y <= '1';
    if x = '1' then
        n_s <= state4;
    else
        n_s <= state3;
    end if;
    when others => n_s <= state0; -- avoid trap states
end case
end process fsm;
state-clocked : process (clk)
begin
    if rising_edge(clk) then
        p_s <= n_s;
    end if;
end process state_clocked;
end architecture state_machine;

```