 


6.111 Lecture # 7

Take another look at that divide by five FSM.



Progression Through States

x	p_s	n_s	y
1	0	1	0
0	1	2	0
1	2	0	1
1	0	1	0
1	1	3	0
1	3	2	1
1	2	0	1

Here is, roughly what we would expect from the Mealey machine model of that thing with inputs and outputs as specified

Here is the VHDL code from last time, crowded onto a single sheet:

```


library ieee;
use ieee.std_logic_1164.all;
use work.std_arith.all;
entity divby5 is port
    (
        x, clk : in std_logic;
        y      : out std_logic);
end divby5;
architecture state_machine if divby5 is
    type StateType is (state0, state1, state2, state3,
state4);
    signal p_s, n_s : StateType;
begin
    fsm: process (p_s, x)
    begin
        case p_s is
            when state0 => y <= '0';
                if x = '1' then
                    n_s <= state1;
                else
                    n_s <= state0;
                end if;
            when state1 => y <= '0';
                if x = '1' then
                    n_s <= state3;
                else
                    n_s <= state2;
                end if;

```

```

            when state2 =>
                if x = '1' then
                    n_s <= state0;
                    y <= '1';
                else
                    n_s <= state4;
                    y <= '0';
                end if;
            when state3 => y <= '1';
                if x = '1' then
                    n_s <= state2;
                else
                    n_s <= state1;
                end if;
            when state4 => y <= '1';
                if x = '1' then
                    n_s <= state4;
                else
                    n_s <= state3;
                end if;
            when others => n_s <= state0;
        -- avoid trap states
        end case
    end process fsm;
    state-clocked : process (clk)
    begin
        if rising_edge(clk) then
            p_s <= n_s;
        end if;
    end process state_clocked;
end architecture state_machine;

```

 


Modification to register the output:

```
library ieee;
use ieee.std_logic_1164.all;
use work.std_arith.all;
entity divby5 is port
    (
        x, clk : in std_logic;
        y      : out std_logic);
end divby5;

architecture state_machine of divby5 is
    type StateType is (state0, state1, state2, state3,
state4);
    signal p_s, n_s : StateType;
    signal ans : std_logic := '0'; -- new
begin
    fsm: process (p_s, x)
    begin
        case p_s is
            when state0 => ans <= '0';
                if x = '1' then
                    n_s <= state1;
                else
                    n_s <= state0;
                end if;
            when state1 => ans <= '0';
                if x = '1' then
                    n_s <= state3;
                else
                    n_s <= state2;
                end if;
        end case;
```

```
        when state2 =>
            if x = '1' then
                n_s <= state0;
                ans <= '1';
            else
                n_s <= state4;
                ans <= '0';
            end if;
        when state3 => ans <= '1';
            if x = '1' then
                n_s <= state2;
            else
                n_s <= state1;
            end if;
        when state4 => ans <= '1';
            if x = '1' then
                n_s <= state4;
            else
                n_s <= state3;
            end if;
        when others => n_s <= state0; -- avoid
    end case;
end process fsm;
state_clocked : process (clk)
begin
    if rising_edge(clk) then
        p_s <= n_s;
        y <= ans;    -- register output
    end if;
end process state_clocked;
end architecture state_machine;
```

 

On simulation, we note that:


- 1. Each of the output bits is one clock cycle long**
- 2. But the output is delayed one clock cycle**

Topics for today

Certain issues in timing and handling pulse like signals

Lab 2

Consider a simple finite state machine:

 

		Q1 Q0			
		00	01	11	10
u	0	0	0	X	0
	1	0	1	X	1

$$D1 = u \cdot Q0 + u \cdot Q1$$

		Q1 Q0			
		00	01	11	10
u	0	0	0	X	1
	1	1	0	X	0


$$D0 = u \cdot /Q0 \cdot /Q1 + /u \cdot Q1$$

This is a very small up/down counter

The logic is straightforward to design

Note it has two flip flops but does not use all four states

 Here is a simple implementation, easily implemented in TTL



But look at a possible timing issue:

IF we are in state 10

IF $u = 1$, we stay in state 10

IF $u=0$, we go to state 01



IF $u=0$ and then makes a transition to 1, we still want to stay in state 10

BUT if $u=0$ and then makes a transition to 1 too close to the clock edge,

The transition of D0 from 1 to 0 is delayed with respect to D1

(by one gate delay)

  
And if this happens the thing goes into a state it isn't supposed to



Design Rule:

 - 1. Synchronize ALL external signals**
- 2. Any asynchronous input must affect ONLY ONE flip-flop (which is switched synchronously with all of the other flip-flops)**

"Metastable" problem: if input is too close to an edge, the next state is not well determined.




But if inputs are synchronized according to the rule, the (single) FF will make the transition on the NEXT clock edge

Timing techniques

One problem is to catch a signal that may be shorter than your clock cycle.

Catch an edge or a short pulse

 

Note that here we have one use for the S-R latch.

This does well at catching a very short pulse, but if \overline{GO} is low for several clock cycles, P will have several pulses.


You might want to think about how to design a circuit which takes a \overline{GO} signal of arbitrary length and produces a **SINGLE** pulse in response.

Here is a candidate for that

It generates a single pulse (one clock cycle wide)

But note that A has to be asserted on a positive going clock edge

 Or turn a level into a finite-width pulse:



VHDL Code for short pulse catcher

```
library ieee;
use ieee.std_logic_1164.all;
entity spulse is
    port(N_GO, CLK, CLKIN: in std_logic;
         P: out std_logic);
end spulse;

-- purpose: catch a short pulse
architecture behavioral of spulse is
    signal A, N_A, X, N_X, N_CLK: std_logic;
    attribute synthesis_off of A: signal is true;
    attribute synthesis_off of N_A: signal is true;
begin -- behavioral
    A <= (not N_GO) or (not N_A);
    N_A <= (not A) or (not N_X);
    N_X <= (not X);
    P <= X and N_CLK;
    N_CLK <= (not CLKIN);
ff: process(CLK)
begin
    if rising_edge(CLK) then
        X <= A;
    end if;
end process ff;
end behavioral;
```

Note the rather odd looking syntax here: using the attribute `synthesis_off` tells the compiler to not optimize away the latch

This combinatoric part of the code describes the SR latch and the output


The process describes the d- flip-flop

VHDL Code for pulse shaper

```
library ieee;
use ieee.std_logic_1164.all;
entity pform is
    port(A, CLK, CLKIN: in std_logic;
         P: out std_logic);
end pform;

-- purpose: catch a short pulse
architecture behavioral of pform is
    signal X, N_Y: std_logic;
begin -- behavioral
ff: process(CLK)
begin
    if rising_edge(CLK) then
        X <= A;
        N_Y <= (NOT X);
    end if;
end process ff;
    P <= (X AND N_Y);
end behavioral;
```

 Lab 2 assignment is yet another traffic light
This time you control it
It looks like a familiar situation
Main and side streets, with a walk light on demand



Main street part of cycle is longer than side street
($T_{base} + T_{ext}$)

But side street has a traffic sensor which keeps it green a bit longer. (T_{ext})

Traffic sensor must be synchronized.

Walk button must be latched and serviced at the right time, and unlatched after it has been serviced

Details: walk is R-Y.
Blink is Main Y, Side R,
ON/OFF, equal intervals (T_{blink}).

Design Procedure:

Start with a simple block diagram


Break design down into more, simpler blocks

Here is a top level block diagram for a controller

Inputs

Outputs (light signals)

 
Note this GO signal is similar to what we were discussing earlier: a single pulse in response to a pushbutton (which could be any length)



This is a conceptual developed block diagram for the machine

The FSM should be implemented in a CPLD

 We want you to use REAL RAM, do not include it in your CPLD



The Hex LED's are used to examine memory

It is your call if you want to implement the timer and divider in the CPLD (We expect you probably will want to do it this way)

Inputs To Your FSM:

RESET	(from a switch)
GOSYNC	(from Synchronizer)
F1, F0	Function Selection (from switches)
L1, L0	RAM Address
Sensor	Traffic Sensor (synchronized from a switch)
WR	Walk Request (Re-settable latch from pushbutton)
EXPIRED	Signal that timer has timed out

Outputs From Your FSM

A1, A0	SRAM Address
WE	SRAM Write Enable (source of bus signal)
StartTimer	Resets 1 second increment timer
Gm, Ym, Rm, Gs, Ys, Rs	Traffic light control signals

Control Specifications

Here are the functions your controller must implement

F1 F0	are the function control switches
0 0	Examine Memory Location Specified by Switches
0 1	Store Value in Memory Location Specified by Switches
1 0	Run Traffic Lights
1 1	Blink

And for writing to or examining memory (functions 0 and 1) you should use these addresses:

A1 A0	
0 0	TYEL Time for yellow light
0 1	TBASE Base interval
1 0	TEXT Extension interval
1 1	TBLINK Blink Interval