

L11: Major/Minor FSMs




Acknowledgements: Rex Min


- Quiz will be **Closed Book Tuesday, March 21, 2006**, 7:30pm-9:30pm Covers Problem Sets 1-3, Lectures 1-10 (through Analog), Labs 1-3
- Some of the topics to be covered include
 - Combinational Logic: Boolean Algebra, Karnaugh Maps, MSP, MPS, dealing with don't cares
 - Latches and Edge Triggered Registers/Flip-flops
 - Understand the difference between latches, registers and unclocked memory elements (e.g., SR-Flip Flop)
 - Different memory types: SR, D, JK, T
 - Understand setup/hold/propagation delay and how they are computed
 - System Timing (minimum clock period and hold time constraint)
 - Impact of Clock skew on timing
 - Counters and simple FSMs (understand how the '163 and '393 work)
 - FSM design (Mealy/Moore, dealing with glitches)
 - Combinational and sequential Verilog coding
 - Continuous assignments, blocking vs. non-blocking, etc.

- **Tri-states basics**
- **Dealing with glitches**
 - When are glitches OK?
 - How do you deal with glitches in digital system design? (registered outputs, appropriate techniques to gate a clock, etc.)
- **Memory Basics**
 - Understand differences between DRAM vs. SRAM vs. EEPROM
 - Understand timing and interfacing to the 6264
- **Arithmetic**
 - Number representation: sign – magnitude, Ones complement, Twos complement
 - Adder Structures: Ripple carry, Carry Bypass Adder, Carry Lookahead Adder
 - False Paths and Delay Estimation
 - Shift/add multiplier, Baugh-Wooley Multiplier (Twos complement multiplication)
- **Analog Design**
 - Basics of ADC and DAC, interfaces


- Consider the following abstract FSM:

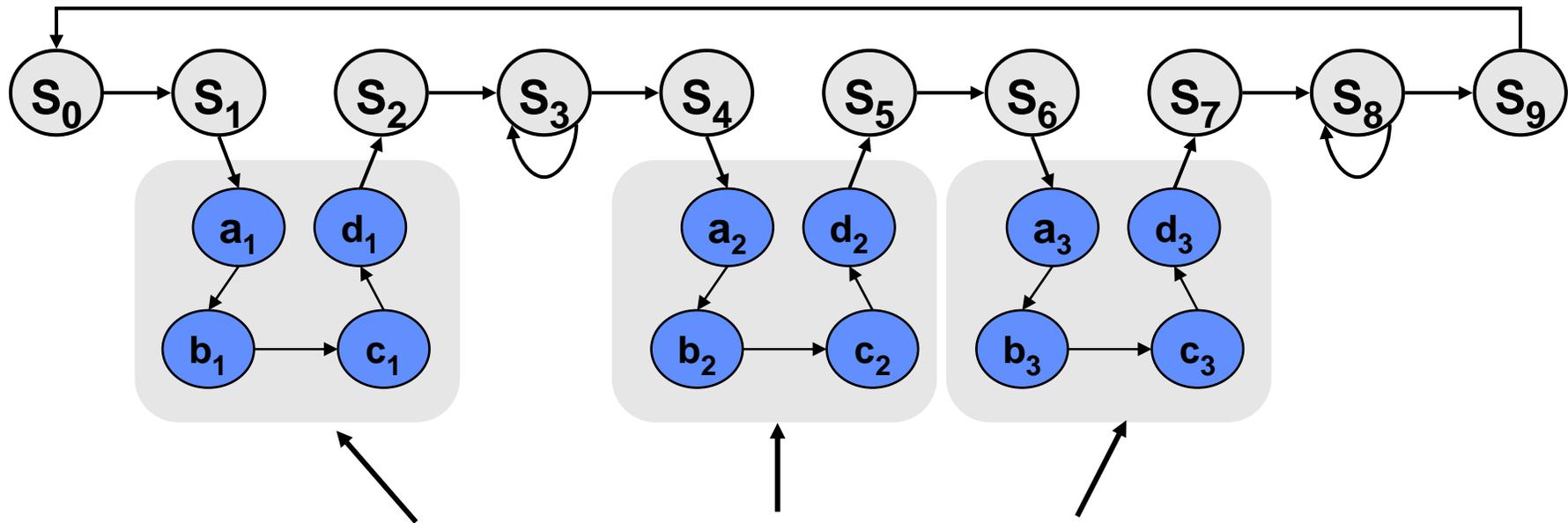

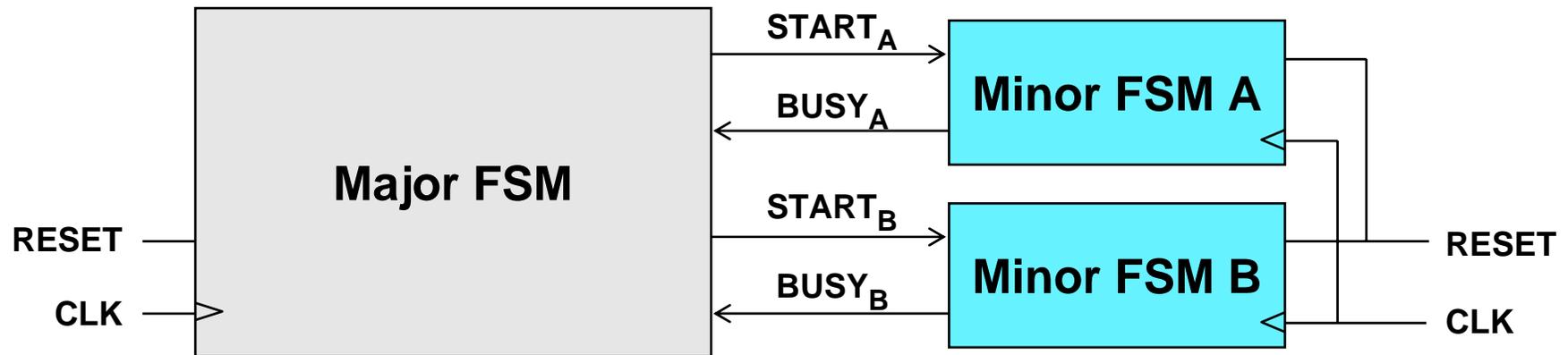- Suppose that each set of states $a_x \dots d_x$ is a “sub-FSM” that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?
No! The outputs may be the same, but the next-state transitions are not.
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?




- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
 - **START**: tells the minor FSM to begin operation (the call)
 - **BUSY**: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
 - Modular designs (*always* a good thing)
 - Tasks that occur often but in different contexts
 - Tasks that require a variable/unknown period of time
 - Event-driven systems


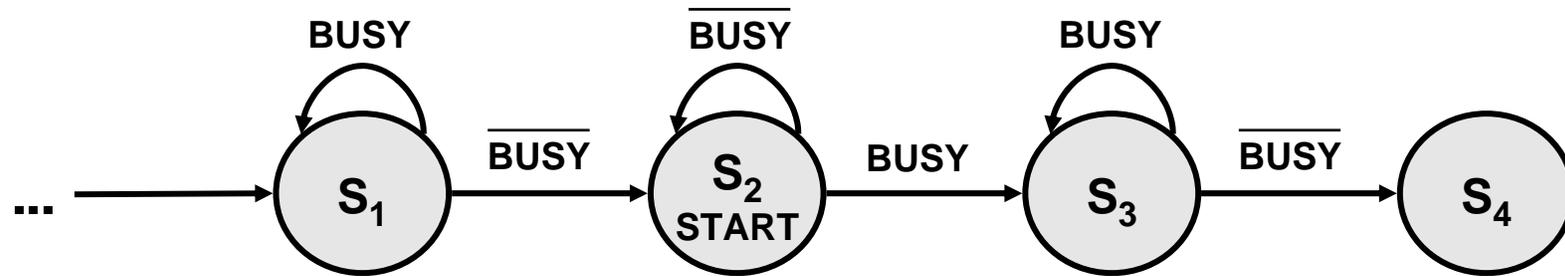


1. Wait until the minor FSM is ready


2. Trigger the minor FSM (and make sure it's started)

3. Wait until the minor FSM is done

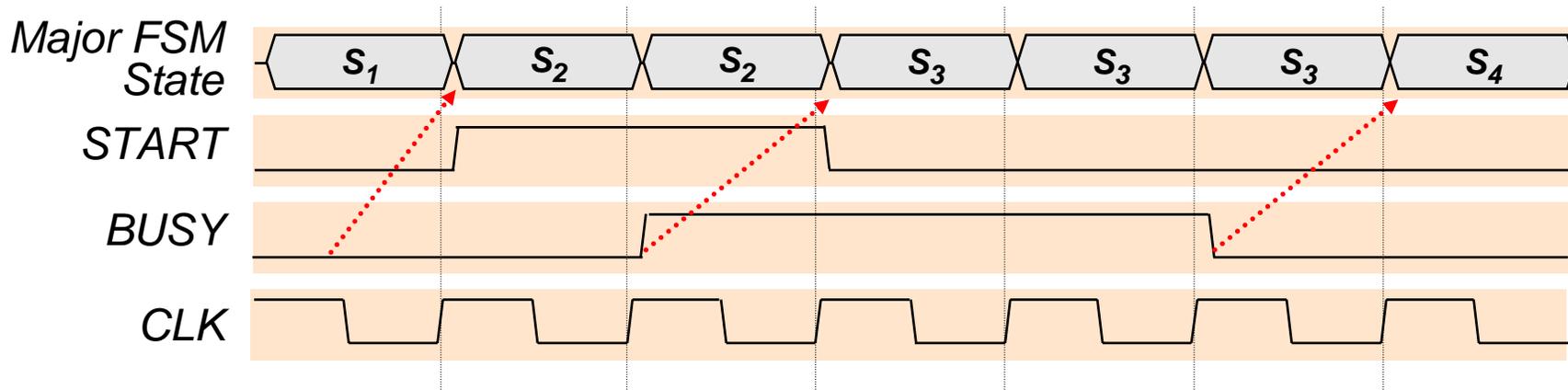

  


 Good idea: de-assert BUSY one cycle early




Bad idea #1:


T_4 may not immediately return to T_1

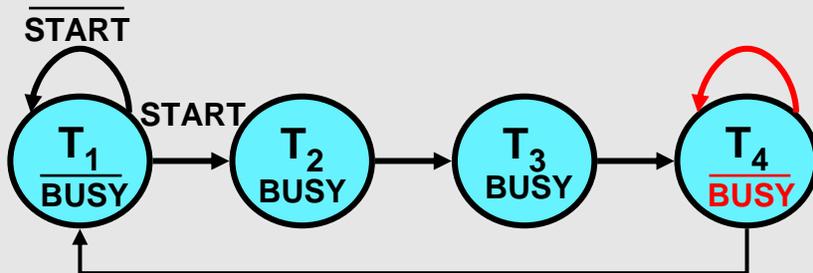

Bad idea #2:


BUSY never asserts!

 

 

Operating Scenario:

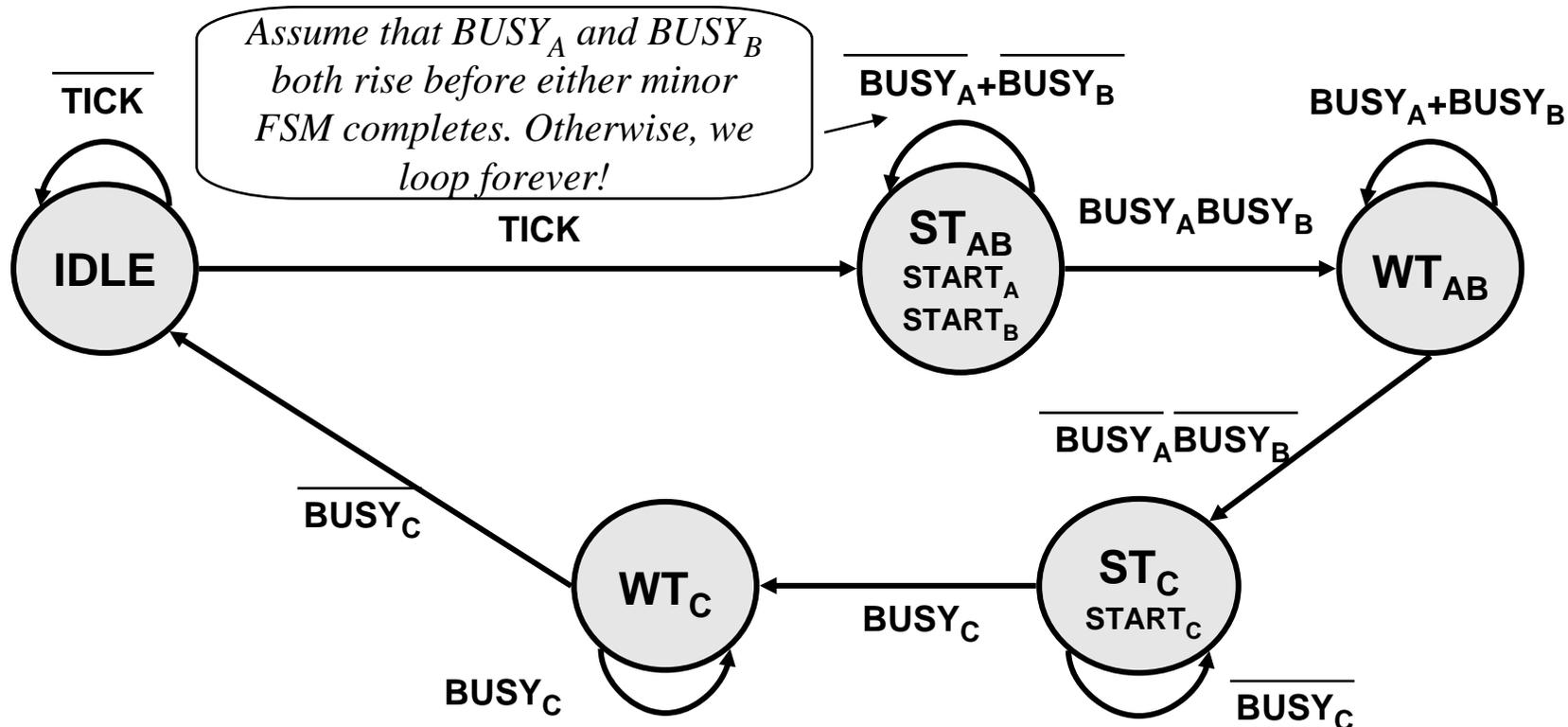- Major FSM is triggered by TICK
- Minors A and B are started simultaneously
- Minor C is started once both A and B complete
- TICKs arriving before the completion of C are ignored



Four-FSM Sample Waveform

