

L2: Combinational Logic Design


(Construction and Boolean Algebra)



Acknowledgements:



Materials in this lecture are courtesy of the following people and used with permission.

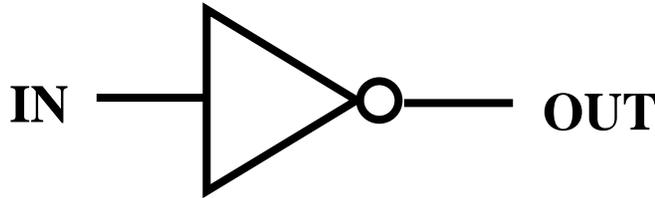- Randy H. Katz (University of California, Berkeley, Department of Electrical Engineering & Computer Science)
- Gaetano Borriello (University of Washington, Department of Computer Science & Engineering, <http://www.cs.washington.edu/370>)
- Rabaey, A. Chandrakasan, B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice Hall, 2003.



Truth Table

IN	OUT
0	1
1	0

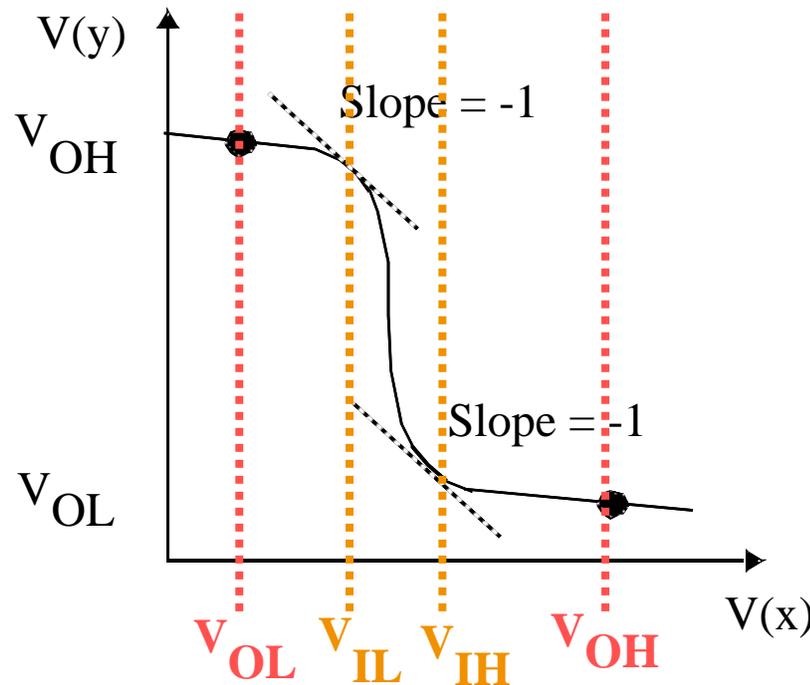
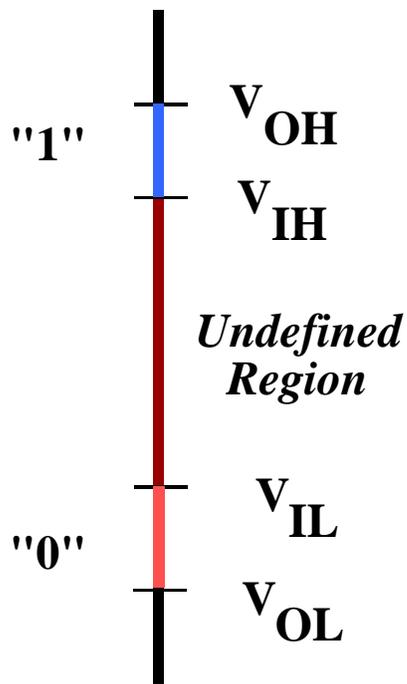


$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$


- Large noise margins protect against various noise sources

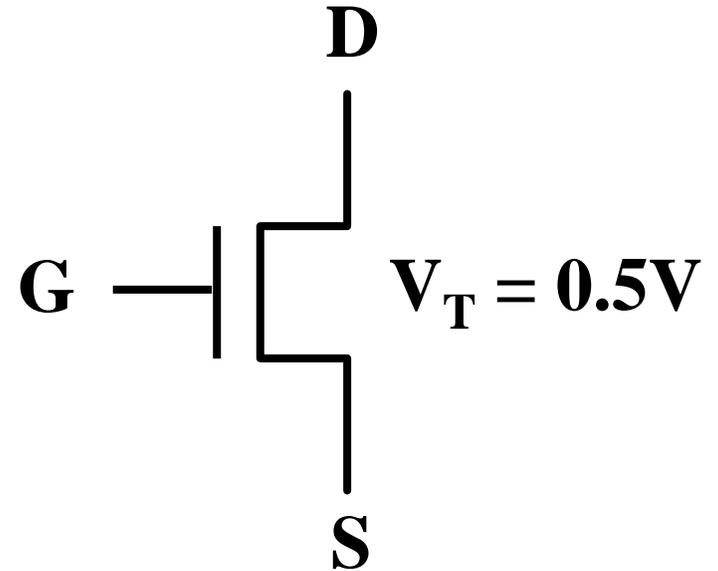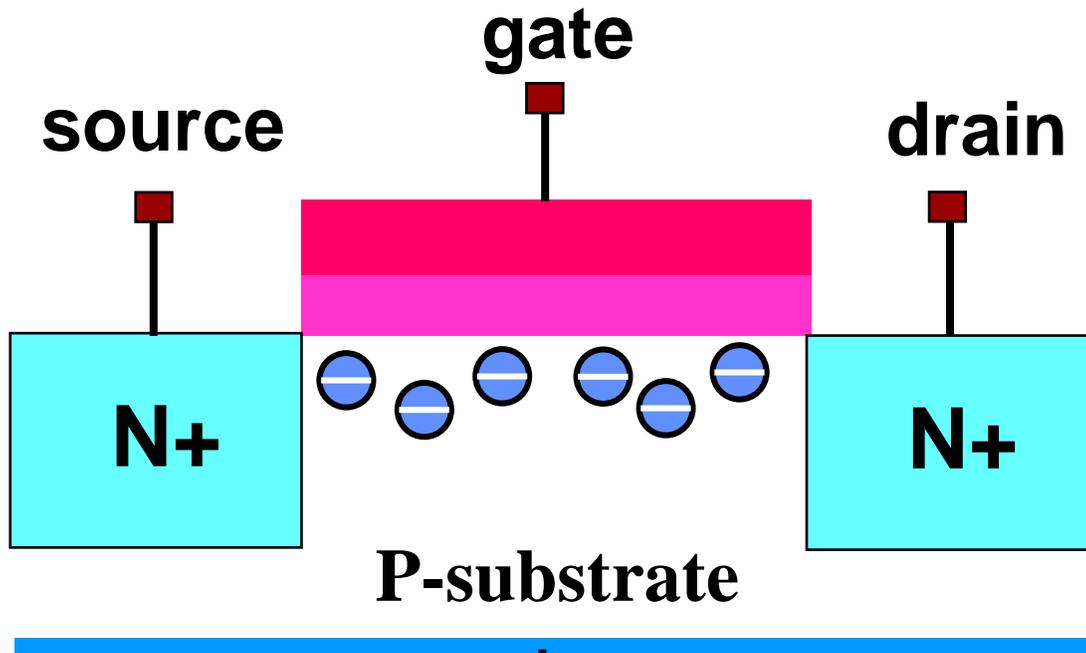74LS04 (courtesy Texas Instruments)
Image removed due to copyright restrictions




Switch Model

OFF


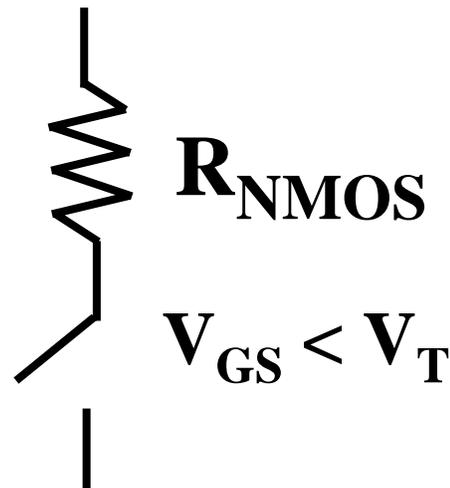


ON


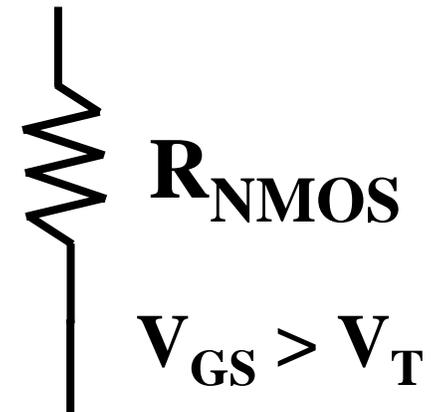


NMOS ON when Switch Input is High

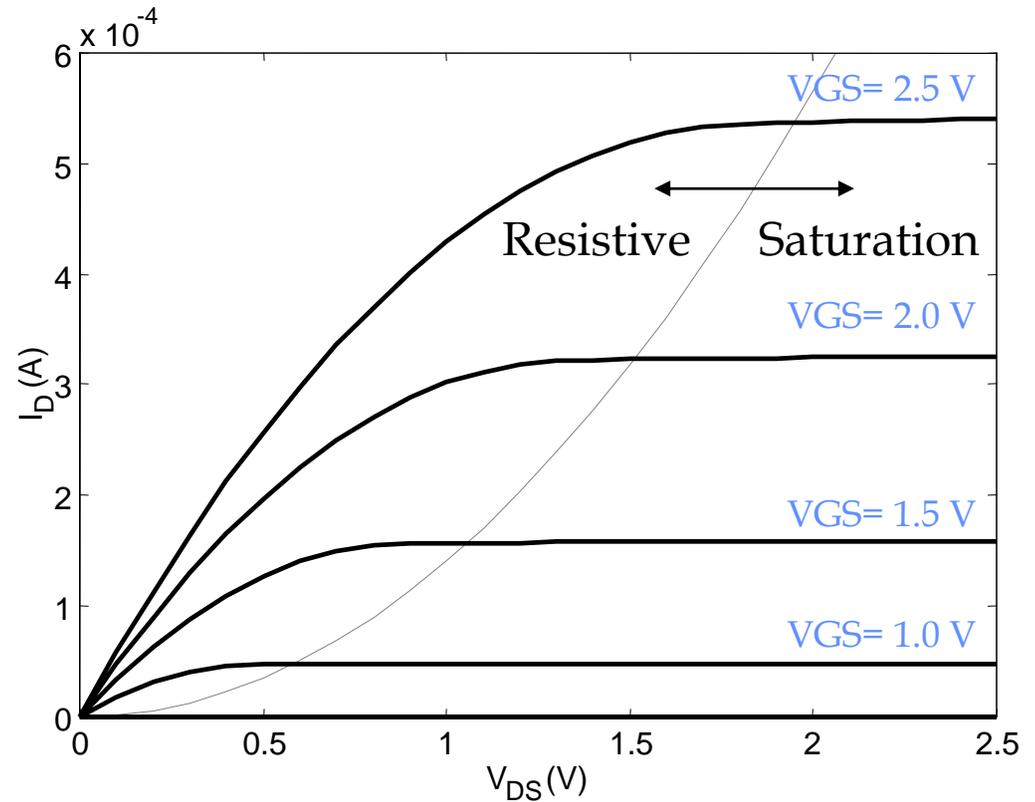
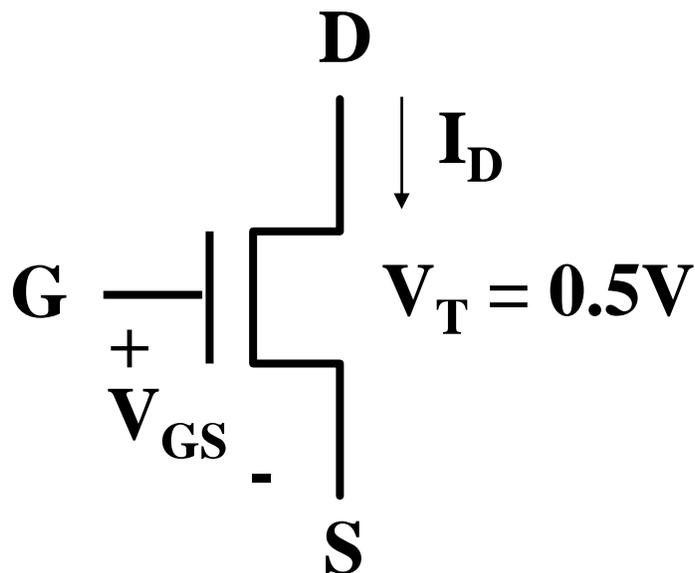
Picture of an NMOS Device
 Picture removed due to copyright restrictions



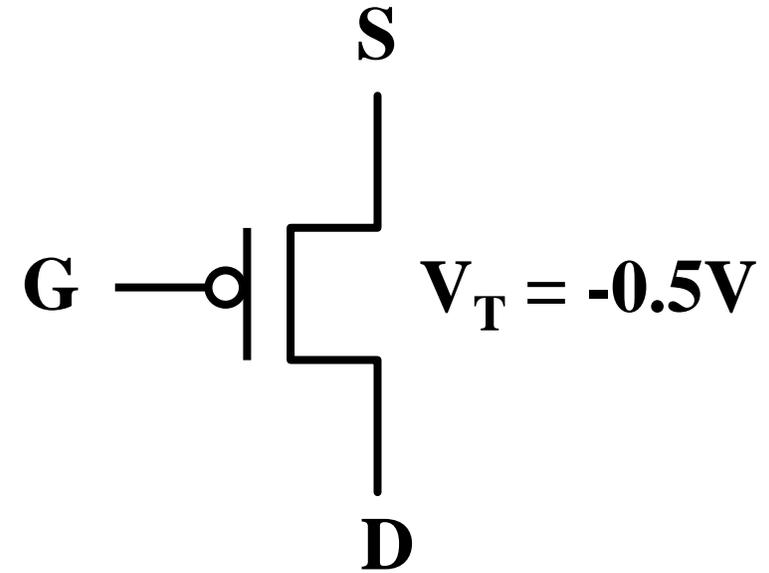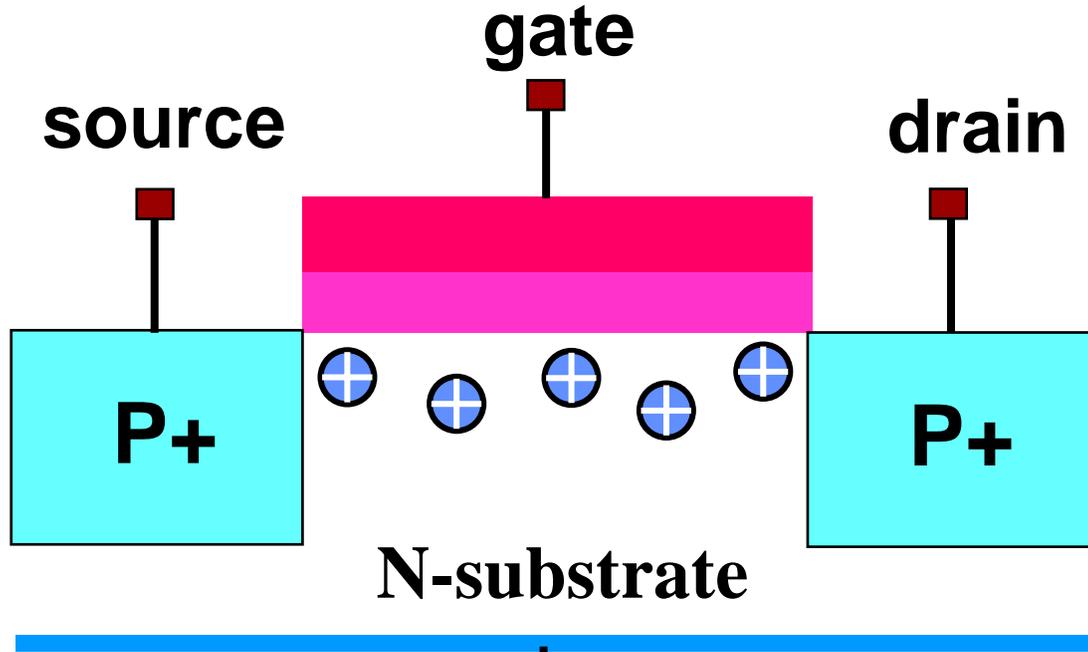- **MOS is a very non-linear.**
- **Switch-resistor model sufficient for first order analysis.**





Switch Model


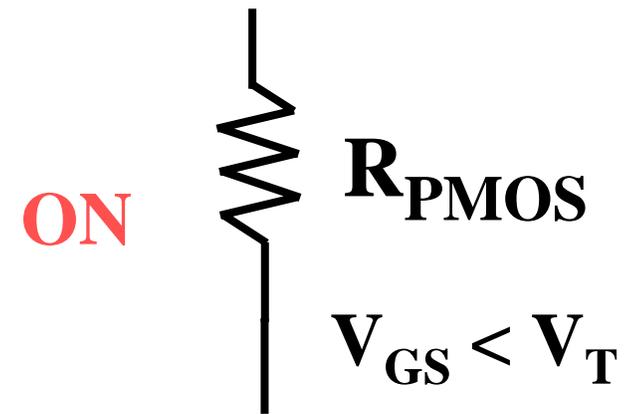
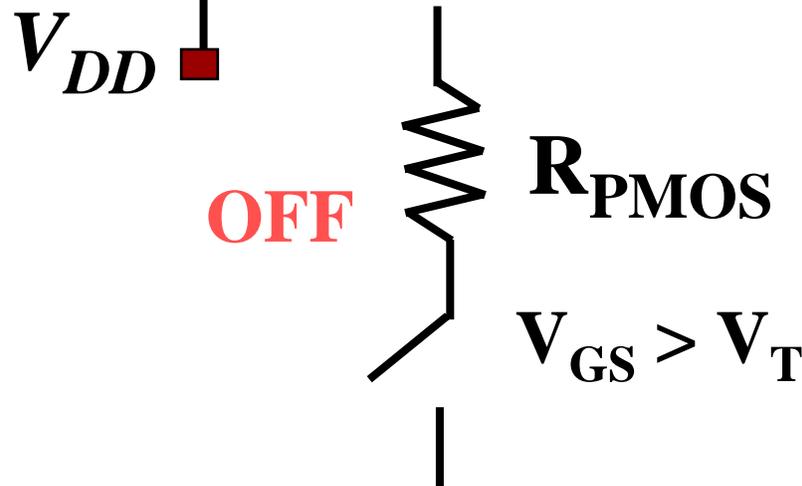


PMOS ON when Switch Input is Low

Switch Model

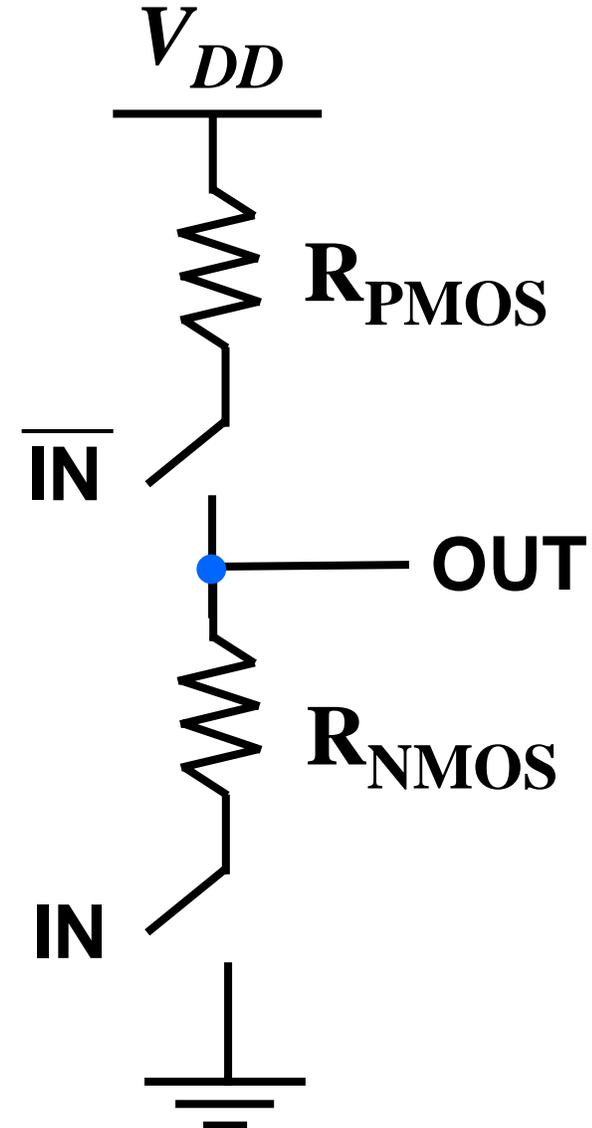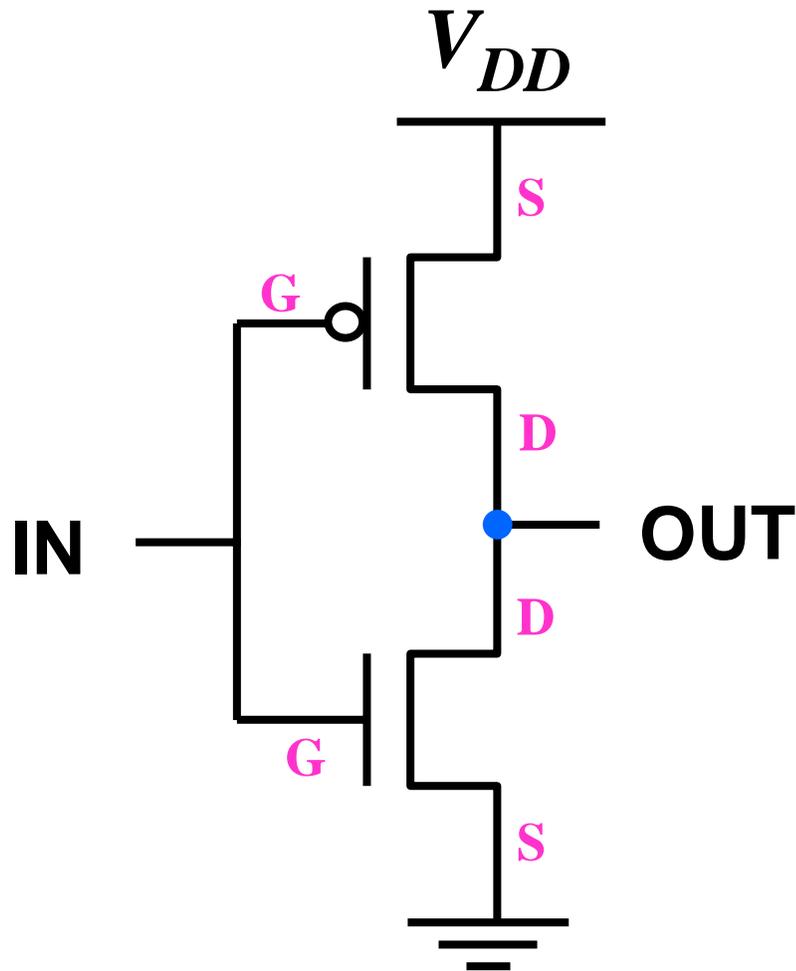

Rail-to-rail Swing in CMOS

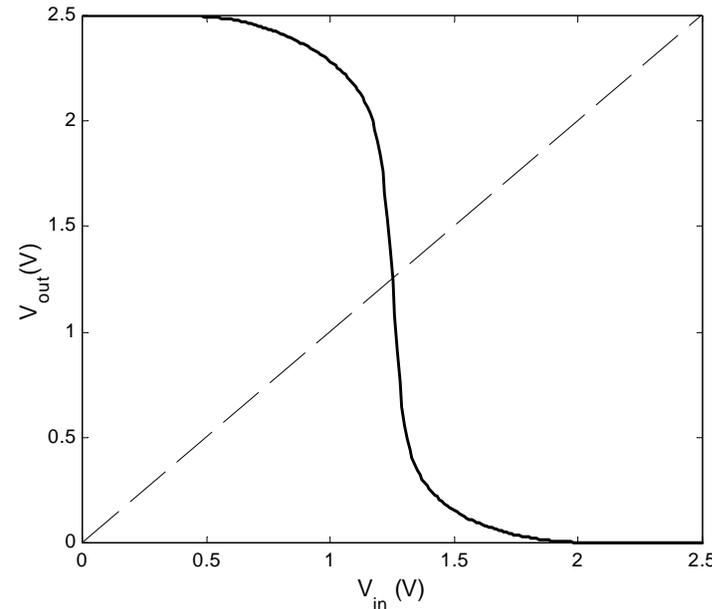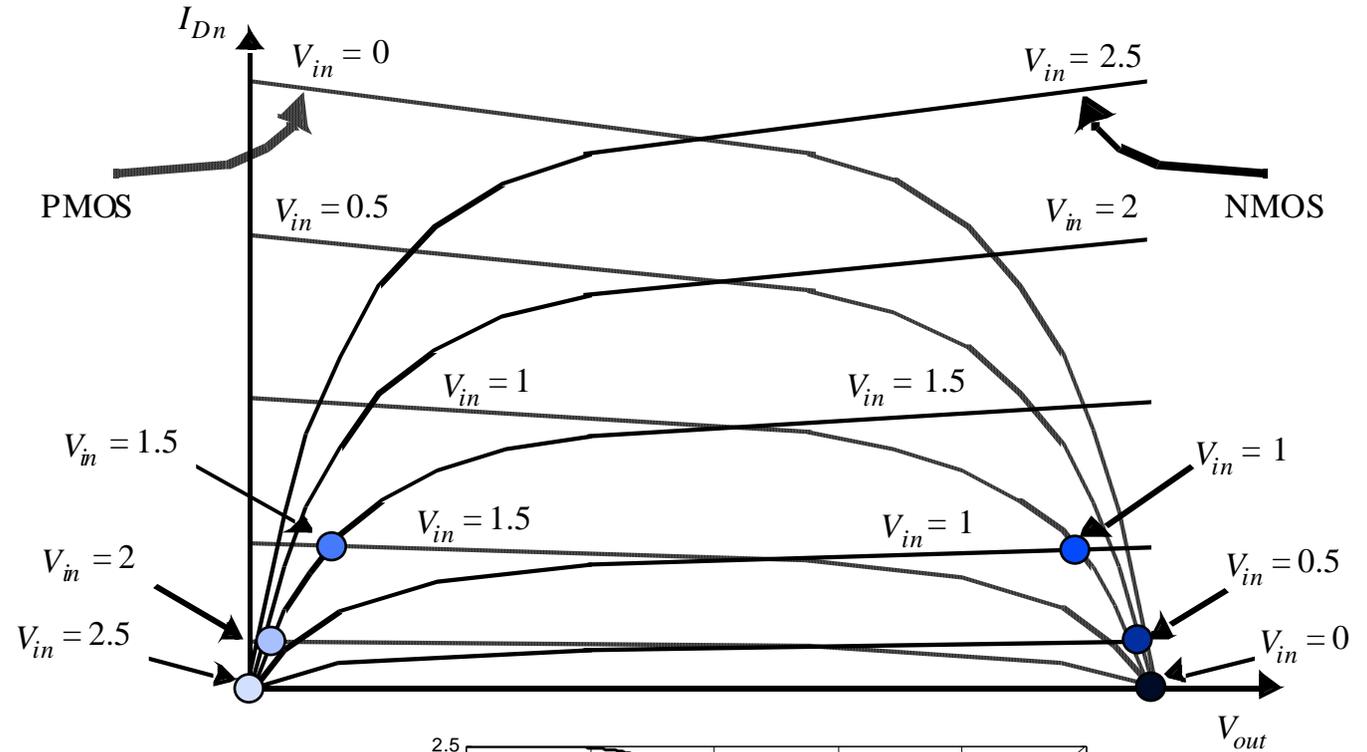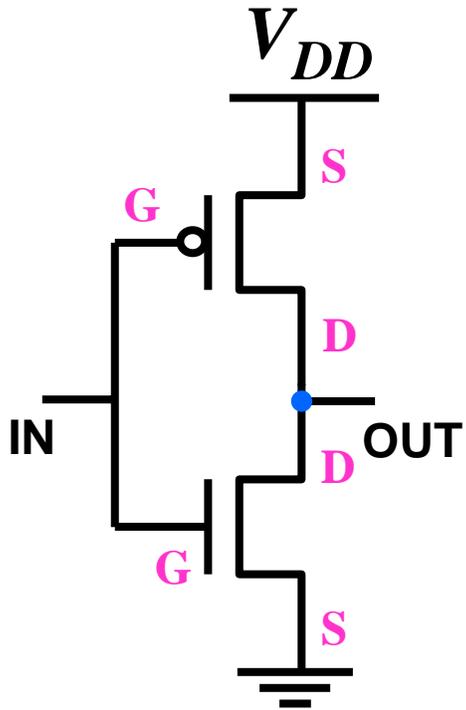

CMOS gates have:

- Rail-to-rail swing (0V to V_{DD})
- Large noise margins
- “zero” static power dissipation

There are 16 possible functions of 2 input variables:



X	Y	16 possible functions (F_0 – F_{15})																
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1

0 \swarrow $X \text{ AND } Y$
 $X \swarrow$
 $Y \swarrow$ $X \text{ XOR } Y$
 $X \text{ OR } Y$
 $X \text{ NOR } Y$
 $\text{NOT } (X \text{ OR } Y)$
 $X = Y$
 $\text{NOT } Y$ $\text{NOT } X$
 $X \text{ NAND } Y$
 $\text{NOT } (X \text{ AND } Y)$

In general, there are $2^{(2^n)}$ functions of n inputs


Gate

Symbol

Truth-Table

Expression


NAND

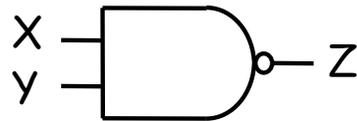

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = \overline{X \cdot Y}$$


AND

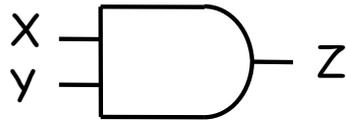

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

$$Z = X \cdot Y$$


NOR

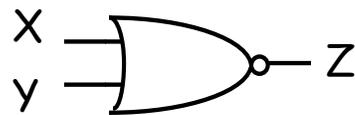

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

$$Z = \overline{X + Y}$$


OR

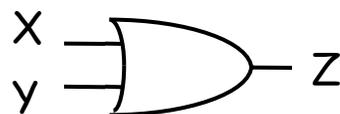

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

$$Z = X + Y$$


XOR
($X \oplus Y$)

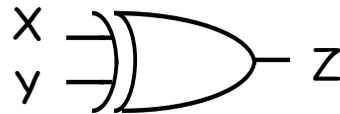

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$Z = X \bar{Y} + \bar{X} Y$
X or Y but not both
("inequality", "difference")


XNOR
 $\overline{(X \oplus Y)}$

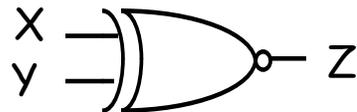


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$Z = \bar{X} \bar{Y} + X Y$
X and Y the same
("equality")

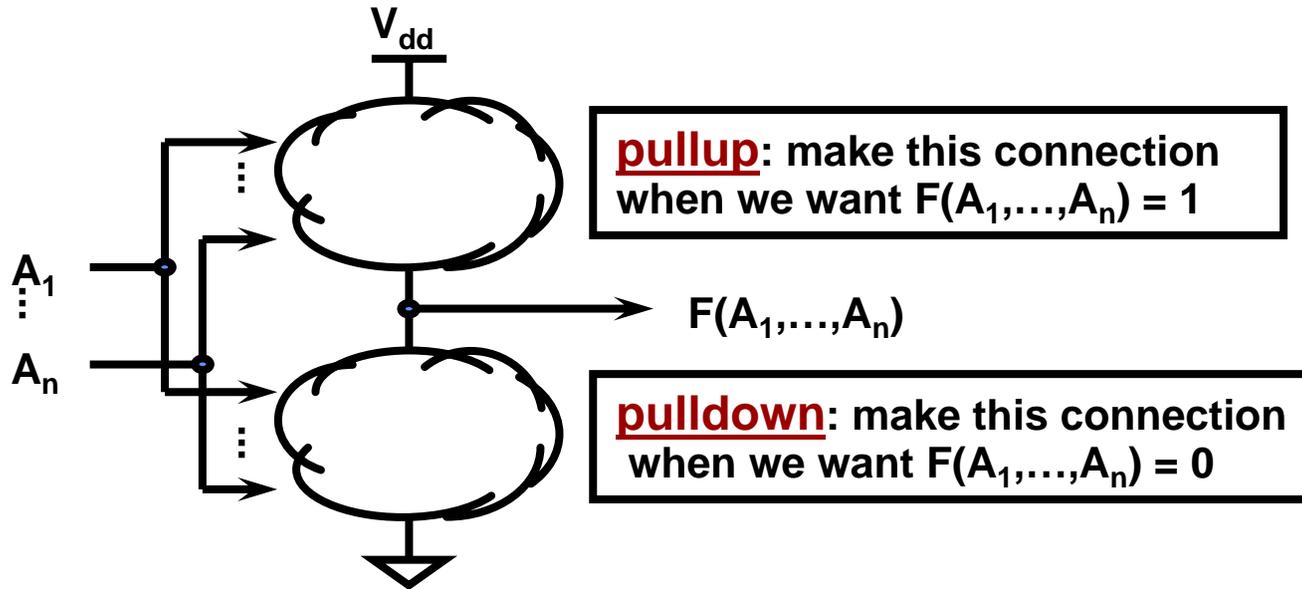Widely used in arithmetic structures such as adders and multipliers



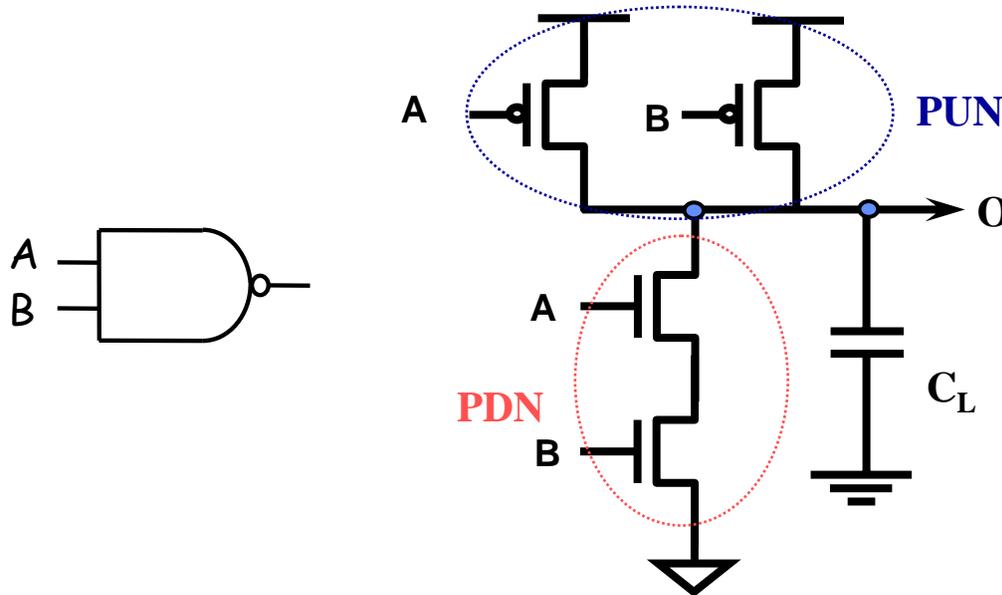Note: CMOS gates result in inverting functions!
 (easier to build NAND vs. AND)



A	B	PDN	PUN	O
0	0	Off	On	1
0	1	Off	On	1
1	0	Off	On	1
1	1	On	Off	0

How do you build a 2-input NOR Gate?

■ Elementary

$$1. X + 0 = X$$

$$2. X + 1 = 1$$

$$3. X + X = X$$

$$4. \overline{\overline{X}} = X$$

$$5. X + \overline{X} = 1$$

$$1D. X \cdot 1 = X$$

$$2D. X \cdot 0 = 0$$

$$3D. X \cdot X = X$$

$$5D. X \cdot \overline{X} = 0$$

■ Commutativity:

$$6. X + Y = Y + X$$

$$6D. X \cdot Y = Y \cdot X$$

■ Associativity:

$$7. (X + Y) + Z = X + (Y + Z)$$

$$7D. (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

■ Distributivity:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

■ Uniting:

$$9. X \cdot Y + X \cdot \overline{Y} = X$$

$$9D. (X + Y) \cdot (X + \overline{Y}) = X$$

■ Absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + \overline{Y}) \cdot Y = X \cdot Y$$

$$11D. (X \cdot \overline{Y}) + Y = X + Y$$

■ Factoring:

$$12. (X \cdot Y) + (X \cdot Z) = X \cdot (Y + Z)$$

$$12D. (X + Y) \cdot (X + Z) = X + (Y \cdot Z)$$

■ Consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (\bar{X} \cdot Z) = X \cdot Y + \bar{X} \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (\bar{X} + Z) = (X + Y) \cdot (\bar{X} + Z)$$

■ De Morgan's:

$$14. \overline{(X + Y + \dots)} = \bar{X} \cdot \bar{Y} \cdot \dots$$

$$14D. \overline{(X \cdot Y \cdot \dots)} = \bar{X} + \bar{Y} + \dots$$

■ Generalized De Morgan's:

$$15. f(\bar{X}_1, \bar{X}_2, \dots, \bar{X}_n, 0, 1, +, \cdot) = f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$


■ Duality

□ Dual of a Boolean expression is derived by replacing \cdot by $+$, $+$ by \cdot , 0 by 1, and 1 by 0, and leaving variables unchanged

$$\square f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

■ 1-bit binary adder

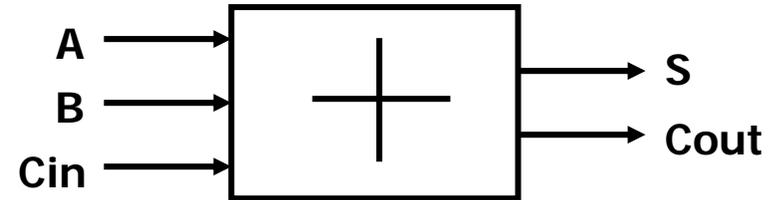- inputs: A, B, Carry-in
- outputs: Sum, Carry-out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum-of-Products Canonical Form

$$S = \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in}$$

$$C_{out} = \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in}$$

■ Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- Each variable appears exactly once, in true or inverted form (but not both)

$$\begin{aligned}
 C_{out} &= \overline{A} B C_{in} + A \overline{B} C_{in} + A B \overline{C_{in}} + A B C_{in} \\
 &= \overline{A} B C_{in} + A B C_{in} + A \overline{B} C_{in} + A B C_{in} + A B \overline{C_{in}} + A B C_{in} \\
 &= (\overline{A} + A) B C_{in} + A (\overline{B} + B) C_{in} + A B (\overline{C_{in}} + C_{in}) \\
 &= B C_{in} + A C_{in} + A B \\
 &= (B + A) C_{in} + A B
 \end{aligned}$$

$$\begin{aligned}
 S &= \overline{A} \overline{B} C_{in} + \overline{A} B \overline{C_{in}} + A \overline{B} \overline{C_{in}} + A B C_{in} \\
 &= (\overline{A} \overline{B} + A B) C_{in} + (A \overline{B} + \overline{A} B) \overline{C_{in}} \\
 &= \overline{(A \oplus B)} C_{in} + (A \oplus B) \overline{C_{in}} \\
 &= A \oplus B \oplus C_{in}
 \end{aligned}$$

- Product term** (or minterm): ANDed product of literals – input combination for which output is true

A	B	C	minterms	
0	0	0	$\overline{A} \overline{B} \overline{C}$	m0
0	0	1	$\overline{A} \overline{B} C$	m1
0	1	0	$\overline{A} B \overline{C}$	m2
0	1	1	$\overline{A} B C$	m3
1	0	0	$A \overline{B} \overline{C}$	m4
1	0	1	$A \overline{B} C$	m5
1	1	0	$A B \overline{C}$	m6
1	1	1	$A B C$	m7

short-hand notation form in terms of 3 variables

F in canonical form:

$$F(A, B, C) = \sum m(1,3,5,6,7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$F = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + A B \overline{C} + ABC$$

canonical form \neq minimal form

$$F(A, B, C) = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + ABC + ABC \overline{C}$$

$$= (\overline{A} \overline{B} + \overline{A} B + A \overline{B} + AB)C + ABC \overline{C}$$

$$= ((\overline{A} + A)(\overline{B} + B))C + ABC \overline{C}$$

$$= C + ABC \overline{C} = ABC \overline{C} + C = AB + C$$

- Sum term** (or maxterm) - ORed sum of literals – input combination for which output is false

A	B	C	maxterms	
0	0	0	$A + B + C$	M0
0	0	1	$A + B + \overline{C}$	M1
0	1	0	$A + \overline{B} + C$	M2
0	1	1	$A + \overline{B} + \overline{C}$	M3
1	0	0	$\overline{A} + B + C$	M4
1	0	1	$\overline{A} + B + \overline{C}$	M5
1	1	0	$\overline{A} + \overline{B} + C$	M6
1	1	1	$\overline{A} + \overline{B} + \overline{C}$	M7

short-hand notation for maxterms of 3 variables

F in canonical form:

$$F(A, B, C) = \prod M(0,2,4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

canonical form \neq minimal form

$$F(A, B, C) = (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C)$$

$$= (A + B + C) (A + \overline{B} + C)$$

$$(A + B + C) (\overline{A} + B + C)$$

$$= (A + C) (B + C)$$

1. **Minterm to Maxterm conversion:**
 rewrite minterm shorthand using maxterm shorthand
 replace minterm indices with the indices not already used

E.g., $F(A,B,C) = \sum m(3,4,5,6,7) = \prod M(0,1,2)$

2. **Maxterm to Minterm conversion:**
 rewrite maxterm shorthand using minterm shorthand
 replace maxterm indices with the indices not already used

E.g., $F(A,B,C) = \prod M(0,1,2) = \sum m(3,4,5,6,7)$


3. **Minterm expansion of F to Minterm expansion of F':**
 in minterm shorthand form, list the indices not already used in F

$$\begin{array}{lcl} \text{E.g., } F(A,B,C) = \sum m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \sum m(0,1,2) \\ & \longrightarrow & = \prod M(3,4,5,6,7) \\ & & = \prod M(0,1,2) \end{array}$$




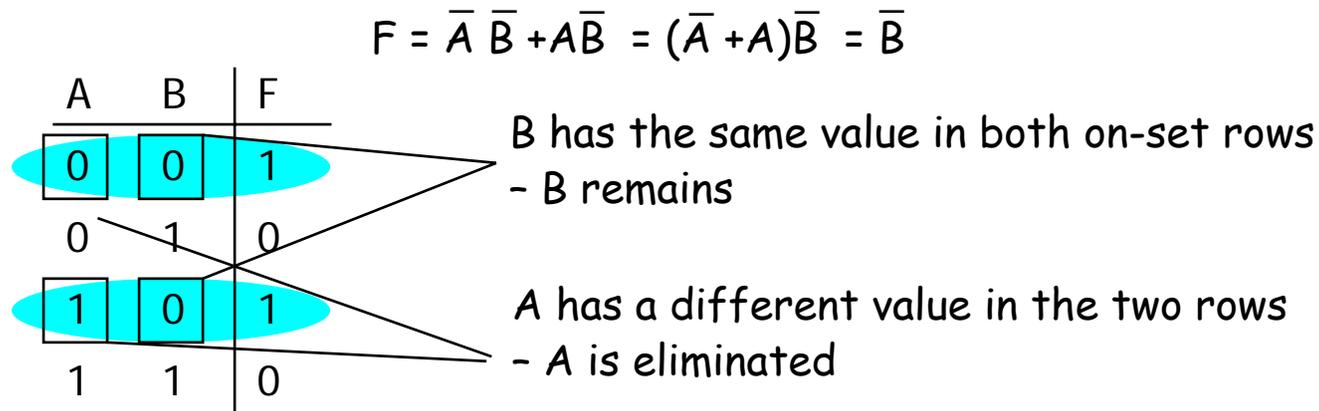
4. **Minterm expansion of F to Maxterm expansion of F':**
 rewrite in Maxterm form, using the same indices as F

$$\begin{array}{lcl} \text{E.g., } F(A,B,C) = \sum m(3,4,5,6,7) & \longrightarrow & F'(A,B,C) = \prod M(3,4,5,6,7) \\ & \longrightarrow & = \sum m(0,1,2) \\ & & = \prod M(0,1,2) \end{array}$$

- Key tool to simplification: $A(\bar{B} + B) = A$
- Essence of simplification of two-level logic
 - Find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements




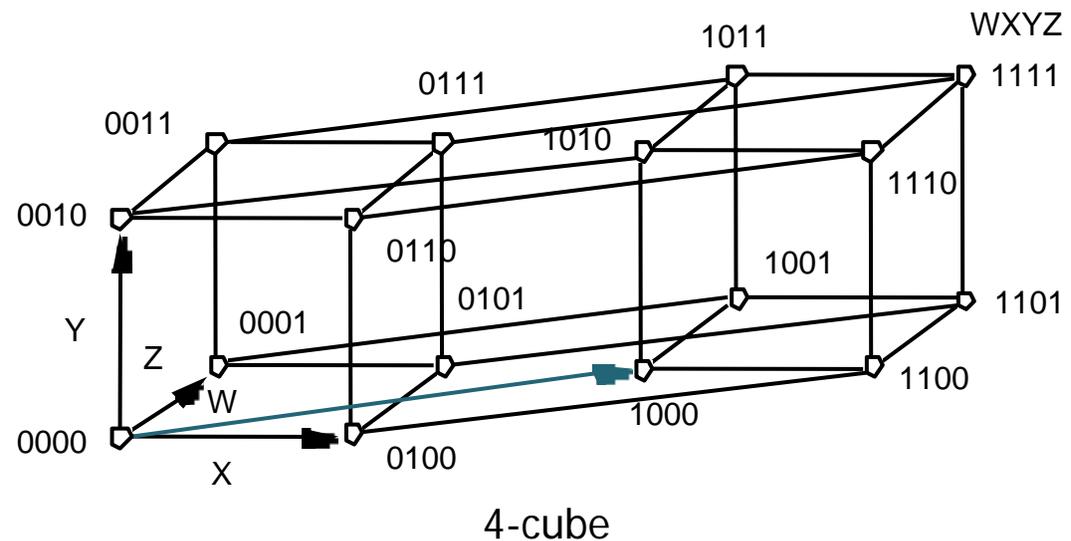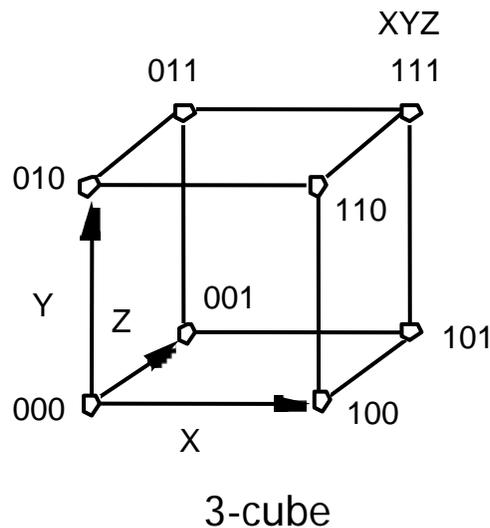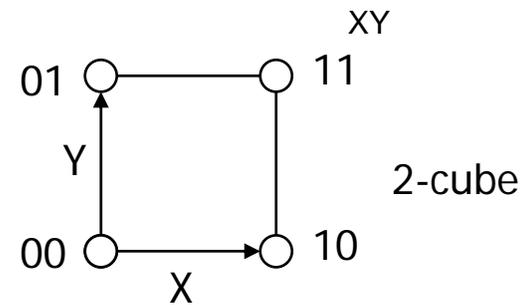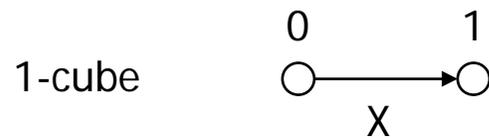- Just another way to represent truth table
- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n -dimensional "cube"



■ Uniting theorem

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

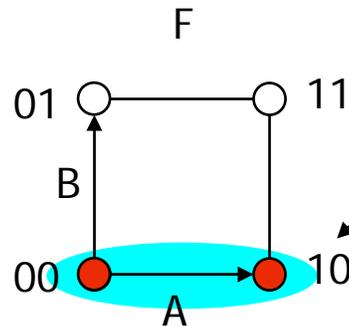


Circled group of the on-set is called the *adjacency plane*. Each adjacency plane corresponds to a product term.

ON-set = solid nodes
OFF-set = empty nodes

A varies within face, B does not
this face represents the literal \bar{B}


■ Three variable example: Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

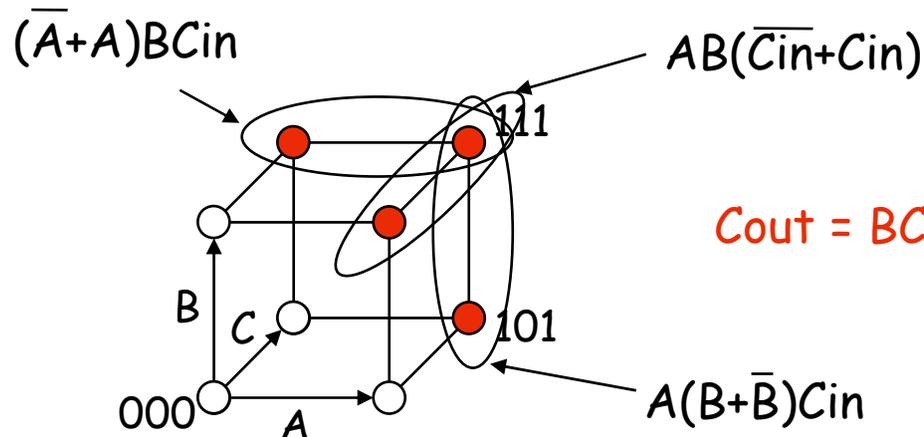

$$Cout = BCin + AB + ACin$$

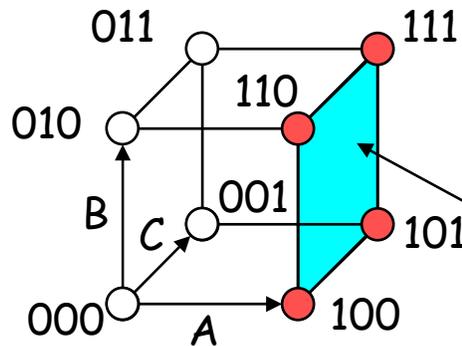The on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times



$$F(A,B,C) = \sum m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2 (2-D adjacency plane)

represents an expression in one variable
i.e., 3 dimensions - 2 dimensions

A is asserted (true) and unchanged
B and C vary

This subcube represents the literal A

■ In a 3-cube (three variables):

- 0-cube, i.e., a single node, yields a term in 3 literals
- 1-cube, i.e., a line of two nodes, yields a term in 2 literals
- 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
- 3-cube, i.e., a cube of eight nodes, yields a constant term "1"

■ In general,

- m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals

- **Alternative to truth-tables to help visualize adjacencies**
 - **Guide to applying the uniting theorem - On-set elements with only one variable changing value are adjacent unlike in a linear truth-table**

	A	0	1
B		0	1
0		0	1
1		1	0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

- **Numbering scheme based on Gray-code**

- **e.g., 00, 01, 11, 10 (only a single bit changes in code for adjacent map cells)**

2-variable K-map


	A	0	1
B		0	1
0		0	2
1		1	3

3-variable K-map


		AB	00	01	11	10
C			0	1	6	4
0			0	2	6	4
1			1	3	7	5

		AB	00	01	11	10
CD			0	4	12	8
00			0	4	12	8
01			1	5	13	9
11			3	7	15	11
10			2	6	14	10

4-variable K-map

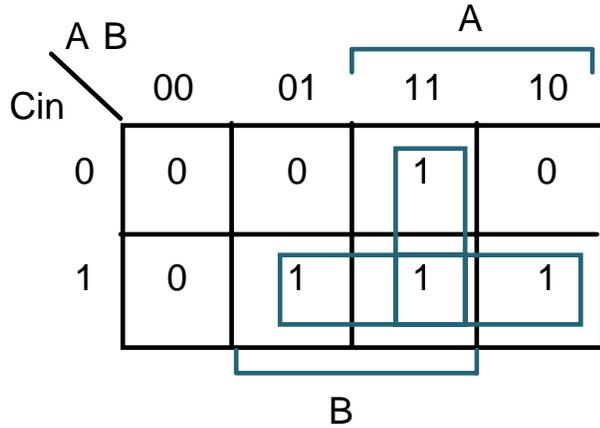


Cout =

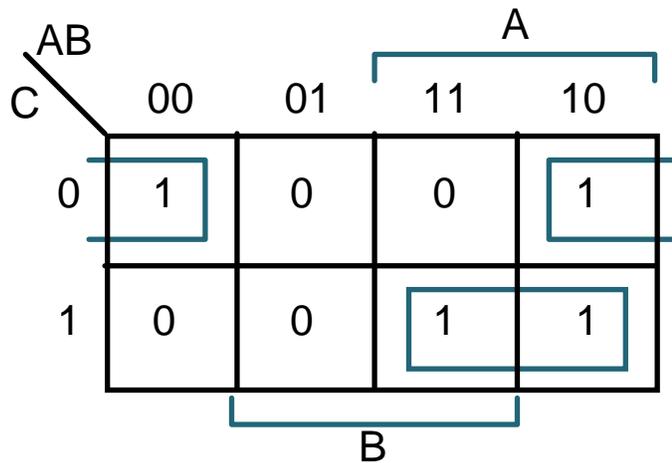


$$F(A,B,C) = \sum m(0,4,5,7)$$

F =

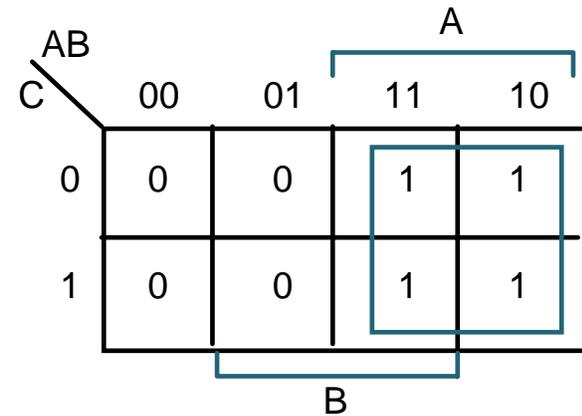


F(A,B,C) =

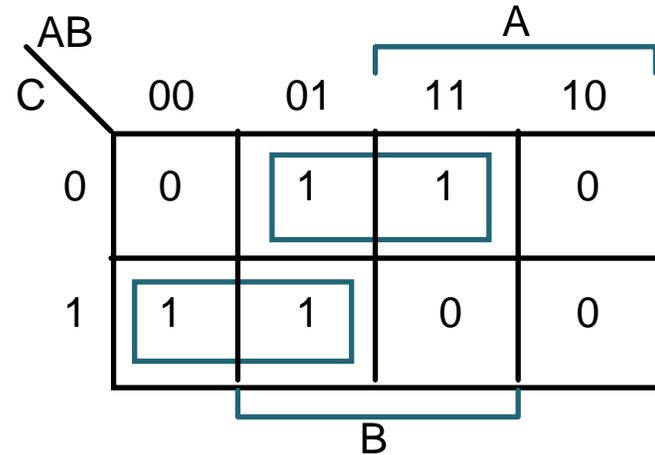

F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6)$$


F' =

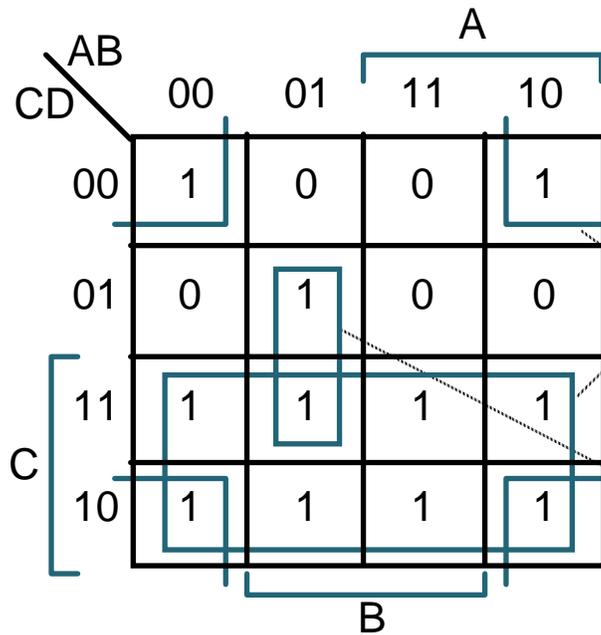

$$F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$$


$$F = C + \bar{A} B D + \bar{B} \bar{D}$$

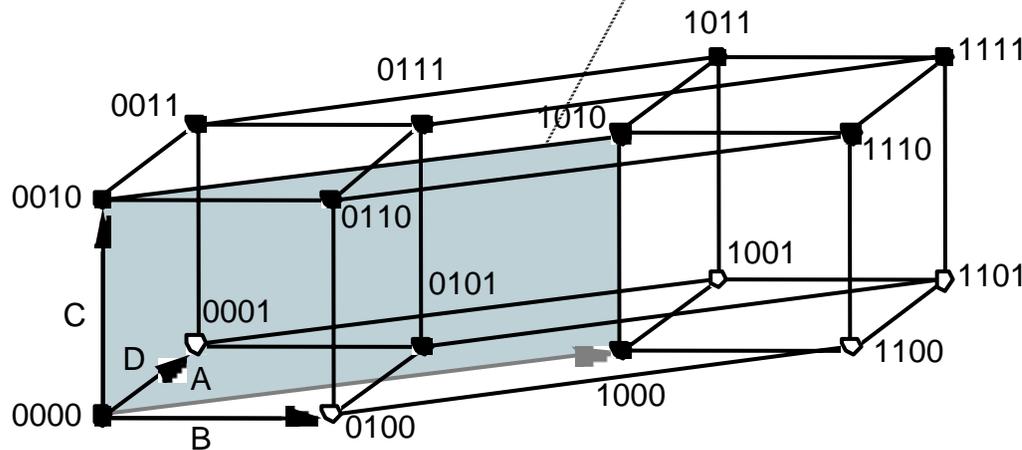Find the smallest number of the largest possible subcubes that cover the ON-set



K-map Corner Adjacency Illustrated in the 4-Cube

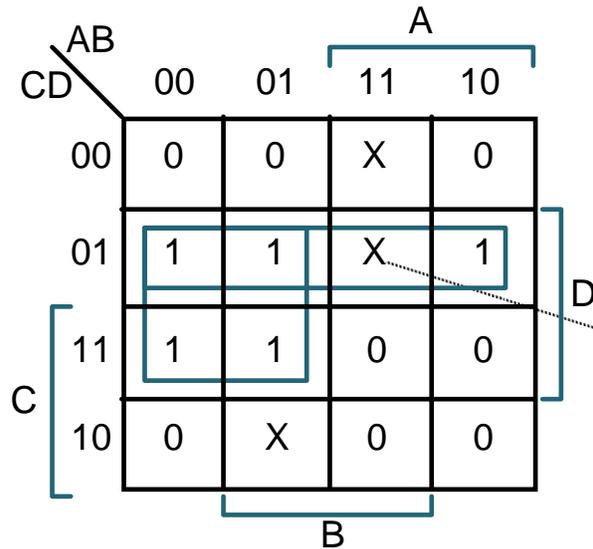Don't Cares can be treated as 1's or 0's if it is advantageous to do so



$$F(A,B,C,D) = \Sigma m(1,3,5,7,9) + \Sigma d(6,12,13)$$


$$F = \bar{A} D + \bar{B} \bar{C} D \text{ w/o don't cares}$$

$$F = \bar{C} D + \bar{A} D \text{ w/ don't cares}$$

By treating this DC as a "1", a 2-cube can be formed rather than one 0-cube


In PoS form: $F = D (\bar{A} + \bar{C})$

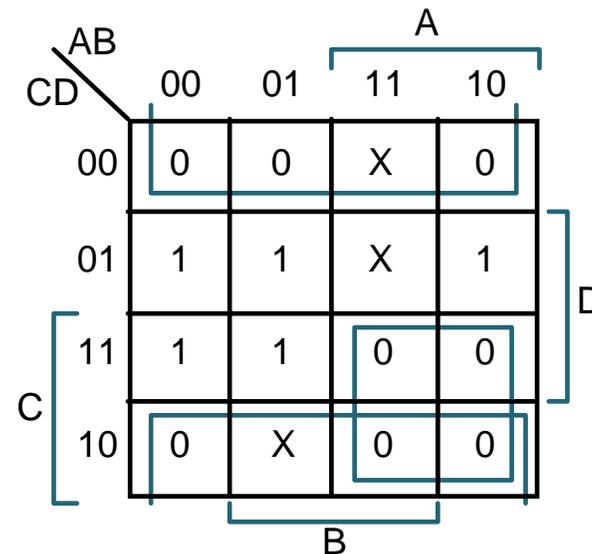Equivalent answer as above,
but fewer literals




Static Hazards: Consider this function:

$$F = A * \bar{C} + B * C$$

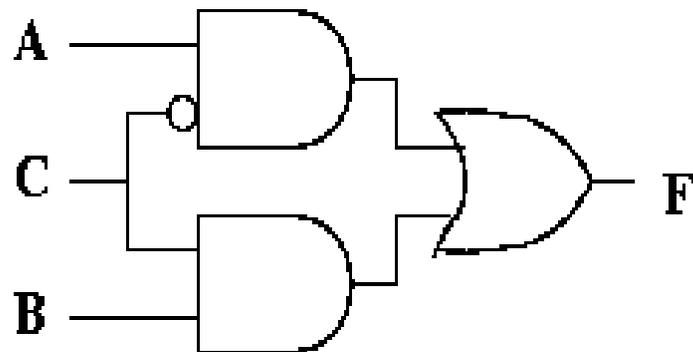


		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0


A = B = 1

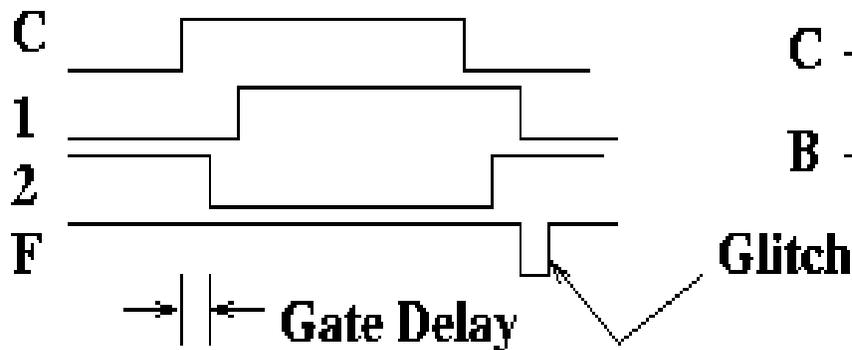

Implemented with MSI gates:

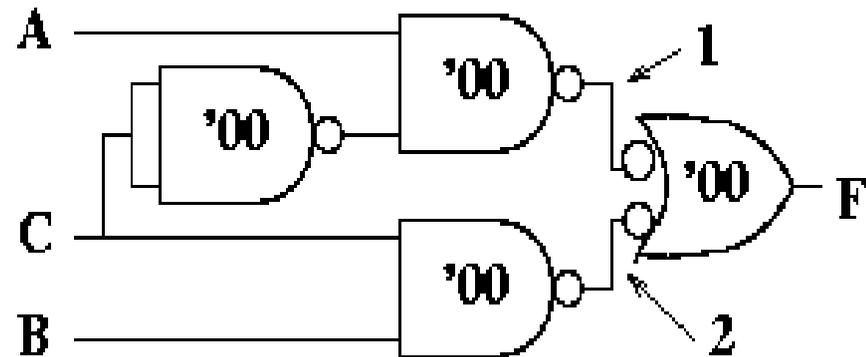

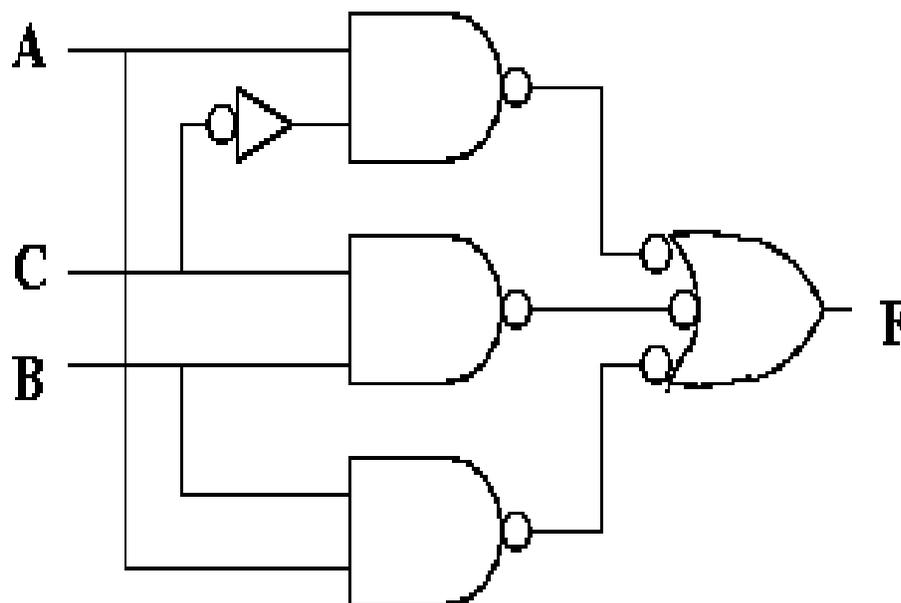The glitch is the result of timing differences in parallel data paths. It is associated with the function jumping between groupings or product terms on the K-map. To fix it, cover it up with another grouping or product term!



		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

$$F = A * \bar{C} + B * C + A * B$$

- In general, it is difficult to avoid hazards – need a robust design methodology to deal with hazards.**