

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.334 Power Electronics  
Spring 2007


For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

# Power Electronics Notes - D. Perreault

## ★★ Isolated DC/DC Converters


- motivations:
1. Galvanic Isolation between input + output
  2. High Conversion ratios
  3. Ease of generating multiple outputs
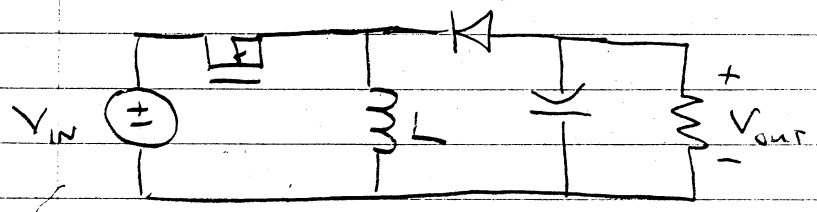
### ★ First example: Flyback Converter (indirect converter)



$$\frac{V_{out}}{V_{in}} = \frac{D}{1-D}$$


INSERT XFORMER

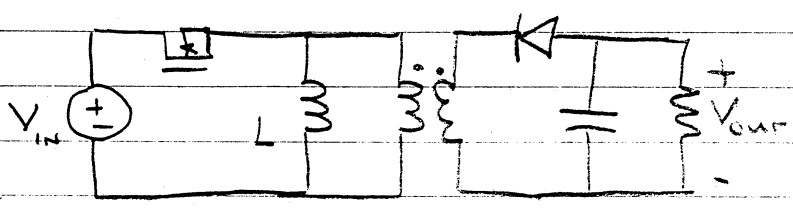

$$DV_{in} + (1-D) \frac{N_1}{N_2} V_{out} = 0$$

$$\frac{V_{out}}{V_{in}} = \frac{D}{1-D} \left( \frac{N_2}{N_1} \right)$$

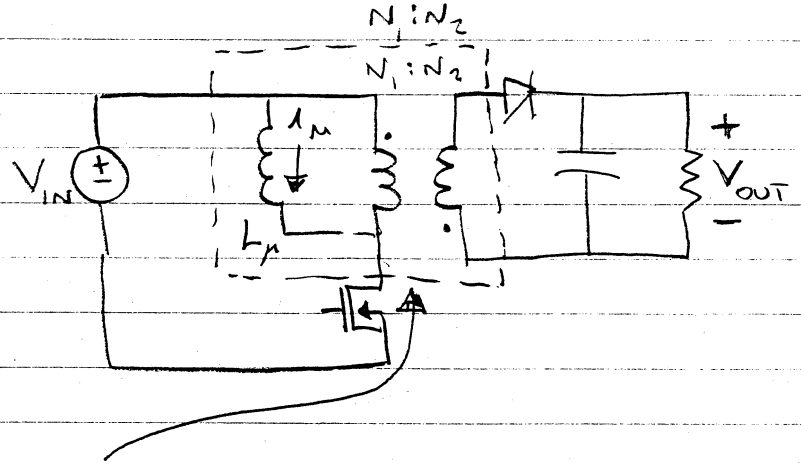
Δ Switch Positions, V<sub>out</sub> definition



$$\frac{V_{out}}{V_{in}} = \frac{D}{1-D} \left( \frac{N_2}{N_1} \right)$$

Design magnetics as one element: A gapped transformer where the energy is stored in the magnetizing inductance of the transformer [Like a flyback inductor w/ a second winding]

e.g. Flyback Xformer

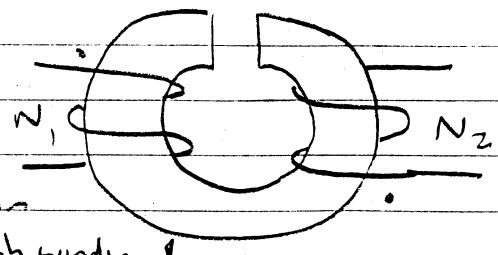

1<sup>st</sup> part of cycle: Energy is stored in Xformer through winding 1

2<sup>nd</sup> part of cycle: Energy is removed from Xformer through winding 2.


Δ L<sub>M</sub> is ≈ constant, but switches between terminals

## Power Electronics Notes - D. Perreault

- ① Energy stored in magnetizing inductance of transformer  
(Design like inductor, but w/ 2<sup>nd</sup> winding)
- ② Voltage inversion of nonisolated indirect may be eliminated  
(if desired) by winding direction
- ③ Can use ground-referenced primary switch
- ④ Turns ratio helps reduce switch + component ratings (keep D near 0.5)
- ⑤ Could add more outputs by adding more windings.

Isolation can also be added in direct converters, e.g.:

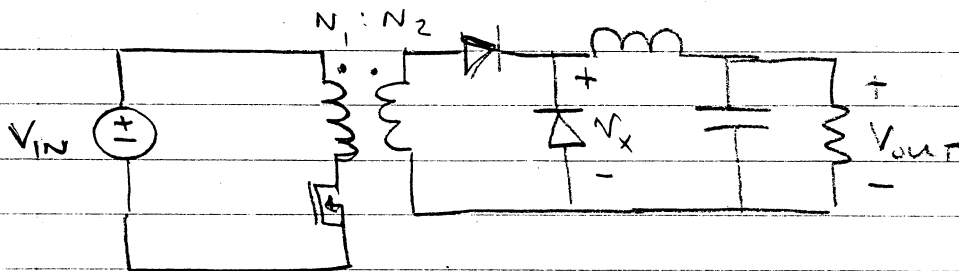★ Single-ended forward converter (isolated buck converter)



This is essentially a buck w/a transformer inserted.

$$\left. \begin{array}{l} \text{switch on} \quad V_x = \left(\frac{N_2}{N_1}\right) V_{IN} \\ \text{switch off} \quad V_x = 0 \end{array} \right\} \frac{V_{OUT}}{V_{IN}} = \left(\frac{N_2}{N_1}\right) D$$



But consider the effect of (undesired) magnetizing inductance  $L_m$   
 $\rightarrow$  we need  $\langle V_{Lm} \rangle = 0$  or core will saturate  
 $\rightarrow$  must provide a path for  $L_m$  until core "resets" to zero flux

(Unlike in the flyback converter, the magnetizing inductance is not a desired circuit element!)

Power Electronics Notes - D. Perreault


We must reset the core flux to zero each cycle!

One simple method: Clamp reset circuit

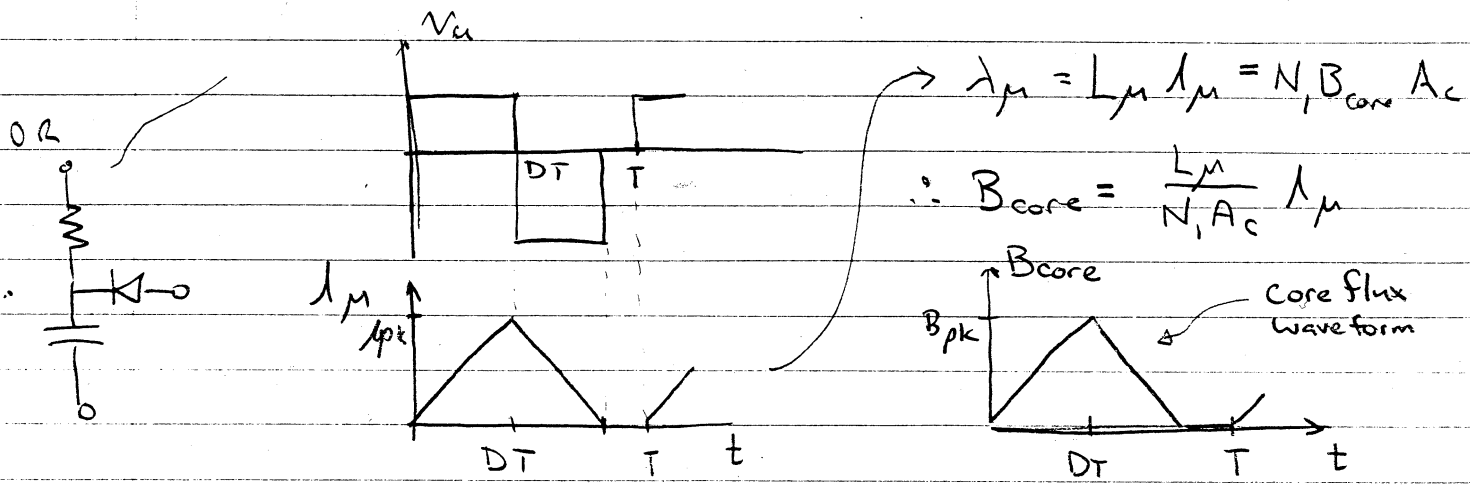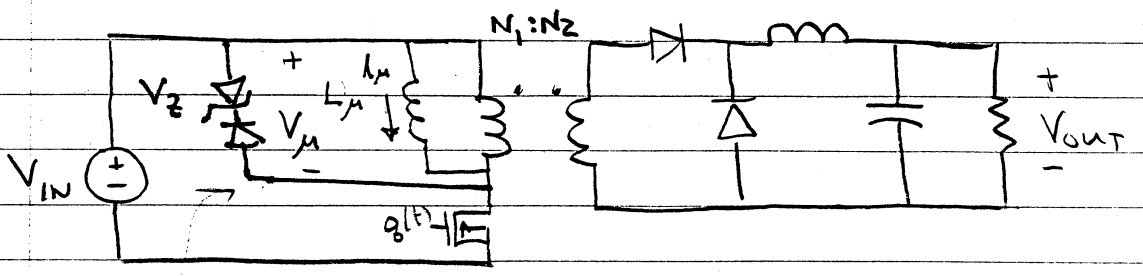

peak core flux:  $B_{pk} = \frac{V_{IN} D T}{N_1 A_c}$

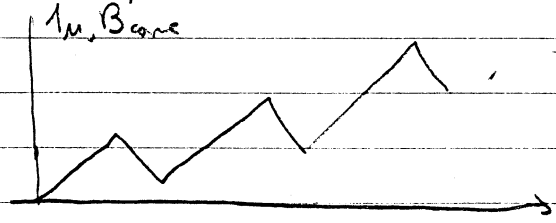We need to ensure that  $\int V_M dt \rightarrow 0$  (to reset the core).  
 Otherwise,  $I_M, B_{core}$  can "run away" over time and saturate the core



The required Zener voltage for the clamp is:

$$\therefore V_Z (1-D) T \geq V_{IN} D T \Rightarrow V_Z \geq V_{IN} \frac{D}{1-D}$$

\* The peak switch voltage is:  $V_{pk} = V_{IN} + V_Z$

$$\therefore V_{pk} \geq V_{IN} \left( \frac{1-D}{1-D} \right) + V_{IN} \left( \frac{D}{1-D} \right) = \frac{V_{IN}}{1-D}$$

@  $D_{max} = 0.5 \rightarrow V_{pk} = 2 V_{IN}$

$D_{max} = 0.75 \rightarrow V_{pk} = 4 V_{IN}$

This is poor compared to the nonisolated case, where  $V_{pk} = V_{IN}$ !

# Power Electronics Notes - D. Perreault

How much power do we lose resetting the core this way?

$$W_{diss} = \frac{1}{2} L_{\mu} I_{\mu, pk}^2 = \frac{1}{2} L_{\mu} \left( \frac{V_{IN} D T}{L_{\mu}} \right)^2 = \frac{V_{IN}^2 D^2 T^2}{2 L_{\mu}}$$


$$\Rightarrow P_{diss} = (W_{diss}) \left( \frac{1}{T} \right) = \frac{V_{IN}^2 D^2 T}{2 L_{\mu}}$$

↑  
f

∴ we want  $L_{\mu}$  as big as possible to minimize energy stored in xformer + dissipated. ∴ We typically use an ungapped (or minimally-gapped) core to maximize  $L_{\mu}$ , and minimize reset loss.

Other clamp methods allow us to recover magnetizing energy:

## ① Tertiary winding clamp

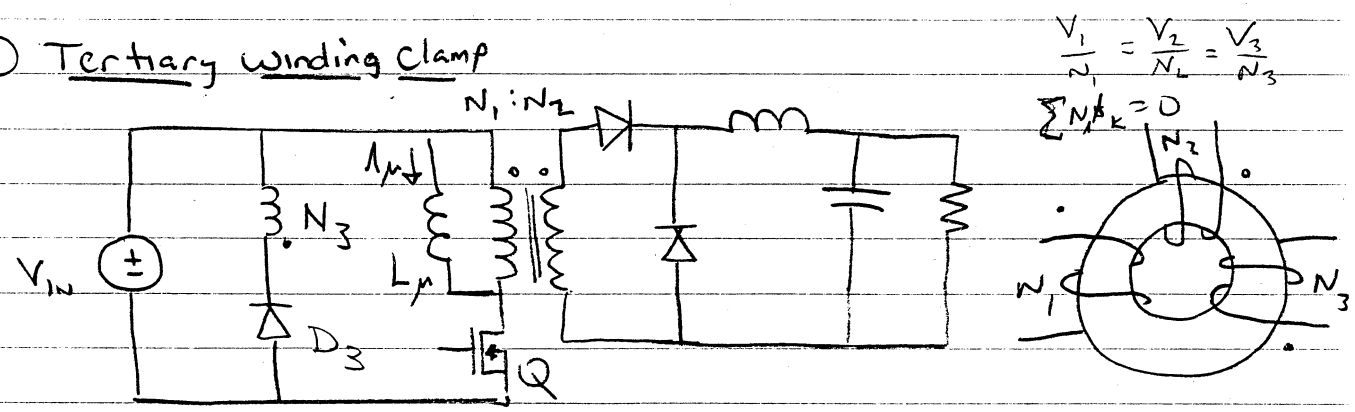

magnetizing energy returned to  $V_{IN}$  (when Q off,  $D_3$  on to discharge  $L_{\mu}$ )

To reset core, we require  $\frac{N_1}{N_3} V_{IN} (1-D) T \geq V_{IN} D T$


∴ The voltage stresses are the same (neglecting leakage L)

Advantages: Magnetizing energy is mostly recovered

Disadvantages: Still need a snubber to handle leakage inductance  
more transformer windings

Power Electronics Notes - D. Perreault

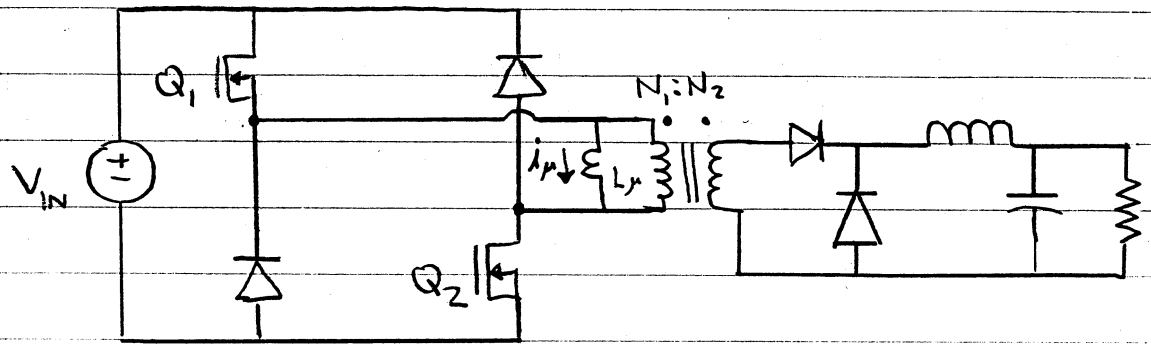(2) Two-switch single-ended forward converter




- Turn switches  $Q_1$  and  $Q_2$  on and off together with duty ratio  $D$
- Diodes conduct to reset core (recovering energy to input)
  - $\Rightarrow 0 \leq D < 0.5$  to guarantee core reset
  - $\Rightarrow$  leakage energy of transformer is also recaptured
- Requires two switches rated at  $V_{IN}$  (only one gnd referenced)

\* MULTIPLE OUTPUTS FROM ISOLATED CONVERTERS

- To get additional outputs having proportionally-related outputs, we need only add additional transformer windings and output stages

e.g., flyback

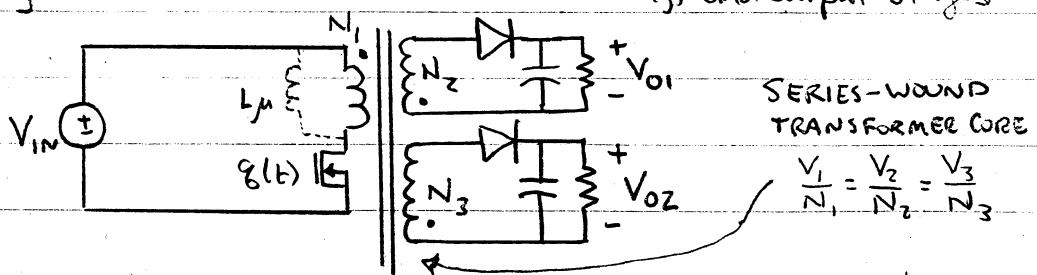

IDEALLY:  $\frac{V_{O1}}{V_{IN}} = \frac{D}{1-D} \left( \frac{N_2}{N_1} \right), \frac{V_{O2}}{V_{IN}} = \frac{D}{1-D} \left( \frac{N_3}{N_1} \right) \Rightarrow \frac{V_{O2}}{V_{O1}} = \frac{N_3}{N_2}$


- We can get multiple outputs with only modest increases in complexity
- Additional outputs often used to power converter control logic (with bootstrap!)
- Transformer nonidealities can become a significant issue (nonideal voltage relationships)

# Power Electronics Notes - D. Perreault
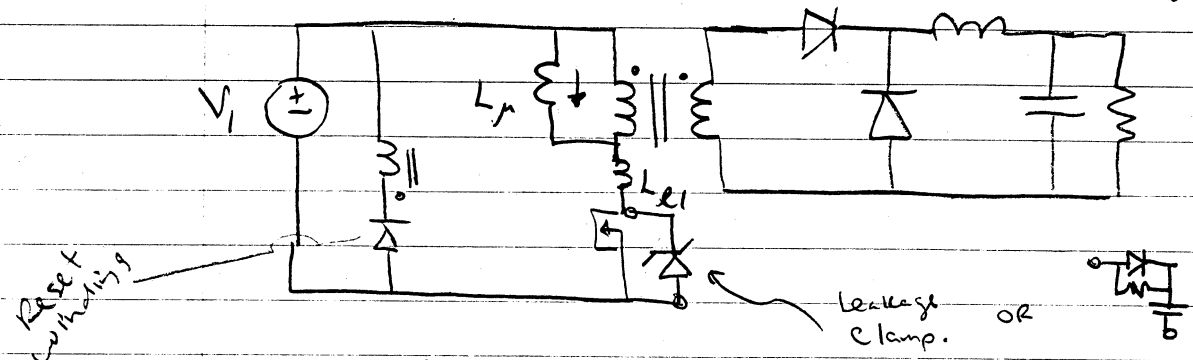
## \* TRANSFORMER LEAKAGE INDUCTANCES


Leakage inductance parasitics also influence operation:

Consider a forward converter with primary leakage (only)




when we turn off the main switch, the reset winding can handle magnetizing current/energy, but not primary-side leakage inductance. We may need to add additional circuitry to absorb or recycle this energy! (e.g. Zener).

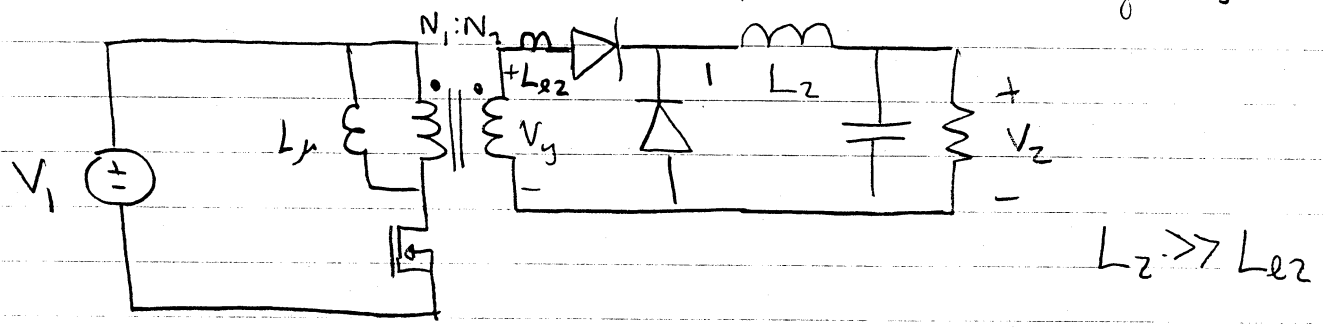Consider a forward converter with secondary-side leakage only




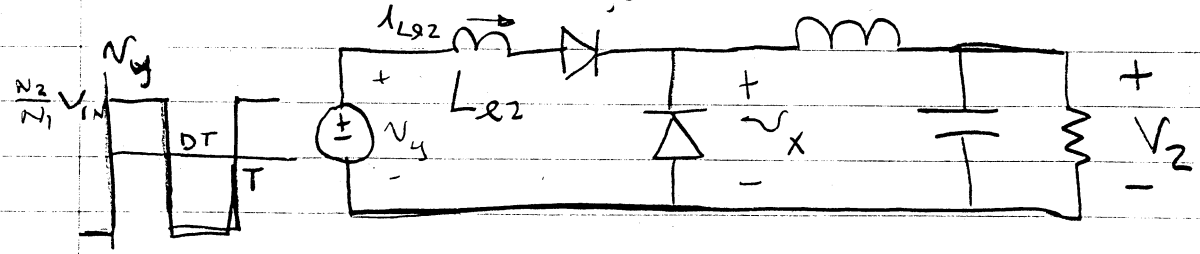We can model the secondary side as:  $\rightarrow I_2$



From this, we can calculate the voltage conversion ratio  
 $\Rightarrow$  Load regulation effects due to secondary leakage result in a load current + dependence of the conversion ratio!
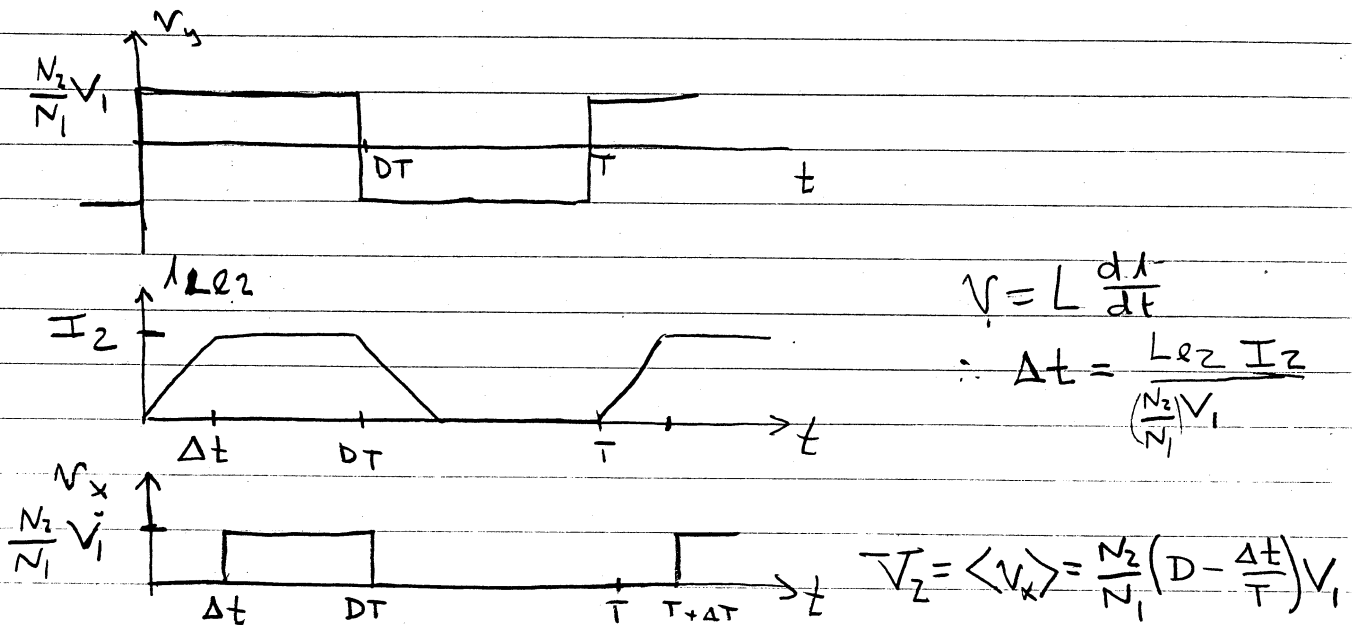
## Power Electronics Notes - D. Perreault



So we may calculate the conversion ratio as:

$$V_2 = \frac{N_2}{N_1} D V_1 - \frac{L_{\text{eq}}}{T} \cdot I_2$$

SO THE CONVERSION RATIO NOW NOT ONLY DEPENDS ON DUTY RATIO, BUT LOAD CURRENT

- WE WILL HAVE TO INCREASE DUTY RATIO AS LOAD  $\uparrow$
- THIS IS CALLED LOAD REGULATION! (as with rectifiers)

This becomes VERY IMPORTANT with multiple outputs.

- we can only adjust  $D$  to regulate one output
- since conversion ratios now depends on load currents, the output voltages are not related by turns ratio (adjusting for load variations on one output can change the voltage at the other output!)

$\Rightarrow$  This is called "cross regulation" + is undesirable!



$\therefore$  The transformer parasitics are important for isolated converter operation



# Power Electronics Notes - D. Perreault
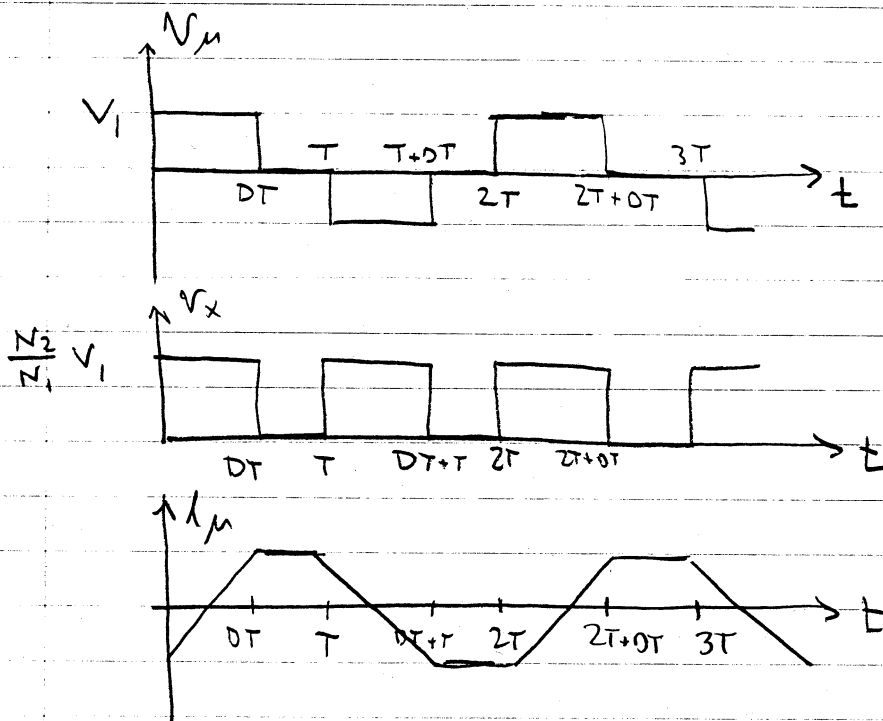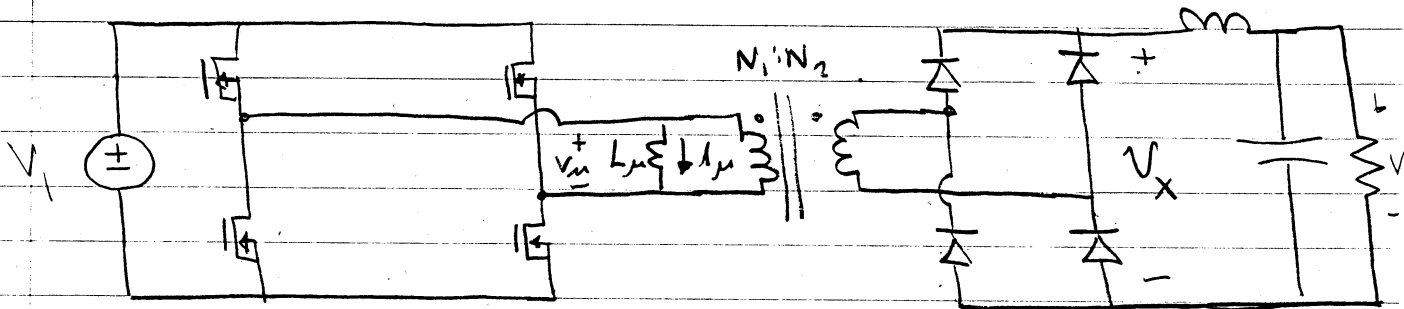
## \* Double-Ended Converters:

So far we have considered converters that only use unidirectional primary-side & former magnetizing current. We can better utilize the transformer with bidirectional current/flux.



Fundamental ripple frequency doubles!  
(smaller filters, xformer)



Core flux swing is bidirectional  
- Bmax to + Bmax  
instead of 0 to Bmax

- Bidirectional flux swing allows smaller xformer
- Frequency doubling allows smaller filters
- However we must use control or a blocking capacitor to ensure that  $\langle I_m \rangle \sim 0$ , or we will saturate the transformer! (TRICKY)
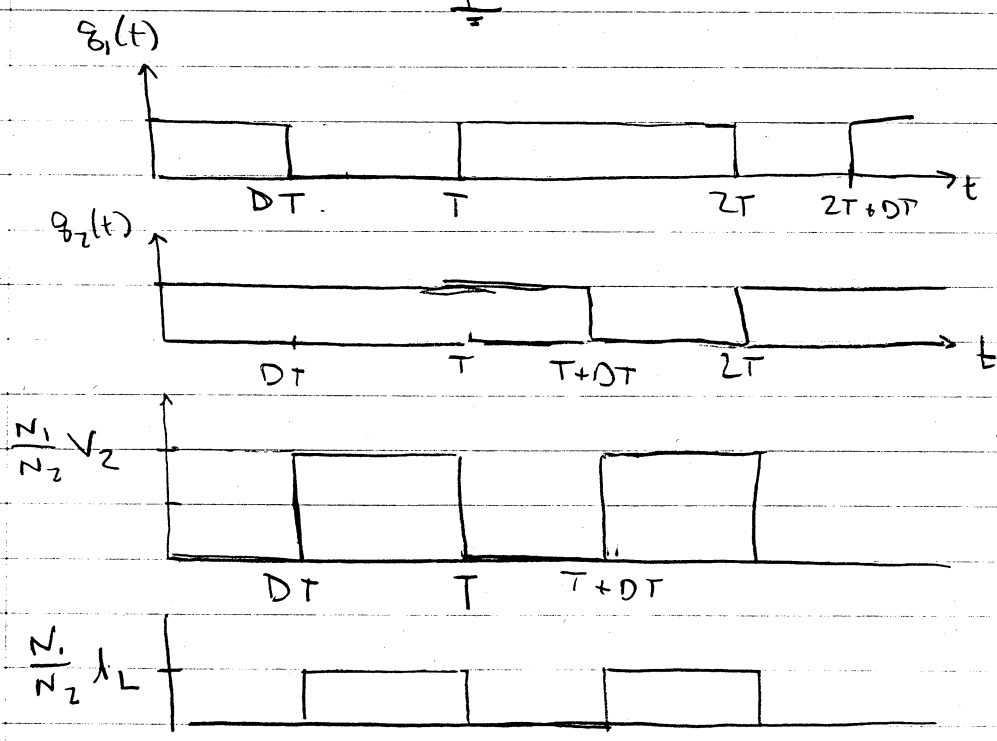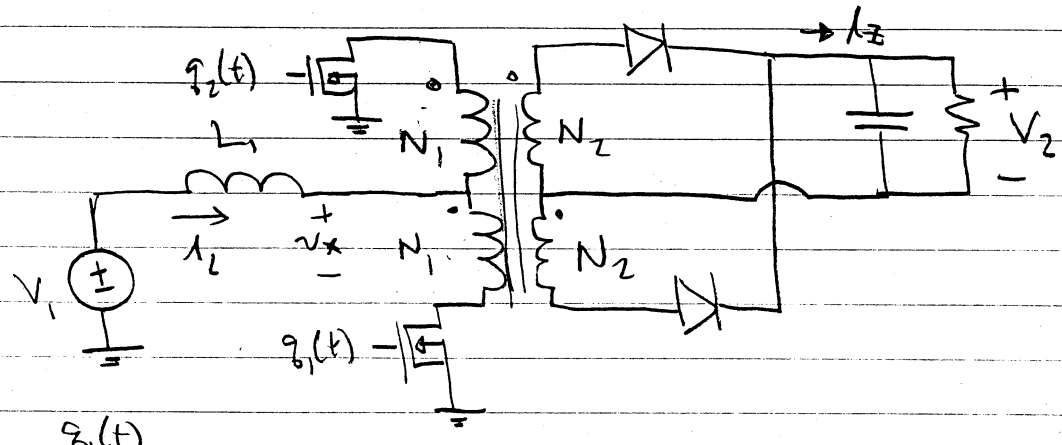
# Power Electronics Notes - D. Perreault

MANY OTHER KINDS OF ISOLATED CONVERTER VARIANTS EXIST!

e.g. current-fed push-pull (like isolated boost)



like a boost

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} \frac{1}{1-D}$$

we can also create structures that don't exist in nonisolated, and use different rectifiers (e.g. current doubler)

e.g. flyback