

Review

METH. ASSUMED STATES


1. Assume a state (on/off) for all switches
 2. Calculate voltages/currents in system
 3. Check if any switch condition violated
 4. If not → ok
- If so, assume a different set of states

PERIODIC STEADY STATE :

Converter waveforms repeat every cycle

$$\text{In P.S.S. } \langle i_c \rangle = C \left\langle \frac{di_c}{dt} \right\rangle = 0$$
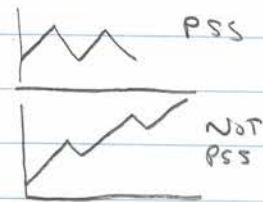
$$\langle v_L \rangle = L \left\langle \frac{dv_L}{dt} \right\rangle = 0$$




usually not used for line regulation, but often appears in dc/dc conv.

Today: Rectifiers + dc-side characteristics.


⇒ Have us show + tell: Alternator, isolated dc/dc conv.

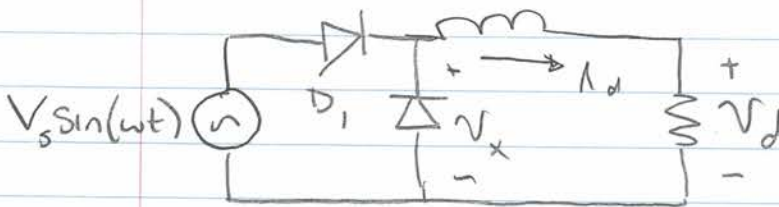LAST time we introduced a half-wave rectifier



By M.A.S.

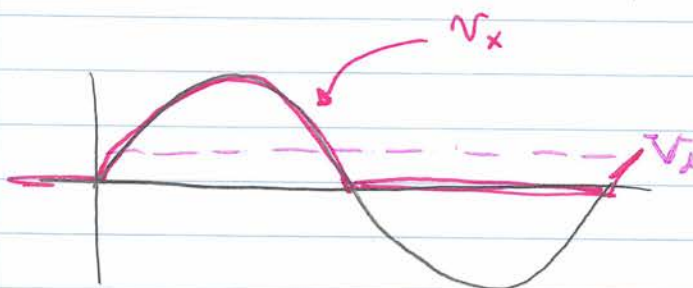- $V_s \sin(\omega t) > 0 \rightarrow D_1 \text{ on}$
- $V_s \sin(\omega t) < 0 \rightarrow D_2 \text{ on}$



$$\langle v_d \rangle = \langle v_x \rangle$$

$$= \frac{1}{2\pi} \int_0^\pi V_s \sin(\phi) d\phi$$

$$= \frac{V_s}{\pi}$$

$$i_d \approx I_d = \frac{V_s}{\pi R}$$


6.334 Lecture Notes

Load Regulation

Now consider adding some ac-side inductance L_c (reactance $X_c \triangleq \omega L_c$)

This is a relevant issue. L_c can be

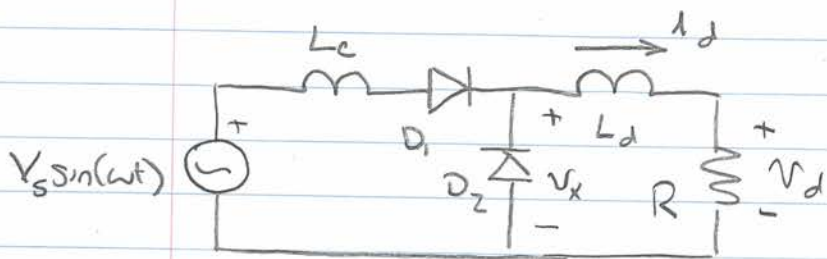1. transformer leakage inductance (ac power or dc-dc)
2. generator machine leakage
3. line inductance.




Typically $L_d \gg L_c$ (filter much bigger than leakage) \Rightarrow for simplicity, assume $L_d \rightarrow \infty$ so load looks like a current-source.

It is a "special" current source since $\langle V_L \rangle = 0$ in P.S.S.

$$\therefore I_d = \langle V_x / R \rangle$$

Simplified model

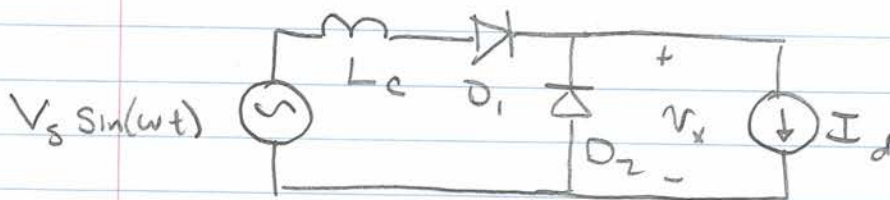

Visual presentation:


Draw voltage cycle on board & then fill in as we calculate.

Assume we start with D_2 conducting, D_1 off, $V_s \sin(\omega t) < 0$, what happens when $V_s \sin(\omega t)$ crosses zero?

- D_1 off is no longer valid ($V_d > 0$) ∴ D_1 turns on
- after turn on i_1 still = 0 (no instant change in L_c) ∴ D_2 remains on

During Commutation, both devices are on

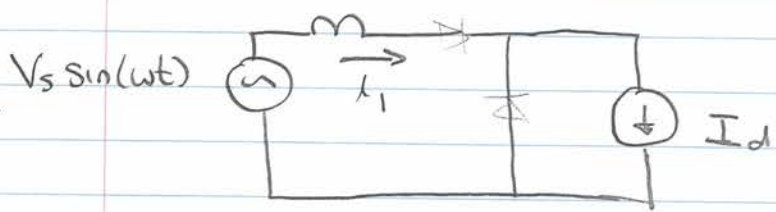(NB: Commutation means to switch or track between points)



$$L_c \frac{di_1}{dt} = V_s \sin(\omega t) \Rightarrow i_1 = \frac{V_s}{\omega L_c} \int_0^{\omega t} \sin(\omega t) d(\omega t)$$

$$i_1 = \frac{V_s}{\omega L_c} [\cos(0) - \cos(\omega t)] = \frac{V_s}{\omega L_c} [1 - \cos(\omega t)]$$

this is valid until some electrical angle $\omega t = u$, when the current through D_2 reaches zero ($i_1 = I_d$)

$$I_d = \frac{V_s}{\omega L_c} [1 - \cos(u)]$$


Commutation interval u such that

$$\cos u = 1 - \frac{\omega L_c I_d}{V_s}$$

The dimensionless term $\frac{\omega L_c I_d}{V_s} = \frac{X_c I_d}{V_s}$ comes up

a lot in rectifiers + is called Reactance Factor

waveforms

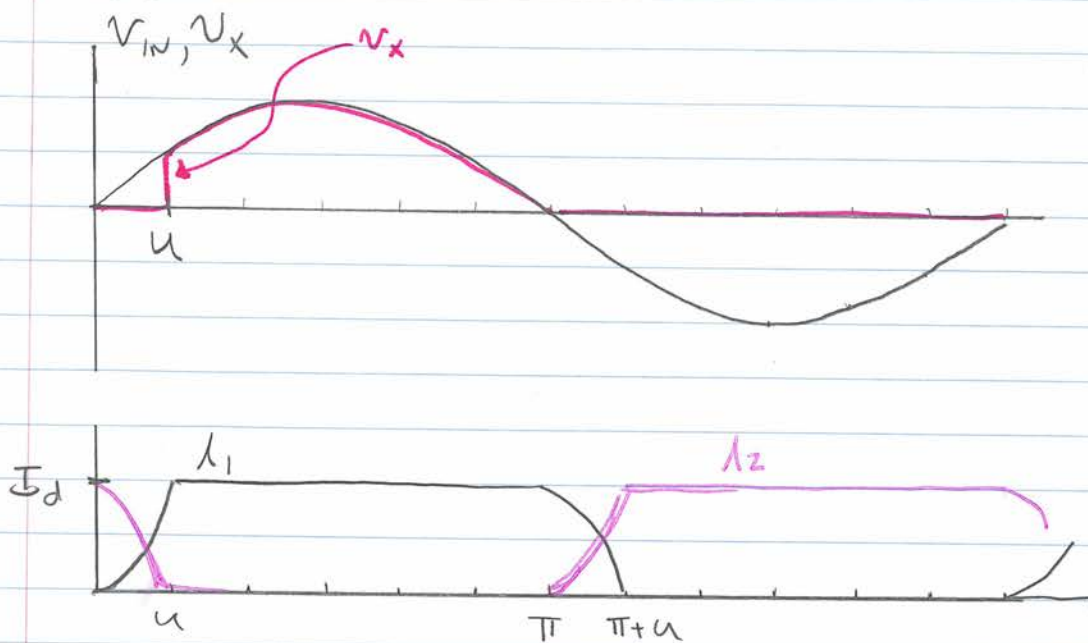

We lose a piece of V_x (and average output voltage) due to commutation (during which V_x is zero.) This in turn causes a reduction in filtered output voltage

$$\begin{aligned}
 V_o = \langle V_x \rangle &= \frac{1}{2\pi} \int_{\alpha}^{\pi} V_s \sin(\varphi) d\varphi \\
 &= \frac{V_s}{2\pi} \left[\cos(\alpha) - \cos(\pi) \right]
 \end{aligned}$$


Plugging in for $\cos(\alpha)$ from our previous calculation

$$V_o = \langle V_x \rangle = \frac{V_s}{2\pi} \left[2 - \frac{\omega L_c I_d}{V_s} \right]$$

$$\star \quad V_o = \frac{V_s}{\pi} \left[1 - \frac{1}{2} \frac{\omega L_c I_d}{V_s} \right]$$


From this we can see:

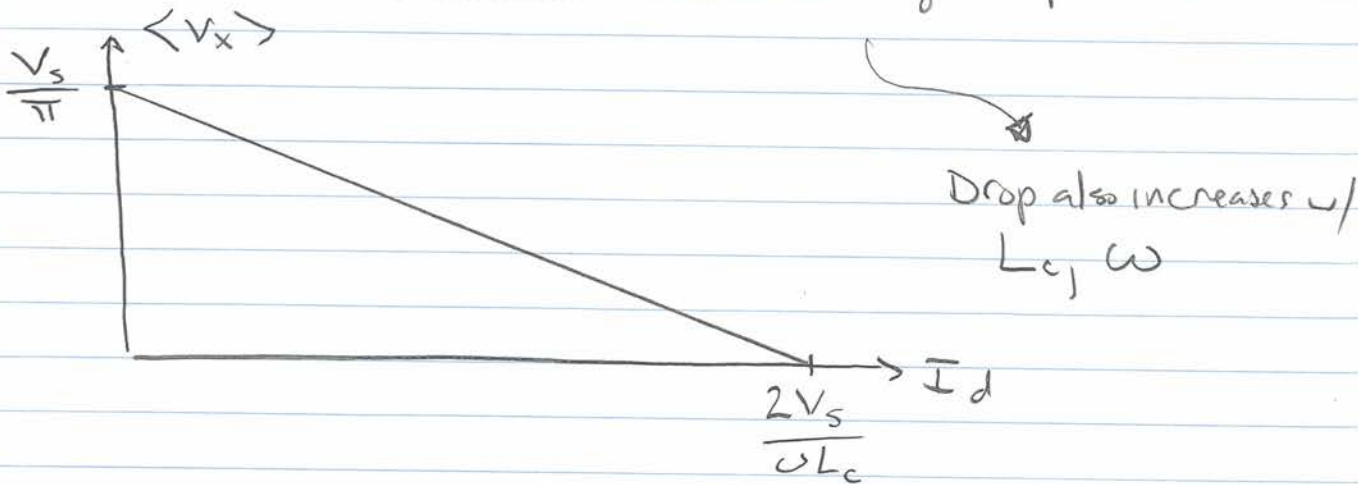as load current increases output voltage drops!



@ open ckt we get same $\langle V_o \rangle$ as with no L_c . As current increases, V_o drops. This is known as LOAD REGULATION, and is typically disliked (we often want constant output voltage independent of load.)

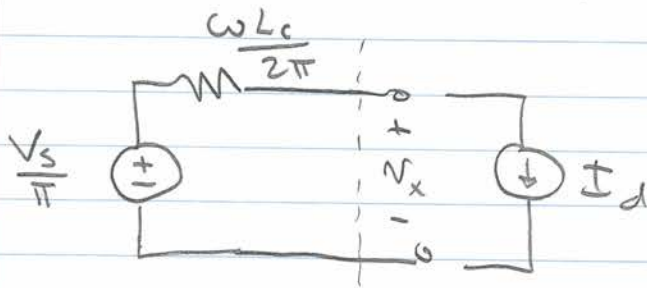we could model this (in an Average sense) as



Note that this is only valid in terms of average $V-I$ characteristics. No Real dissipation occurs!

Note: Load regulation is important in many applications.

1. It dominates the performance of automotive alternators
2. It impacts the behavior of dc/dc converters
3. It determines how circuits behave under short-circuit conditions

MAIN POINTS :

1. AC-side reactance in rectifier circuits introduces a commutation interval during which multiple devices are on so current can switch between them. This period is μ long. For HW rectifier

$$\cos \mu = 1 - \frac{x_c I_d}{V_s}$$

2. The commutation period causes the output voltage to be held low during commutation. The longer the commutation, the lower the output voltage.

\Rightarrow This introduces load regulation of the output.

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>