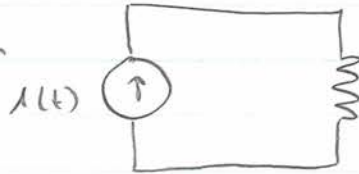


DEFINITIONS + IDENTITIES

1. The RMS (root-mean-square) of a waveform:

$$X_{\text{rms}} \triangleq \sqrt{\frac{1}{T} \int_{\langle T \rangle} X^2(t) dt}$$

This is useful: given



$$p(t) = i(t)^2 R$$

$$\langle P \rangle = \frac{1}{T} \int i(t)^2 R dt = I_{\text{RMS}}^2 R$$

The rms is the dc (current or voltage) that gives the same avg. power dissipation in a resistor as the time-varying waveform.

2. Two waveforms are orthogonal on $[a, b]$ iff

$$\int_a^b x(t)y(t) dt = 0$$

Now $\int_0^{2\pi} \sin(mt) \sin(nt + \theta) d(\omega t) = 0$ if $n \neq m$

\Rightarrow sinusoids w/ different frequencies are orthogonal

$$\int_0^{2\pi} \sin(\omega t) \cos(\omega t) = 0$$

\Rightarrow sin + cos are orthogonal

In general


$$\frac{1}{2\pi} \int_0^{2\pi} \sin(\omega t) \sin(\omega t + \phi) d(\omega t) = \frac{1}{2} \cos \phi$$

6.334 Lecture Notes

Power Factor

BACKGROUND:

Suppose we plug a resistor into the wall

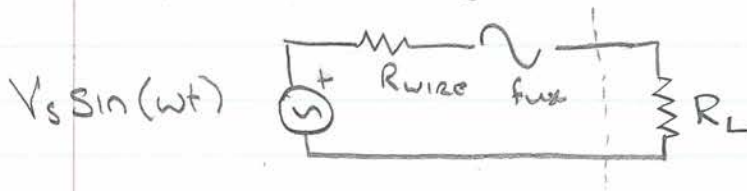

NEGLECTING R_{WIRE} :


$$P = \langle V(t) I(t) \rangle$$

$$= \langle I(t)^2 R \rangle$$

$$= I_{\text{RMS}}^2 R_L$$

@ 115 V_{rms}, 15 A fuse, we can draw $P \approx 1.7 \text{ kW}$ from wall (neglecting R_{WIRE})

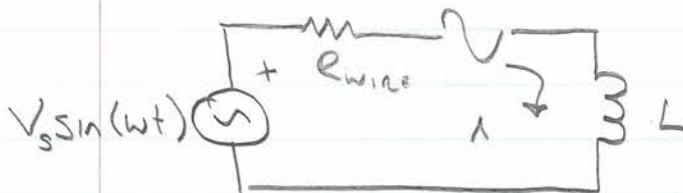Suppose instead we plug an inductor into the wall



NEGLECTING R_{WIRE}

$$I = \int \frac{V}{L} dt = -\frac{V_s}{\omega L} \cos(\omega t)$$

$$\text{so } \langle P \rangle = -\frac{1}{2\pi} \frac{V_s^2}{\omega L} \int_0^{2\pi} \sin(\omega t) \cos(\omega t) d(\omega t) = \textcircled{1}$$

BECAUSE SINE, COSINE ARE ORTHOGONAL.

⇒ THIS MAKES SENSE. INDUCTORS STORE ENERGY, NOT DISSIPATE IT.
(we slosh energy back + forth with the source)

However, while no Average power is drawn, there is instantaneous power (slosh energy into + out of wall) and rms current draw

$$I_{\text{RMS}} = \frac{V_s}{\sqrt{2} \omega L}$$

@ 115 V_{rms}, 60 Hz

⇒ $L < 20 \text{ mH} \rightarrow I_{\text{RMS}} > 15 \text{ A!}$

6.334 Lecture Notes Power Factor

While we don't dissipate energy in the load, we still dissipate energy in R_{wire} ($I_{rms} > 0$), and can blow the fuse.


⇒ In this case we are not using the power capability of the source well.

★ To provide a measure of the utilization of the source, we define Power Factor:


$$P.F. \triangleq \frac{\langle P \rangle}{V_{rms} I_{rms}}$$

← Real power P
← Apparent power S

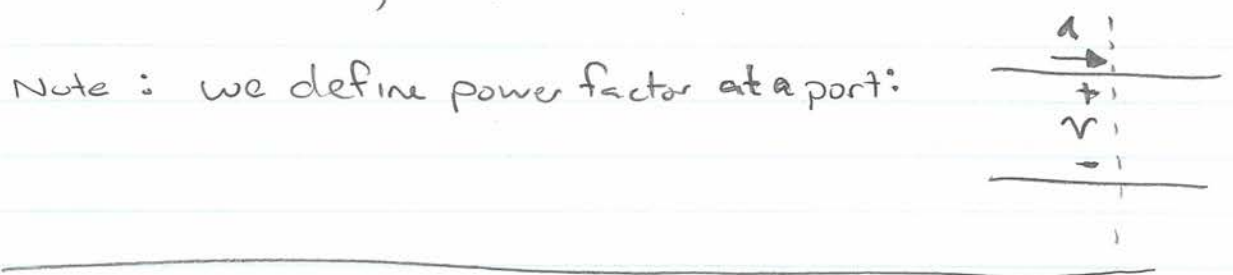For a resistor, $\langle P \rangle = V_{rms} I_{rms} \rightarrow P.F. = 1$
 an inductor, $\langle P \rangle = 0 \rightarrow P.F. = 0$



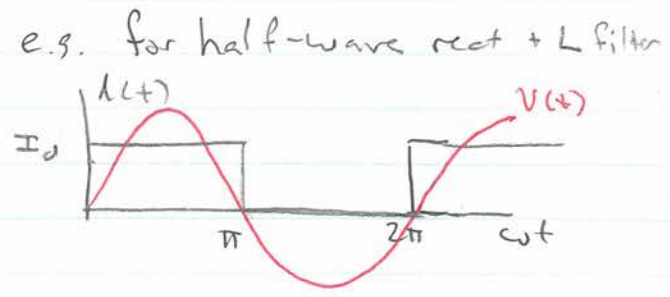★ Consider a rectifier drawing some current waveform



6.334 Lecture Notes

Power Factor

In P.S.S. we can express $i(t)$ as a Fourier Series

$$i(t) = \sum_{n=0}^{\infty} I_n \sin(n\omega t + \phi_n) \quad \text{where } \phi_0 = 90^\circ$$

For this it is easy to show:

$$I_{RMS} = \sqrt{I_0^2 + \frac{I_1^2}{2} + \frac{I_2^2}{2} + \dots + \frac{I_n^2}{2} + \dots}$$

we can calculate power as:

$$\begin{aligned} \langle P \rangle &= \frac{1}{2\pi} \int_0^{2\pi} V_s \sin(\omega t) \sum_{n=0}^{\infty} I_n \sin(n\omega t + \phi_n) d(\omega t) \\ &= \sum_{n=0}^{\infty} V_s I_n \cdot \frac{1}{2\pi} \int_0^{2\pi} \sin(\omega t) \sin(n\omega t + \phi_n) d\omega t \end{aligned}$$

from our orthogonality theorem, all but $n=1$ term $\rightarrow 0$

$$\langle P \rangle = V_s I_1 \cdot \frac{1}{2\pi} \int_0^{2\pi} \sin(\omega t) \sin(\omega t + \phi_1) d(\omega t)$$

from identity

$$\langle P \rangle = \frac{1}{2} V_s I_1 \cos(\phi_1)$$

$$\text{or } \langle P \rangle = V_{RMS} I_{1,RMS} \cos(\phi_1)$$

So the only current that contributes to real power (average power) is the portion of the fundamental current in phase with the voltage!

6.334 Lecture Notes

Power Factor

Now: $PF = \frac{\langle P \rangle}{V_{rms} I_{rms}}$

$$= \frac{V_{rms} I_{1,rms} \cos(\phi_1)}{V_{rms} I_{rms}}$$

$$\therefore P.F. = \underbrace{\left(\frac{I_{1,rms}}{I_{rms}} \right)}_{k_d \text{ distortion factor}} \cdot \underbrace{\cos(\phi_1)}_{k_\theta \text{ displacement factor}} = k_d \cdot k_\theta$$

k_d distortion factor ($0 \leq k_d \leq 1$) tells us how much utilization is reduced because of harmonic currents that don't contribute real power

k_θ = Displacement factor ($|k_\theta| < 1$) tells us how much utilization of the source is reduced because of phase shift between voltage + fundamental current

★ SHOW DEMO HERE ⇒ SEE NEXT PAGE

Note: ① point out that since voltage is sinusoidal, due to orthogonality we only xfer power from fundamental current, and only from that component in-phase with the voltage -


② Breakdown ^{+ interpretation} becomes more complex if both $v + i$ are nonsinusoidal. Less usual case but we can still define P.F.

$$k_d = \sqrt{\frac{1}{1 + (THD)^2}} \quad \left[\frac{1}{k_d^2} = 1 + (THD)^2 \right]$$

If time, introduce $THD \triangleq \sqrt{\frac{\sum_{n \neq 1} I_n^2}{I_1^2}}$ Total Harmonic Distortion

Rms of Harmonic content normalized to rms of fundamental
 → assumes no dc content

DEMO

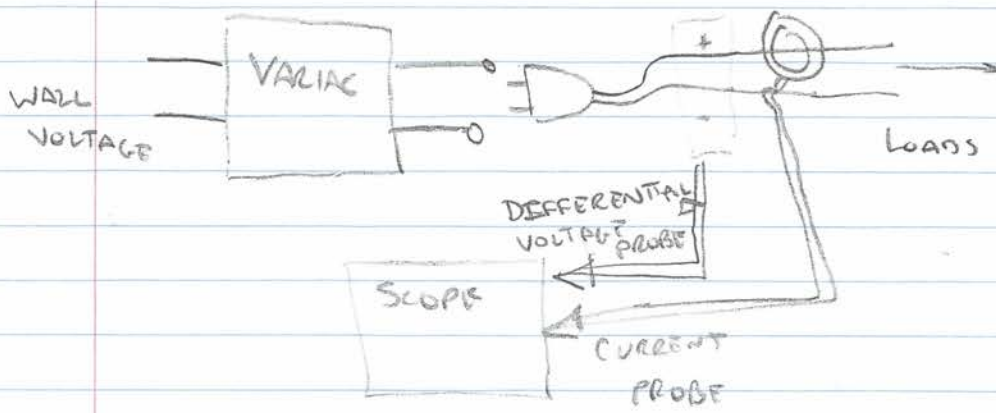

① DESK LAMP
W/ AC CONTROLLER

② PEAK DETECT
RECTIFIER W/
LIGHTBULB

③ 1 ϕ INDUCTION
MOTOR
PF \approx 0.25, $\frac{1}{3}$ HP

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>