

## Lecture 5 — Intro to DC/DC

**1 First Averaged Circuit Rules**

KCL

$$\sum_j i_j = 0$$

$$\frac{1}{T} \int_T \sum_j i_j dt$$

$$\sum_j \frac{1}{T} \int_T i_j dt$$

$$\sum_j \langle i_j \rangle = 0$$

KCL applies to time averaged currents (constant charge).


The same is true for KVL ( $\sum_k \langle V_k \rangle = 0$ ).

So for a power converter in periodic steady state:


1. Averaged KCL  $\sum_j \langle i_j \rangle = 0$
2. Averaged KVL  $\sum_k \langle V_k \rangle = 0$
3. Capacitor in P.S.S.  $\langle \lambda_c \rangle = 0$
4. Inductor in P.S.S.  $\langle V_L \rangle = 0$
5. If system lossless (Conservation of energy)  $\langle P_{in} \rangle = \langle P_{out} \rangle$
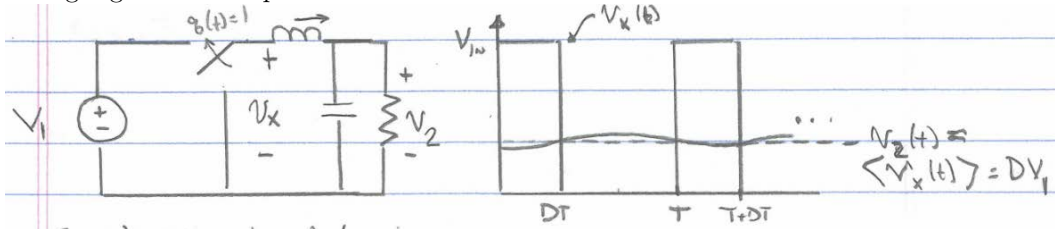
## 2 Review

Switching regulator example "Buck Converter"



Sometimes implemented as:

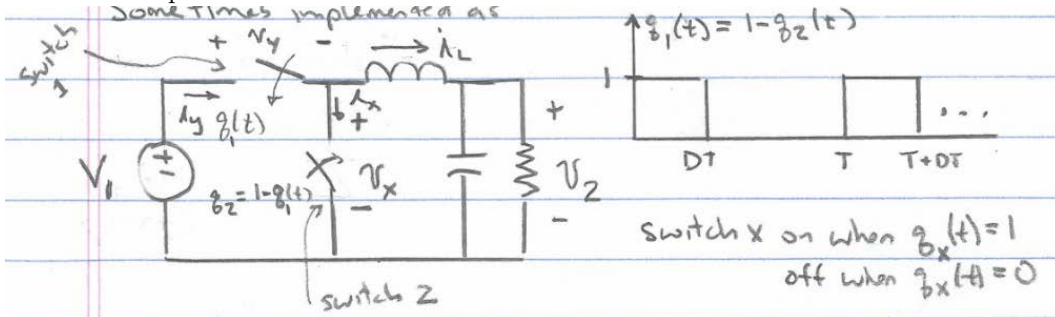

Text on bottom: Switch X on when \$q\_x(t) = 1\$, off when \$q\_x(t) = 0\$


Assuming \$L\_s\$ and \$C\_s\$ are very big: \$v\_0(t) = V\_0, i\_2(t) = I\_2\$

Using average relation in P.S.S. \$\langle v\_L \rangle = \langle v\_x \rangle - \langle v\_2 \rangle\$

$$\langle v_L \rangle = \frac{1}{T} [DT(v_1 - v_2) + (1 - D)T(-v_2)] = 0 \Rightarrow V_2 = DV_1$$
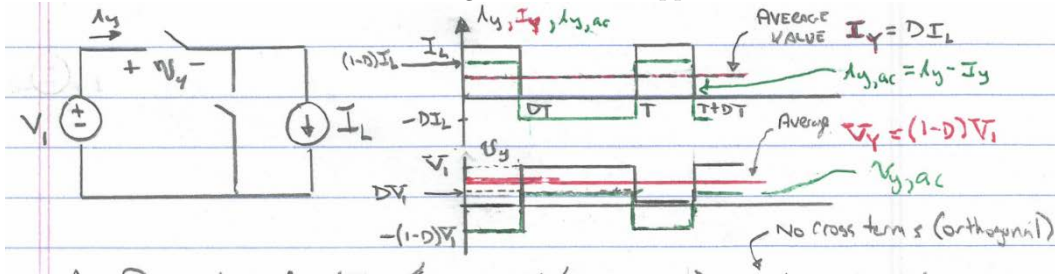
### 2.1 Aside

What do switch 1 and switch 2 do? Let's ignore inductor ripple.



Average power into switch 1:

$$\langle P_1 \rangle = \langle (V_Y + v_{Y,AC})(I_Y + i_{Y,AC}) \rangle = \langle V_Y I_Y \rangle + \langle v_{Y,AC} i_{Y,AC} \rangle$$

Where the right side has no cross terms (orthogonal)

$$\begin{aligned} \langle P_1 \rangle &= D(1 - D)I_L V_1 + \{D[-(1 - D)^2 I_L V_1] + (1 - D)[-D^2 I_L V_1]\} \\ &= D(1 - D)I_L V_1 - D(1 - D)I_L V_1 = 0 \end{aligned}$$

Where the **first term is average power into switch due to \$i\_L v\$** and the **second term is average power into switch due to \$i\_{ac,l}, v\$** (Could not exactly read this part from original notes)

Switch \$S\_1\$ takes average power in from the current, voltage and puts equal power out at ac current, voltage. Converts power (efficiently) from dc to ac waveforms! ("inverting" "switch") \$S\_2\$ does the opposite (converts power from ac waveforms to dc waveforms!) (rectifying switch)

### 3 Review

Consider input current:


L's, C's big,  $i_1(t) \approx I_L$

P.S.S.  $\langle i_{c2} \rangle = 0 \therefore I_2 = I_L$

P.S.S.

$$\langle I_{c1} \rangle = 0 \therefore I_1 = \langle i_1 \rangle = \langle i_y \rangle = DI_2$$

$$\therefore I_1 = DI_2$$

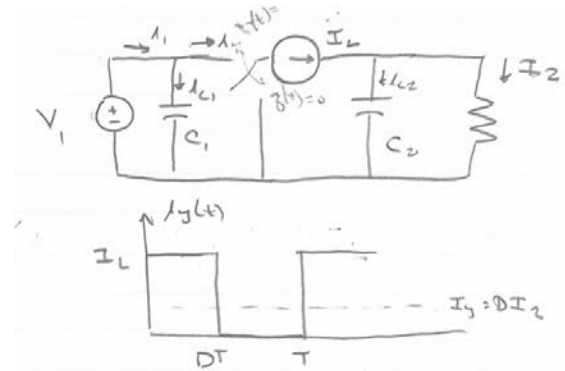


Combining with previous result that  $DV_1 = V_2$ :  $I_1V_1 = I_2V_2 \leftarrow$  Lossless system!

Note: The trick is to be careful about when one is dealing with instantaneous variables and when one is dealing with average variables!

e.g. at a given instant,  $i_y(t) \neq \langle i_y(t) \rangle$

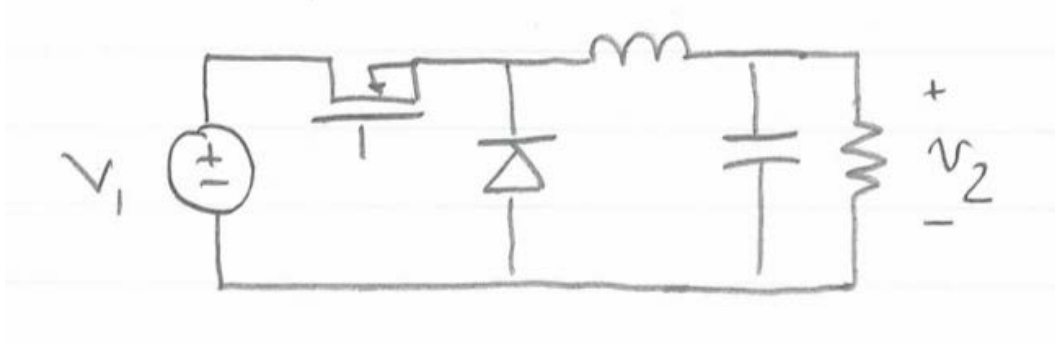
Switch implementation for this case,  $v_1, v_2 > 0$



Power flows from 1 to 2.


"Down" or "buck" converter. A type of "direct" converter because in one switch state, power flows directly from input to output.

Suppose we switch source and resistor.

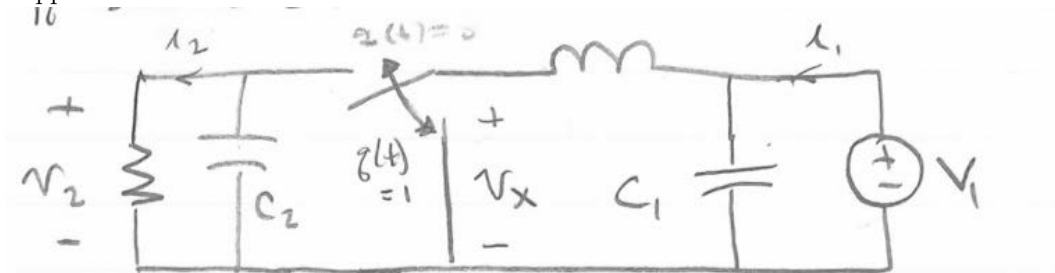

\*note: redefine  $q(t) = 1$  as switch "down" position.

If C's, L's big, same analysis:

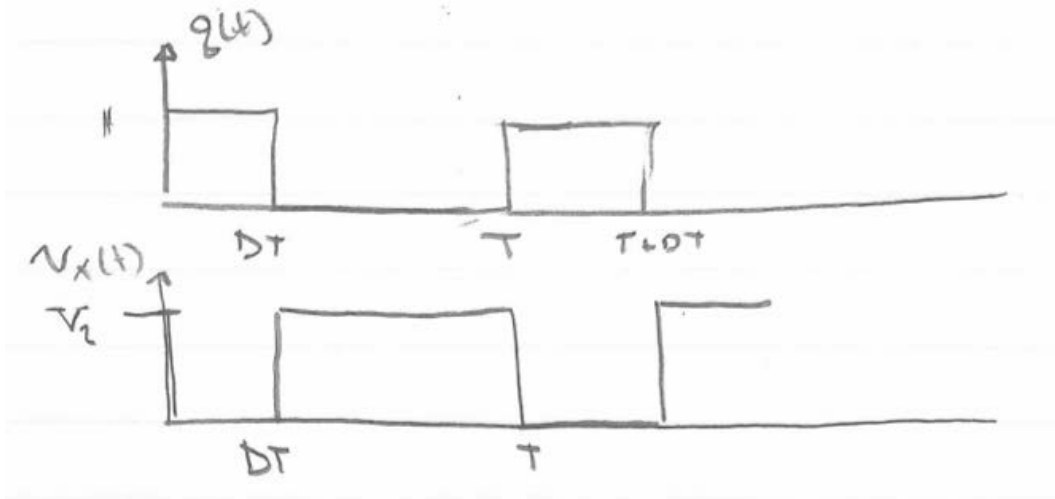



$$\langle v_L \rangle = 0 \therefore \langle v_x \rangle = (1 - D)V_2 = V_1$$

$$\therefore V_2 = \frac{V_1}{1 - D} \text{ and } \frac{I_2}{1 - D} = I_1$$


If  $v_1, v_2 > 0$ , then power flows from 2  $\leftarrow$  1 and  $v_2 > v_1$

Boost converter (or "up" converter):

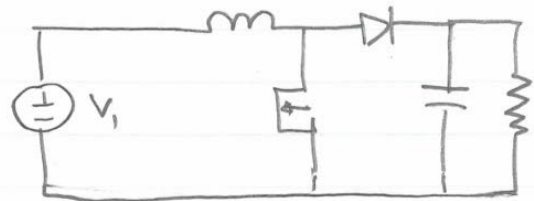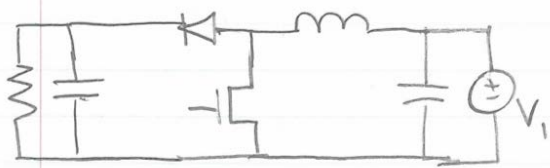Sometimes drawn  $L \rightarrow R$  power flow (But nothing fundamental about it).



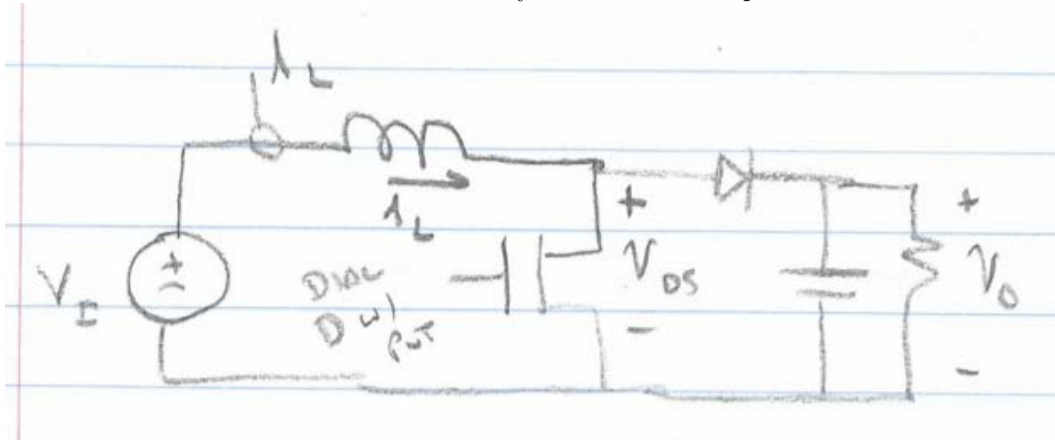\* Show boost converter demo circuit built by Katie R. and Sauparna Das



Show:


1.  $v_{DS}$
2.  $i_L$
3.  $v_0$  on scope

Explain boost operation:

- Switch turns on,  $i_L$  rises and incrementally stores energy in L from  $V_I$
- Switch turns off and this energy plus additional energy from  $V_I$  is transformed to output
- Steady state voltages are determined by  $V_2 = \frac{V_1}{1-D}$

---

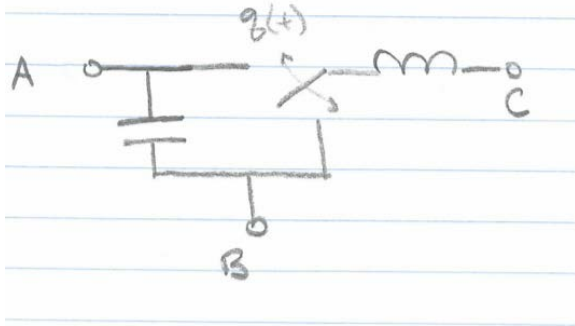Either buck or boost can be viewed as a connection of a "canonical cell"



- Direct connection has B common
- one cannot tell power flow direction without knowing
  1. external networks
  2. switch implementation
  3. control

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>