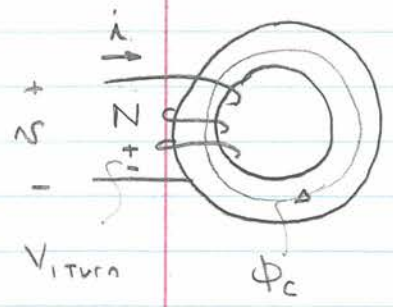


Brief review: * Given a magnetic structure, we can use Maxwell's eqn's to find the magnetic flux in the core. For magnetic materials w/ characteristic $B = \mu H$, $\Phi \propto N \cdot i$



* From Faraday's law, voltage on 1-turn of the winding is $V = - \int_{1\text{-turn}} E \cdot dl = - \frac{d\Phi_c}{dt}$ (direction by Lenz's law)

* If the flux links N turns of a winding

$$V_{\text{Total}} = N \frac{d\Phi_c}{dt}$$

Defining flux linkage $\lambda = N\Phi_c \Rightarrow V_{\text{Total}} = \frac{d\lambda}{dt} \left\{ = \frac{d}{dt}(N\Phi_c) \right\}$


* From above, we have $\lambda \propto i \Rightarrow \lambda = Li$ { Proportionality constant is L, $\propto N^2$ }

⇒ Can show DEMO of voltage buildup across turns of an inductor (Circuit on last page. Can also be used for B-H loops, Hysteresis, ...)

To rapidly calculate Φ in complicated structures (and find inductance, voltages, etc.) we can use reluctance models (magnetic circuit models)

Magnetic Circuits: An analogue of electric circuits for magnetics

Electric		Magnetic
v	↔	Magnetomotive Force/MMF Ni
	↔	magnetic flux Φ
Resistance $R = \frac{l_x}{\sigma_x A_x}$	↔	Reluctance $\mathcal{R} = \frac{l_x}{\mu_x A_x}$

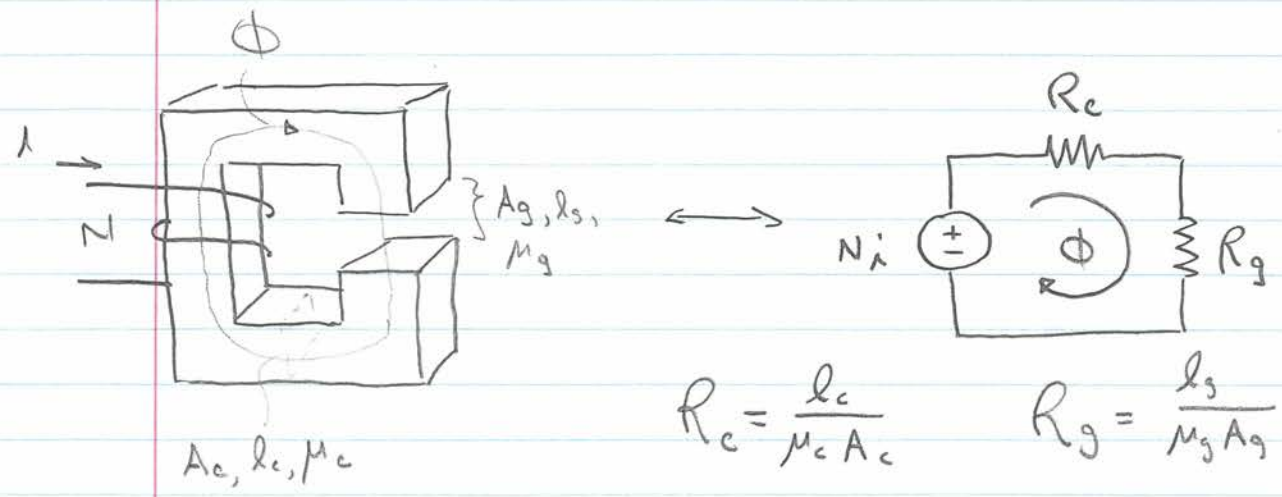

$$R_c = \frac{l_c}{\mu_c A_c} \quad R_g = \frac{l_g}{\mu_g A_g}$$


$$\therefore \phi = \frac{Ni}{R_c + R_g} = \frac{Ni}{\frac{l_c}{\mu_c A_c} + \frac{l_g}{\mu_g A_g}} = \frac{N^2}{R_{NET}} \cdot i$$

To find terminal voltage, find λ ; $v = \frac{d\lambda}{dt}$

$$\lambda = N\phi = \left[\frac{N^2}{\left(\frac{l_c}{\mu_c A_c} + \frac{l_g}{\mu_g A_g} \right)} \right] \cdot i = Li$$

Note:
 $L \propto N^2$
 + depends on μ , geometry
 $L = \frac{N^2}{R_{NET}} = A_L N^2$
 "specific inductance"

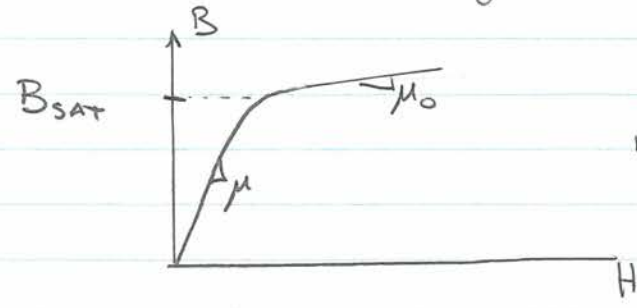Notes: ① These relations rely on material property
 $B = \mu H$. More generally, however, we see $B = f(H)$




Above some flux density B_{SAT} , material saturates $\frac{\partial B}{\partial H} \rightarrow \mu_0$

★ We must operate $B < B_{SAT}$ to use the simple model
 (Iron $B_{sat} \sim 2T$, $\mu \sim 10^4 \mu_0$)

② This simple "lumped element" model assumes simple, well-defined paths through which flux flows. Becomes more accurate for $\mu_c \gg \mu_0$, $l_c \gg \sqrt{A_c}$, $l_g \ll \sqrt{A_c}$, ...

Transformers:

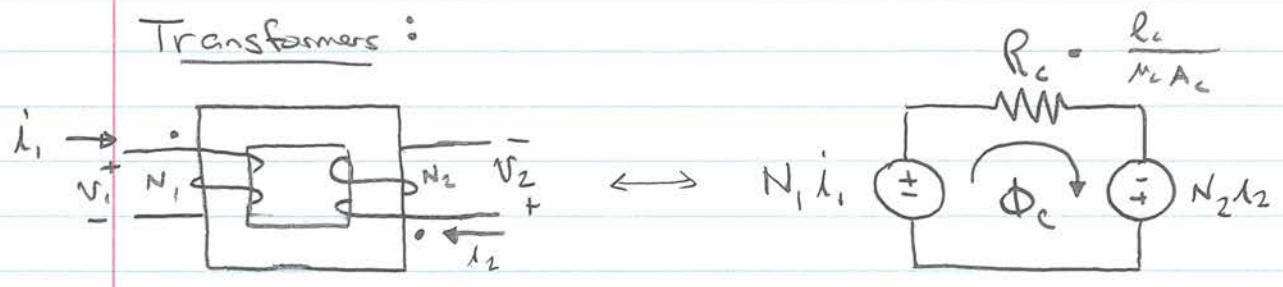


* "Dot" convention: currents into the dots throw flux around the core in the same direction

$$\left. \begin{aligned} v_1 &= \frac{d\lambda_1}{dt} = N_1 \frac{d\Phi_c}{dt} \\ v_2 &= \frac{d\lambda_2}{dt} = N_2 \frac{d\Phi_c}{dt} \end{aligned} \right\} \boxed{v_2 = \frac{N_2}{N_1} v_1} \quad (\text{Note polarity wrt dots!})$$

currents: $\Phi_c = \frac{N_1 i_1 + N_2 i_2}{R_c} \Rightarrow N_1 i_1 + N_2 i_2 = \Phi_c R_c$

If $\mu_c \rightarrow \infty, R_c \rightarrow 0$, so for finite Φ_c : $\boxed{N_1 i_1 = -N_2 i_2}$

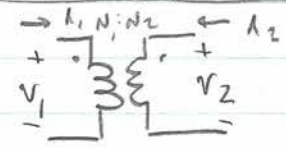⇒ These are the "ideal" transformer relations



Consider nonidealities: #1 Magnetizing


Since $\mu_c < \infty, R_c > 0 \therefore N_1 i_1 + N_2 i_2 = \Phi_c R_c \neq 0$
(there is an error in the current relation)

Consider $i_2 = 0$ (open circuit secondary)

$$\Phi = \frac{N_1 i_1}{R_c} \rightarrow v_1 = \frac{N_1^2}{R_c} \frac{d\lambda_1}{dt} = L_{\mu_1} \frac{d\lambda_1}{dt}$$

6.334 Lecture

Magnetics #2

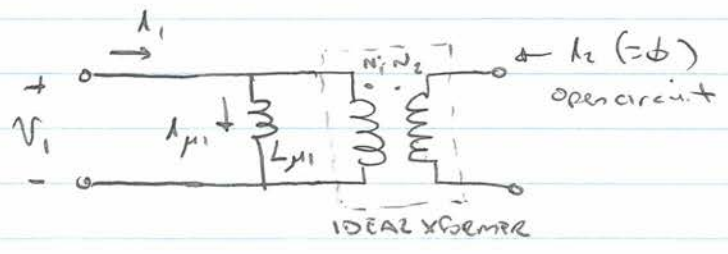

Magnetizing Inductance reflects the fact that there is some nonzero energy stored in the core ($\frac{1}{2} L_{\mu 1} i_1^2$) in the process of inducing voltage between windings

Could place magnetizing L on other side of transformer with appropriate scaling for turns ratio $L_{\mu 2} = (\frac{N_2}{N_1})^2 L_{\mu 1}$

Magnetization of the core is the reason transformers can't work @ dc

$$V_1 = N_1 \frac{d\Phi}{dt} \Rightarrow \Phi_c = \frac{1}{N_1} \int V_1(t) dt$$


we require $\Phi_c < B_{SAT} A_c$

$$\therefore \int V_1(t) dt < N_1 B_{SAT} A_c$$

we have a fundamental Volt-sec limit on the transformer to avoid saturation!

Leakage Inductance

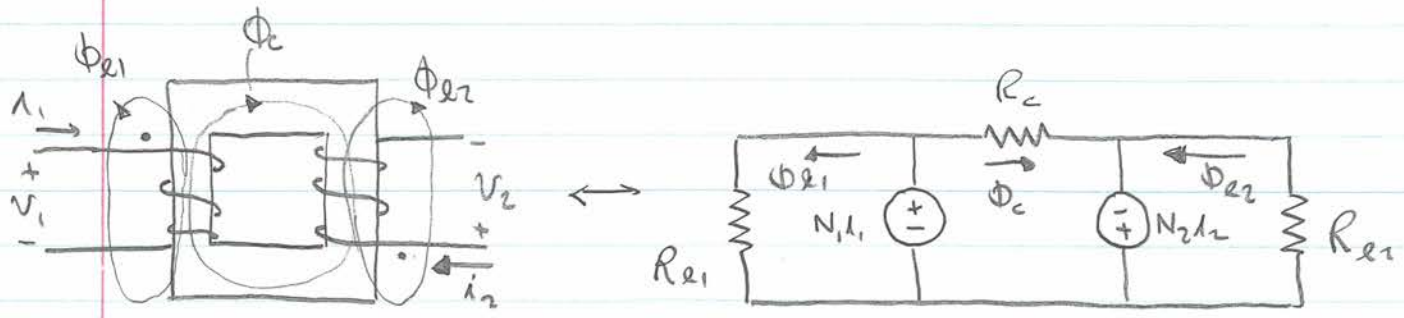In reality, all flux does not follow the core, so some flux from each winding does not link the other:



$$\Phi_{e1} = \frac{N_1 i_1}{R_{e1}} \quad \Phi_c = \frac{N_1 i_1 + N_2 i_2}{R_c} \quad \Phi_{e2} = \frac{N_2 i_2}{R_{e2}}$$

$$\lambda_1 = N_1 (\Phi_{e1} + \Phi_c) = \frac{N_1^2}{R_c} i_1 + \frac{N_1^2}{R_{e1}} i_1 + \frac{N_1 N_2}{R_c} i_2$$


$$\lambda_2 = N_2 (\Phi_c + \Phi_{e2}) = \frac{N_1 N_2}{R_c} i_1 + \frac{N_2^2}{R_c} i_2 + \frac{N_2^2}{R_{e2}} i_2$$

$$\begin{bmatrix} \lambda_1 \\ \lambda_2 \end{bmatrix} = \begin{bmatrix} \frac{N_1^2}{R_c} + \frac{N_1^2}{R_{e1}} & \frac{N_1 N_2}{R_c} \\ \frac{N_1 N_2}{R_c} & \frac{N_2^2}{R_c} + \frac{N_2^2}{R_{e2}} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} L_{11} & L_M \\ L_M & L_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L_{11} & L_M \\ L_M & L_{22} \end{bmatrix} \begin{bmatrix} \dot{i}_1 \\ \dot{i}_2 \end{bmatrix} \quad \begin{matrix} \text{Inductance Matrix} \\ \text{Description} \end{matrix}$$

Both magnetizing inductance + leakage inductance are important effects in practical xformers!

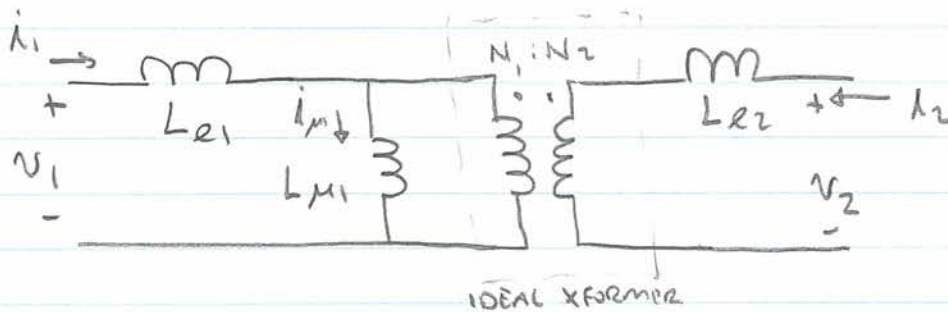It is easy to show that this description corresponds to a circuit model:



where: $L_{e1} = \frac{N_1^2}{R_{e1}} \quad L_{m1} = \frac{N_1^2}{R_c} \quad L_{e2} = \frac{N_2^2}{R_{e2}}$

and $L_{11} = L_{e1} + L_{m1} \quad L_{22} = L_{e2} + \left(\frac{N_2}{N_1}\right)^2 L_{m1} \quad L_M = \left(\frac{N_2}{N_1}\right) L_{m1}$

So: Leakage adds "independent inductors" in series w/ xformer Leads!

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>