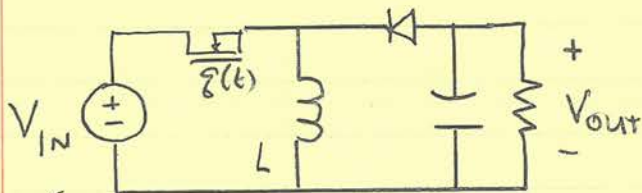


Isolated converter motivations:


1. Galvanic isolation between input + output (+ different reference nodes)
2. High conversion ratios
3. Ease of generating multiple outputs

Example #1: "Flyback" converter (isolated buck/boost)



$$\frac{V_{out}}{V_{in}} = \frac{-D}{1-D}$$


INSERT XFORMER

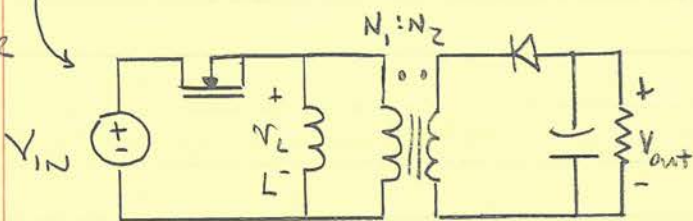

$$\langle V_L \rangle = DV_1 + (1-D) \frac{N_1}{N_2} V_2 = 0$$

$$\therefore \frac{V_2}{V_1} = -\frac{N_2}{N_1} \frac{D}{1-D}$$

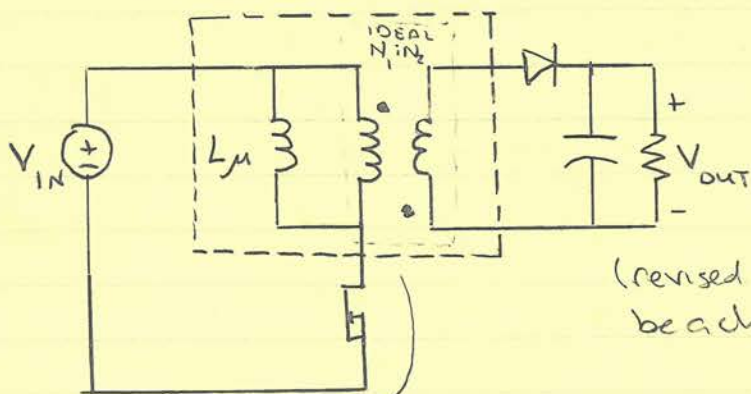No common ref:  
Can Δ switch positions + definition of V<sub>out</sub>



$$\frac{V_2}{V_1} = +\frac{N_2}{N_1} \frac{D}{1-D}$$


(revised output polarity can be achieved when desired)

Design magnetics as one element: A gapped (energy storage) xformer where the energy is stored in the magnetizing inductance (like a buck-boost inductor w/ a second winding)  
 ⇒ most energy stored in the gap!

1<sup>st</sup> part of cycle: store energy in xformer through winding #1

2<sup>nd</sup> part of cycle: remove energy from xformer through winding #2

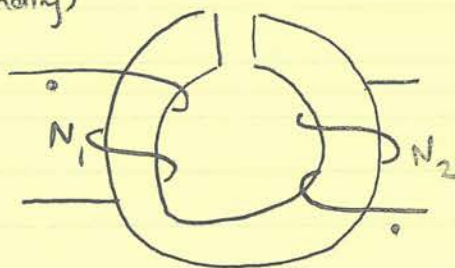
⇒ Magnetizing energy is continuous, but Lμ switches between terminals



- Notes
- ① Energy stored in the magnetizing inductance of the xformer. Design like an inductor (with gap for the energy storage) but add a second winding
  - ② Voltage inversion required in non-isolated version may be eliminated if desired by changing polarity of definition (no common terminals, so this is easy)
  - ③ Can use ground-referenced active switch
  - ④ Turns ratio helps reduce switch + component ratings (keep D near 0.5)  
Consider 1kW @  $V_{in} = 100$ ,  $V_{out} = 10$  V  
Buck/Boost  $V_{sw}, V_D = 110$  Vpk  
 $I_{sw}, I_D = 110$  Apk  
Flyback @  $N_2:N_1 = 1:10$   
 $V_{sw} = 200$  V,  $V_D = 20$  V  
 $I_{sw} = 20$  A,  $I_D = 200$  A
  - ⑤ EASY TO OBTAIN MULTIPLE OUTPUTS BY ADDING MORE WINDINGS

BETTER BALANCES DEVICES

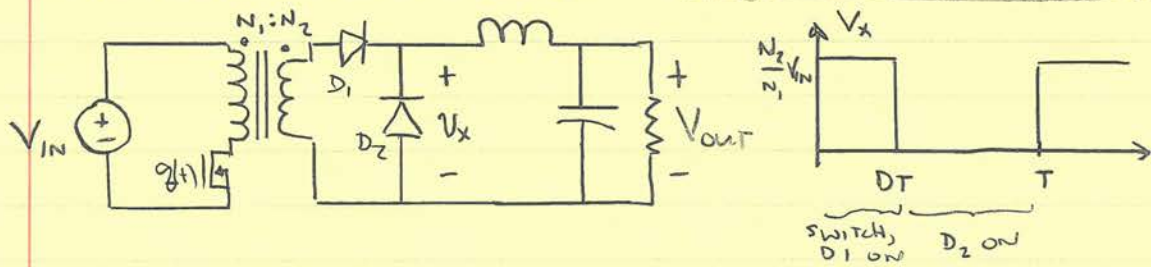Isolation in a direct converter: Single-Ended Forward Conv.



This is essentially a buck converter w/ a transformer!

$$\langle V_{out} \rangle = \langle V_x \rangle = D \left( \frac{N_2}{N_1} V_{in} \right) + (1-D) \cdot 0 \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{N_2}{N_1} D}$$




But consider the effect of the (undesired) magnetizing inductance  $L_m$  of the transformer!

- we must keep  $\langle V_{Lm} \rangle = 0$  or xformer will saturate
- must provide a path for  $L_m$  until core "resets" to zero flux

\* ⇒ Unlike in the flyback converter, the magnetizing inductance is not a desired circuit element, + hurts performance



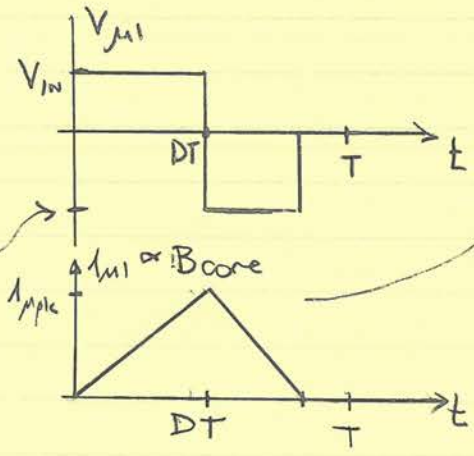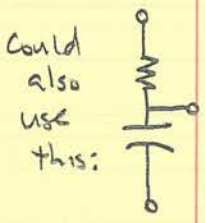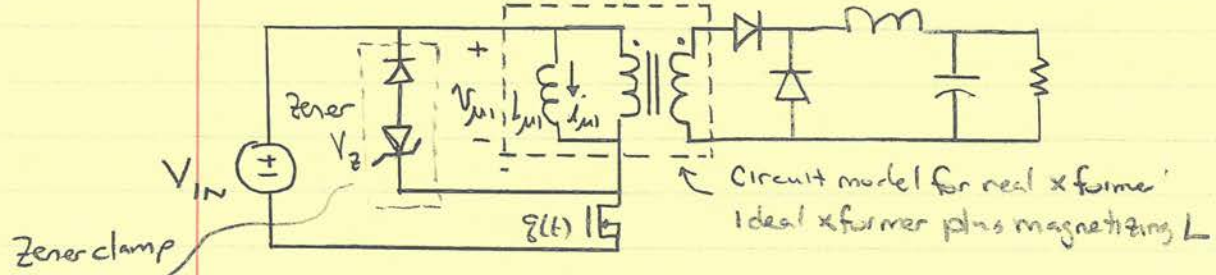We must "reset" the core flux to zero each cycle!  
 one simple method: "clamp" reset circuit



$$\lambda_{\mu 1} = L_{\mu 1} i_{\mu 1} = N_1 B_{\text{core}} A_c$$


$$\therefore B_{\text{core}} = \frac{L_{\mu 1}}{N_1 A_c} \cdot i_{\mu 1} = \frac{\lambda_1}{N_1 A_c}$$

Peak core flux  $\Delta \lambda_{\mu 1} = \frac{V_1}{L_{\mu 1}} DT$

$$\therefore B_{\text{pic}} = \frac{V_1 DT}{N_1 A_c}$$

$-V_Z$   
 (neglecting reset diode drop)

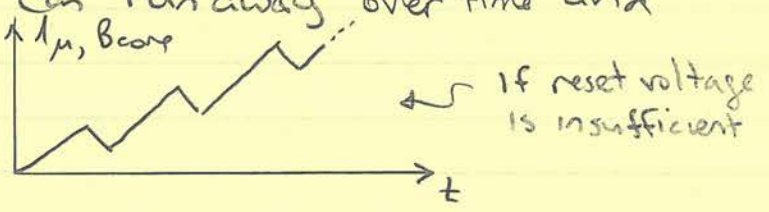We need to ensure that  $\int V_{\mu} dt \rightarrow 0$  to "reset" the core. Otherwise  $i_{\mu}$ ,  $B_{\text{core}}$  can "run away" over time and saturate the core:



To reset the core:

$$V_Z(1-D)T \geq V_{IN}DT \Rightarrow V_Z \geq V_{IN} \frac{D}{1-D}$$

The peak switch voltage is  $V_{sw,pic} = V_Z + V_{IN}$

$$\text{So, } V_{pic} \geq V_{IN} \left( \frac{1-D}{1-D} \right) + V_{IN} \left( \frac{D}{1-D} \right) = V_{IN} \frac{1}{1-D}$$

@  $D_{\text{max}} = 0.5 \rightarrow V_{sw,pic} = 2V_{IN}$   
 $D_{\text{max}} = 0.75 \rightarrow V_{sw,pic} = 4V_{IN}$  } with minimum clamp voltage

This is poor compared to the non-isolated buck where  $V_{pic} = V_{IN}$ !

6.334 Lecture Notes

Isolated dc-dc #1

How much power do we lose in resetting the core this way? (we dissipate stored magnetizing energy in zero)

$$= \frac{N^2 \mu_r \mu_0 A_c}{l_c}$$


$$W_{Diss} = \frac{1}{2} L_{\mu} I_{\mu, peak}^2 = \frac{1}{2} L_{\mu} \left( \frac{V_{IN} D T}{L_{\mu}} \right)^2 = \frac{V_{IN}^2 D^2 T^2}{2 L_{\mu}}$$

$$P_{Diss} = \left( \frac{1}{T} \right) \cdot W_{Diss} = \frac{V_{IN}^2 D^2 T}{2 L_{\mu}} \quad \leftarrow f_{sw}$$

∴ we want  $L_{\mu}$  as big as possible to minimize energy stored in xformer + dissipated. ∴ we typically use an ungapped (or minimally gapped) core to maximize  $L_{\mu}$  and minimize reset loss.

Other clamp methods allow us to recover magnetizing energy:

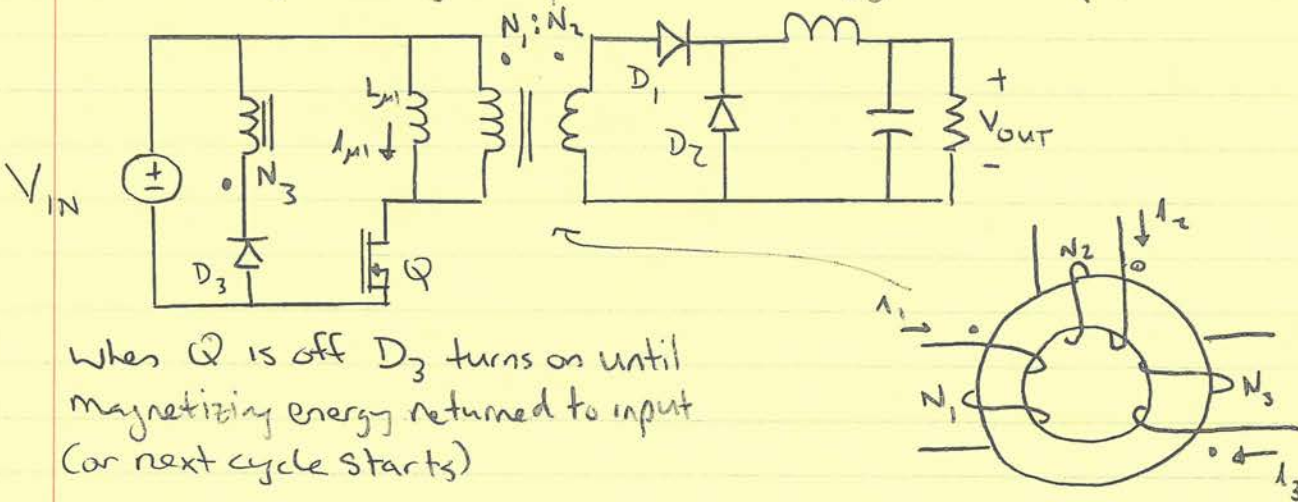① Tertiary winding clamp: recover energy back to input



When Q is off  $D_3$  turns on until magnetizing energy returned to input (or next cycle starts)

To reset the core we require


$$D V_{IN} T \leq (1-D) \left( \frac{N_1}{N_3} \right) V_{IN} T$$

The voltage stresses are the same (neglecting leakage inductance effects)

- Advantages: Magnetizing energy is (mostly) recovered  
 Disadvantages: • still need a snubber to handle leakage inductance  
 • more transformer windings.



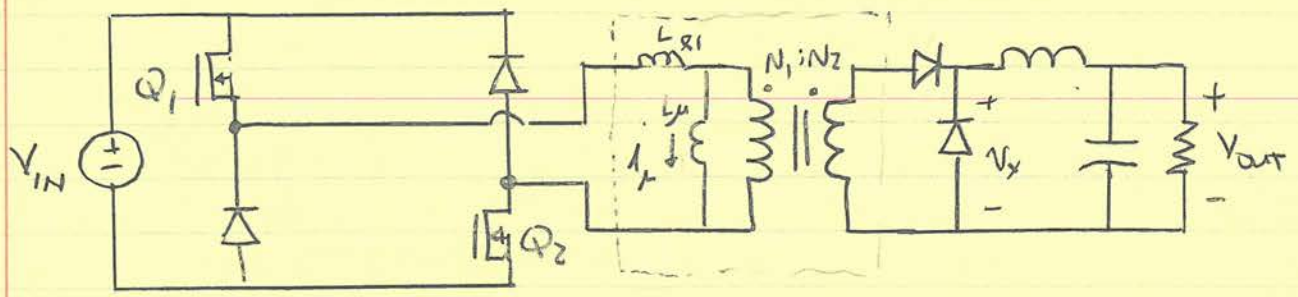② Two-switch single-ended forward converter



- Turn switches  $Q_1, Q_2$  on and off together with duty ratio  $D$ 
  - $\Rightarrow 0 < D < 0.5$  to guarantee core reset (energy recovered back to input)
  - $\Rightarrow$  leakage energy of transformer is also recaptured
- Requires two active switches, each with  $V_{s, pk} > V_{in}$  (only one is ground referenced). This compares to a single switch rated at  $> 2V_{in}$  for a normal forward with a maximum 50% duty ratio.

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>