

6.334 lecture Notes

Switching Losses + Snubbers

Review

Transistor : switch (on-off) or current source \downarrow

Ideal Switches

- instantaneously turn on and turn off
 - on-state: zero voltage drop or zero resistor
 - off-state: zero current flow or infinite resistor
 - no parasitics
- \Rightarrow zero loss

Practical Switches


- finite time for turn on and turn off
 - on-state: a voltage drop or a resistor
 - off-state: leakage current
 - parasitics: include a parallel capacitor
 - may include an anti-parallel diode
 - \Rightarrow non-zero losses
- conduction loss
 switching loss \leftarrow snubbers
 gating loss
 other losses

on-state: a voltage drop


fully-controlled

recall DC/DC lecture 2



can: block +v carry +i

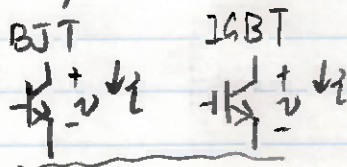

half-controlled

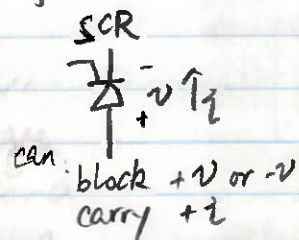


uncontrolled

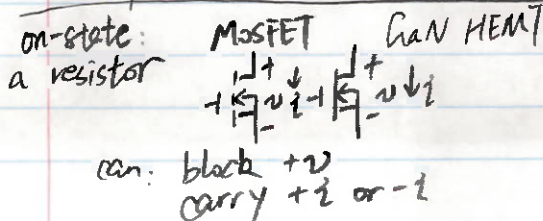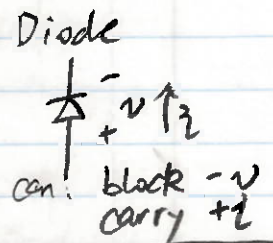

Semiconductor Losses (Back of the envelope)

Example: Buck converter:

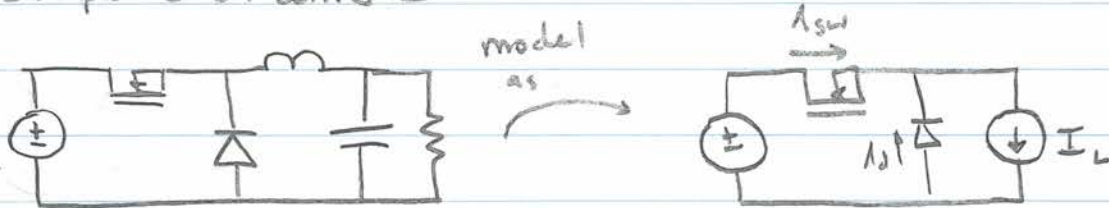


Assume non-ideal switch, ideal diode

Device Conduction losses:

MOSFETS look ~ resistor $P_{FET, cond} \approx I_{sw, rms}^2 R_{ds, on} = (I_L^2 D) R_{ds, on}$
 Diodes look ~ const drop $P_{d, cond} \approx \langle I_d \rangle V_{d, on} = I_L D' V_{d, on}$

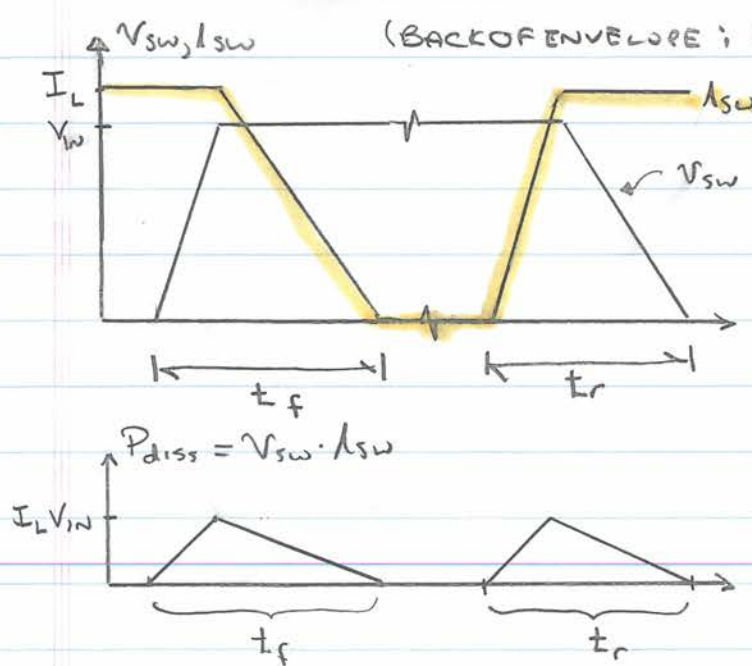Device Switching losses: { occur as switches turn on and off }



★ TURN OFF OF MOSFET
 Current falls AFTER device voltage rises, because diode can't turn on (carry current) until $V_d \rightarrow 0$

★ TURN ON OF MOSFET
 Current in mosfet must rise to full value (diode current goes to 0) before diode turns off + blocks voltage

t_f, t_r governed by devices + drivers

$$P_{sw, fet} \approx \left[\frac{1}{2} t_f I_L V_{in} + \frac{1}{2} t_r I_L V_{in} \right] f_{sw}$$

(Based on approximate linear transitions. Other losses and diode losses exist)



6.334 Lecture Notes

Switching Losses + Snubbers

Note: major loss component $\propto f_{sw}$. We want $f_{sw} \uparrow$ to make $L, C \downarrow$ but losses ultimately limit us.

We would like $t_r, t_f \downarrow$ to reduce switching loss, but other factors come into play:

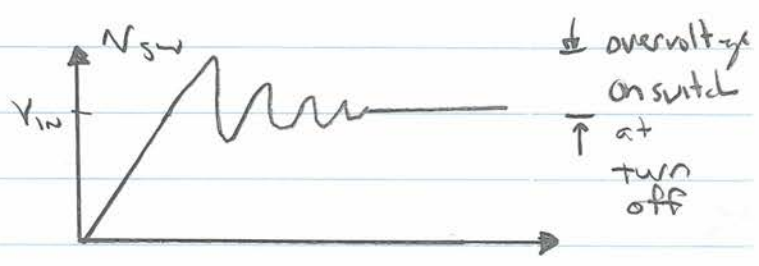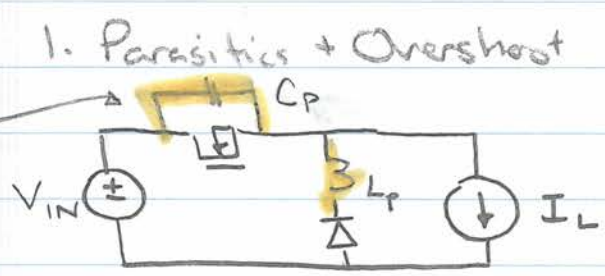lose capacitor energy
 $W = \frac{1}{2} C_p V_{sw}^2$
Switch turn on



2. EMI

High $\frac{dI}{dt}, \frac{dV}{dt}$ lead to EMI, may affect control circuits

$\frac{dI}{dt} \rightarrow$ magnetic coupling $V = L_M \frac{dI}{dt}$

$\frac{dV}{dt} \rightarrow$ capacitive coupling $I = C \frac{dV}{dt}$

3. Rate limits

\rightarrow MOSFETS are immune to these effects.


Some devices (BJT, GTO, MCT) have limits on allowed $\frac{dV}{dt}, \frac{dI}{dt}$

high $\frac{dI}{dt} \rightarrow$ destroy device on turn on

high $\frac{dV}{dt} \rightarrow$ can trigger device back on

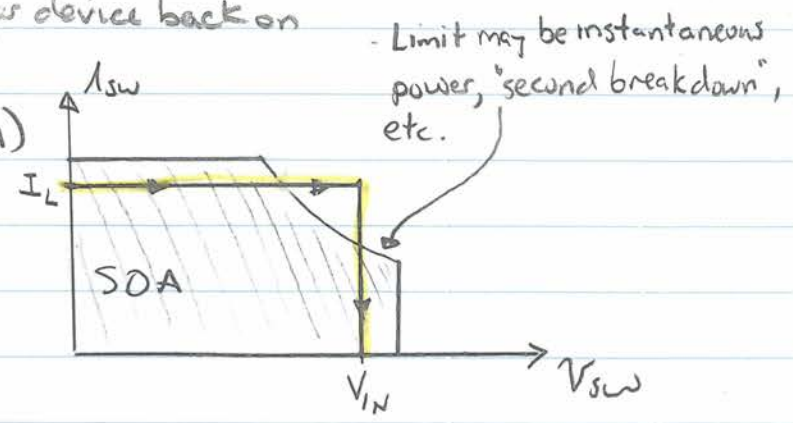4. SAFE OPERATING AREA (SOA)


Some devices cannot sustain high Simultaneous V, I .



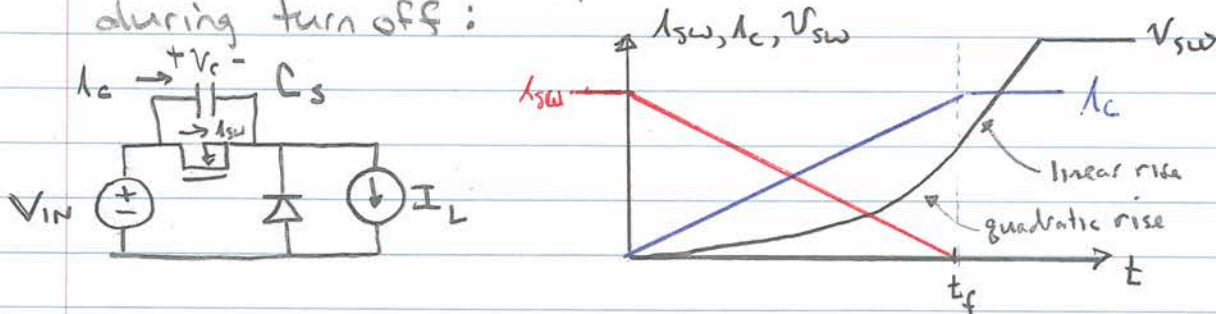6.334 Lecture Notes Switching Loss + Snubbers

- Snubbers
1. Control switching locus
 2. Reduce internal device dissipation

Suppose we placed a capacitor across the device during turn off:



I_L diverted through C_s while switch turns off:

$$I_{sw} = I_L \left(1 - \frac{t}{t_f}\right) \quad 0 < t < t_f$$

$$I_c = I_L \frac{t}{t_f} \quad 0 < t < t_f$$

$$V_c = \frac{1}{C} \int_0^t I_c dt = \frac{I_L t^2}{2 t_f C} \quad 0 < t < t_f$$

$$P_{diss,sw} = I_{sw} \cdot V_c = I_L \left(1 - \frac{t}{t_f}\right) \cdot \frac{I_L t^2}{2 t_f C} \quad 0 < t < t_f$$

$$E_{diss} = \int_0^{t_f} I_{sw} \cdot V_c dt = \frac{I_L^2}{2 t_f C} \int_0^{t_f} \left(t^2 - \frac{t^3}{t_f}\right) dt$$

$$E_{diss} = \frac{I_L^2}{2 t_f C} \left(\frac{1}{3} t_f^3 - \frac{1}{4} t_f^3 \right) = \frac{I_L^2 t_f^2}{24 C}$$

We reduce device turn-off loss with the capacitor!

We also store energy in the capacitor $E_{stored} = \frac{1}{2} C V_{in}^2$



this is $\geq \frac{1}{2} C \frac{I_L^2 t_f^4}{4 t_f^2 C^2} = \frac{I_L^2 t_f^2}{8 C}$

So: we reduce device loss @ turn off, as $C \uparrow$ loss \downarrow

- ★ But \uparrow @ switch turn on, E_{stored} on cap gets dumped into switch!
 - \rightarrow could destroy switch!
 - \rightarrow dumped energy increases as $C \uparrow$


To build effective snubbers, we remove or recover the stored energy in some other fashion!

e.g. RCD turn-off snubber

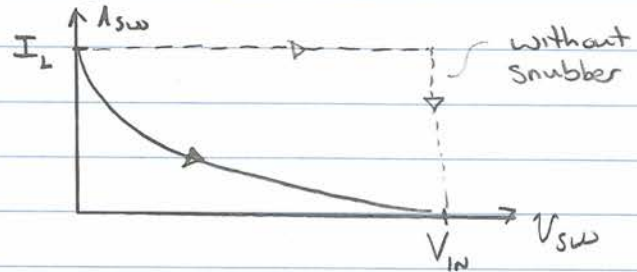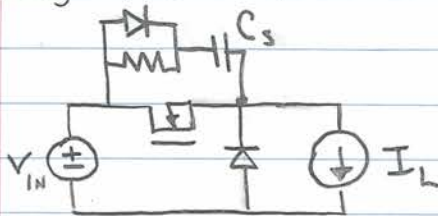

- During turn off, C_s is effectively in parallel w/ the switch
- When switch is on, capacitor stored energy is slowly dissipated in R (we need some on-time to complete the discharge)
- Snubber only operates during switching transitions
 - \Rightarrow SWITCHING LOCUS IMPROVED (SOA, lower $\frac{dV}{dt}$)
 - \Rightarrow DEVICE LOSS REDUCED (BUT TOTAL DEVICE + RESISTOR LOSS IS TYPICALLY HIGHER!)

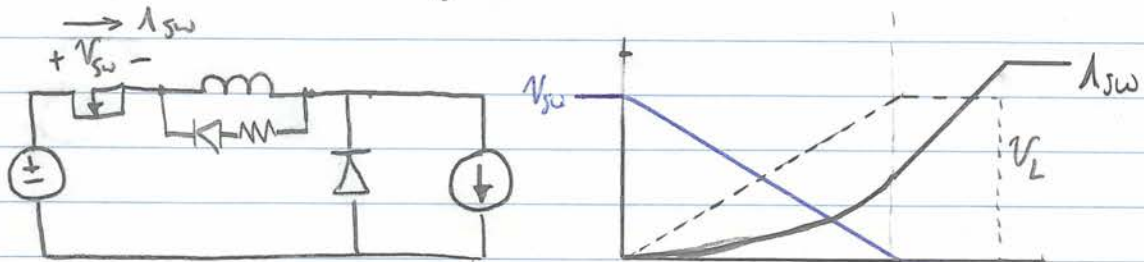We can do similar things at device turn on!



- Reduces Switch turn on losses
 - Total switch + Resistor losses may be higher with snubber
 - does not reduce loss associated with parasitic capacitance across the switch
 - controls switching locus (SOA, $dI/dt \downarrow$)
 - results in slightly increased switch voltage

NOTE: INSERT DIODE RECOVERY?

→ Could also describe gate drive techniques to get differential on/off transitions

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>