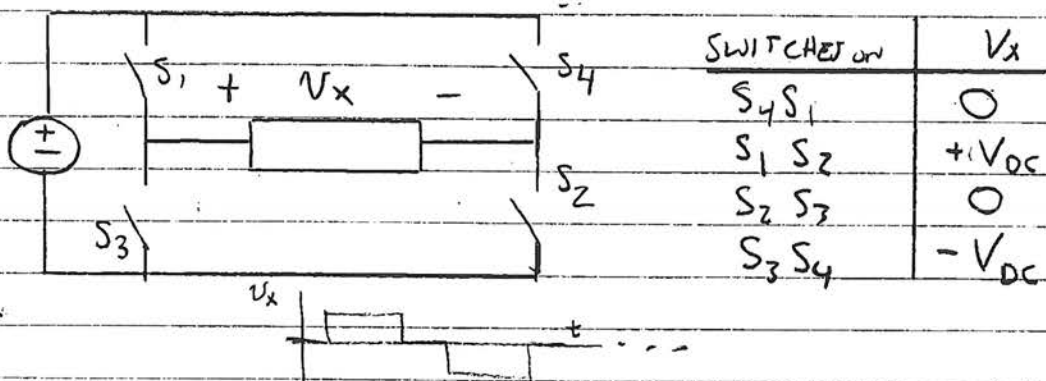


FROM LAST TIME :

1 ϕ VSI inverter bridge structure



- WE CAN SYNTHESIZE PULSING VOLTAGES +, 0, - over time,
- Filter to get desired output waveform (e.g., sinusoid.)
- Switching frequency limitations are often a practical constraint

★ \Rightarrow SHOW INVERTER MODULE FROM A TOYOTA PRIUS AS EXAMPLE

To reduce filtering requirements, we often use waveform symmetries to reduce unwanted content

$$f(t) = \frac{b_0}{2} + \sum_{n=1}^{\infty} a_n \sin(n\omega t) + b_n \cos(n\omega t)$$

$$a_n = \frac{2}{T} \int_{\langle T \rangle} f(t) \sin(n\omega t) dt, \quad b_n = \frac{2}{T} \int_{\langle T \rangle} f(t) \cos(n\omega t) dt$$

\Rightarrow for odd/even waves, synthesize odd/even patterns

\Rightarrow for half-wave symmetric outputs $f(t) = -f(t - T/2)$
 synthesize half-wave symmetric pulse patterns

(a_{2k}, b_{2k} harmonics do not exist!)

NOTE: WE CAN EXTRACT COMPONENTS IN TIME

$$f_{HWS} = \frac{f(t) - f(t - T/2)}{2} \quad ; \quad f_{HWR} = \frac{f(t) + f(t - T/2)}{2} \quad ; \quad f(t) = f_{HWS} + f_{HWR}$$

HALF-WAVE SYMMETRIC HALF-WAVE REPEATING


We have seen that by control of the width of one pulse per half cycle (and each device switching on/off once per full cycle) we can

- maintain half-wave symmetry (no even harmonics)
- eliminate triple-n harmonics (especially 3rd harmonic)
- keep odd symmetry (no cosine components)

Why? With only odd components, nth harmonic amplitude is:

$$V_n = \frac{2}{T} \int_{\langle T \rangle} f(t) \sin(n\omega_0 t) dt$$

$$f = \frac{\pi}{C}$$

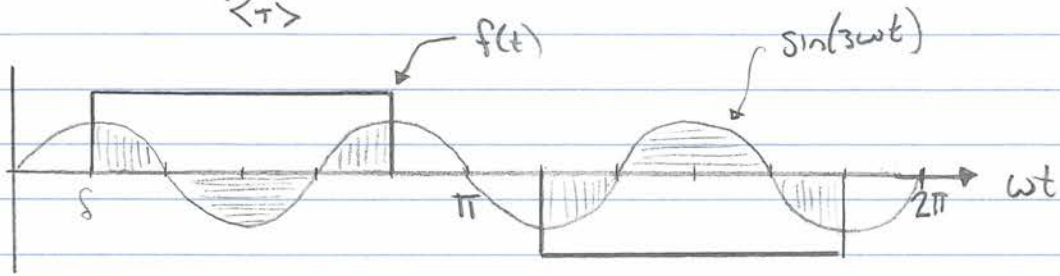


Positive area of $f(t)\sin(3wt)$ cancels negative area \therefore integral = 0!

\Rightarrow We can introduce more notches in each half cycle (for more switching transitions in each cycle) so that higher harmonics (e.g. 5th) are cancelled) while not disturbing the nulling of the 3rd. (see one example, next page)

In general: Harmonic Elimination / Programmed PWM

- \rightarrow can eliminate one odd harmonic for each pulse per half cycle (and each switching transition per a cycle)
- \rightarrow more harmonics eliminated, the higher the net device switching frequency
- \rightarrow precise timing required (μP)

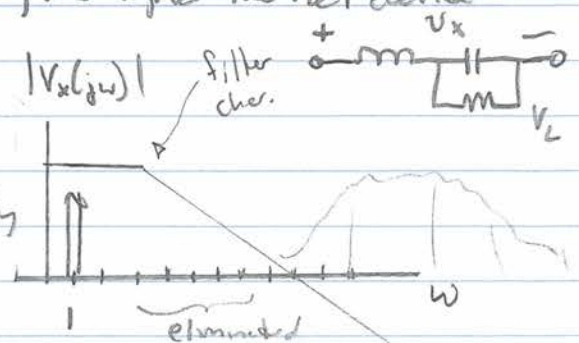\Rightarrow As more low-order harmonics are eliminated, high-order harmonics actually increase, but these are more easily filtered!



Power Electronics Notes - D. Perreault

Note: see classic papers for more on this area:

1. H. S. Patel and R. G. Hoft. "Generalized Techniques of Harmonic Elimination and Voltage Control in Thyristor Inverters: Part I—Harmonic Elimination Techniques," *IEEE Trans. Industry Applications* IA-9 (3): 310-317 (May/June 1973).
2. H. S. Patel and R. G. Hoft. "Generalized Techniques of Harmonic Elimination and Voltage Control in Thyristor Inverters: Part II—Voltage Control Techniques," *IEEE Trans. Industry Applications* IA-10 (5): 666-673 (September/October 1974).

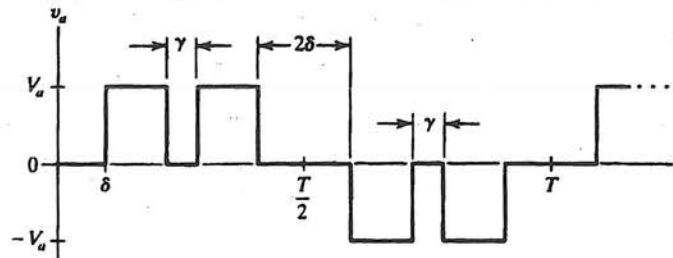


Figure 8.5 A tristate waveform containing notches of width γ .

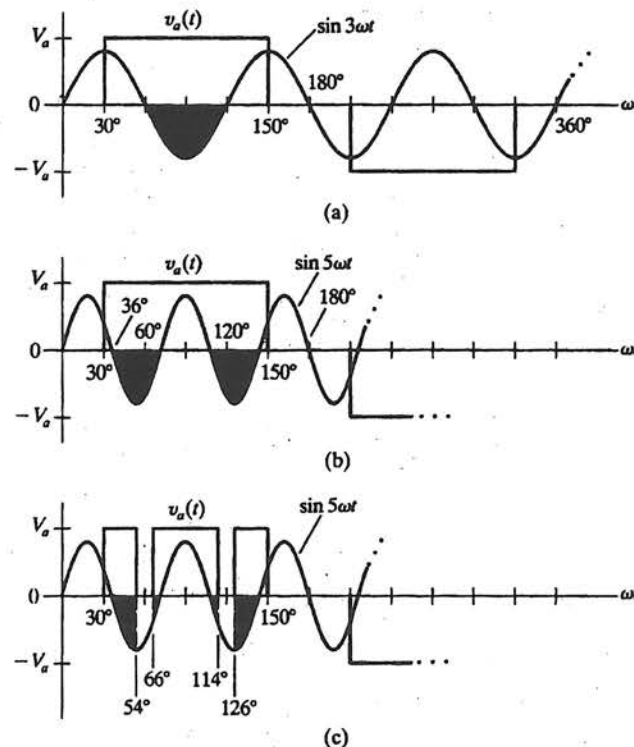


Figure 8.6 (a) Graphic representation of the integrand of (8.14). The positive (lightly shaded) and negative (heavily shaded) areas are equal, canceling the third harmonic of the square wave. (b) The third-harmonic free waveform of (a) superimposed on a fifth-harmonic sine wave. (c) The square wave notched so that it is free from both third and fifth harmonics. A fifth-harmonic sine wave illustrates that the product of it and $v_a(t)$ has zero net area.


Power Electronics Notes - D. Perreault

★ Harmonic Cancellation


Add up time-shifted waveforms to cancel desired harmonic component(s)

$$\begin{aligned} \text{IF } x(t) &= \sum A_n \sin(n\omega_0 t + \phi_n) \\ \therefore x(t-t_1) &= \sum A_n \sin(n\omega_0(t-t_1) + \phi_n) \\ &= \sum A_n \sin(n\omega_0 t + \underbrace{\phi_n - n\omega_0 t_1}_{\phi'_n}) \end{aligned}$$

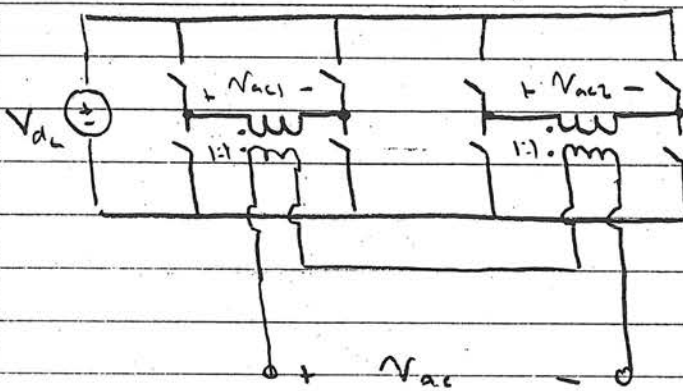
IF we time-shift to change the fundamental by an angle $\Delta\theta = -\omega_0 t_1$, we shift the n^{th} harmonic by an angle $\Delta\phi_n = n\Delta\theta$



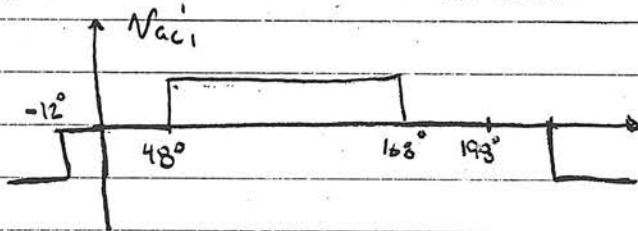
Sum 2 waveforms
 \rightarrow shift fundamentals by 36° ($\pm 18^\circ$)
 \rightarrow shift 5^{th} harmonics by 180° ($\pm 90^\circ$)



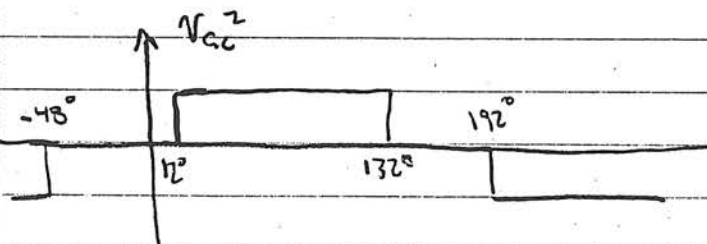1^{st} harm \rightarrow shifted by $+18^\circ$



Summed wave has no 5^{th} harmonic

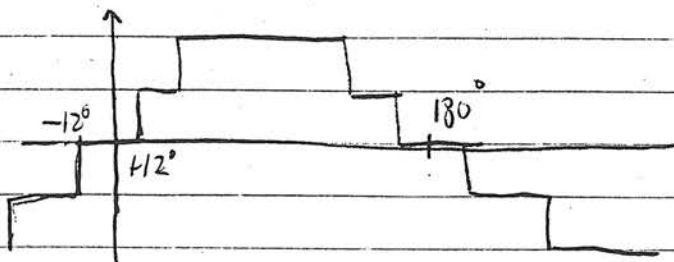

no third, 5^{th} harmonic



by adding waveforms time shifted so that their 5^{th} harmonics are 180° out of phase, the 5^{th} harmonic is cancelled in the summed waveform!

6.334 Lecture Notes Inverters # 2

Harmonic Cancellation and Harmonic Elimination can also be applied in other forms of power converters.

For example, in dc-dc conversion, we have a desired frequency (dc) and undesired components (all ac ripple). We can suppress these, reducing ripple content + increasing fundamental ripple frequency.

e.g. Interleaving for cancellation

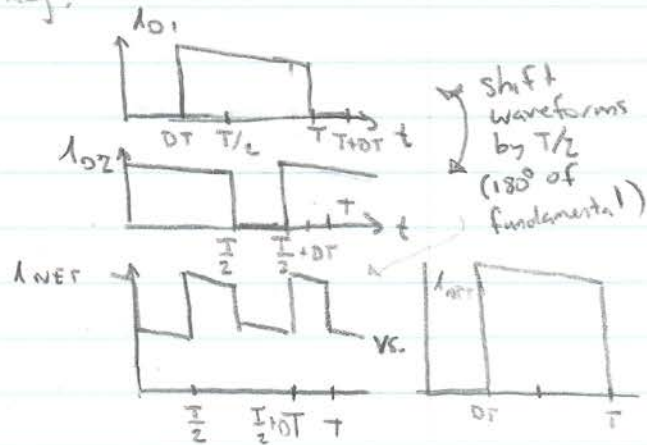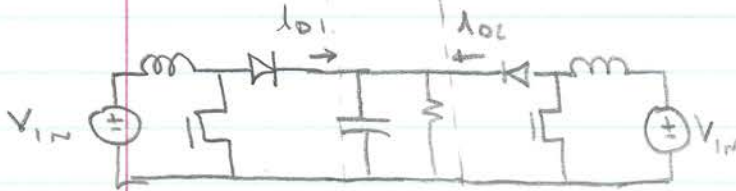

* With two converters, fundamental ripple

1. Frequency doubles!
2. Also, p-p current ripple (net) is half that of a single high-power unit.

We can interleave N identical converters by phase-shifting them by $\Delta t = T/N$ ($\omega_p \Delta t = 2\pi/N$). The net ripple frequency in the input and output waveforms will ideally be N times the individual switching frequency!

→ This trick is very widely used, including in the converters for most PC power supplies feeding the final low voltage to the microprocessor

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>