 



6.334 Lecture

Inverters #3

We have seen that we can use harmonic elimination to eliminate low-frequency harmonic content at the expense of higher switching frequency, (with resulting undesired content at high frequency where it is easily filtered)



 If we can add waveforms we can also realize harmonic cancellation which cancels out some harmonic content, resulting in stepped waveforms looking closer to the target




★ We can realize more sophisticated multi-level inverters that can directly synthesize more intermediate levels in an output waveform, facilitating nice harmonic cancelled output content.

Example: Neutral-point clamped inverter (also called "diode clamped" multilevel inverter.) Active switches are sometimes used instead of diodes (Active Clamp NPC inverter)

Developed by Nabae ~1980


★ NEUTRAL POINT MUST BE $I_c = 0$ in use to maintain voltage

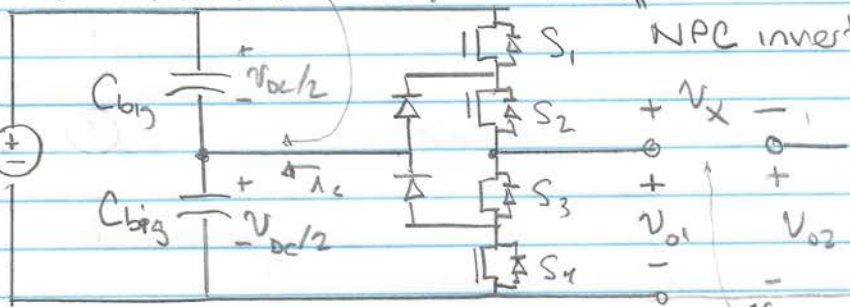Note: ideally, each of S_1-S_4 only needs block $\frac{1}{2}V_{DC}$



Switch states	V_{o1}
$S_1 S_2$	V_{DC}
$S_2 S_3$	$\frac{1}{2}V_{DC}$
$S_3 S_4$	0


So we can have lower switch rating

 

We can synthesize 3 levels ($0, \frac{1}{2}V_{DC}, V_{DC}$) instead of 2 for a half-bridge ($0, V_{DC}$) So converters built with this kind of structure are called "3 level inverters", a subclass of "multilevel inverters"

This is sometimes called a "3-level waveform", as each of V_{o1}, V_{o2} can take on 3 levels. We can do both elimination + cancellation with this capability!

 Another category of multi-level inverters is the so-called "Flying capacitor" approach:



"Flying Capacitor Multilevel Inverter" or FCML Inverter (Meynard ~ 1992)

SA + SA' switched oppositely
SB + SB' switched oppositely
Control Vc to ≈ Vdc/2

switch state on	V _{o1}
SA SB	V _{dc}
SA SB'	V _{dc} - V _c ≈ V _{dc} /2
SA' SB	V _c ≈ V _{dc} /2
SA' SB'	0

Notes: • If V_c ≈ V_{dc}/2 each switch sees max V_{dc}/2


- we can charge or discharge C by which combination we chose for V_{o1} ≈ V_{dc}/2 ⇒ can "balance" V_c
- unlike the diode clamped approach, we can deliver dc current @ V_{o1} (can make dc-dc FCML converters)
- Flying Capacitor + diode clamped converters are examples of "multilevel" converters. This approach has become very common @ high power (and sometimes in low-voltage CMOS designs!)
- Balancing of the intermediate voltage levels is always an issue
- Each of these approaches can be extended to more intermediate levels (≥ 7 levels in use!)
- Device voltages are reduced compared to the full bus voltage but by how much depends upon balancing, startup, # of levels, ...

"Sine-Triangle PWM"

Suppose we can switch many times per cycle and/or would like the ability to synthesize an arbitrary waveform in real time.


We can do such a synthesis using similar techniques as with PWM dc-dc converters, but with a varying reference command.

 e.g. consider a half-bridge leg (like a "synchronous" buck converter):



- If $g(t)$ has duty cycle d
 $\langle v_x \rangle = d \cdot V_{dc} = \langle v_L \rangle$
- $\omega_{sw} = 2\pi f_{sw} = \frac{2\pi}{T_{sw}} \Rightarrow R/L$
- If we vary d slowly wrt $\omega_c = \frac{R}{L}$ then v_L will track $d(t) \cdot V_{dc}$

 
- We often implement such PWM based on a comparison between a triangle wave and a reference voltage. (We can use any Δ wave, e.g. a sawtooth, but the harmonic content is best with a balanced Δ wave.)



6.334 Lecture Notes

Inverters # 3

To get a bipolar output we could use one bridge leg to PWM synthesize $|V_{ref}|$ and another bridge leg to "unfold" the output voltage (change polarity):

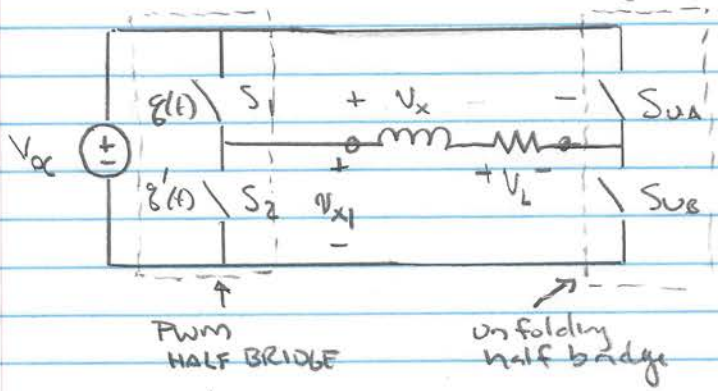

If $V_{REF} > 0$:

- S_{vB} ON
- $g(t) : d(t) = \frac{|V_{REF}|}{V_{dc}}$

If $V_{REF} < 0$:

- S_{vA} ON
- $g(t) : d(t) = \left| -\frac{|V_{REF}|}{V_{dc}} \right|$
- OR $g'(t) : d(t) = \frac{|V_{REF}|}{V_{dc}}$




- We change the PWM control + which unfolding switch is on based on the polarity of the reference voltage, with PWM related to $|V_{ref}|$ for a bipolar V_{ref} signal.
- This gives an output PWM ripple in V_L with frequency content centered at f_{sw} of the PWM half-bridge + harmonics, with sum and difference frequencies around f_{sw} and its harmonics based on the frequency content of V_{ref} . i.e. @ $n \cdot f_{sw} \pm m \cdot f_{ref}$ for a reference voltage that is $\sin(\omega_{ref} t)$
- The PWM half-bridge switches at f_{sw} (high frequency) while the unfolding half-bridge switches at (eg.) f_{ref} (low frequency). So, in this case it is desirable to optimize the switch designs for S_1, S_2 differently than S_{vA}, S_{vB} .
- ★ We can instead have a PWM scheme that treats each half-bridges equally, operating at a frequency f_{sw} , with output voltage V_x and V_L seeing ripple centered near $2 \cdot f_{sw}$ and its harmonics.

⇒ This is like having two buck converters with their outputs connected differentially, and switching them 180° out of phase!

6.334 Lecture Notes

Inverters # 3



Note:
see
ppt
slides

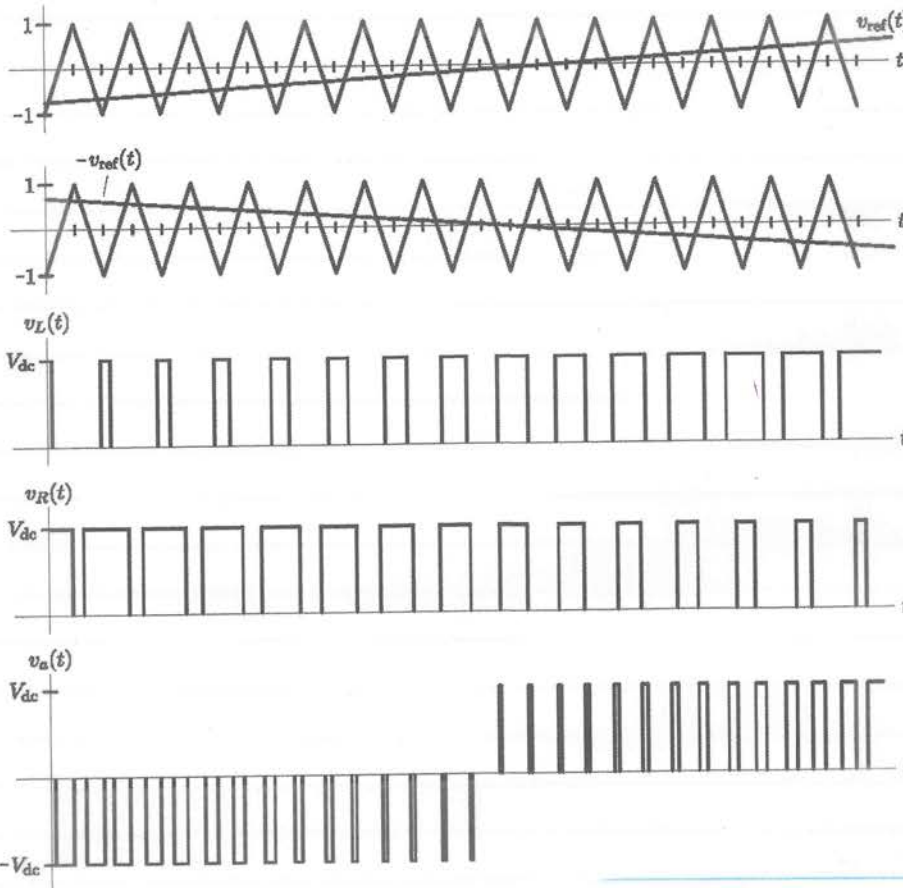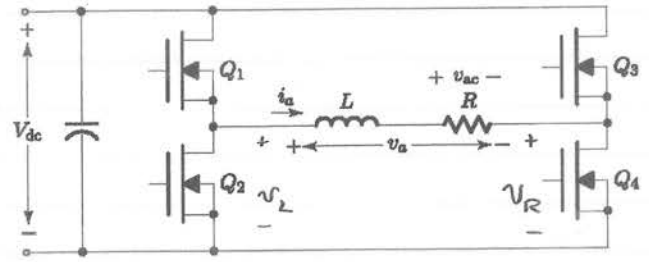 

Left HB switches
@ $f_{sw} = \frac{1}{T}$ based
on V_{ref}
Right HB switches
@ $f_{sw} = \frac{1}{T}$ offset
by $\frac{1}{2}$ cycle based
on $-V_{REF}$

Output is the
difference of
the 2 HB
PWM waves,
has switching
@ $2f_{sw}$

  In many cases (e.g. motor drives) we're actually interested in controlling output current. One way to do this is to generate the voltage reference $V_{REF}(t)$ based on the difference (error) between the sensed output current (to the load) i_{out} and a desired reference current i_{REF} :




- This approach exactly uses the PWM techniques shown so far, and yields devices in the inverter switching with the constant specified switching frequency.
- However, the ripple current amplitude in the output will necessarily vary over a cycle (e.g. $\Delta i_L = \frac{1}{L} v_L \cdot \Delta t$, and v_L varies with output)


CURRENT CONTROL (Hysteresis current control)

★ An alternative scheme is to switch the inverter switches to directly command the output current to closely track a current reference

 Control law: compare i_{out} to i_{REF}
 IF $i_{out} < i_{REF} - \Delta I$ turn S_1 on S_2 off
 IF $i_{out} > i_{REF} + \Delta I$ turn S_2 on S_1 off



 (can control other half-bridge switches to "unfold" based on V_{out} polarity or as inverse of q_1, q_2)



- In hysteretic current control we get precise control over the instantaneous ripple current (error current always $\leq \Delta I$), but the switching frequency (and frequency content of the ripple) varies over time (sometimes not desirable)
- If we control the right hand half-bridge as complement of the left hand half bridge we get no "zero state" so switching frequency is higher than it needs to be. This problem is mitigated if we use the rh half bridge as an "unfolder" based on the polarity of V_{out} . (more sophisticated schemes for full bridge control are also available that do not require knowledge of V_{out}).
- Both fixed-frequency PWM current control + hysteretic current control are used in practice, and there are variants that try to bridge their differences as well.

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>