

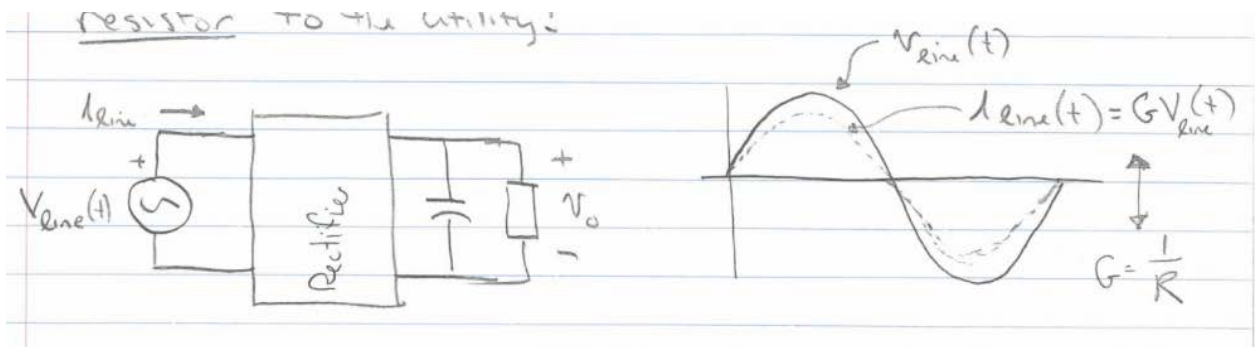


Lecture 20 - Switched-Mode Rectifiers

- Phase controlled rectifiers allow control of output voltage or current but the power factor becomes poor very quickly $\{(e.g., V_o = V_{do} \cos(\alpha)) k_p = \frac{4}{\pi\sqrt{2}} \cos(\alpha)\}$
- Power quality issues and regulations are requiring rectifiers loads on the utility to achieve high power factor (e.g., IEC 1000 -i fixed limits on harmonic content of current)
- When lots of power is needed, we must draw it at high pf. to stay within breaker/fuse thermal limits of source (e.g., 1.7 kW from 110V/15A)
- We need to draw close to sinusoidal current in phase w/ the voltage =i We want to look like a resistor to the utility!

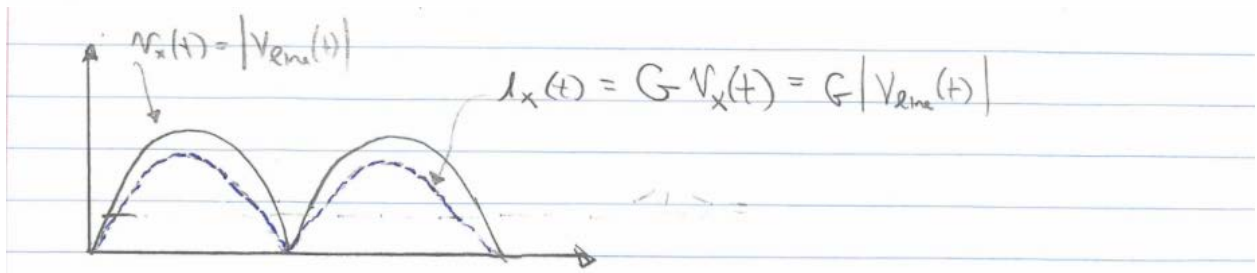

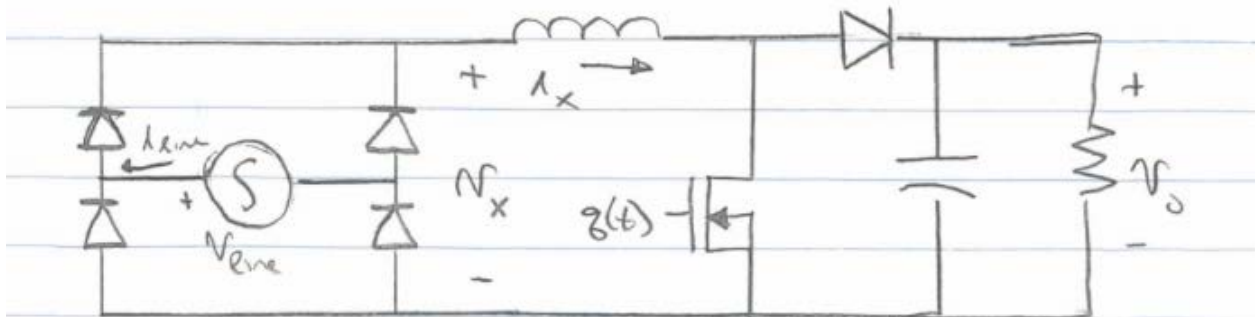To do this, use a switch-mode rectifier (SMR)
 UPF boost rectifier (simulation in sinerct.seh)




For ideal devices

$$\begin{aligned} \overline{P_{in}} &= \overline{P_{out}} = \langle V_x i_x \rangle \\ &= \langle G V_x V_x \rangle = \frac{1}{2} G |V_{line}|^2 \end{aligned}$$


So we can control output power to be desired value by making rectifier input current \propto to input voltage with a controlled proportionality constant

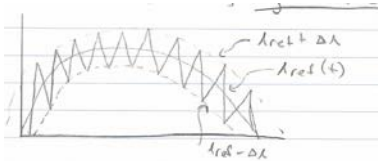- Current control could be done by hysteresis control (from before)




Control $q(t)$ to make i_x track reference within bounds.

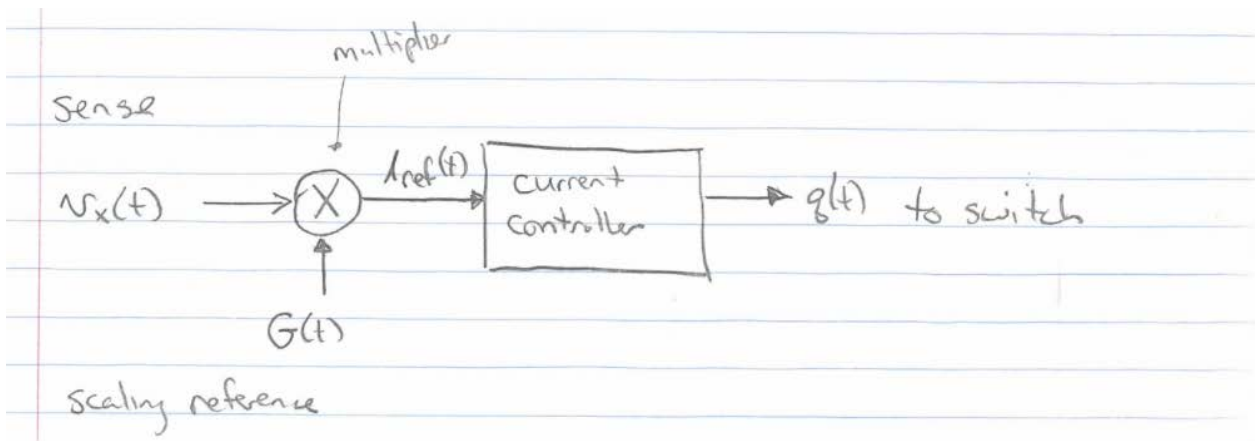- Could use peak current control (as we discussed in control lectures), or average current control or many similar versions
- These techniques start with a current reference we desire to track. to do this:



The output voltage is controlled by adjusting the scaling K (since $P_{out} = \frac{1}{2} K |V_{line}|^2$)

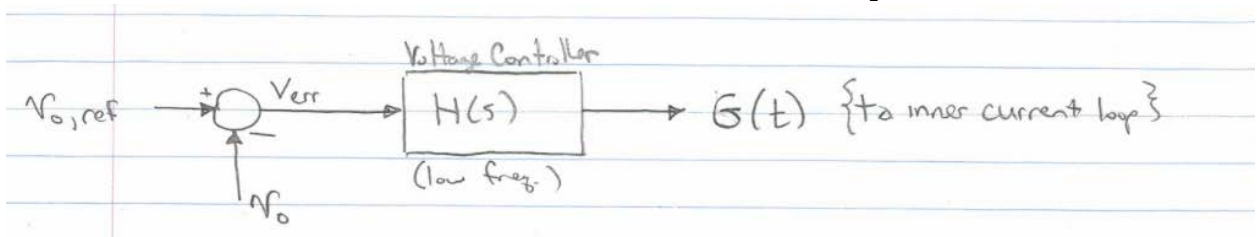


We get unity power factor (input current will be \propto to voltage)

But:

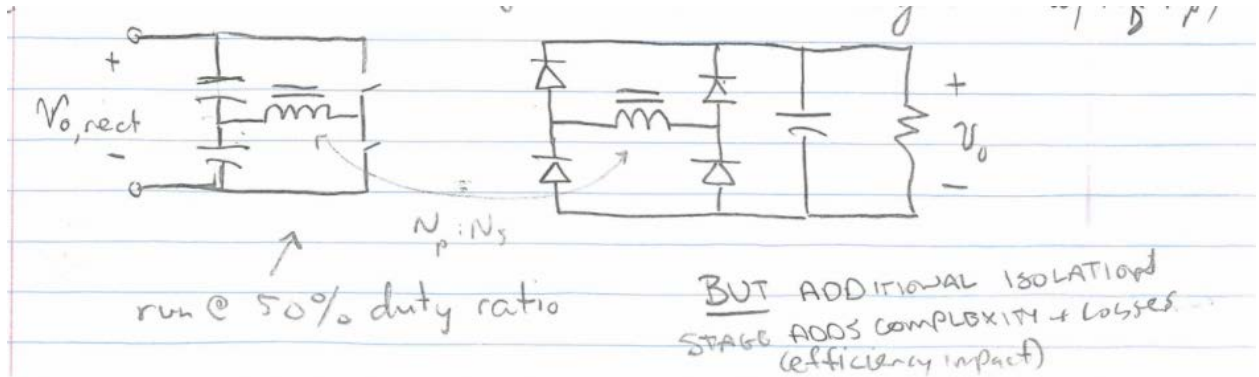
1. The outer loop (* control bandwidth) must be much slower than $Z\omega_{line}$ so $G(t)$ does not change much within a line cycle.
2. To compute the current ref we need a multiplier (which can be costly) \rightarrow some techniques get around this (e.g., edge of dcm mode)
3. Isolation is needed for most off-line applications

This topology does not provide isolation, output must float wrt ground unless we either use a 60Hz xformer at input (big, heavy) or provide an isolation stage. (Note: an isolation stage also provides transformation to a final output voltage)

Follow-on isolation stage (can also scale voltage down w/ $N_s : N_p$)




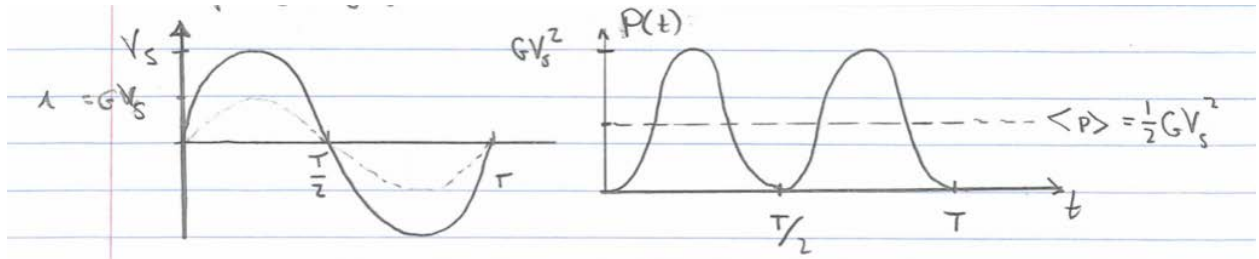4. Single-phase UPF (or PFC) power supplies require large capacitors to buffer the power pulsations from the line:




$$P(t) = GV_s^2 \sin^2(\omega t) = \frac{1}{2}GV_s^2 - \frac{1}{2}GV_s^2 \cos(2\omega t)$$
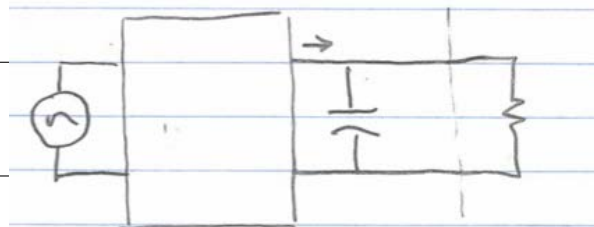
$$\begin{aligned} \langle P \rangle &= \frac{1}{2}GV_c^2 \\ &= P_{out} \end{aligned}$$



If power to the load is constant, the capacitor must source
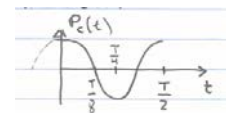
$$P_c = \frac{1}{2}GV_s^2 \cos(2\omega t) = P_{out} \cos(2\omega t)$$



Peak-to-peak energy swing:

$$\Delta E_{c,pp} = \int_{\frac{T}{8}}^{\frac{9T}{8}} P_{out} \cos(2\omega t) dt = \frac{P_{out}}{2\omega} [\sin(2\frac{\omega T}{8}) - \sin(-2\frac{\omega T}{8})]$$

$$\Delta E_{c,pp} = \frac{P_{out}}{\omega}$$

$$\Delta E_{c,pp} = \frac{1}{2}CV_{max}^2 - \frac{1}{2}CV_{min}^2 = \frac{1}{2}C(V_{max}^2 - V_{min}^2)$$

If $V_{min} = KV_{max}$, $\Delta E_{c,pp} = \frac{1}{2}CV_{max}^2(1 - K^2) = \frac{P_{out}}{\omega}$


$$\therefore \boxed{\Delta E_{c,pp} = \frac{P_{out}}{\omega}} \quad @P_{out} = 1KW, V_{max} = 200V, K = 0.95, \omega = 377 \frac{rad}{sec} \Rightarrow C \geq 1.4mF$$

Much ongoing research on single-stage UPF converters


1. Unity double factor
2. Output voltage control
3. Isolation

All with a single converter step

One example: DCM flyback converter

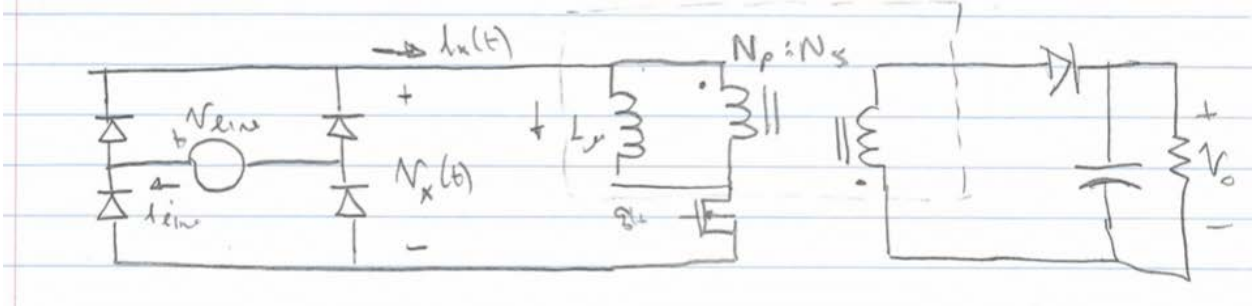

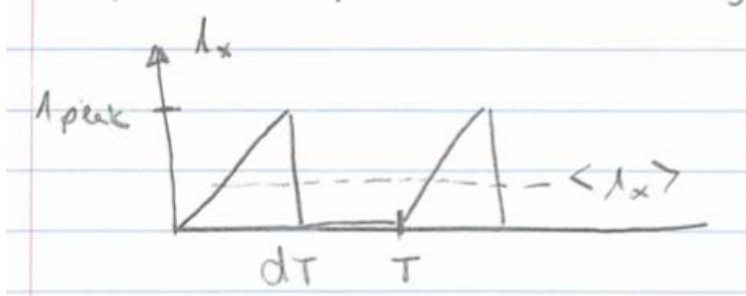Suppose we operate under duty-ratio control in DCM



$$i_{peak} = \frac{v_x(t)}{L_\mu} dT$$

$$\therefore \overline{i_x(t)} = \frac{1}{T} \left[\frac{\overline{V_x(t)}}{2L_\mu} (dT)^2 \right] = d^2 \frac{T}{2L_\mu} \overline{V_x(t)}$$

- So for a given duty ratio (constant over $\frac{1}{2}$ line cycle), we get a current $i_x(t)$ that tracks $V_x(t)$ and unfolded $i_{line}(t)$ follows $V_{line}(t)$ (no multiplier needed!) \Rightarrow UPF operation
 - We get isolation without an extra stage
 - We can control output power, output voltage simply by controlling duty ratio
 - BUT: High device magnetic stresses / need much input filtering (high ripple)
- \Rightarrow If time, cover 3 Φ SMR systems

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>