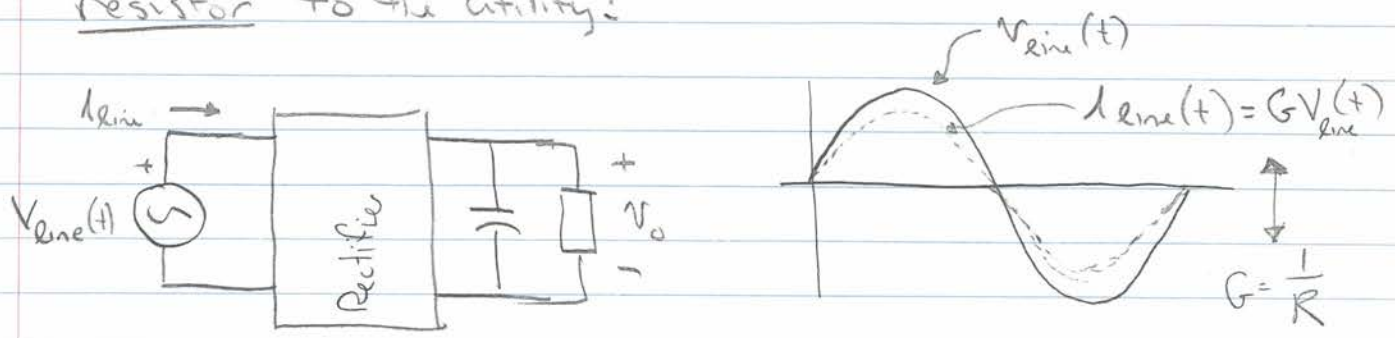


6.334 Lecture 5.3 C2 Switched-Mode Rectifiers

Phase-controlled rectifiers allow control of output voltage or current but the power factor becomes poor: very quickly $\left\{ V_o^{avg} = V_{do} \cos(\alpha) \quad k_p = \frac{4}{\pi \sqrt{2}} \cos(\alpha) \right\}$


- power quality issues and regulations are requiring rectifier loads on the utility to achieve high power factor (e.g. IEC 1000 \rightarrow fixed limits on harmonic content of current)
- When lots of power is needed, we must draw it at high p.f. to stay within breaker/fuse/thermal limits of source (e.g. $\sim 1.7 \text{ kW}$ from $110 \text{ V} / 15 \text{ A}$)

We need to draw close to sinusoidal current in phase w/ the line voltage \Rightarrow We want to look like a resistor to the utility!




To do this, use a switched-mode rectifier (SMR)

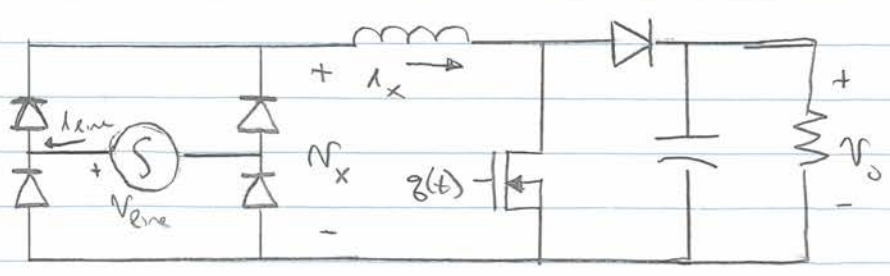e.g., UPF Boost Rectifier (simulation in sinerctd.seh)



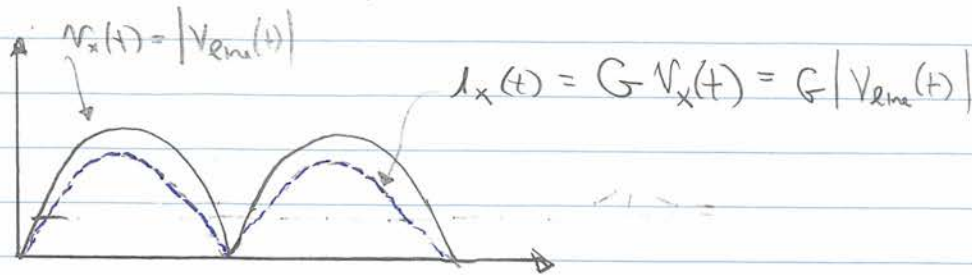
6.334 Lecture 7, 7.1 Switched-Mode Rectifiers



For ideal devices $P_{in} = P_{out} = \langle v_x i_x \rangle$
 $= \langle G v_x v_x \rangle = \frac{1}{2} G |V_{line}|^2$


So we can control output power to be desired value by making rectifier input current i_x to input voltage with a controlled proportionality constant.

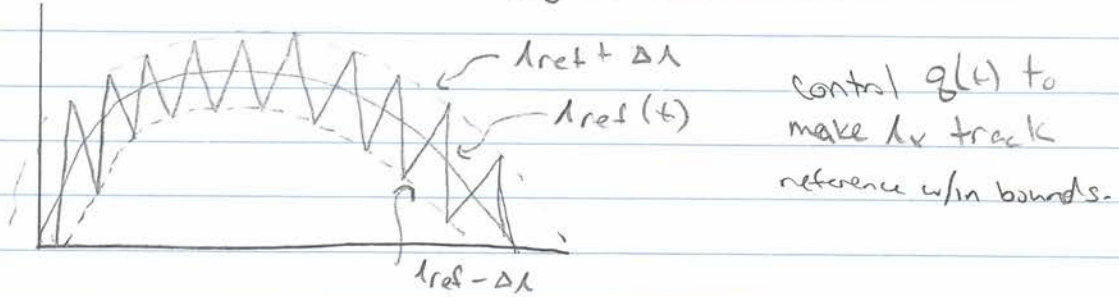→ current control could be done by hysteresis control (from before)



→ could use peak current control (as we discussed in Control lectures), or average current control or many similar versions.

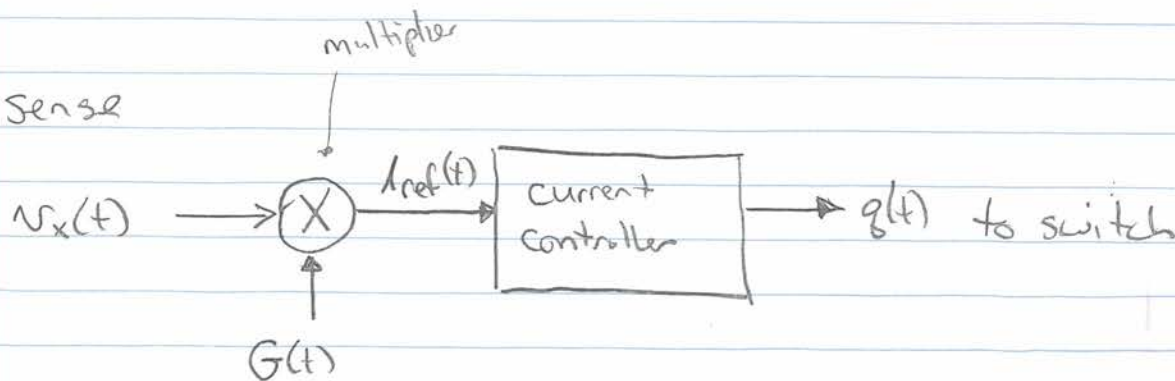→ these techniques start with a current reference we desire to track; To do this:




scaling reference

6.334 Lecture Switched-Mode Rectifiers

The output voltage is controlled by adjusting the scaling K
 (since $P_{out} = \frac{1}{2} K |V_{line}|^2$)

[SHOW SIMULATION!]
 Sine rect. sch

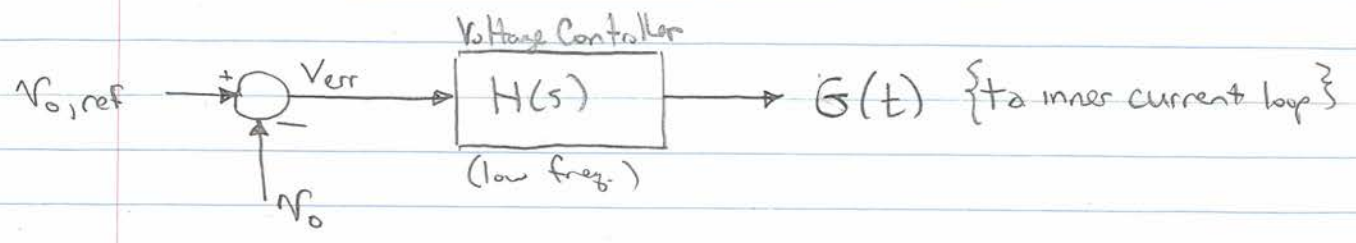

• we get Unity Power Factor (input current will be \propto to voltage)


But: ① The outer loop (\star control bandwidth L) must be much slower than $Z\omega_{line}$ so $G(t)$ does not change much within a line cycle.

② To compute the current ref, we need a multiplier (which can be costly) \rightarrow some techniques get around this (e.g., edge of dem mode)

③ Isolation is needed for most off-line applications

This topology does not provide isolation. output must float wrt ground unless we either use a 60 Hz X-former at input (big + heavy) or provide an isolation stage

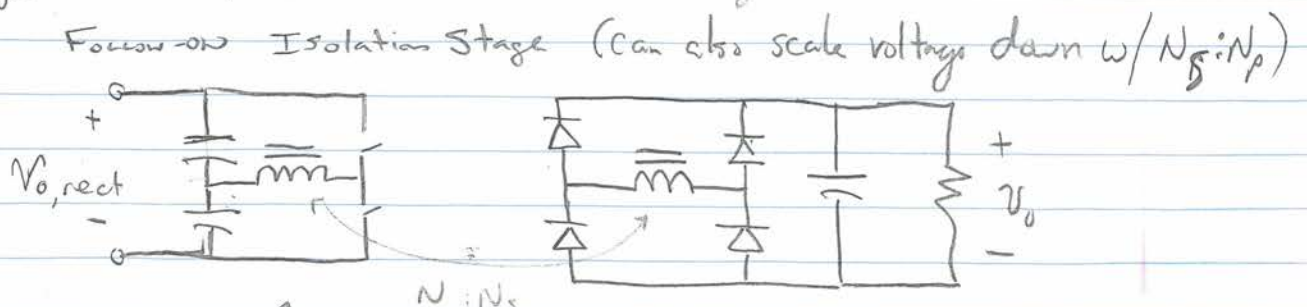
NOTE: An ISOLATION STAGE ALSO PROVIDES TRANSFORMATION TO A FINAL OUTPUT VOLTAGE



run @ 50% duty ratio

BUT ADDITIONAL ISOLATION STAGE ADDS COMPLEXITY + LOSSES (efficiency impact)

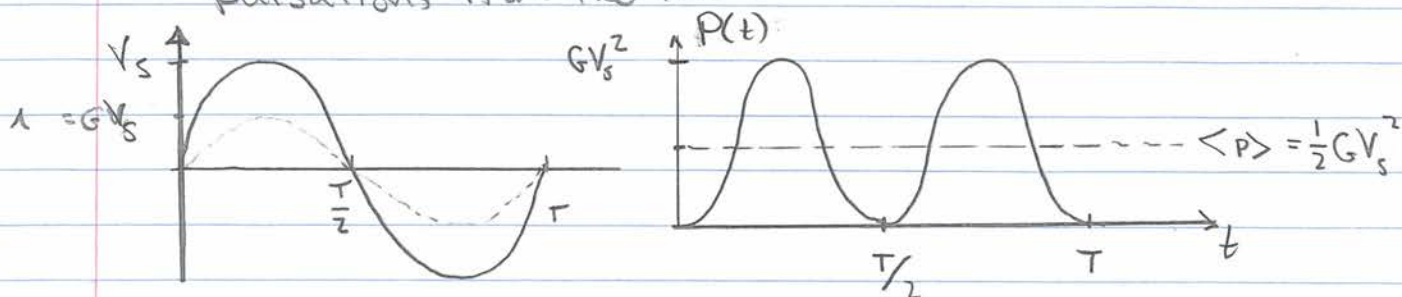
④ Single-Phase UPF (or PFC) power supplies require large capacitors to buffer the power pulsations from the line:



$$P(t) = G V_s^2 \sin^2(\omega t) = \frac{1}{2} G V_s^2 - \frac{1}{2} G V_s^2 \cos(2\omega t)$$


$$\langle P \rangle = \frac{1}{2} G V_s^2$$

$$= P_{out}$$

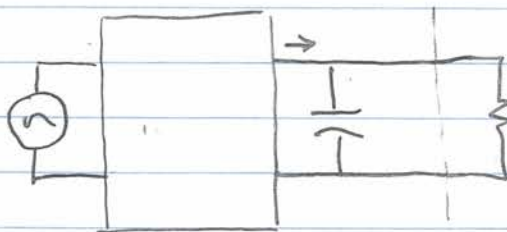

If power to the load is constant, the capacitor must source
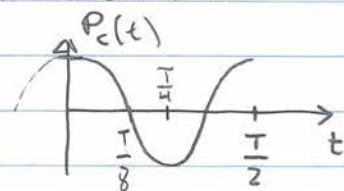
$$P_c = \frac{1}{2} G V_s^2 \cos(2\omega t) = P_{out} \cos(2\omega t)$$



Peak-to-Peak energy swing:

$$\Delta E_{c,pp} = \int_{-T/8}^{T/8} P_{out} \cos(2\omega t) dt = \frac{P_{out}}{2\omega} \left[\sin\left(2\frac{\omega T}{8}\right) - \sin\left(-2\frac{\omega T}{8}\right) \right]$$

$$\Delta E_{c,pp} = \frac{P_{out}}{\omega}$$

$$\Delta E_{c,pp} = \frac{1}{2} C V_{max}^2 - \frac{1}{2} C V_{min}^2 = \frac{1}{2} C (V_{max}^2 - V_{min}^2)$$

If $V_{min} = k V_{max}$

$$\Delta E_{c,pp} = \frac{1}{2} C V_{max}^2 (1 - k^2) = \frac{P_{out}}{\omega}$$

$$C \geq \frac{2 P_{out}}{\omega V_{max}^2 (1 - k^2)}$$

@ $P_{out} = 1 \text{ kW}$
 $V_{max} = 200 \text{ V}$
 $k = 0.95, \omega = 377 \frac{\text{rad}}{\text{sec}} \Rightarrow C \geq 1.4 \text{ mF}$

★ Required buffer capacitance ∝ to Power!


6.334-1 Lecture 7.2 = Switched-Mode Rectifiers

Much ongoing research on SINGLE-STAGE UPF Converters


- do 1. UNITY POWER FACTOR
- 2. OUTPUT VOLTAGE CONTROL
- 3. ISOLATION

All with a single conversion step.

One example: DCM Flyback converter

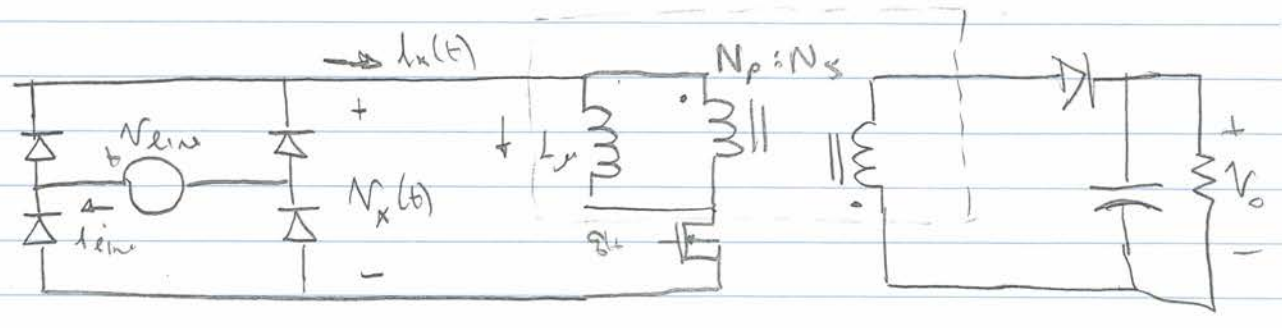

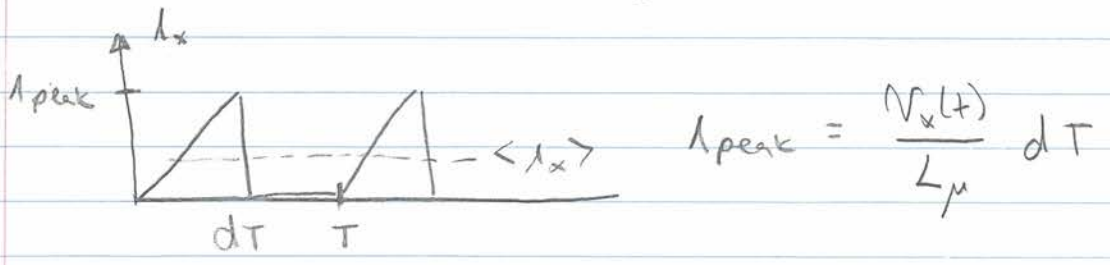Suppose we operate under duty-ratio control in DCM



$$\therefore \bar{I}_x(t) = \frac{1}{T} \left[\frac{\bar{V}_x(t)}{2L_p} (dT)^2 \right] = d^2 \frac{T}{2L_p} \bar{V}_x(t)$$

- so for a given duty ratio (const over 1/2 line cycle) we get a current $i_x(t)$ that tracks $V_x(t)$, and unfolded $i_{line}(t)$ follows $V_{line}(t)$ (no multipliers needed!) → UPF operation
- we get isolation without an extra stage
- we can control output power, output voltage simply by controlling duty ratio

BUT: High device, magnetic stresses, need much input filtering (high ripple)

⇒ IF Time, cover 3φ SMR systems (Note: ~10min exist to do so.)

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>