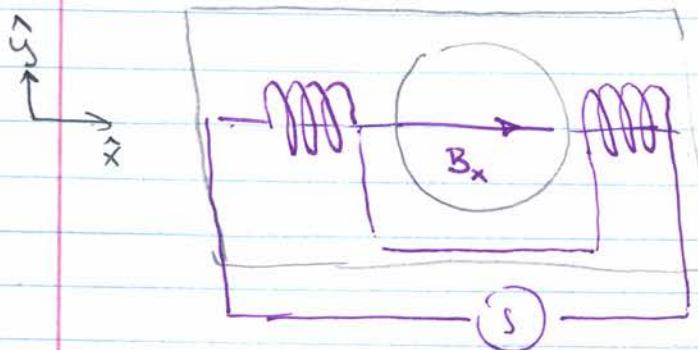


6.334 3-phase Systems #1

The origins of polyphase

Suppose we wanted to build an AC machine where we wanted to use magnetic fields (or flux) from a winding on the stator to generate forces on the rotor:




with an appropriate sinusoidal drive we'd get

$$\vec{B} = B_0 \cos(\omega t) \hat{x}$$

This could generate a force on a rotor (e.g. to align with \vec{B} (e.g. by magnetic poles attracting))

Unfortunately, if the rotor were already aligned with the \hat{x} direction, we'd get no force or torque.

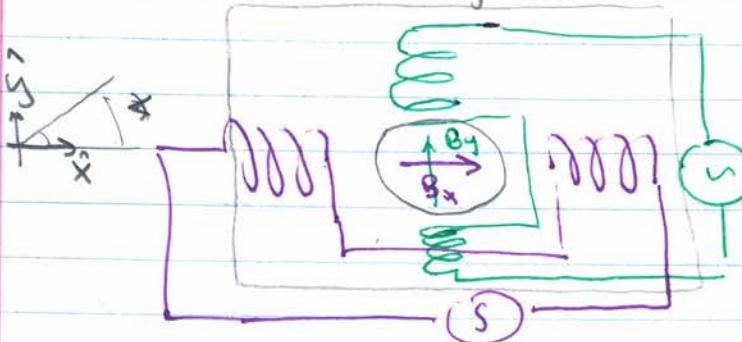What if we added another winding orthogonal in space and made its drive orthogonal in time also?




$$\vec{B} = B_0 \cos(\omega t) \hat{x} + B_0 \sin(\omega t) \hat{y}$$

$$|\vec{B}| = B_0$$

$$\angle \vec{B} = \text{ATAN} \left(\frac{\sin(\omega t)}{\cos(\omega t)} \right) = \omega t$$

* we get a magnetic field (or flux) of constant magnitude that rotates in space! The rotor will be pulled rotationally at all conditions!

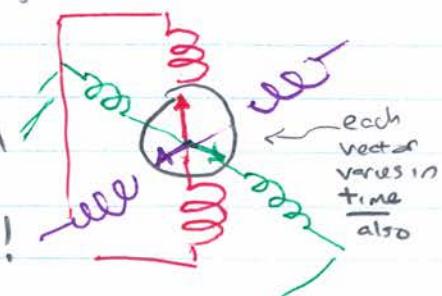This type of characteristic was one that motivated early polyphase work (Tesla and others). Instead of 2 orthogonal phases, we also get this with 3 phases spaced in time + phase by 120° !



6.334 Lecture

3-Phase Systems #1

A three-phase voltage set is three sources separated by 120° in phase ($\frac{2\pi}{3}$ radians). The voltages sum to zero at all times.


$$\text{e.g. } V_A = V_s \sin(\omega t) = \text{Re} \left\{ V_s e^{-j\frac{\pi}{2}} \cdot e^{j\omega t} \right\}$$

$$V_B = V_s \sin(\omega t - \frac{2\pi}{3})$$

$$V_C = V_s \sin(\omega t + \frac{2\pi}{3})$$


We can represent these as phasors
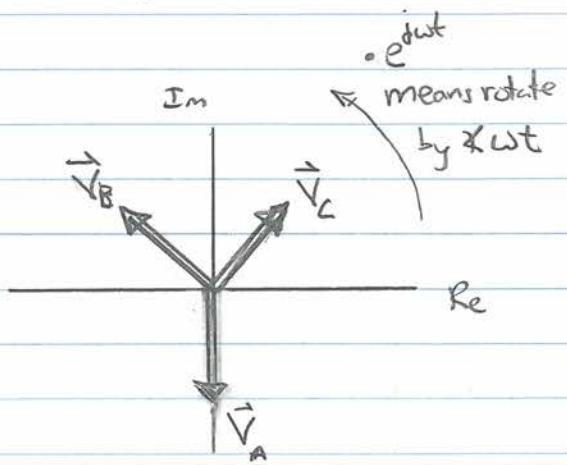
$$V_x(t) = \text{Re} \left\{ \vec{V}_x e^{j\omega t} \right\}$$




Connection of 3Φ Sources

Most common: Y connection

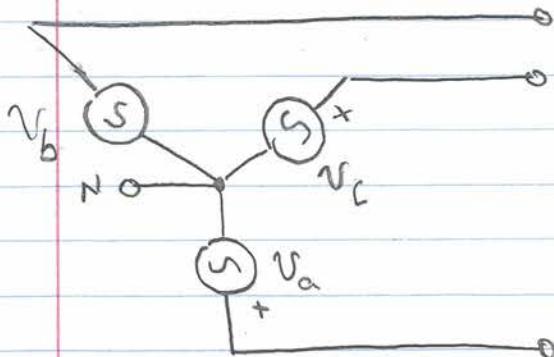


Δ connection (neutral)

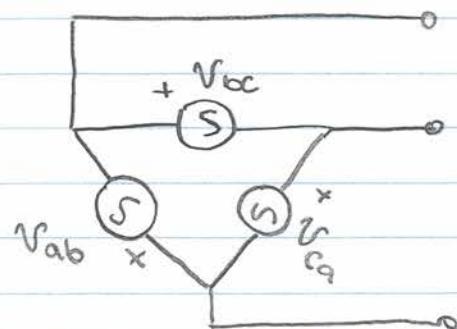

Why 3Φ?

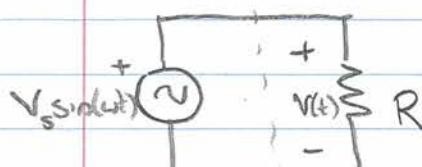
- Consider power sourcing capability of 1Φ (best case @ unity P.F.)



$$P(t) = \frac{V(t)^2}{R} = \frac{V_s^2}{R} \sin^2(\omega t)$$

$$= \frac{V_s^2}{2R} [1 - \cos(2\omega t)]$$

$$T = \frac{1}{\omega}$$

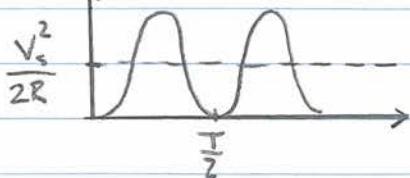


Even at unity power factor we get power pulsations between 0 and 2× average power at twice the line frequency. This makes sense, as we cannot draw power when $V \rightarrow 0$. This is bad for supplying power to machines, electronics, etc.

→ torque pulsations in machine

→ 2×f_{line} energy storage needed to maintain const electronic load power

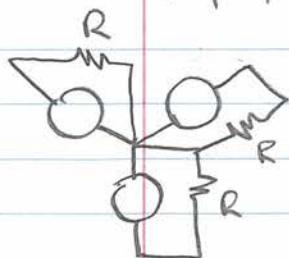3Φ power solves this fluctuation problem!



$$P_{TOTAL} = \frac{V_s^2}{R} \left[\sin^2(\omega t) + \sin^2\left(\omega t - \frac{2\pi}{3}\right) + \sin^2\left(\omega t + \frac{2\pi}{3}\right) \right]$$

$$= \frac{V_s^2}{2R} \left[3 - \cos(2\omega t) - \underbrace{\cos\left(2\omega t - \frac{4\pi}{3}\right) - \cos\left(2\omega t + \frac{4\pi}{3}\right)}_{} \right]$$

This 3Φ set always adds to zero

$$\boxed{P_{TOTAL} = \frac{3V_s^2}{2R}}$$


We can source constant power into a balanced 3Φ load w/ n. energy storage.

* Two-phase can also do this, as $\sin^2(\varphi) + \cos^2(\varphi) = 1$

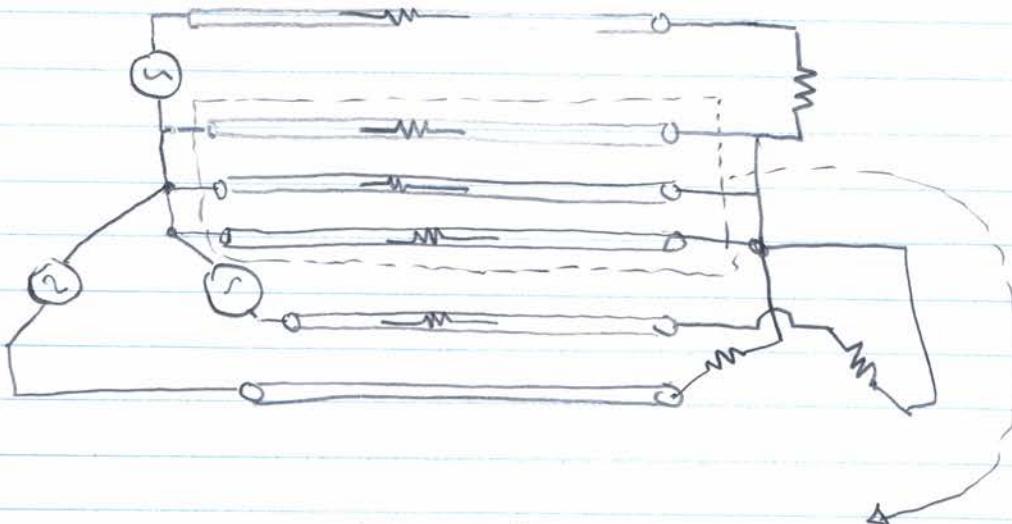6.334 Lecture

Three-phase Systems #1

Consider distribution loss benefits of 3 ϕ vs. 1 ϕ or 2 ϕ : If the load is far from the source.




- Because the 3 phase voltages add to zero, if the loads are balanced (equal) the net currents in the return lines add to zero! Ideally, then we can remove the return lines (saving loss + \$). At minimum we can use a single small return line to carry only the "imbalance" current (3-phase, 4-wire). This doesn't happen with 2-phase, since voltage vectors don't add to zero.
 - Just as voltages (+currents) may add to zero in polyphase, Transformer fluxes add to zero with 3 phase legs, and we can build 3-phase transformers that are smaller and/or more efficient than 3 1- ϕ transformers would be
 - Similar benefits can be applied to help improve electric machines
- ⇒ 3 ϕ provides decided benefits compared to both 1 ϕ and 2 ϕ

6.334 Lecture



Three-Phase Systems #1

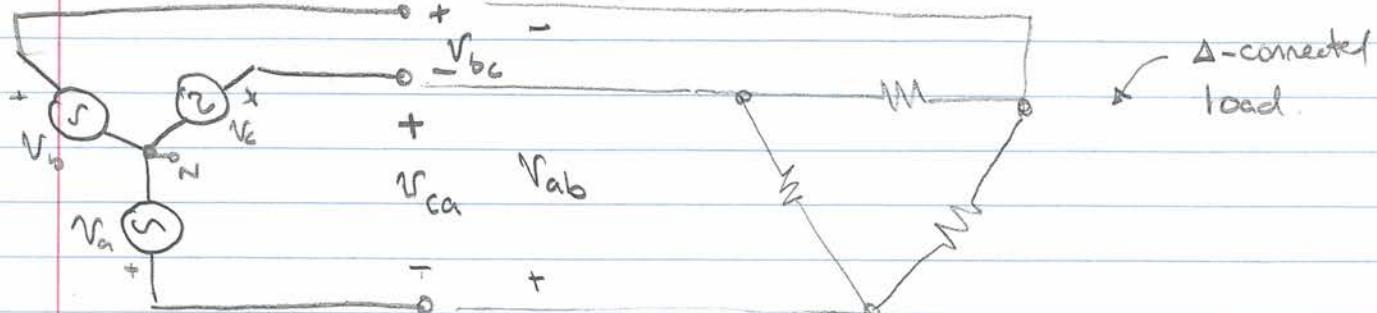- (2) With a 3 ϕ set we can form a balanced 3 ϕ load or line-to-line. (cannot do this w/ 2 ϕ)



We can find line-to-line voltages from vector analysis
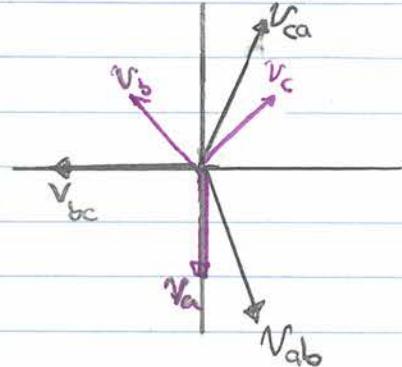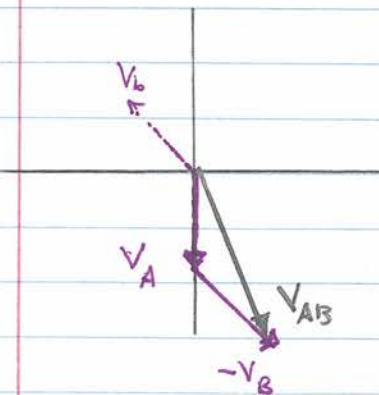
$$\begin{aligned} V_{ab} &= V_a - V_b \\ &= \sqrt{3} V_s \sin(\omega t + \frac{\pi}{6}) \end{aligned}$$



- l-l voltages are $\sqrt{3}$ larger in magnitude than l-n ($120\text{V l-n} \rightarrow 208\text{V l-l}$)
- l-l voltages are shifted by $\frac{\pi}{6}$ (30°) from l-n voltages.

This can be handy depending on the desired load characteristics


- * Also, we can create balanced voltage sets with any phase shift by appropriate summing of voltages (e.g. w/ transformers)
 - ⇒ Very handy for some designs.

6.334 Lecture

Three-Phase Systems #1

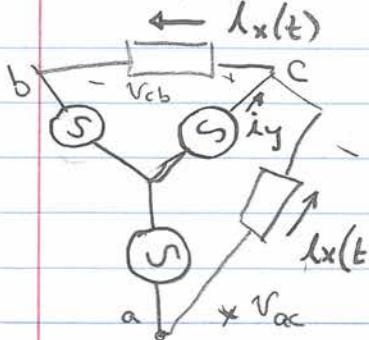- (3) 3 ϕ systems allow cancellation of all triple harmonics
(harmonics that are multiples of 3x fundamental frequency)

How? Consider a "Δ" connected load on a "Y" source



if load is balanced, l-l currents are the same but shifted in time by $T/3$

$$\therefore I_y = I_x(t) - I_x(t - T/3) \quad T/3 \text{ is } 120^\circ \text{ @ fundamental}$$

$\therefore 3n$ harmonics of $I_x(t)$ disappear
in I_y by harmonic cancellation

That is, if $f(t) = \sum a_n \sin(nwt + \phi_n)$

$$f(t) - f(t - T/3) = \sum_n a_n [\underbrace{\sin(nwt + \phi_n)}_{\text{Content cancels for } n \text{ any multiple of 3}} - \underbrace{\sin(nwt + \frac{nT}{3} - \phi_n)}]$$

Since the current waveforms have fundamentals that differ by $120^\circ = 2\pi/3$ radians, they are time shifted by $T/3$, and the triple-n harmonic content gets cancelled.

\Rightarrow No even harmonics, 3n's gone $\Rightarrow 5^{\text{th}}, 7^{\text{th}}, 11^{\text{th}}, 13^{\text{th}}, \dots$ left

MIT OpenCourseWare

<https://ocw.mit.edu>

6.622 Power Electronics

Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>