
# Lecture 24 - Control 1

## 1 Modeling and Control

#### 1.1 Direct circuit averaging


Consider a boost converter

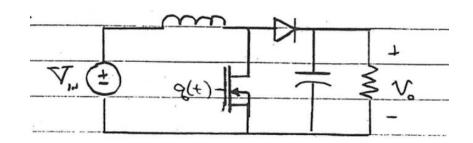




Desire to regulate the output voltage  $v_0$  in the face of

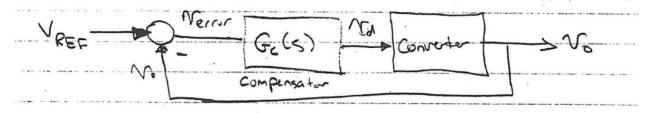- 1. Load disturbances  $\Rightarrow R_{min} \leq R \leq R_{max}$
- 2. Input voltage variations  $\Rightarrow V_{min} \leq V \leq V_{max}$
- $\Rightarrow$  Feedforward has problems
- 1. Control depends on idealized modeling assumptions
- 2. Doesn't let us control response to load variations
- $\Rightarrow$  Use <u>feedback!!</u> Change d depending on output voltage. (Check % that had 6.302...)



 $V_d$  is a voltage of 0 <  $V_d$  < 1 representing duty ratio  $\Rightarrow$  generate q(t) switching fn

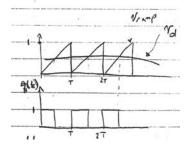Over 1 cycle  $\langle q(t) \rangle = \langle v_d \rangle \rightarrow \text{PWM generation}$ 



We need a <u>dynamic model</u> for the converter Switched <u>models</u> are not easy to use

- They carry too much information about the waveforms
- We want to know about low frequency variations, not switching

(See example simultation of boost to illustrate this: Ex  $1 \to \text{can show demo boost } d < t \ (@ fixed D))$  To study low-frequency "averaged" behavior, we can look at the local average value of the waveforms.

Define local average operator:

$$\overline{x(t)} = \frac{1}{T} \int_{t-T}^{t} X(\tau) d\tau$$

(Moving average over 1 cycle)

 $\rightarrow$  local average tracks low freq variations, suppresses switching ripple info Properties of this operator

differentiation

$$\overline{(\frac{dx}{dt})} = \frac{d}{dt}(\overline{x})$$

(Proof trivial)

Note: in general  $\overline{x(t)y(t)} \neq \overline{x}(t)\overline{y}(t)$ But if x(t) or y(t) has both

- 1. small ripple
- 2. slow variation wrt

Then  $\overline{x(t)y(t)} \approx \overline{x}(t)\overline{y}(t)$ 

Linearity  $\overline{(ax+by)} = a\overline{x} + b\overline{y}$ 

(proof trivial)

Time invariance  $\overline{x(t-t_0)} = \overline{x}(t-t_0)$ 

(proof trivial)


# 2 Local average operator


Operator definition

$$\overline{X(t)} = \frac{1}{T} \int_{0}^{t} (t - T)^{t} x(\tau) d\tau$$

Transfer function
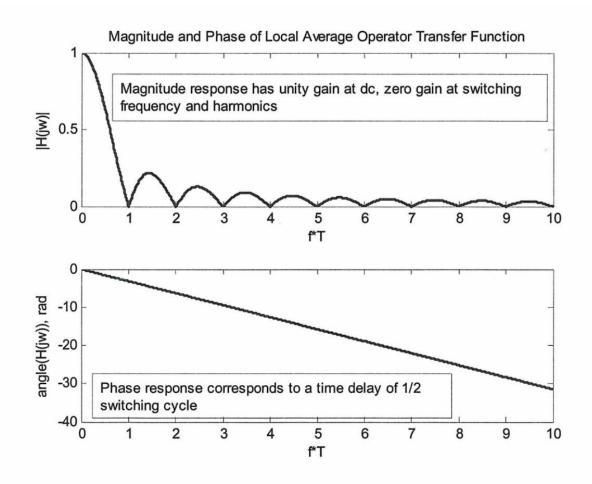
$$H(j\omega) = \frac{\overline{X}(j\omega)}{X(j\omega)} = \frac{1 - e^{-j\omega T}}{j\omega T} = sinc(\frac{\omega T}{2\pi}) \cdot e^{-j\omega T/2}$$



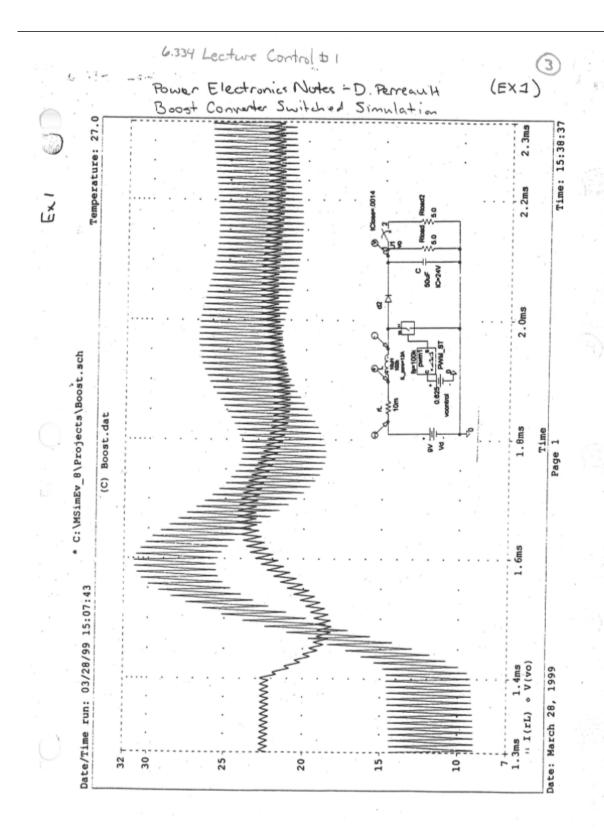


Consider the use of this operator on a circuit: because LTI, KVL + KCL are satisfied for average vars


KVL:  $\Sigma v_{ij} = 0 \rightarrow \Sigma \overline{v_{ij}} = 0$ KCL:  $\Sigma i_j = 0 \rightarrow \Sigma \overline{i_j} = 0$ 

We can apply averaging in circuits

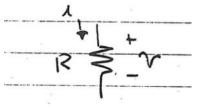Consider constitutive laws for averaged vars:



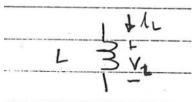
$$v(t) = i(t)R$$
$$\overline{v(t)} = \overline{i(t)}R$$



$$v(t) = L\frac{di}{dt}$$
$$\overline{v(t)} = L\frac{d\overline{i}}{dt}$$

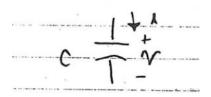
LTI circuit elements constitutive relationships do not change!




$$i(t) = C\frac{dv}{dt}$$

$$\overline{i(t)} = C \frac{d\overline{v}}{dt}$$

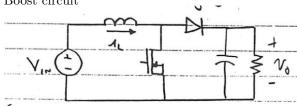Nonlinear or time varying elements do change! Boost circuit



Model with switching function

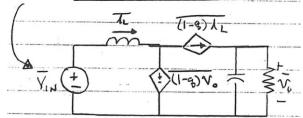

 $\overline{x(t)y(t)} \neq \overline{x}(t)\overline{y}(t)$ <u>but</u> if x(t) or y(t) has


- 1. small ripple
- 2. and slow variation wrt T

$$\Rightarrow \overline{x(t)y(t)} \approx \overline{x}(t)\overline{y}(t)$$

To average, place line over all variables (LTI elements do not change)

If  $i_L$  has small ripple, slow variation  $: \overline{(1-q)i_L} \approx \overline{1-q} \cdot \overline{i_L} = d'\overline{i_L}$   $v_c$  has small ripple, slow variation (ie  $\approx$  const over a cycle)  $: \overline{(1-q)v_0} \approx \overline{1-q} \cdot \overline{v_0} = d'\overline{v_0}$ Where  $\overline{\Sigma d(t)} = \overline{q(t)}$ 

### 3 Averaged circuit model

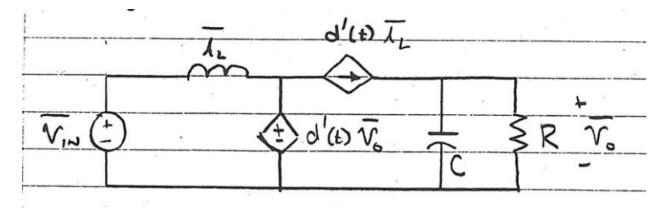

- In this circuit model, we have no more switching (only depends on averaged duty cycle  $d(t) = \overline{q(t)}$ )
- model is not linear in our control variable d(t) (because of  $d'v_0$ ,  $d'i_L$  terms)
- model is very simple, + should be accurage for averaged variables if our assumptions are valid (ie  $\overline{qi_L} = \overline{qi_L}$ , etc)


Ex2. (Show simulation w/ both switched averaged models.)

- 1. good results (small offset due to evice mods)
- 2. will be very useful for control!!

Note: not useful for some things. Ex switch power dissipation

$$P(t) = V(t)i(t)$$

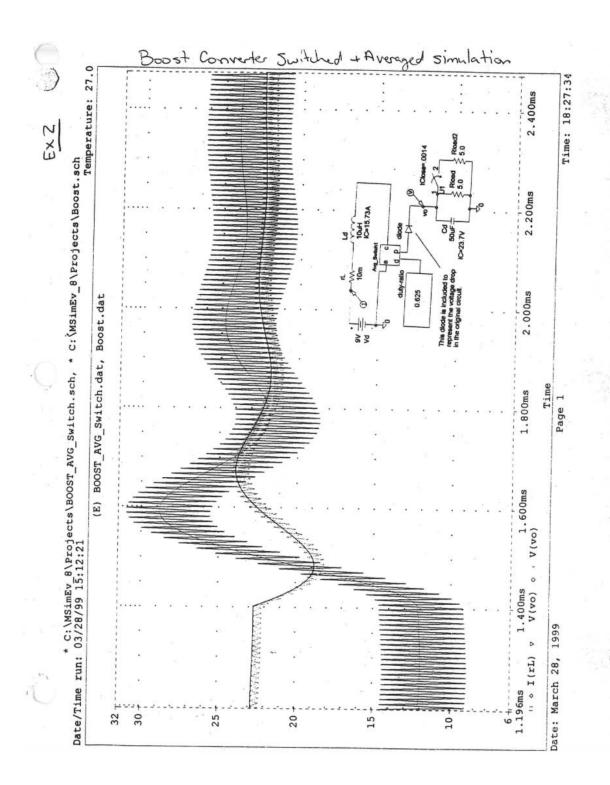 $\overline{P(t)} = \overline{V(t)i(t)} \neq \overline{V(t)i(t)}$  (small ripple assumtion not met)



MIT OpenCourseWare <a href="https://ocw.mit.edu">https://ocw.mit.edu</a>

6.622 Power Electronics Spring 2023

For information about citing these materials or our Terms of Use, visit: <a href="https://ocw.mit.edu/terms">https://ocw.mit.edu/terms</a>