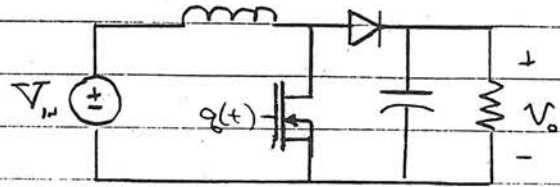


Power Electronics Notes - D. Perreault

- ★★ Modeling And Control
- * Direct Circuit Averaging
- READ KSV 11.1-11.3.4

Consider a Boost Converter

$$V_o = \frac{V_{in}}{1-D}$$



Desire to regulate the output voltage V_o in the face of:


1. Load disturbances $\rightarrow R_{min} \leq R \leq R_{max}$
2. Input voltage variations $\rightarrow V_{min} \leq V \leq V_{max}$

\rightarrow Feedforward has problems

1. control depends on idealized modeling assumptions
2. doesn't let us control response to load variations


\Rightarrow Use Feedback!! change d depending on output voltage.

(check % that has had 6.302...)

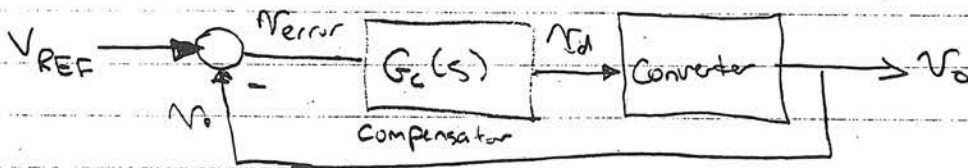

V_d is a voltage $0 < V_d < 1$ representing duty ratio
 \Rightarrow generate $q(t)$ switching fn.

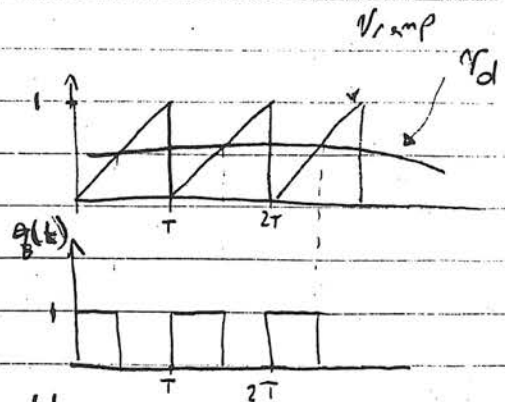over 1 cycle $\langle q(t) \rangle = \langle V_d \rangle$
 \rightarrow PWM generation



★ \Rightarrow 1.1.10 still need... 1.1.10... 1.1.10...

Power Electronics Notes - D. Perreault

We need a dynamic model for the converter.

Switched models are not easy to use

→ they carry too much information about the waveforms

→ we want to know about low frequency variations, not switching

Ex 1

(see example simulation of boost to illustrate this: Ex 1)

→ Can show demo boost ckt (e fixed D)

To study low-frequency "averaged" behavior, we can look at the local average value of the waveforms.

Define Local Average operator:

$$\bar{X}(t) = \frac{1}{T} \int_{t-T}^t X(\tau) d\tau$$

(moving avg over 1 cycle)

→ local average tracks low freq. variations, suppresses switching ripple info.

Properties of this operator

differentiation $\overline{\left(\frac{dx}{dt}\right)} = \frac{d}{dt}(\bar{X})$ (proof trivial)

Note: in general $\overline{X(t) y(t)} \neq \bar{X}(t) \bar{y}(t)$

But if $X(t)$ or $y(t)$ has both 1.) small ripple
2.) slow variation wrt

then $\overline{X(t) y(t)} \approx \bar{X}(t) \bar{y}(t)$

linearity $\overline{aX + bY} = a\bar{X} + b\bar{Y}$

(proof trivial)

time invariance $\overline{X(t-t_0)} = \bar{X}(t-t_0)$ (proof trivial)


Local Average Operator

Operator Definition

$$\bar{X}(t) = \frac{1}{T} \int_{t-T}^t x(\tau) d\tau$$

Transfer function

$$H(j\omega) = \frac{\bar{X}(j\omega)}{X(j\omega)} = \frac{1 - e^{-j\omega T}}{j\omega T} = \text{sinc}\left(\frac{\omega T}{2\pi}\right) \cdot e^{-j\omega T/2}$$

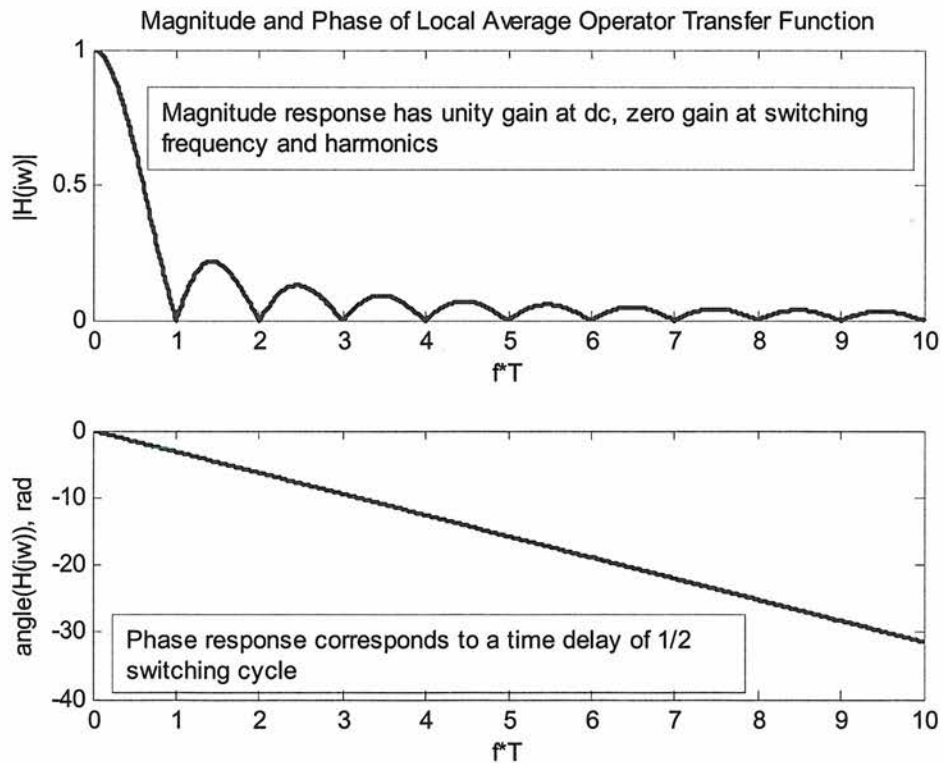

Ex 1



6.334 Lecture Control # 1

Power Electronics Notes - D. Perreault Boost Converter Switched Simulation

(EX 1) 3

* C:\MSimEv_8\Projects\Boost.sch

Date/Time run: 03/28/99 15:07:43

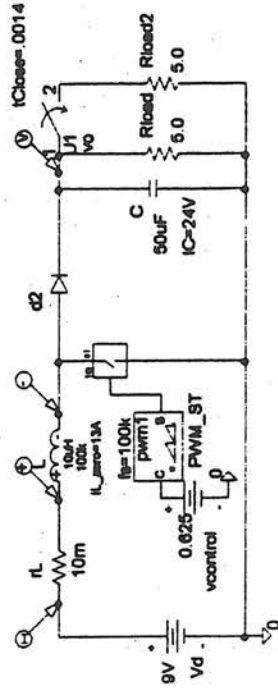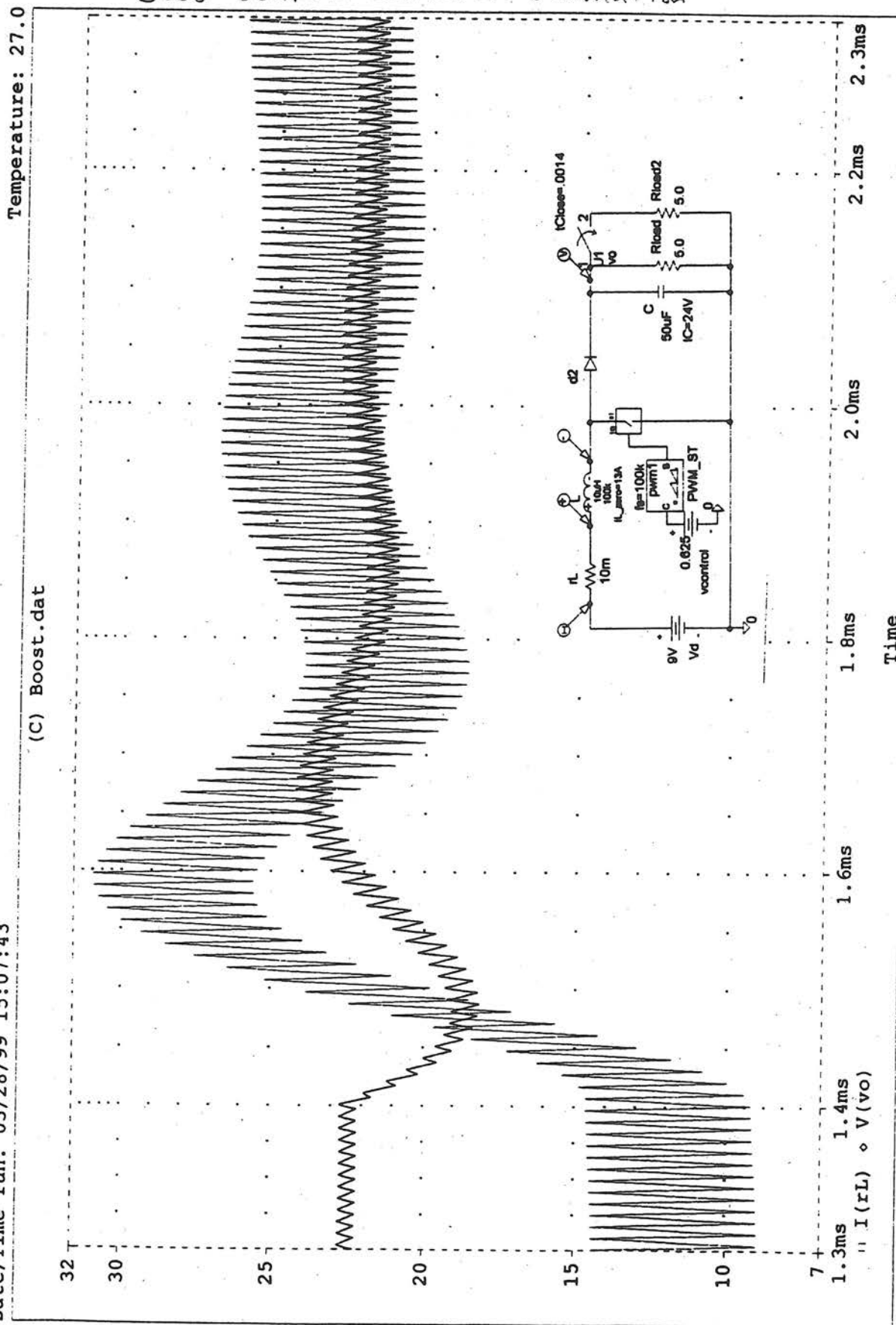

Time: 15:38:37

Page 1


Date: March 28, 1999

Power Electronics Notes - D. Perreault

Consider the use of this operator on a circuit:


→ Because LTI, KVL + KCL are satisfied for averaged vars
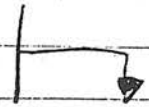
$$\begin{aligned} \text{KVL: } \sum V_{ij} &= 0 \rightarrow \sum \bar{V}_{ij} = 0 \\ \text{KCL: } \sum I_i &= 0 \rightarrow \sum \bar{I}_i = 0 \end{aligned}$$




We can apply avgms in circuits

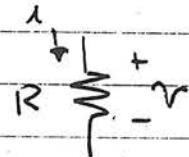Consider constitutive laws for averaged vars:


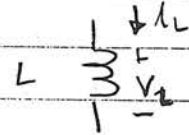
$$\begin{aligned} v(t) &= i(t) R \\ \bar{v}(t) &= \bar{i}(t) R \end{aligned}$$



$$\begin{aligned} v &= L \frac{di}{dt} \\ \bar{v} &= L \frac{d\bar{i}}{dt} \end{aligned}$$




$$\begin{aligned} i &= C \frac{dv}{dt} \\ \bar{i} &= C \frac{d\bar{v}}{dt} \end{aligned}$$

LTI circuit elements
Constitutive relationships
do not change!


Nonlinear or time varying elements do change!

Boost ckt

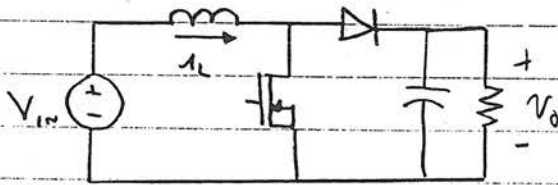

$$\begin{aligned} X(t) y(t) &\neq \bar{X}(t) \bar{y}(t) \\ \text{but IF } X(t) \text{ or } y(t) \text{ has} \\ &1. \text{ Small ripple} \\ &2. \text{ slow variation wrt } T \\ \Rightarrow X(t) y(t) &\approx \bar{X}(t) \bar{y}(t) \end{aligned}$$

model w/switching function

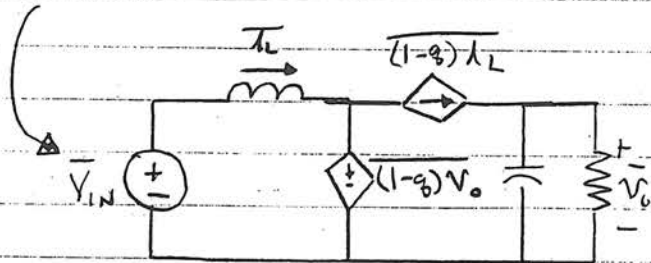


to average, place $\bar{\quad}$ over all variables.
(LTI elements do not change)

IF i_L has small ripple, slow variation $\therefore \overline{(1-d)i_L} \approx \overline{1-d} \cdot \bar{i}_L = d' \bar{i}_L$
 v_o has small ripple, slow variation $\therefore \overline{(1-d)v_o} \approx \overline{1-d} \cdot \bar{v}_o = d' \bar{v}_o$
 i.e. \approx const over a cycle where $d(t) = \bar{d}(t)$

Power Electronics Notes - D. Perreault

Averaged Circuit model

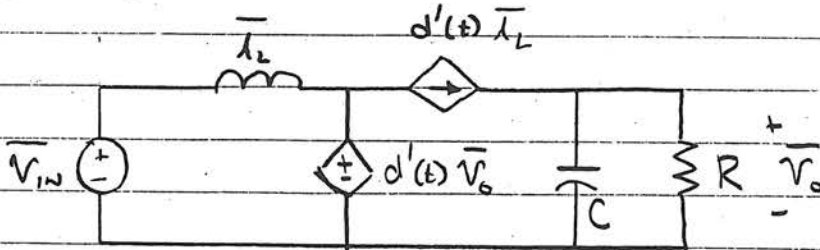

* \rightarrow in this circuit model we have no more switching
(only depends on averaged duty cycle $d(t) = \overline{q(t)}$)

* \rightarrow model is not linear in our control variable $d(t)$
(because of $d'\overline{V}_o$, $d'\overline{I}_L$ terms)

* \rightarrow model is very simple, + should be accurate for averaged variables if our assumptions are valid
(i.e. $\overline{qI_L} = \overline{q} \overline{I_L}$, etc.)

Ex 2 (show simulation w/ both switched + avg'd models.)

\rightarrow good results (small offset due to device mods.)

* \rightarrow will be very useful for control !!

Note: not useful for some things. Ex. switch power dissipation

$$P(t) = V(t)I(t)$$

$$\overline{P(t)} = \overline{V(t)I(t)} \neq \overline{V(t)} \overline{I(t)}$$

\hookrightarrow small ripple assumption not met...



\rightarrow Review how we got here + address questions!

EX2

* C:\MSimEv_8\Projects\BOOST_AVG_Switch.sch, * C:\MSimEv_8\Projects\Boost.sch
Date/Time run: 03/28/99 15:12:21

Temperature: 27.0

(E) BOOST_AVG_Switch.dat, Boost.dat

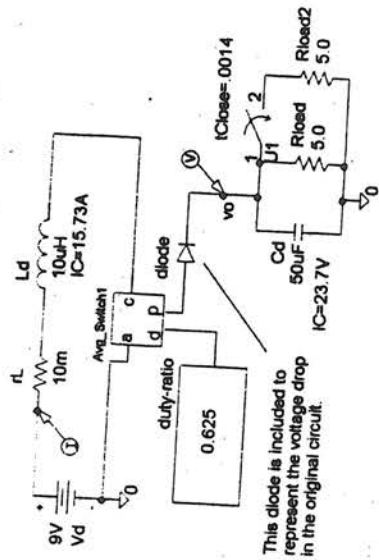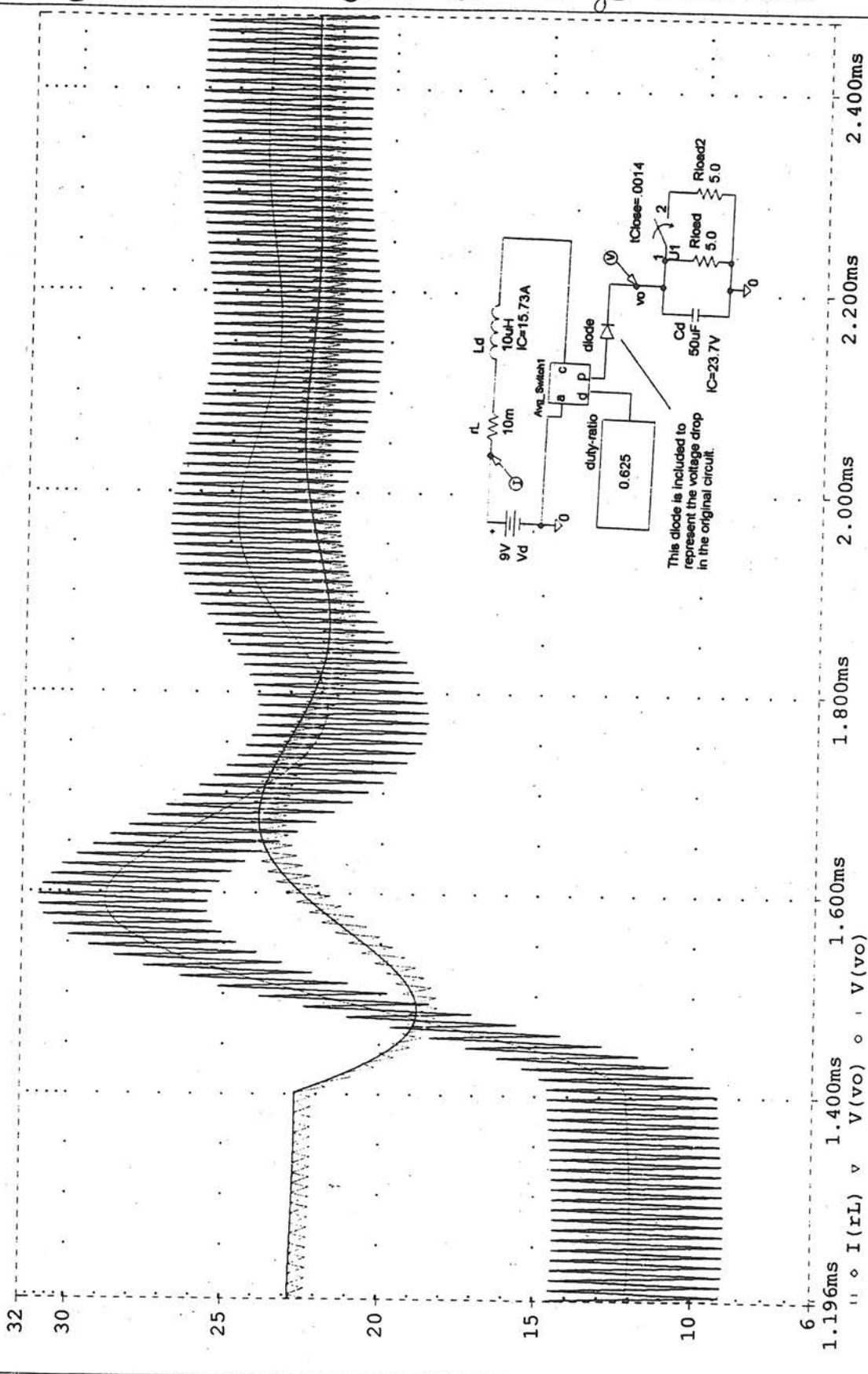

Time

Page 1

Date: March 28, 1999

Time: 18:27:34

6.334 Lecture Control #1

Power Electronics Notes - D. Perreault (EX2)

Boost Converter Switched + Averaged simulation

6

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>