

# Lecture 25 - Control 2

## 1 State-space averaging, Linearization

Reading: KS+V 12.1-12.4, 13.1-13.2

### 1.1 Intro

State space averaging: different (more methodical) approach to the same type of model we built last time


Review:

Local average

$$\bar{x}(t) = \frac{1}{T} \int_{t-T}^t x(\tau) d\tau$$

1. Linear
2. Time invariant
3.  $\overline{\left(\frac{dx}{dt}\right)} = \frac{d\bar{x}}{dt}$
4.  $\overline{x(t)y(t)} \approx \bar{x}(t)\bar{y}(t)$  if only x or y has only slow variation and small ripple

Boost converter:

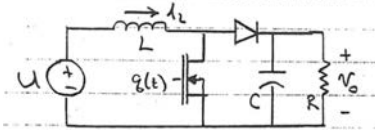

$q(t) =$   
 1 switch on  
 0 switch off

$d(t) = \bar{q}$   
 $d'(t) = q'$


State equations:  $i_L, v_o$  are state variables

$$\begin{cases} \frac{di_L}{dt} = \frac{u}{L}q(t) + \frac{(u-v_o)}{L}(1-q(t)) \\ \frac{dv_o}{dt} = -\frac{1}{RC}v_o(t) + \left(\frac{1}{C}i_L - \frac{1}{RC}v\right)(1-q(t)) \end{cases}$$

Regroup and average:

$$\begin{cases} \frac{d\bar{i}_L}{dt} = \frac{\bar{u}}{L} + \frac{\overline{(v_o)}}{L}q'(t) \approx \frac{1}{L}\bar{u} - \frac{1}{L}\bar{v}d' \\ \frac{d\bar{v}_o}{dt} = -\frac{1}{RC}\bar{v}_o + \frac{1}{C}\bar{i}_Lq'(t) \approx -\frac{1}{RC}\bar{v}_o + \frac{1}{C}\bar{i}_Ld' \end{cases}$$

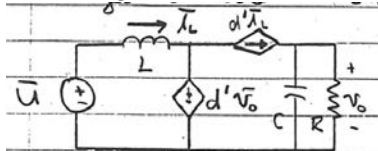Averaged ckt model from direct ckt averaging



$$\begin{cases} \frac{d\bar{i}_L}{dt} = \frac{\bar{u}}{L} + \frac{\overline{(v_o)}}{L}d'(t) \\ \frac{d\bar{v}_o}{dt} = -\frac{1}{RC}\bar{v}_o + \frac{1}{C}\bar{i}_Ld' \end{cases}$$

Same state equations: circuit average and state avg are the same! (circuit view vs equation view)

## 2 Linearization


To do linear control design, linearize system about operating point → explain what linearized dynamics mean

$$x = \bar{X} + \tilde{x} \Rightarrow \tilde{x} = x - \bar{X}$$

$$\text{Formal definition } \bar{u} = U + \tilde{u}, \bar{i}_L = I_L + \tilde{i}_L, \bar{v}_0 = V_0 + \tilde{v}_0, d = D + \tilde{d}$$

given

$$\begin{aligned} \frac{dx}{dt} &= f(x, r, t), f(\bar{X}, R, t) = 0 \\ \Rightarrow \frac{\bar{X}}{dt} + \frac{\tilde{d}}{dt} &= \frac{\partial f}{\partial x} \Big|_{\bar{X}, R} \tilde{x} + \frac{\partial f}{\partial r} \Big|_{\bar{X}, R} \tilde{r} + f(\bar{X}, R) \end{aligned}$$

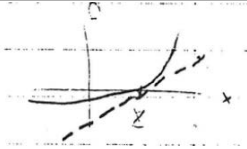

Approx f with a line near  $x = \bar{X}$

Intuitive approach: substitute expanded variables in + simplify (all purely S.S. terms must go away by definition of S.S.)

$$\begin{cases} \frac{dI_L}{dt} + \frac{di_L}{dt} = \frac{1}{L}U + \frac{1}{L}\tilde{u} - \frac{1}{L}(V_0 + \tilde{v}_0)(1 - D - \tilde{d}) \\ \frac{dv_0}{dt} + \frac{d\tilde{v}_0}{dt} = -\frac{1}{RC}V_0 - \frac{1}{RC}\tilde{v}_0 + \frac{1}{C}(I_L + \tilde{i}_L)(1 - D - \tilde{d}) \\ \frac{di_L}{dt} = \frac{1}{L}U - \frac{1}{L}V_0D' + \frac{1}{L}\tilde{u} - \frac{D'}{L}\tilde{v}_0 + \frac{V_0}{L}\tilde{d} + \frac{1}{L}\tilde{v}_0\tilde{d} \\ \frac{d\tilde{v}_0}{dt} = -\frac{1}{RC}V_0 + \frac{D'I_L}{C} - \frac{1}{RC}\tilde{v}_0 + \frac{D'}{C}\tilde{i}_L - \frac{I_L}{C}\tilde{d} - \frac{1}{C}\tilde{i}_L\tilde{d} \end{cases}$$

$$\begin{aligned} \frac{di_L}{dt} &= \frac{1}{L}\tilde{u} - \frac{D'}{L}\tilde{v}_0 + \frac{V_0}{L}\tilde{d} \\ \frac{d\tilde{v}_0}{dt} &= -\frac{1}{RC}\tilde{v}_0 + \frac{D'}{C}\tilde{i}_L - \frac{I_L}{C}\tilde{d} \end{aligned}$$

Linearized model at op pt. U, D,  $V_0$ ,  $I_L$

Assume  $u = U$  (no perturbation in U); Laplace transform:

$$\begin{cases} s\tilde{i}_L = -\frac{D'}{L}\tilde{v}_0 + \frac{V_0}{L}\tilde{d} \\ s\tilde{v}_0 = -\frac{1}{RC}\tilde{v}_0 + \frac{D'}{C}\tilde{i}_L - \frac{I_L}{C}\tilde{d} \end{cases}$$

$$s\tilde{v}_0 = -\frac{1}{RC}\tilde{v}_0 + \frac{D'}{sC}\left(-\frac{D'}{L}\tilde{v}_0 + \frac{V_0}{L}\tilde{d}\right) - \frac{I_L}{C}\tilde{d}$$

$$\left(S + \frac{D'^2}{sCL} + \frac{1}{RC}\right)v_0 = \left(\frac{v_0D'}{sLC} - \frac{I_L}{C}\right)\tilde{d}$$

$$\frac{\tilde{v}_0}{\tilde{d}} = \frac{-s\frac{I_L}{C} + \frac{V_0D'}{LC}}{s^2 + \frac{1}{RC}s + \frac{D'^2}{LC}}$$

2nd order system

- 2 LHP poles (underdamped)
- 1 RHP zero (yuck!)

Poles move w/ operating point!!

Ex/  $U = 9V$ ,  $V=24V$ ,  $D=0.625$ ,  $I_L \approx 25.6A$ ,  $L = 10\mu H$ ,  $C = 50\mu F$ ,  $R = 2.4\Omega$



$$\frac{\tilde{v}_0}{\tilde{d}} = \frac{-512000s + 1.8 \times 10^{10}}{s^2 + 8000s + 2.81 \times 10^8}$$

$$\left\{ \begin{array}{l} \text{zero @ } s = 35,156 \frac{rad}{sec} \\ \text{poles @ } s = -4000 \pm j 16,279 \frac{rad}{sec} \end{array} \right.$$

EX 2
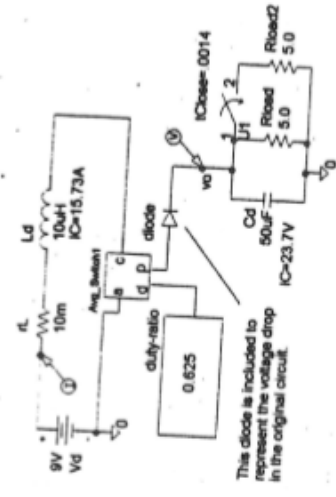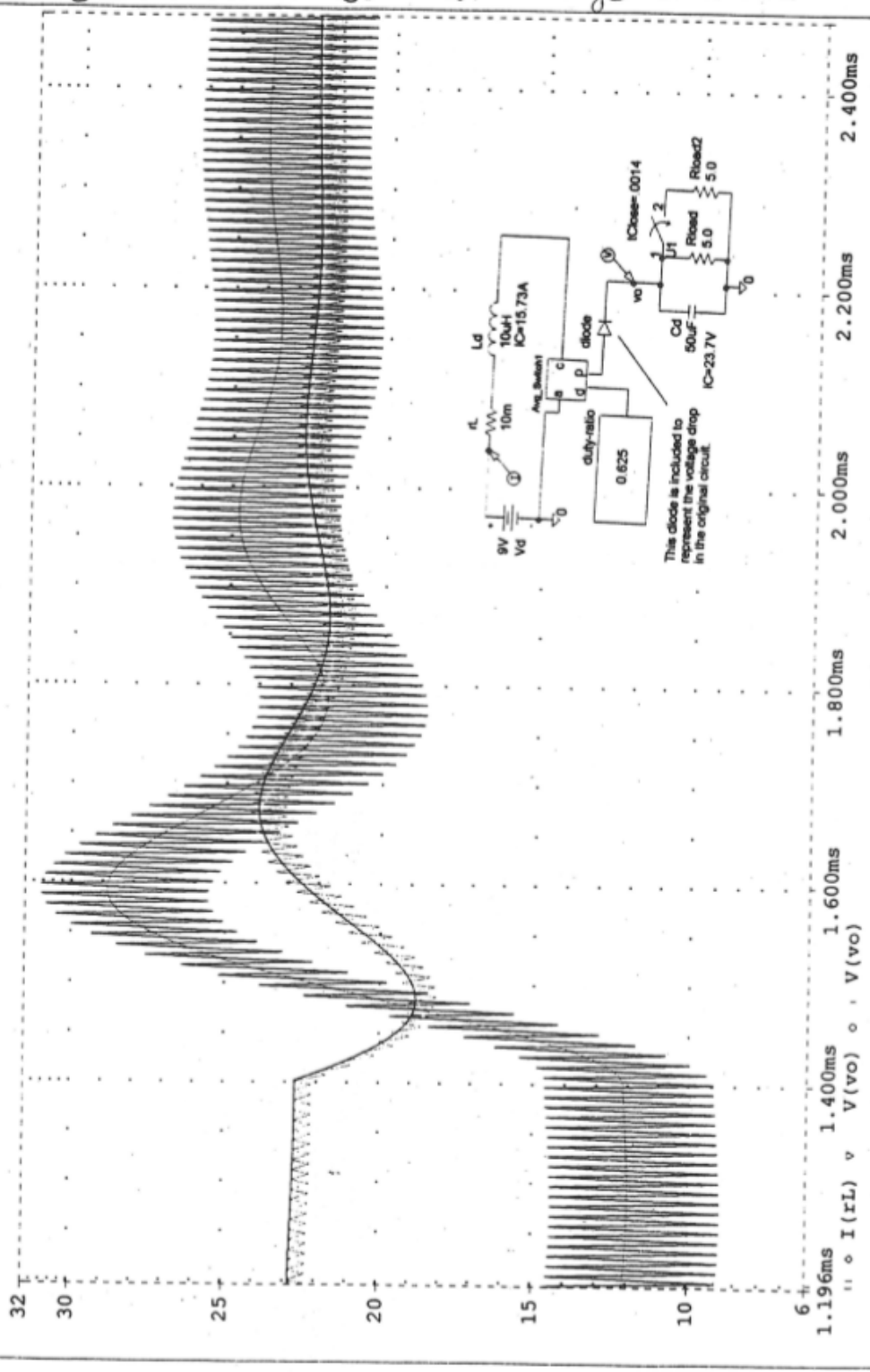
# Boost Converter Switched + Averaged simulation

\* C:\MSimEv\_8\Projects\BOOST\_AVG\_Switch.sch, \* C:\MSimEv\_8\Projects\Boost.sch  
Date/Time run: 03/28/99 15:12:21  
Temperature: 27.0  
(E) BOOST\_AVG\_Switch.dat, Boost.dat



Date: March 28, 1999  
Page 1  
Time: 18:27:34

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>