

# Power Electronics Notes - D. Perreault

## ★ State-Space Averaging, Linearization

Reading: KS+V 12.1-12.4, 13.1-13.2


Intro: State-space averaging: different (more methodical) approach to the same type of model we built last time.

→ Review:

$$\bar{X}(t) = \frac{1}{T} \int_{t-T}^t X(\tau) d\tau$$

- 1. Linear
- 2. Time Invariant
- 3.  $\overline{\left(\frac{dx}{dt}\right)} = \frac{d\bar{x}}{dt}$
- 4.  $\overline{xy(t)} \approx \bar{X}(t)\bar{Y}(t)$  if  $X$  or  $Y$  has slow variation & small ripple

### Boost Converter

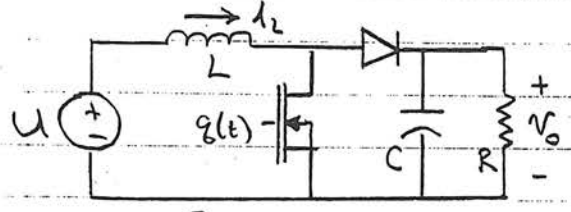

$$q(t) = \begin{cases} 1 & \text{switch on} \\ 0 & \text{switch off} \end{cases} \quad q' = 1 - q$$

$$\begin{aligned} d(t) &= \bar{q} \\ d'(t) &= \bar{q}' \end{aligned}$$

State equations:  $i_L, V_o$  are state variables

$$\begin{cases} \frac{di_L}{dt} = \frac{U}{L} q(t) + \frac{(U - V_o)}{L} (1 - q(t)) \\ \frac{dV_o}{dt} = -\frac{1}{RC} V_o + \left[ \frac{1}{C} i_L - \frac{1}{RC} V_o \right] (1 - q(t)) \end{cases}$$


neglect  
+  
average

$$\begin{cases} \frac{d\bar{i}_L}{dt} = \frac{\bar{U}}{L} - \frac{\bar{V}_o}{L} \bar{q}'(t) \approx \frac{1}{L} \bar{U} - \frac{1}{L} \bar{V}_o d' \\ \frac{d\bar{V}_o}{dt} = -\frac{1}{RC} \bar{V}_o + \frac{1}{C} \bar{i}_L \bar{q}'(t) \approx -\frac{1}{RC} \bar{V}_o + \frac{1}{C} \bar{i}_L d' \end{cases} \quad \star$$

because  $\overline{xy} \approx \bar{X}\bar{Y}$

Power Electronics Notes - D. Perreault

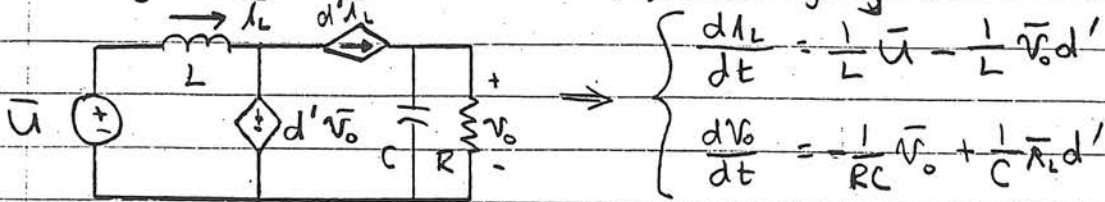Averaged ckt model from direct ckt. averaging



Same state eqns: Circuit avg, + state space avg, are the same! (circuit view vs. eqn. view.)

★ Linearization

To do linear control design, Linearize system about operating point.

→ explain what linearized dynamics mean.  $x = \bar{x} + \tilde{x} \Rightarrow \tilde{x} = x - \bar{x}$  (deviation from S.S.)

$$\bar{u} = U + \tilde{u} \quad \bar{i}_L = I_L + \tilde{i}_L \quad \bar{v}_0 = V_0 + \tilde{v}_0 \quad d = D + \tilde{d}$$

formal def: Given  $\frac{dx}{dt} = f(x, r, t)$ ,  $f(\bar{x}, \bar{r}, t) = 0$  (op. point)

$$\Rightarrow \frac{d\tilde{x}}{dt} + \frac{d\bar{x}}{dt} = \frac{\partial f}{\partial x} \bigg|_{\bar{x}, \bar{r}} \tilde{x} + \frac{\partial f}{\partial r} \bigg|_{\bar{x}, \bar{r}} \tilde{r} + f(\bar{x}, \bar{r})$$

$\frac{\partial f}{\partial x}, \frac{\partial f}{\partial r}$  must be continuous!!

intuitive approach: substitute expanded variables in + simplify (all purely S.S. terms must go away by definition of S.S.)

approx f with a line near  $x = \bar{x}$

$$\begin{cases} \frac{d\tilde{i}_L}{dt} + \frac{d\tilde{i}_L}{dt} = \frac{1}{L} U + \frac{1}{L} \tilde{u} - \frac{1}{L} (V_0 + \tilde{v}_0) (1 - D - \tilde{d}) \\ \frac{d\tilde{v}_0}{dt} + \frac{d\tilde{v}_0}{dt} = -\frac{1}{RC} V_0 - \frac{1}{RC} \tilde{v}_0 + \frac{1}{C} (I_L + \tilde{i}_L) (1 - D - \tilde{d}) \end{cases}$$

1st order Taylor Expansion of f about  $\bar{x}, \bar{r}$

$$\frac{d\tilde{i}_L}{dt} = \frac{1}{L} U - \frac{1}{L} V_0 D' + \frac{1}{L} \tilde{u} - \frac{D'}{L} \tilde{v}_0 + \frac{V_0}{L} \tilde{d} + \frac{1}{L} \tilde{v}_0 \tilde{d}$$

$$\frac{d\tilde{v}_0}{dt} = -\frac{1}{RC} V_0 + \frac{D' I_L}{C} - \frac{1}{RC} \tilde{v}_0 + \frac{D'}{C} \tilde{i}_L - \frac{I_L}{C} \tilde{d} - \frac{1}{C} \tilde{i}_L \tilde{d}$$

$$\begin{cases} \frac{d\tilde{i}_L}{dt} = \frac{1}{L} \tilde{u} - \frac{D'}{L} \tilde{v}_0 + \frac{V_0}{L} \tilde{d} \\ \frac{d\tilde{v}_0}{dt} = -\frac{1}{RC} \tilde{v}_0 + \frac{D'}{C} \tilde{i}_L - \frac{I_L}{C} \tilde{d} \end{cases}$$

Linearized model at op pt.  $U, D, V_0, I_L$

# Power Electronics Notes - D. Perreault

Assume  $u = \bar{U}$  (no perturbation in  $u$ ); Laplace transform:

$$\begin{cases} s \tilde{I}_L = -\frac{D'}{L} \tilde{V}_o + \frac{V_o}{L} \tilde{d} \\ s \tilde{V}_o = -\frac{1}{RC} \tilde{V}_o + \frac{D'}{C} \tilde{I}_L - \frac{I_L}{C} \tilde{d} \end{cases}$$

$$s \tilde{V}_o = -\frac{1}{RC} \tilde{V}_o + \frac{D'}{sC} \left( -\frac{D'}{L} \tilde{V}_o + \frac{V_o}{L} \tilde{d} \right) - \frac{I_L}{C} \tilde{d}$$

$$\left( s + \frac{D'^2}{sCL} + \frac{1}{RC} \right) \tilde{V}_o = \left( \frac{V_o D'}{sLC} - \frac{I_L}{C} \right) \tilde{d}$$

$$\frac{\tilde{V}_o}{\tilde{d}} = \frac{-s \frac{I_L}{C} + \frac{V_o D'}{LC}}{s^2 + \frac{1}{RC} s + \frac{D'^2}{LC}}$$

- 2nd order system
- 2 LHP poles (underdamped)
- 1 RHP zero (yuck!)

★ → poles move w/ operating point !!

one op pt. only! → Ex/  $U = 9V, V = 24V, D = 0.625, I_L \approx 25.6A$   
 $L = 10\mu H, C = 50\mu F, R = 2.5\Omega$

$$\frac{\tilde{V}_o}{\tilde{d}} = \frac{-512000s + 1.8 \times 10^{10}}{s^2 + 8000s + 2.31 \times 10^8}$$

$$\begin{cases} \text{zero @ } s = 35,156 \text{ rad/sec} \\ \text{poles @ } s = -4,000 \pm j16,279 \text{ rad/sec} \end{cases}$$

↑  
≈ .4 msec osc. period

Example from simulation (EX 1/2)  
 ∴ compare to it. !!

EX2

6.334 Lecture Control #1

Power Electronics Notes - D. Perreault (EX2)



6

Boost Converter Switched + Averaged simulation

\* C:\MSimEv 8\Projects\BOOST\_AVG\_Switch.sch, \* C:\MSimEv 8\Projects\Boost.sch

Temperature: 27.0

(E) BOOST\_AVG\_Switch.dat, Boost.dat

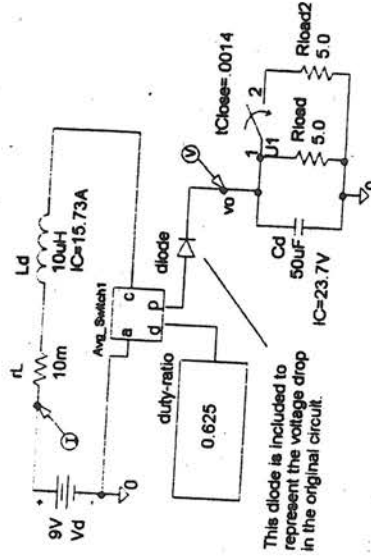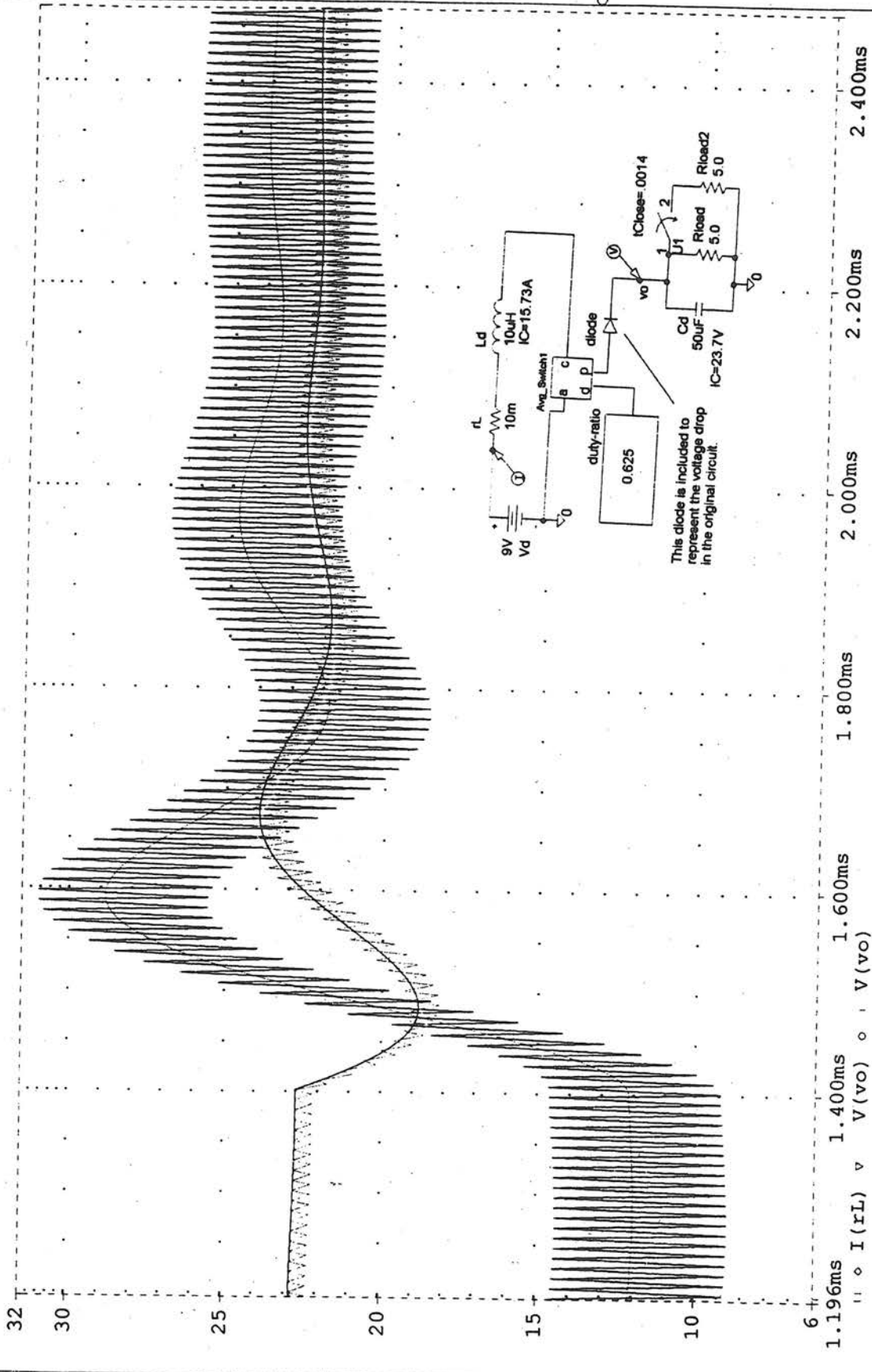

Time

Page 1

Date: March 28, 1999

Time: 18:27:34

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>