


# Lecture 27 - Control 4 (Current-Mode Control)

We have seen that duty-ratio control can yield (in Boost and other converters):

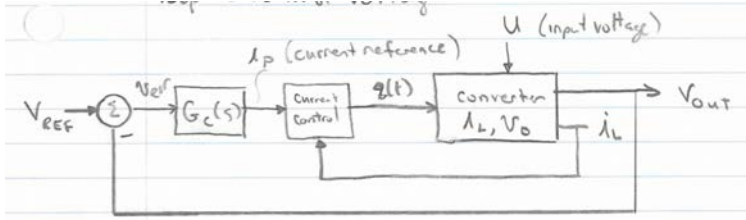1. Nonlinear dynamics (vary w/ operating point)
2. RHP zero + lightly-damped poles

One can partially mitigate damping and operating-point variation with a damping leg. However, a still better strategy is “full-state feedback”: control the converter based on both inductor current and output (capacitor) voltage.

In current-mode control we add an inner feedback loop to control inductor current, and use an outer feedback loop to control voltage.




In peak current control we adjust the switching function  $q(t)$  such that

1. The switch turns on every  $T$  seconds
2. Switch turns off when the peak inductor current reaches (a simple function of) a reference value  $i_p$

$\Rightarrow$  The value of  $i_p$  is set by the (outer) voltage control loop to regulate  $v_{out}$   
This gives

1. better controlled dynamics
2. cycle-by-cycle current limiting

Consider the boost:

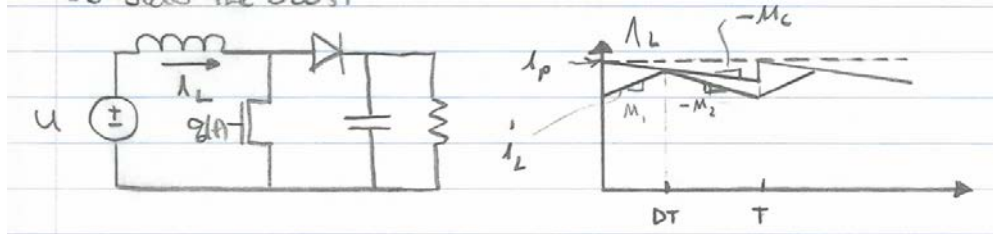


Boost  
 $\mu_1 = \frac{u}{L}$   
 $\mu_2 = \frac{v-u}{L}$

- Switch turns on at beginning of each cycle
- switch turns off when  $i_L$  reaches  $i_p - \mu_c(t - nT)$ 
  - $\rightarrow$  will see reason for adjustment term  $\mu_c$  shortly
  - $\rightarrow$  must sense  $i_L$  (or  $i_{sw}$ ) but often do anyway for protection
- control output voltage by adjusting  $i_p$

Consider system dynamics:

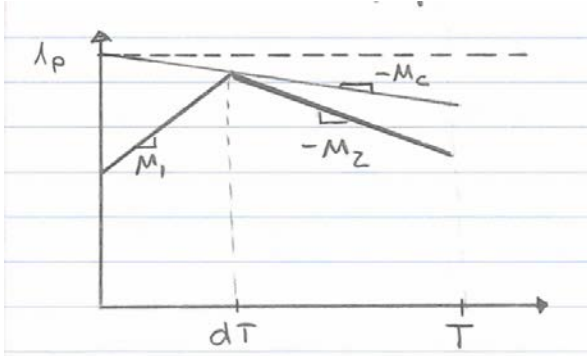Simplest method: start with duty ratio equations, find (approximate) relation between  $d$ ,  $i_p$ ,  $\bar{i}_L$



Look at a 1-cycle window and make a geometric approximation

$$\bar{i}_L \approx (i_p - \mu_c dT) - \frac{1}{T} \left[ \frac{1}{2} \mu_1 d^2 T^2 + \frac{1}{2} \mu_2 (1-d)^2 T^2 \right]$$

$$\bar{i}_L \approx (i_p - \mu_c dT) - \frac{1}{2} \mu_1 d^2 T + \frac{1}{2} \mu_2 (1-d)^2 T$$

Their equation can be used for various types of converters (but for different values of  $\mu_1, \mu_2$ )

For a boost converter:  $\mu_1 = \frac{\bar{v}}{L}, \mu_2 = \frac{\bar{v}-\bar{u}}{L}$

$$\therefore i_L = i_p - \mu_c dT - \frac{1}{2} \frac{\bar{u}T}{L} d^2 - \frac{(\bar{v}-\bar{u})T}{2L} (1-d)^2$$

linearize + solve for  $\tilde{d}$ :


$$\text{(Equation*)} \tilde{d} = \frac{1}{\mu_c T} (\tilde{i}_p - \tilde{i}_L) - \frac{(D^2 - D'^2)}{2L\mu_c} \tilde{u} - \frac{D'^2}{2L\mu_c} \tilde{v}$$

For boost converter

If we substitute Equation \* into the linearized state-spacemodel of the boost converter from before, we eliminated  $\tilde{d}$  and have a new control variable  $\tilde{i}_p$


From new model, we can get new linearized plant transfer function  $H_2(s)$

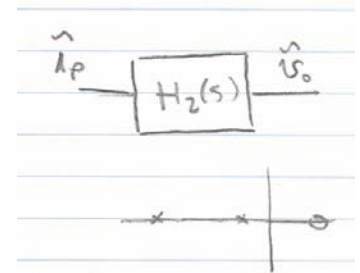1. RHP zero
2. 2 LHP poles
  - low freq, 1 high freq, on real axis (depending on  $\mu_c$ )



⇒ we can achieve much better control performance!

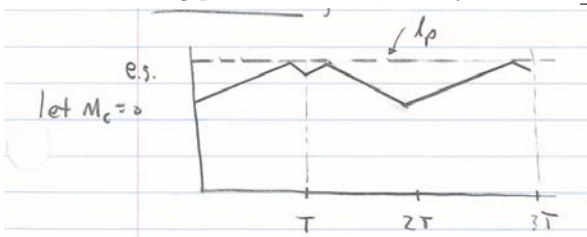
A challenge is Ripple Instability: under some conditions, the system will not settle to a single duty ratio at the switching period. Instead, it may oscillate subharmonically or chaotically!



Bad because

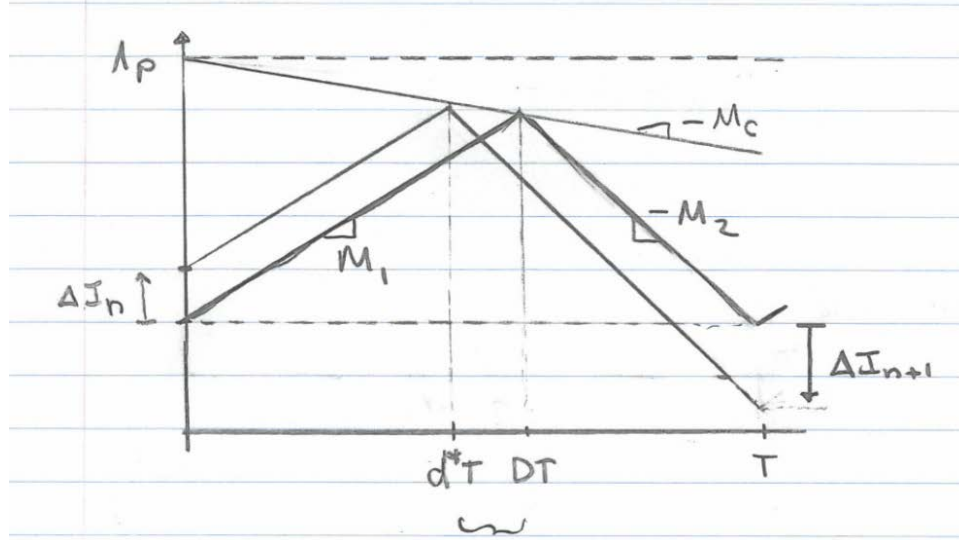1. Low frequency ripple (below  $f_{sw}$ )
2. Large ripple amplitude + spectrum
3. Control is “jittery”

A properly chosen “compensating ramp” (slope  $-\mu_c$ ) can fix this:  $\Rightarrow$  let’s analyze ripple dynamics (can’t use averaged model)



Start w/  $\Delta I$  offset from steady state  $\mu_1 D = \mu_2(1-D)$

Considering the parallel lines in this region

$$\Delta I_n = (\mu_1 + \mu_c)(D - d^*)T$$

$$\Delta I_{n+1} = (\mu_c + \mu_2)(D - d^*)T$$

$$\Delta I_{n+1} = -\frac{\mu_2 - \mu_c}{\mu_1 + \mu_c} \Delta I_n$$

$$\therefore \Delta I_n = \left(-\frac{\mu_2 - \mu_c}{\mu_1 + \mu_c}\right)^n \Delta I_o$$

Unstable for

$$\left|\frac{\mu_2 - \mu_c}{\mu_1 + \mu_c}\right| > 1$$

@  $\mu_c = 0$   $\left|\frac{\mu_2}{\mu_1}\right| > 1 \xrightarrow{\text{boost}} \left|\frac{D}{1-D}\right| > 1 \therefore$  unstable for  $D > 0.5$

$\Rightarrow$  choose  $\mu_c$  to stabilize ripple dynamics ( $\mu_2 = \mu_c$  deadbeat control)

But  $\mu_c$  affects averaged dynamics (steeper  $\mu_c$  looks more like duty ratio control)  $\Rightarrow$  tradeoff.

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>