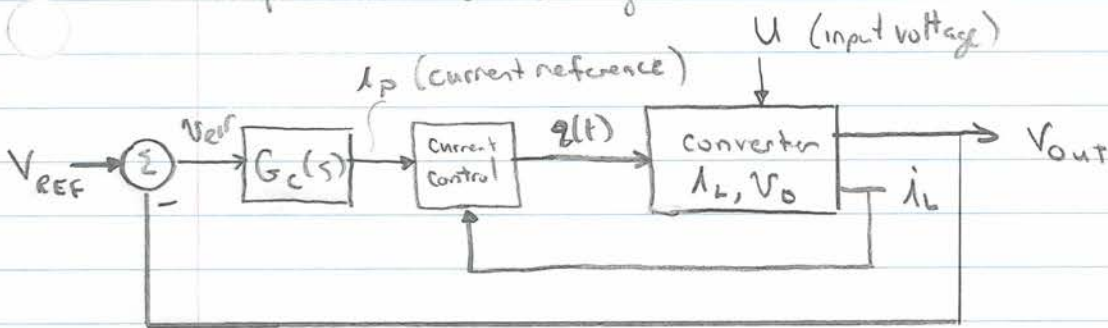


We have seen that duty-ratio control can yield (in Boost and other converters):

- ① Nonlinear dynamics (vary w/ operating point)
- ② RHP zero + lightly-damped poles

One can partially mitigate damping and operating-point variation with a damping leg. However, a still better strategy is "full-state feedback": Control the converter based on both inductor current and output (capacitor) voltage.

In current-mode control we add an inner feedback loop to control inductor current, and use an outer feedback loop to control voltage



In peak current control we adjust the switching function $q(t)$ such that

- ① The switch turns on every T seconds
- ② switch turns off when the peak inductor current reaches (a simple function of) a reference value I_p .



⇒ The value of I_p is set by the (outer) voltage control loop to regulate V_{out}

This gives: ① better controlled dynamics
 ② cycle-by-cycle current limiting

6.334 Lecture

Current-Mode Control

Consider the boost:

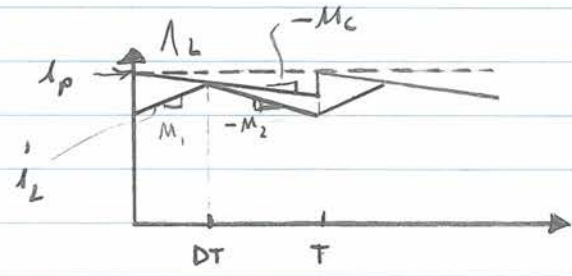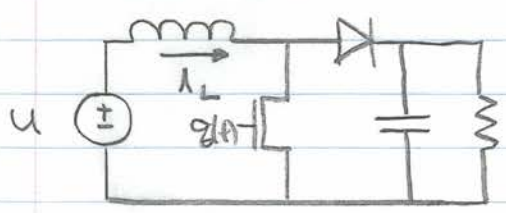


Boost
 $M_1 = \frac{U}{L}$
 $M_2 = \frac{V-U}{L}$

- Switch turns on at beginning of each cycle
- Switch turns off when i_L reaches $\lambda_p - M_c(t-nT)$
 - will see reason for adjustment term M_c shortly
 - must sense i_L (or i_{sw}) but often do anyway for protection
- Control output voltage by adjusting λ_p .

Consider system dynamics:

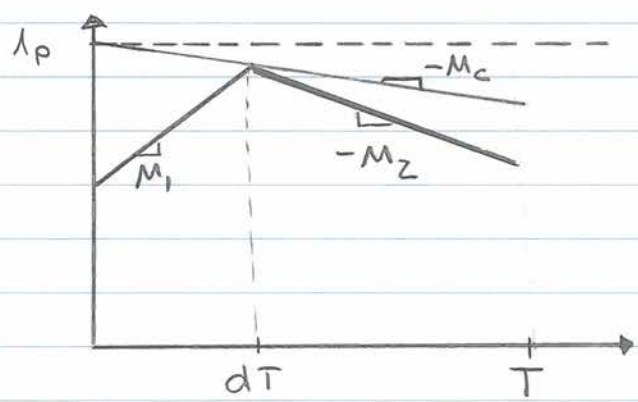Simplest method: start with duty ratio eqns, find (approximate) relation between d , λ_p , \bar{i}_L



Look at a 1-cycle window and make a geometric approximation

$$\bar{i}_L \approx (\lambda_p - M_c d T) - \frac{1}{T} \left[\frac{1}{2} M_1 d^2 T^2 + \frac{1}{2} M_2 (1-d)^2 T^2 \right]$$

$$\bar{i}_L \approx \lambda_p - M_c d T - \frac{1}{2} M_1 d^2 T - \frac{1}{2} M_2 (1-d)^2 T$$

This equation can be used for various types of converters (but for different values of M_1, M_2)

6.334 Lecture

Current-Mode Control

for a boost converter: $M_1 = \frac{\bar{u}}{L}$, $M_2 = \frac{\bar{v}-\bar{u}}{L}$

$$\therefore \lambda_L = \lambda_p - M_c d T - \frac{1}{2} \frac{\bar{u} T}{L} d^2 - \frac{(\bar{v}-\bar{u}) T}{2L} (1-d)^2$$


Linearize + solve for \tilde{d} :

$$\star \tilde{d} = \frac{1}{M_c T} (\tilde{\lambda}_p - \tilde{\lambda}_L) - \frac{(D^2 - D'^2)}{2LM_c} \tilde{u} - \frac{D'^2}{2LM_c} \tilde{v}$$

for boost converter

If we substitute (\star) into the linearized state-space model of the boost converter from before, we eliminate \tilde{d} and have a new control variable $\tilde{\lambda}_p$

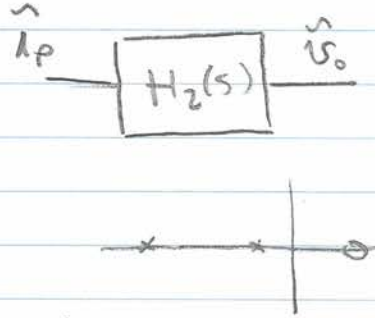
From new model, we can get new linearized plant transfer function $H_2(s)$



- \Rightarrow 1.) RHP zero
- 2.) 2 LHP poles
- \rightarrow low freq, high freq on real axis (depending on M_c)

\Rightarrow we can achieve much better control performance!

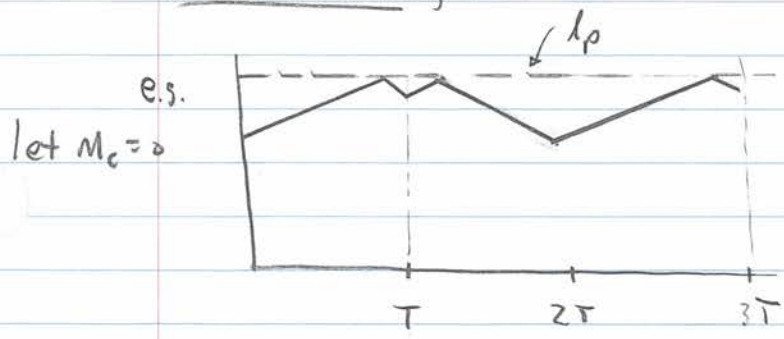A challenge is Ripple Instability: under some conditions, the system will not settle to a single duty ratio at the switching period. Instead, it may oscillate subharmonically or chaotically!




- Bad because
- 1. Low frequency ripple (below f_{sw})
 - 2. larger ripple amplitude + spectrum
 - 3. control is "jittery"

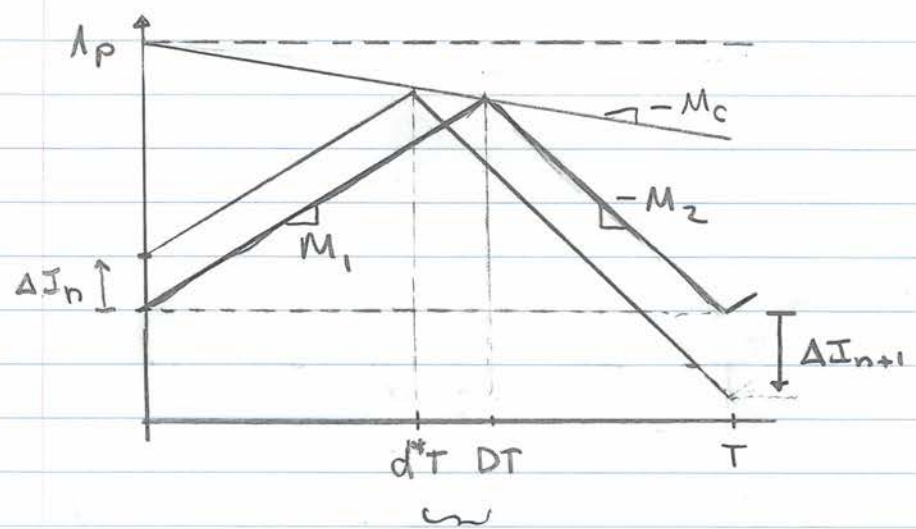6.334 Lecture

Current-Mode Control

A properly chosen "Compensating ramp" (slope = $-M_c$) can fix this:
 \Rightarrow lets analyze ripple dynamics (can't use averaged model)



START w/ ΔI offset
from STEADY STATE
 $M_1 D = M_2 (1-D)$

considering the parallel lines in this region

$$\begin{cases} \Delta I_n = (M_1 + M_c)(D - d^*)T \\ \Delta I_{n+1} = (M_c - M_2)(D - d^*)T \end{cases}$$

$$\therefore \Delta I_{n+1} = -\frac{M_2 - M_c}{M_1 + M_c} \Delta I_n$$

$$\therefore \Delta I_n = \left(-\frac{M_2 - M_c}{M_1 + M_c} \right)^n \Delta I_0$$

unstable for $\left| \frac{M_2 - M_c}{M_1 + M_c} \right| > 1$

@ $M_c = 0$ $\left| \frac{M_2}{M_1} \right| > 1 \xrightarrow{\text{Boost}} \left| \frac{D}{1-D} \right| > 1 \therefore$ unstable for $D > 0.5$

\Rightarrow choose M_c to stabilize ripple dynamics ($M_2 = M_c$ deadbeat control)

But M_c affects averaged dynamics (steeper M_c looks more like duty ratio control) \Rightarrow Tradeoff.

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>