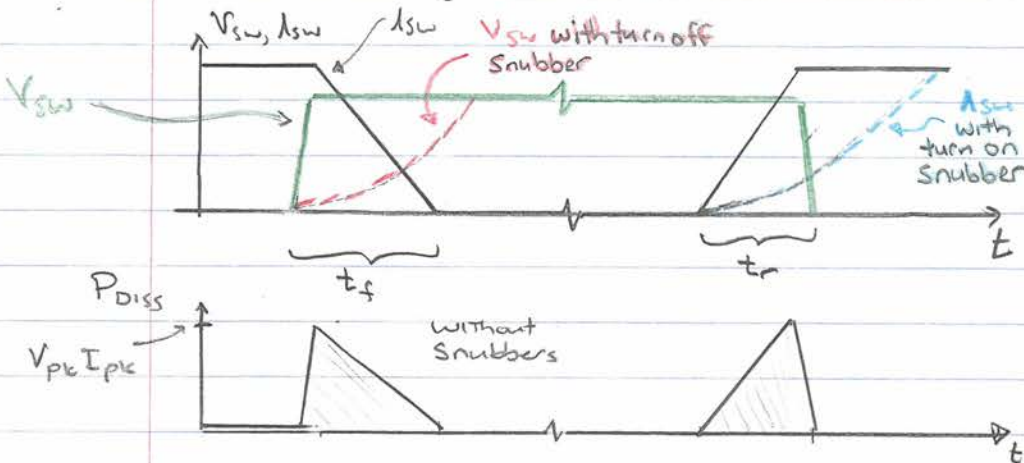


★ NOTE: SHOW DEMO OF HARD-SWITCHED WAVEFORMS AT START

6.334 Lecture Notes

Soft switching # 1

Review: Switching loss + snubbers




But up and
things on board
before class...

The voltage / current overlap (without snubbers) has three deleterious effects:

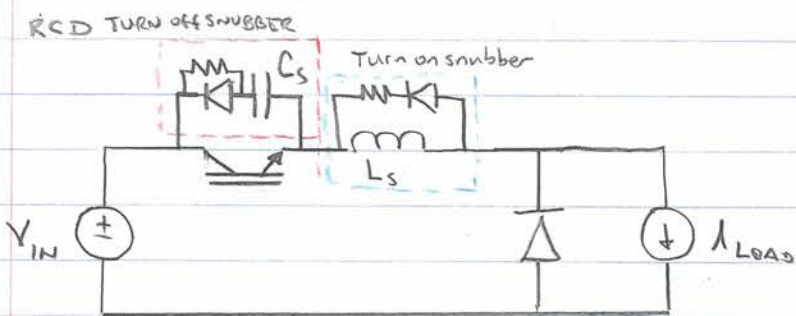1. Loss + limited $\eta + f_{sw}$ (overlap + capacitive discharge loss)
2. EMI due to high $di/dt + dv/dt$
3. Switching locus may exceed SOA + $\frac{di}{dt}, \frac{dv}{dt}$ limits allowed

Snubbers mitigate these effects, but (typically) add losses



Today: Soft-switching techniques try to mitigate these effects without adding loss.

General methods: "zero voltage" switching (ZVS) } can be applied at
"zero current" switching (ZCS) } turn on and/or
turn off



⇒ Turn off snubber looks like ZVS in the limit } But we need to recover the
⇒ Turn on snubber looks like ZCS in the limit } snubber energy!

Soft Switching :

ZERO VOLTAGE

ZERO CURRENT



TURN OFF

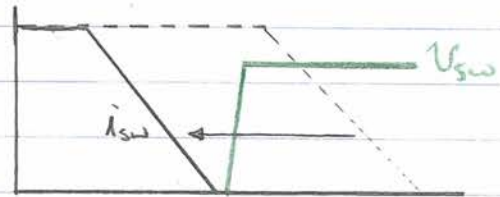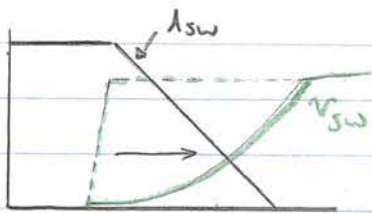

* DELAY V-rise on switch

* MAKE CURRENT IN SWITCH \rightarrow 0 BEFORE turning off switch

TURN ON

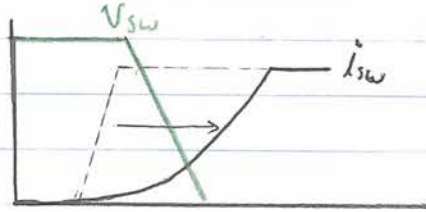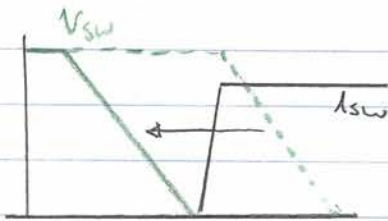

* make switch voltage go to zero before switch turn on

* Delay current rise on switch


- So, we can reduce overlap loss by either delaying voltage or current rise in the switch, or by arranging the switching event to take place when voltage and/or current will naturally be zero.
- These techniques typically require additional control or circuit complexity, or may add conduction loss or peak device stress, but the tradeoff may often be worth it!
- ZVS turn on additionally reduces capacitor discharge loss (important at very high frequencies) while ZCS turn on reduces loss in parasitic inductance.
- Varying degrees of "softness" exist, depending on the degree to which waveform rises are delayed, slopes at transitions, etc.

Example:

ZCS Quasi-Resonant Buck Converter (full wave)

→ see handout/overhead

neglects parasitic capacitance

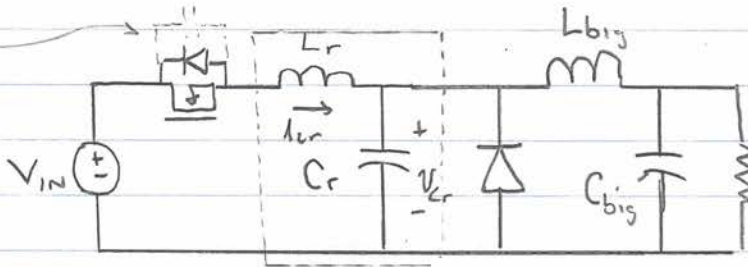

- Go through operational cycle:
- Main switch turns on ZCS
 - main switch/diode turns off ZCS
 - Diode turns on ZCS
 - Diode turns off ZCS

V_{out} controlled by f_{sw} control / pulse density modulation

Show experimental waveforms at light, heavy load


Advantages: smooth (mostly soft) waveform transitions
low switching losses to moderate frequencies

- Disadv:
- ZCS turn on still loses junction cap energy
 - ZCS turn off of device can still have ringing w/ device junction cap
 - High conduction losses (compared to PWM) due to resonant action & energy slosh
 - diode voltage rating 2X
 - requires frequency control over very wide range

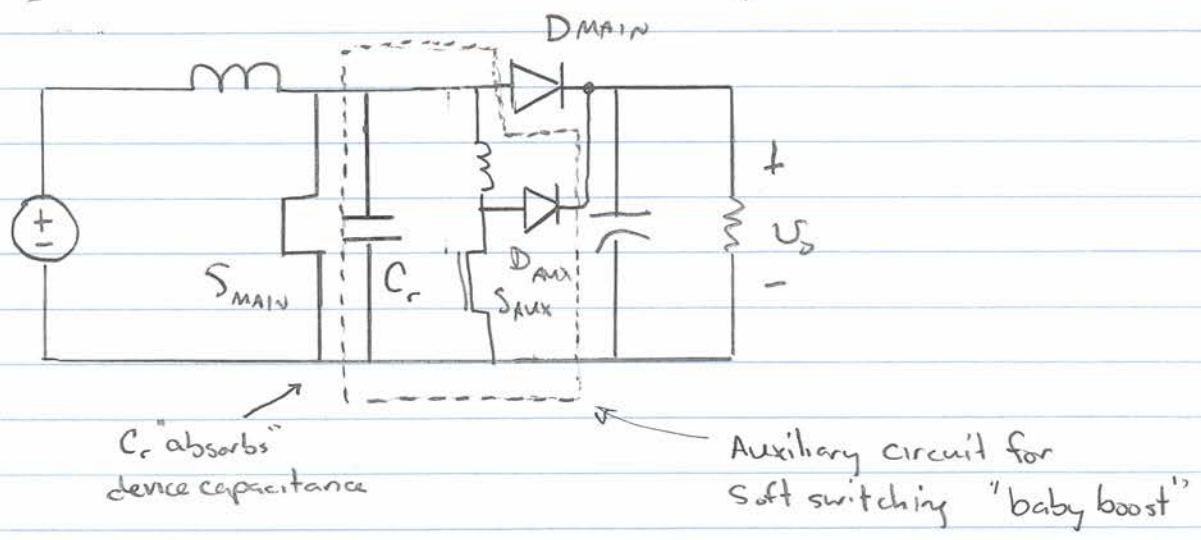EXAMPLE: ZVT Boost Converter

Add an auxiliary circuit to the conventional PWM boost converter to enable the main devices to have ZVS switching

→ The auxiliary "Baby boost" circuit is not fully soft switched, but has a low rating.



- Auxiliary circuit operates only @ switching transitions
 - Allows ZVS switching of main switch and diode
 - especially valuable @ high output voltage where Main diode reverse recovery (+ switch capacitive discharge loss) are important.

- Auxiliary circuit is not fully soft switched (compromise between full soft switching + hard switching)
 - ZCS turn on of S_{AUX} , but capacitive discharge remains
 - SES turn off of D_{AUX}
 - loss is limited because auxiliary circuit elements can be small.

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>