

# Lecture 35 - Resonant Power Conversion 1

## 1 Resonant Power Conversion

In many power converter applications, one converts between dc and high-frequency sinusoidal ac (either as an intermediate or final waveform). Applications include:

1. RF Power amplifiers for communications, radar, etc.
2. High frequency inverters for induction heating
3. “Resonant” dc/dc converters using high-frequency sinusoidal intermediate waveforms & energy storage
4. Electronic ballasts for lighting
5. Power converters using resonant energy storage/transformer structures (e.g., piezoelectric, “electromechanical” transformers)

Here we consider topologies, designs + control methods that are suited to these applications. These applications share certain objectives:


1. High-frequency sinusoidal ac waveforms
2. A desire for high-efficiency power conversion

But

Different applications have different requirements

1. Load characteristics (narrow, well-known range vs wide load variations)
2. Need for or absence of regulation + control of output
3. high sinusoidal waveform purity (required or not)


## 2 Review of Resonant Circuits

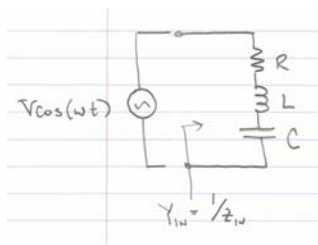

$$Y_{in} = \frac{1}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{R + j(\omega L - \frac{1}{\omega C})}$$

$$|Y_{in}| = \frac{1}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$
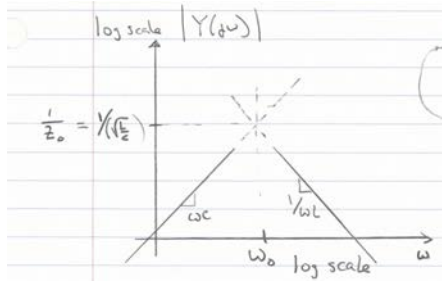
$$\angle = -\tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$



- @ low frequency, capacitor limits admittance  $Y_{in} \approx j\omega C$
- @ high frequency, inductor limits admittance  $Y_{in} = \frac{1}{j\omega L} = \frac{j}{\omega L}$

Both are imaginary with opposite sign.

@ some intermediate frequency, the impedance of L, C and equal and opposite

$$j\omega L = -\frac{j}{\omega C} = 0$$

$$\Rightarrow \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$\omega_0$ : "undamped natural frequency"

$$@\omega_0 : |z_L| = \omega_0 L = \frac{L}{C}, |z_C| = \frac{\omega_0}{C} = \frac{L}{C}$$

"Characteristic impedance"  $z_0 \triangleq \sqrt{\frac{L}{C}}$

$$\star \rightarrow \text{Note } |V_c(\omega_0)| = \frac{|I_L|}{\omega_0 C} = \sqrt{\frac{L}{C}} \cdot |I_L| = z_0 |I_L| \Rightarrow z_0 \text{ relates } |v_c| \text{ to } |i_L| @ \omega_0$$

What happens near  $\omega = \omega_0$ ?


$$@\omega = \omega_0, Y_{in} = \frac{1}{R} \text{ (L, C impedances cancel)}$$

∴ Three possible cases

The behavior depends on relative values of  $z_0, R$

$$R \gg z_0 = \sqrt{\frac{L}{C}}$$

$R \sim Z$  "low Q"

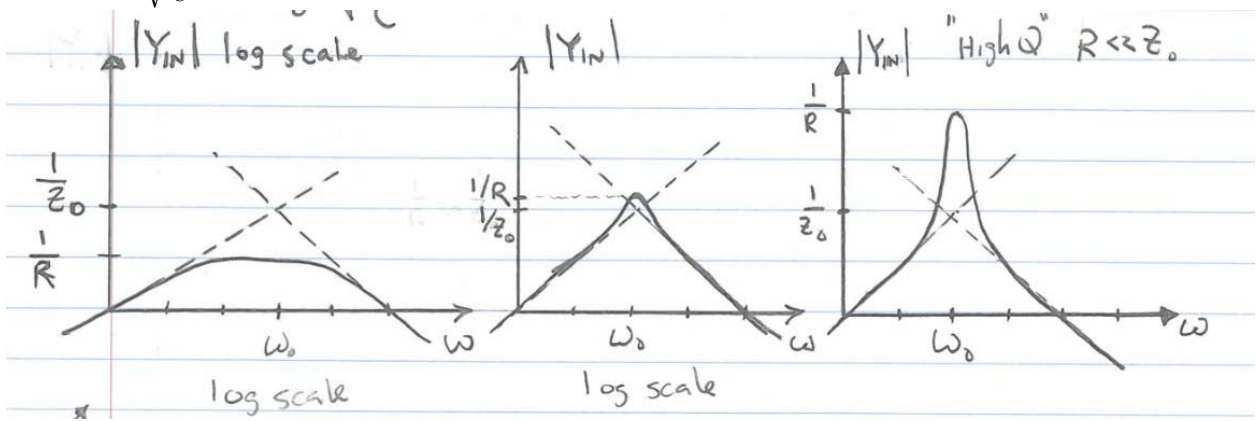


We often discuss "Q" or "quality factor" of a system. The quality factor is proportional to the peak ac energy stored to the energy dissipated in an ac cycle

$$Q \triangleq 2\pi \frac{\text{Peak energy stored}}{\text{Energy dissipated}}$$

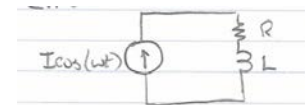Example: a series RL circuit

$$E_{stored} = \frac{1}{2} LI^2$$

$$E_{diss} = \left(\frac{1}{2} I^2 R\right)(T) = \left(\frac{1}{2} I^2 R\right) \cdot \frac{2\pi}{\omega} = \frac{\pi I^2 R}{\omega}$$



$$\Rightarrow Q = 2\pi \cdot \frac{LI^2\omega}{RI^22\pi}$$

$$\Rightarrow Q = \frac{\omega L}{R}$$

Let's consider the Q of the series LRC @  $\omega = \omega_0$


$$i(t) = \frac{V_s}{R} \cos(\omega_0 t)$$

From before @  $I = \frac{V}{R}$

$$E_{diss} = \frac{\pi V_s^2}{\omega_0 R}$$

@  $\omega_0, i_L, v_c$  out of phase  $\therefore i_{L,P} @ v_c = 0$

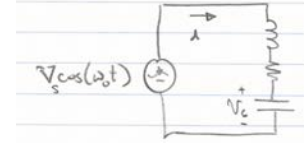
$$E_{stored} = \frac{1}{2} L \left( \frac{V_s}{R} \right)^2 = \frac{1}{2} \frac{L V_s^2}{R^2}$$



$$\therefore Q(\omega_0) = 2\pi \frac{L V_s^2}{2R^2} \cdot \frac{\omega_0 R}{\pi v_s^2} = \frac{\omega_0 L}{R} = \frac{\sqrt{\frac{L}{C}}}{R} = \frac{z_0}{R}$$

So, considering our plot:

1. The resonance peaks up the admittance (due to L, C cancellation) by a factor  $Q(\omega_0) = \frac{z_0}{R}$ !
2. Consider the voltage gain from source voltage  $V_s$  to peak capacitor voltage  $|v_c|$  at drive frequency  $\omega = \omega_0$

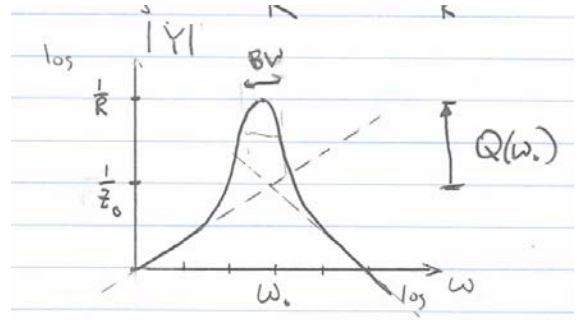

$$V_{c,pk} = \frac{I}{\omega_0 C} = \frac{V_s}{R \cdot \omega_0 C} = V_s \frac{z_0}{R} = V_s \cdot Q(\omega_0)$$

$\therefore$  for large  $Q(@\omega_0)$  we can get large voltage gain from resonance.

This is often used in practice (e.g.) for “striking” the lamp in a lamp ballast)

3. Consider the “bandwidth” over which large resonant peaking occurs. We will consider the bandwidth (or frequency range) over which the power delivered to R is at least half that delivered at  $\omega_0$  (“half-power bandwidth”)

$$@\omega_0, |I| = \frac{V_s}{R}$$

For half-power we get  $|I| = \frac{V_s}{\sqrt{2}R}$

$$\text{or } |Y| = \frac{1}{\sqrt{2}R} = \left| \frac{1}{R + j(\omega L - \frac{1}{\omega C})} \right|$$

$$\therefore \frac{1}{\sqrt{2}R} = \frac{1}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$


$\frac{1}{2}$  power BW is not centered on  $\omega_0$ , but close @ big L Q

$$\therefore \left| \omega L - \frac{1}{\omega C} \right| = R$$

Happens @ two frequencies,  $\omega_1 < \omega_0, \omega_2 > \omega_0$

$$\text{@ } \omega_1 : \omega_1 L - \frac{1}{\omega_1 C} = -R$$

$$\omega_1^2 LC = \omega_1 RC - 1 = 0$$

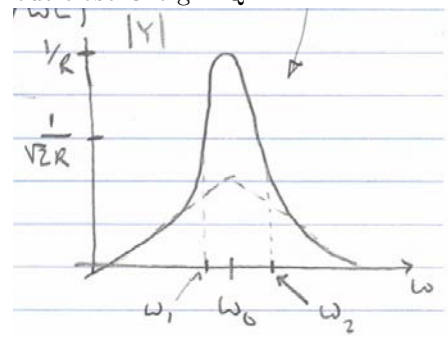

$$\omega_1 = \frac{-RC + \sqrt{(RC)^2 + 4LC}}{2LC} = -\frac{R}{2L} + \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2}$$

$$\text{@ } \omega_2 : \omega_2 L - \frac{1}{\omega_2 C} = R \Rightarrow \omega_2^2 LC - \omega_2 RC - 1 = 0$$

$$\therefore \frac{RC}{2LC} + \sqrt{\left(\frac{RC}{2LC}\right)^2 + \frac{1}{LC}} = \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2} + \frac{R}{2L}$$

Finding the half-power bandwidth  $BW = \omega_2 - \omega_1$

$$\omega_2 - \omega_1 = \frac{R}{L}$$

Normalizing this to  $\omega_0$ , we get:

$$\boxed{\frac{BW}{\omega_0} = \frac{R\sqrt{LC}}{L} = \frac{R}{\sqrt{L/C}} = \frac{R}{z_0} = \frac{1}{Q(\omega_0)}}$$

So we find that the half-power bandwidth (over which the power delivered to R is at least 1/2 that at  $\omega_0$ ) normalized to  $\omega_0$  is  $1/Q$ !

$\Rightarrow$  higher Q gives larger peaking over a narrower bandwidth

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>