
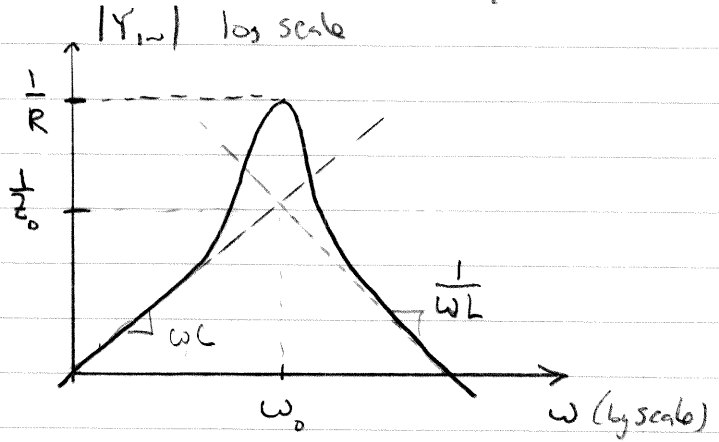


REVIEW:

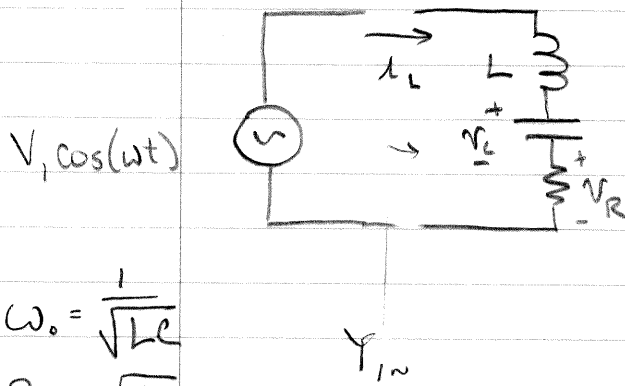RESONANT NETWORKS PROVIDE STRONG IMPEDANCE VARIATION W/ FREQUENCY



$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$Z_0 = \sqrt{\frac{L}{C}}$$

$$Q = \omega_0 Z_0 = \frac{Z_0}{r}$$


⇒ We can control power to load R by varying frequency!

★ "CLASS D" AMPLIFIER IN "SERIES RESONANT" CONVERTER

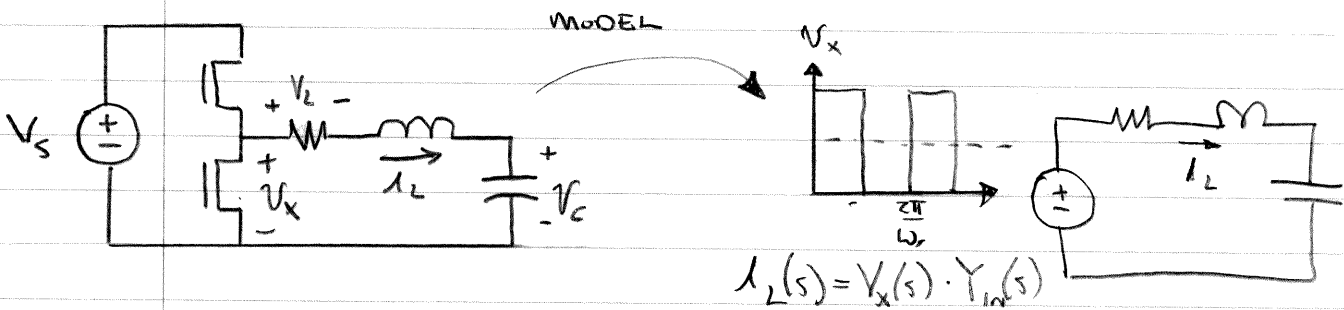Suppose we drive the resonant tank (w/resistive load R) from a half-bridge inverter:



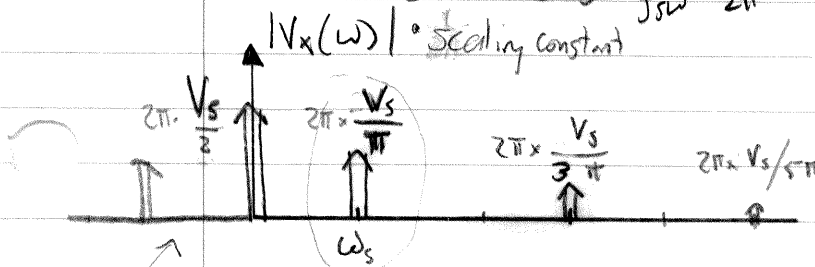IF we switch @ $D=0.5$ $f_{sw} = \frac{\omega_s}{2\pi}$



→ @ high Q { $R \ll \sqrt{\frac{L}{C}}$ }
 ω_s near ω_0
 $i_L \sim$ sinusoidal

Fourier X form based on exponential form of series, has scaling on it (-2pi) o+w p. 298



To control I_L , power to R , we might vary switching frequency above or below resonance

$$|I_L(j\omega_s)| = |V_x(j\omega_s) \cdot Y_{in}(j\omega_s)|$$

- \Rightarrow Above resonance $f_{sw} > \frac{\omega_0}{2\pi}$ network looks inductive
 - \Rightarrow Below resonance $f_{sw} < \frac{\omega_0}{2\pi}$ network looks capacitive
- (Keep: $3f_{sw} \gg \omega_0$ to avoid amplifying harmonic voltage)

Fundamental Harmonic Approximation (FHA):

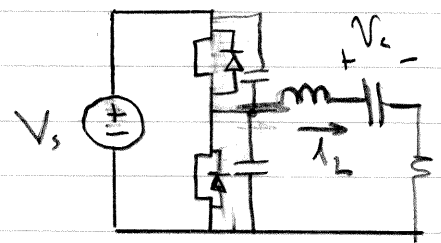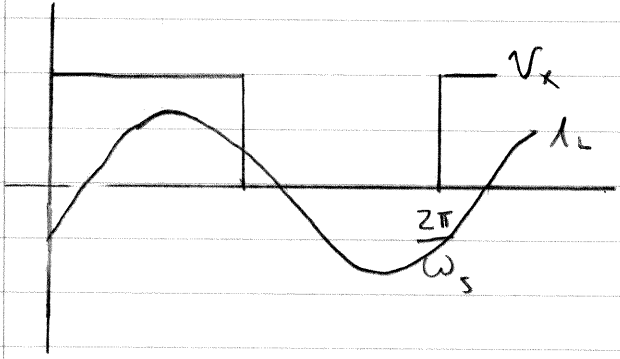\Rightarrow If harmonics well filtered (near resonance, high Q) $I_L \sim$ sinusoidal



could be junction capacitance

Above resonance I_L lags $V_{x,1}$

\Rightarrow If we add capacitors across the switch we can always get ZVS turn on + turn off!

- 0. "nice" characteristic is that device + component currents change proportional to load current (good for efficiency vs. load)
- 1. Note: DEVICE voltages are clamped @ V_s , but I_L, V_C can have large peak values. At resonance

$$\frac{\text{CAP voltage fundamental}}{\text{Drive fundamental}} = \left| \frac{V_C}{V_{x1}} \right|_{\omega=\omega_0} = \sqrt{\frac{L}{C}} = Q! \quad \text{Can be } \gg 1$$

2. CHALLENGE: AS RESISTOR VARIES

- 1. IF R too small $V_s / I_s \uparrow$ or must move away from resonance
- 2. IF R too large tank $Q \downarrow$, low selectivity (wide f var), non-sinusoidal waveforms, can lose soft switching

The load may vary naturally w/ system (e.g. induction cooking). Rectifiers provide loads that vary w/ power + output power.
 having equivalent resistance

6.334 Lecture Notes

Resonant Power Conversion cont'd

WITH THE SERIES CIRCUIT THERE ARE concerns w/ load

Resistor variation



1. IF $R \rightarrow$ too small we must move away from resonance or peak V 's, I 's become large
2. IF $R \rightarrow$ too big selectivity of the tank becomes poor
 \rightarrow current not sinusoidal
 \rightarrow "soft" switching lost

We can get different properties by loading the tanks differently

e.g. parallel loading:

Neglecting C_b (or from other side of C_b):

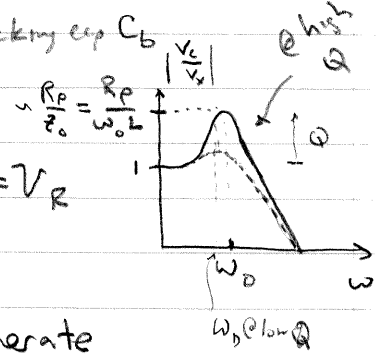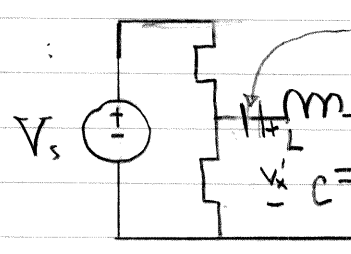
$$\frac{V_c}{V_s} = \frac{1}{s^2 LC + sL/R_p + 1}$$



In this case tank Q becomes high as $R_p \uparrow$ (generate big V 's I 's in tank when $R_p \rightarrow \infty$.) and tank Q \downarrow as $R_p \downarrow$.

This is used to good effect in fluorescent lamp ballasts
 \rightarrow lamp $R \uparrow$ until a big voltage is applied and lamp "strikes"
 \rightarrow once lamp is struck, $R_p \downarrow$ and tank becomes more loaded, delivering appropriate power at lower voltages

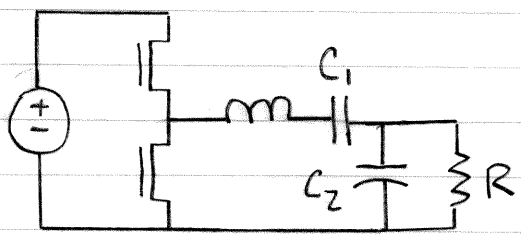To get a balance between series and parallel behavior, the "series parallel" approach is sometimes used: (also called "LCC")



- @ low "R" values R shorts out C_2 and design acts "like" a series resonant
- @ high "R" values the equivalent resonant characteristics change
 [Ceq goes from C_1 to $C_1 || C_2$]



If we increase f_{sw} , we get behavior "like" parallel res.

A further impact of this is that device an component currents don't decline well as power decreases. Efficiency a light load may be a challenge

Q


What about dc-dc conversion? \Rightarrow model the rectifier!

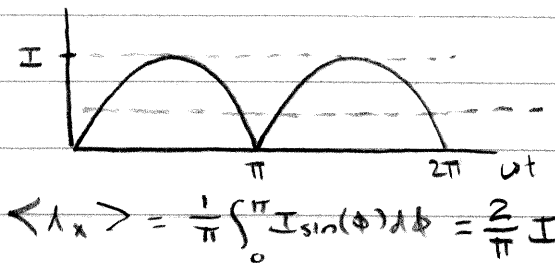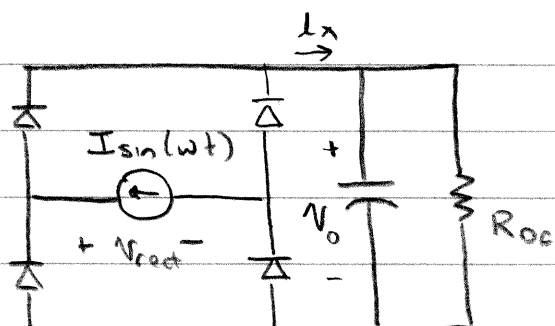We can also use the "Fundamental Harmonic Approximation" to model rectifiers



$$\langle I_x \rangle = \frac{1}{\pi} \int_0^{\pi} I \sin(\phi) d\phi = \frac{2}{\pi} I$$

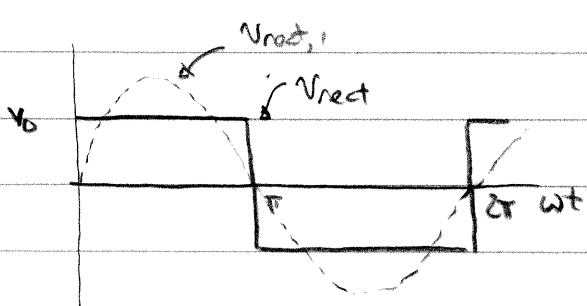$\therefore V_0 = \frac{2}{\pi} I R_{DC}$ If V_0 is determined by a dc load resistor



Fundamental component of V_{rect} is

$$V_{rect,1} = \frac{4}{\pi} V_0 \sin(\omega t)$$

CASES:

① For a fixed output voltage V_0 (not determined by a dc resistor): $P_{AV} = \langle I_x \rangle \cdot V_0 = \frac{2}{\pi} I V_0$ or $I = \frac{\pi}{2} \frac{P_{AV}}{V_0}$

So the FHA ac impedance posed by the rectifier is:

$$R_{ac,eff} = \frac{V_{rect,1}}{I \sin(\omega t)} = \frac{4 V_0}{\pi I} = \frac{4}{\pi} \frac{V_0}{\frac{2 V_0}{\pi} \frac{P_{AV}}{V_0}}$$

$$R_{ac,eff} = \frac{8}{\pi^2} \frac{V_0^2}{P_{AV}}$$

General form for other rectifiers $k \frac{V_0^2}{P_{AV}}$

② IF the rectifier is loaded with a dc resistor R_{dc} :


$$R_{ac,eff} = \frac{V_{rect,1}}{I \sin(\omega t)} = \frac{4 V_0}{\pi I} = \frac{4}{\pi I} \cdot \frac{2 I R_{dc}}{\pi}$$

$$R_{ac,eff} = \frac{8}{\pi^2} R_{dc}$$

General form for other rectifiers $k' \cdot R_{dc}$

Similar expressions may be found for other rectifiers

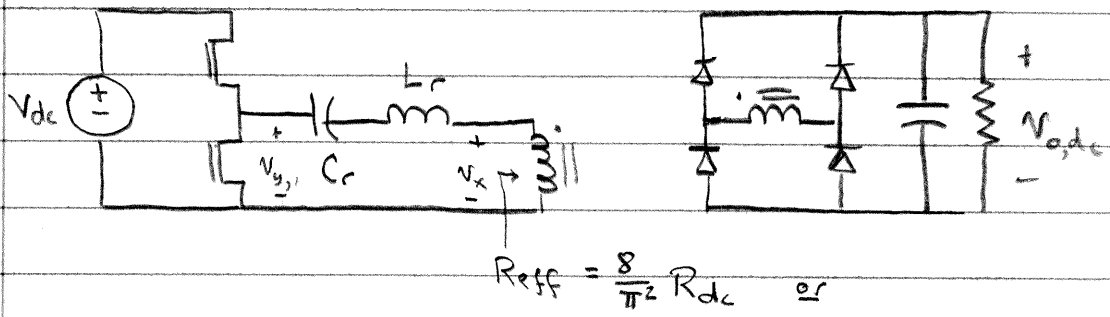Consider a "series resonant" dc-dc converter




- Operate above $\omega_0 = \frac{1}{L_r C_r}$ to get ZVS soft switching
- This works for a "dc gain" such that $|V_{x1}| \leq |V_{gs1}|$
 - ⇒ we can change inverter +/or rectifier topology (full-bridge, half-bridge) to adjust the gain, as well as xformer turns ratio
 - ⇒ For very "light" loads (R_{dc} big) tank selectivity/frequency range becomes a problem.
- can "burst" converter on and off $\Rightarrow R_{eff} = \frac{8}{\pi^2} \frac{V_o^2}{P_{on}}$ power when burst "on"
- Can use a different tank structure, such as parallel, LCC, LLC


• we often pick a tank that meets requirements of an application + or absorbs parasitics in a useful way (e.g. "series-parallel"/LCC or PFC can be used when a high-voltage secondary yields high xformer capacitance +/or rectifier capacitance)

parallel resonant converter

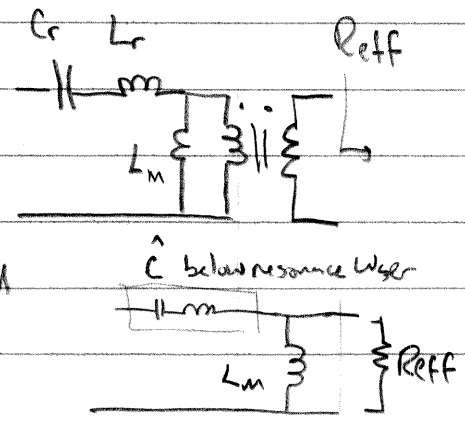
- by gapping the xformer, we can get an "LLC" design
 - above $\omega_{ser} = \frac{1}{\sqrt{L_r C_r}}$ we get behavior a bit like a series-resonant converter, but L_m helps at low power + provides inductive ZVS current
 - below ω_{ser} we can still be inductively loaded and get additional voltage gain by resonance between \hat{C} and L_m "matching" over some range



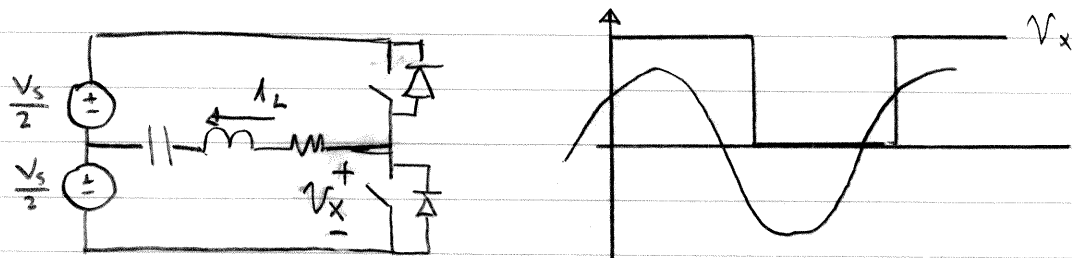We can also operate below resonance in some designs for ZCS, e.g.





Since $i_L \rightarrow 0$

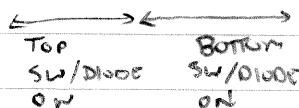

Since $i_L > 0$ before top switch turns on, bottom diode conducts + bottom switch off @ ZCS. Same w/ top switch

A variation of this trick uses multiple resonances to provide ZCS turn on for the switches also. Good for thyristors

MAPHAM INVERTER

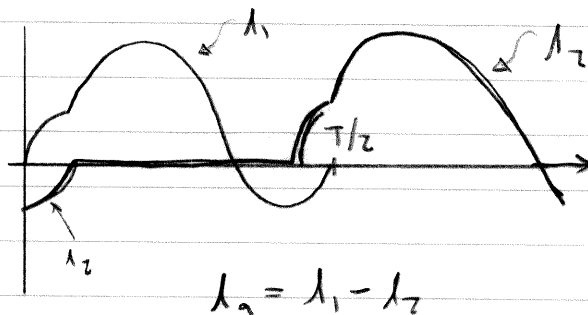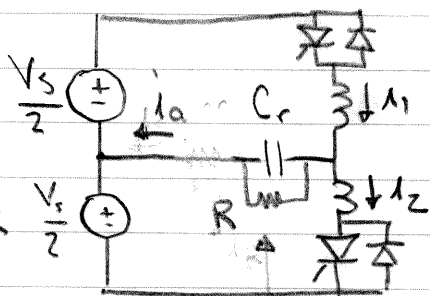

$$i_a = i_1 - i_2$$

- DISTORTED SINE WAVE
- re-position R so in parallel w/ C :
- V_c filters, so i_R is sinusoidal

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>