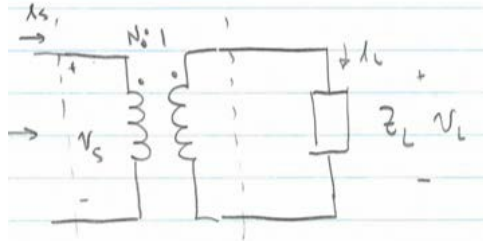


Lecture 37 - Resonant Converters: Matching Networks

1 Matching Networks

In power conversion we often want to scale voltage and current to “match” a load network to a source.

One way to change a load impedance value is with a transformer




Voltage steps up by N
 Current steps down by N
 ⇒ Impedance $\frac{V}{I}$ by N^2 !

$Z_{in} = N^2 Z_L \rightarrow$

If we are concerned with sinusoidal waveforms over a narrow frequency range (as in resonant converters, RF communications, etc.), we can use a reactive matching network to effect impedance transformation.

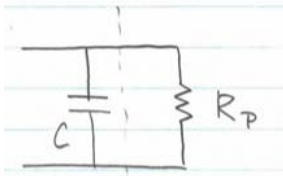Simple example: Suppose we have a known load R_p , and want to transform it to appear as a smaller resistor R_s . At a single frequency ω , we can do this with an LC tank.




Place a capacitor in parallel with R_p

$Z_{eq1} \rightarrow$

$$Z_{eq1} = \frac{R_p / j\omega C}{R_p + 1/j\omega C} = \frac{R_p}{1 + j\omega R_p C} \frac{1 - j\omega R_p C}{1 - j\omega R_p C}$$

$$= \frac{R_p}{1 + (\omega R_p C)^2} - j \frac{\omega R_p^2 C}{1 + (\omega R_p C)^2}$$

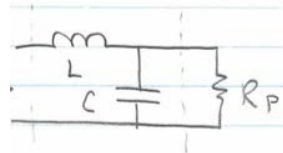Now add an inductance in series to eliminate reactive term:



This is called an “L-section” matching network


$Z_{eq,2} \rightarrow$

$$Z_{eq,2} = \frac{R_p}{1 + (\omega R_p C)^2} + j[\omega L - \frac{\omega R_p^2 C}{1 + (\omega R_p C)^2}]$$

- ∴ By picking C , we can make $\text{Re}\{Z_{eq,2}\} = R_s @ \omega$ (desired value).
- Picking L , we can make $\text{Im}\{Z_{eq,2}\} = 0 @ \omega$ (desired value).
- We effectively transform R_p into an apparent resistance R_s at a single frequency ω .

- This is achieved through the action of the resonant tank L, C .
- Must know R_p, ω in design. Practical transformations are limited by \rightarrow achievable component values, parasitics/losses.

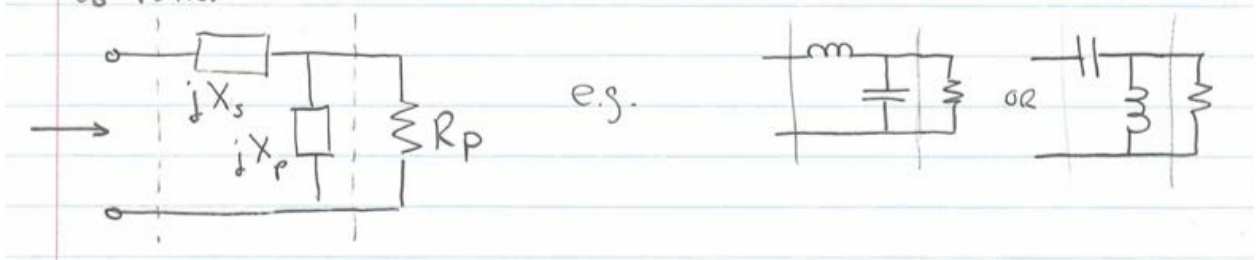
In general, to “step down” resistances, we need two reactances jX_P and jX_S which have opposite signs, configured as follows:



We may choose how to implement the reactances based on (e.g.)

- How dc, harmonic frequencies, etc. are transformed
- how convenient (or reasonable) the values are
- To “absorb” one or both reactances into the circuitry

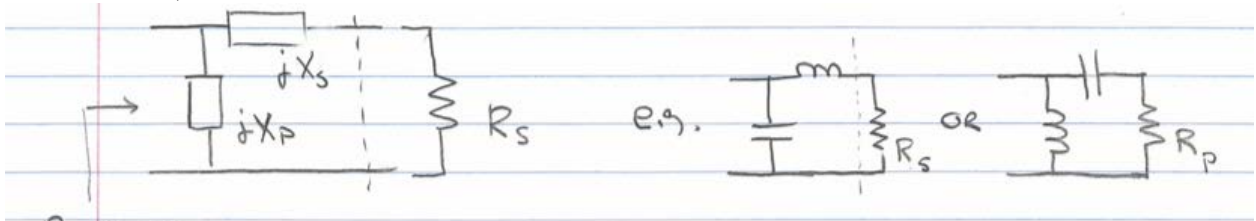To “step up” R_s to a higher value R_p , we can use the same resonant network “backwards”. Again, we need reactances w/ opposite signs:




$R_p \ll \omega$ These networks work in both directions: RF use

These networks work in both directions: If we transform down from R_p to R_s in one direction, we transform up from R_s to R_p in the other direction!

Easy ways to identify values: If we want to “reduce” an apparent resistance, place a reactance in parallel with it. To increase, place a reactance in series with it.

Lets look at the values we get in our original example:
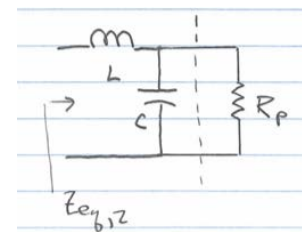
$$Z_{eq,2} = \frac{R_p}{1 + (\omega R_p C)^2} + j[\omega L - \frac{\omega R_p^2 C}{1 + (\omega R_p C)^2}]$$



To achieve $Z_{eq,2} = R_s$, we require:

$$R_s = \frac{R_p}{1 + (\omega R_p C)^2} \Rightarrow \omega R_p C = \sqrt{\frac{R_p}{R_s} - 1}$$

and

$$\omega L = \omega R_p C \frac{R_p}{1 + (\omega R_p C)^2} = R_s \sqrt{\frac{R_p}{R_s} - 1}$$


$$\text{or } \boxed{\frac{\omega L}{R_s} = \sqrt{\frac{R_p}{R_s} - 1}}$$

Defining a “transformation Q” Q_T

$$Q_t \triangleq \sqrt{\frac{R_p}{R_s} - 1}$$

We need for matching:
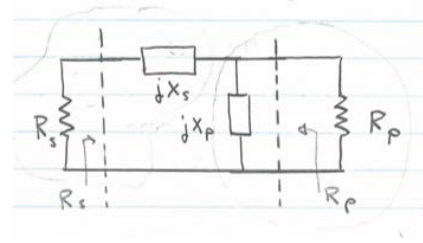
$$\frac{X_s}{R_s} = \frac{R_p}{X_p} = Q_T$$




Result only: shown in handout \rightarrow


If we implement one element as an inductor (quality factor $Q_L = \frac{\omega L}{R_{L,ESR}}$) and one element as a capacitor (quality factor $Q_C = \frac{1}{\omega C R_{C,ESR}}$), we get a matching network efficiency,

$$\boxed{\eta \approx 1 - \frac{Q_T}{Q_L} - \frac{Q_T}{Q_C}}$$

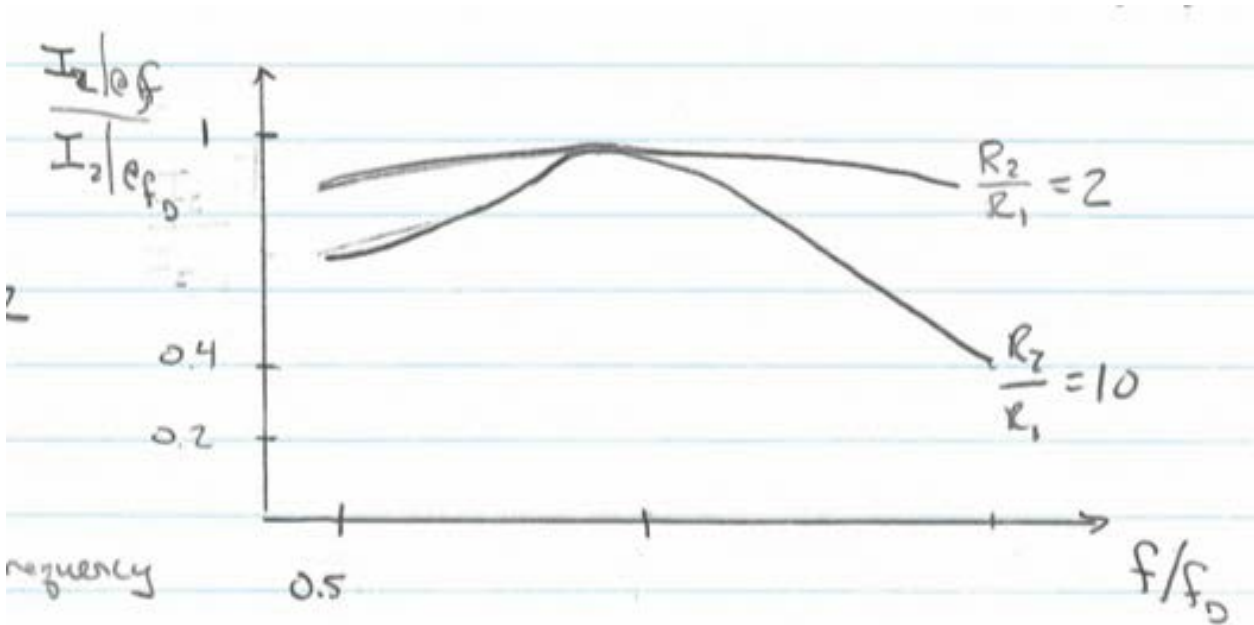- The larger the transformation ratio, the lower the efficiency!
- Note: The larger the transformation ratio we want, the more narrowband the transformation becomes (high Q).




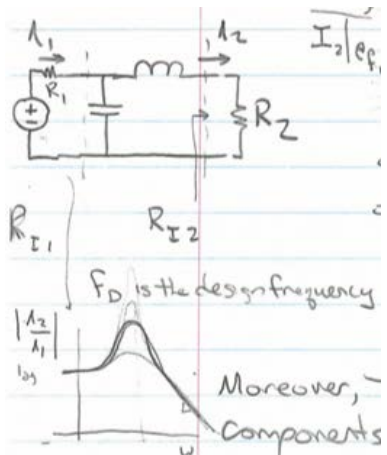See Everitt + Anner “Communication Engineering” 3rd Edition p. 412




Moreover, the transformation requires increasingly high Q components to remain efficient.

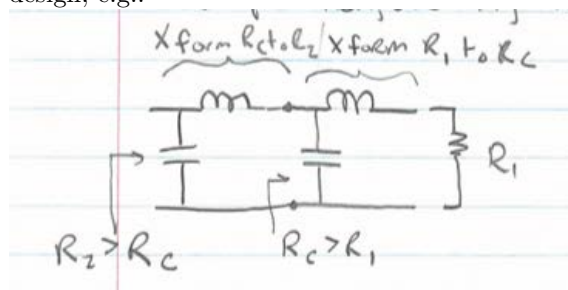For limited available size +Q of components or for wider-band operation, we may choose a multi-stage design, e.g.:




e.g., select $R_c = \sqrt{R_1 R_2}$

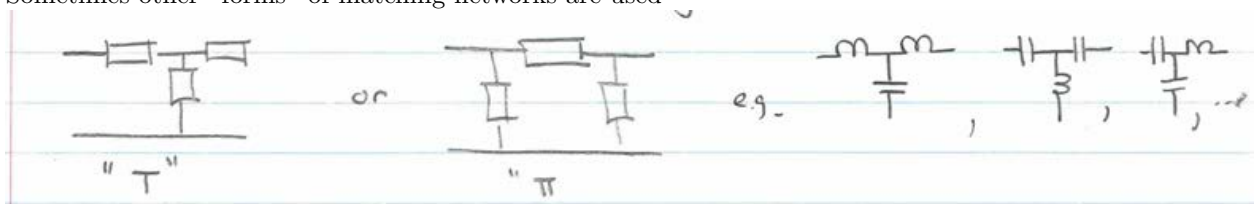Sometimes other "forms" of matching networks are used



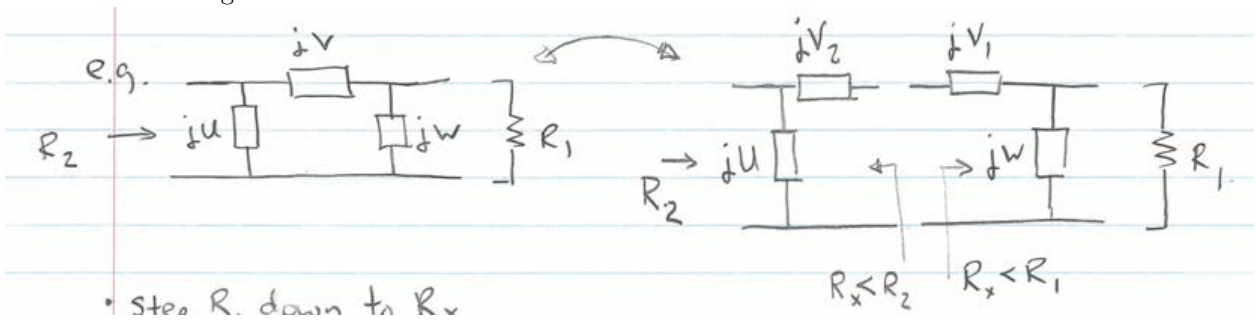These can be thought of as "back-to-back" L-section networks




- Step R_1 down to R_x
- Step R_x up to R_2

⇒ L-section networks are broader-band and more efficient than T or Π networks, but are fully determined by the required transformation ratio and frequency.

⇒ T + Π sections allow an additional degree of freedom (R_x), which can be used to:

- provide narrower bandwidth (selectable),
- use more desirable component values,
- control phase shift of waveforms at input and output.

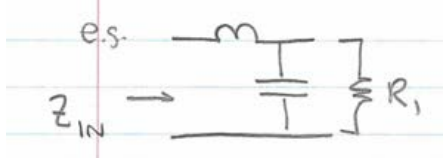It is also useful to note how variations affect our designs



$$Re\{Z_{in}\} = \frac{R_1}{1 + \omega^2 R_1^2 C} = R_2$$

As $R_1 \uparrow, R_2 \downarrow$ and vice versa “inversion”!

T and Π networks double invert, so as $R_1 \uparrow, R_2 \uparrow$ also

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>