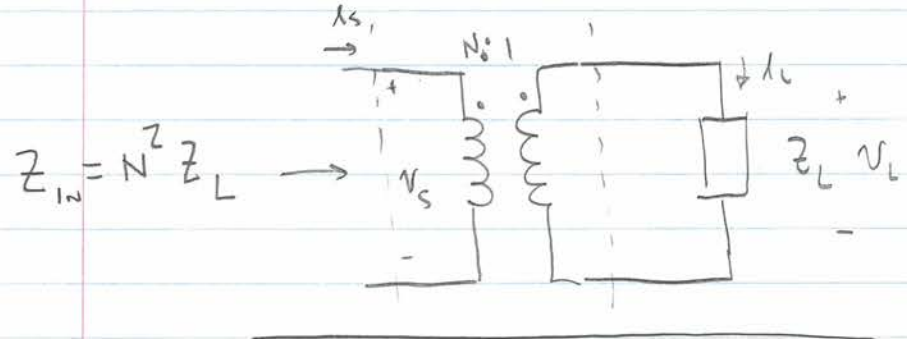


Matching Networks: In power conversion we often want to scale voltage + current to "match" a load network to a source


One way to change a load impedance value is with a transformer



Voltage steps up by  $N$   
current steps down by  $N$   
 $\Rightarrow$  Impedance  $\frac{V}{I}$  by  $N^2!$

If we are concerned with sinusoidal waveforms over a narrow frequency range (as in resonant converters, RF communications, etc.) we can use a reactive matching network to effect impedance transformation

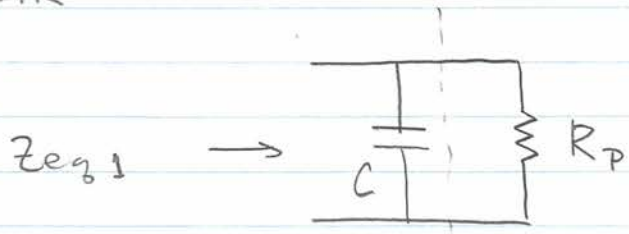Simple example: Suppose we have a known load  $R_p$ , and want to transform it to appear as a smaller resistor  $R_s$ . At a single frequency  $\omega$ . We can do this with an LC tank




Place a capacitor in parallel with  $R_p$

$$Z_{eq1} = \frac{R_p / j\omega C}{R_p + 1/j\omega C} = \frac{R_p}{1 + j\omega R_p C} \left( \frac{1 - j\omega R_p C}{1 - j\omega R_p C} \right)$$

$$= \frac{R_p}{1 + (\omega R_p C)^2} - j \frac{\omega R_p^2 C}{1 + (\omega R_p C)^2}$$
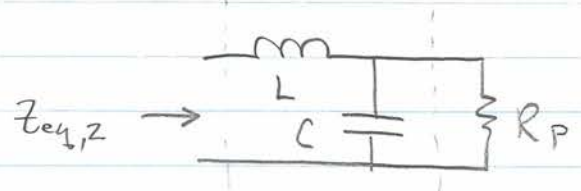
# 6.334 Lecture Resonant Converters: Matching Networks

Now add an inductance in series to eliminate reactive term:



This is called an "L-section" matching network

$$Z_{eq,2} = \frac{R_P}{1 + (\omega R_P C)^2} + j \left[ \omega L - \frac{\omega R_P^2 C}{1 + (\omega R_P C)^2} \right]$$

- ∴ By Picking C we can make  $Re\{Z_{eq,2}\} = R_S @ \omega$  (desired value)
- Picking L we can make  $Im\{Z_{eq,2}\} = 0 @ \omega$  (desired value)


- we effectively transform  $R_P$  into an apparent resistance  $R_S$  at a single frequency  $\omega$
- This is achieved through the action of the resonant tank L, C
- Must know  $R_P, \omega$  in design. Practical transformations limited by → achievable component values, parasitics/losses

In general, to "step down" resistances, we need two reactances  $jX_p$  and  $jX_s$  which have opposite signs, configured as follows:



- We may choose how to implement the reactances based on (e.g.)
- How dc, harmonic frequencies, etc. are transformed
  - how convenient (or reasonable) the values are
  - to "absorb" one or both reactances into other circuitry

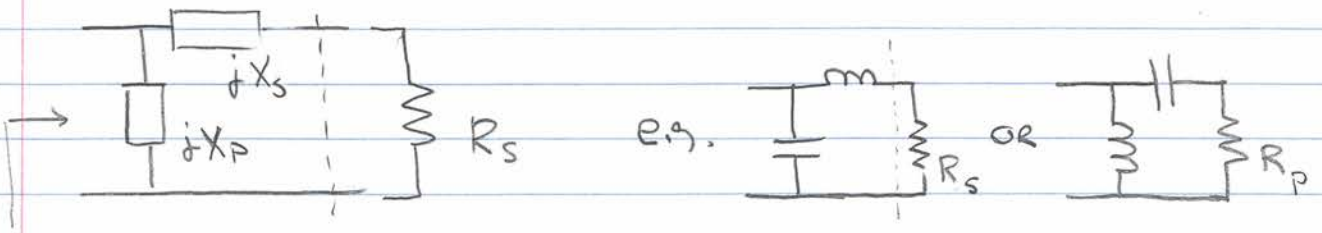To "step up"  $R_s$  to a higher value  $R_p$ , we can use the same resonant network "backwards".  
 Again, we need reactances w/ opposite signs:




$R_p @ \omega$  These networks work in both directions: If we transform down from  $R_p$  to  $R_s$  in one direction, we transform up from  $R_s$  to  $R_p$  in the other direction!

Easy ways to identify values: If we want to "reduce" an apparent resistance, place a reactance in parallel with it. To increase, place a reactance in series with it.

Lets look at the values we get in our original example:
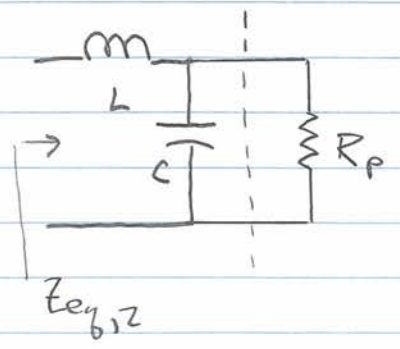
$$Z_{eq,2} = \frac{R_p}{1 + (\omega R_p C)^2} + j \left[ \omega L - \frac{\omega R_p^2 C}{1 + (\omega R_p C)^2} \right]$$



To achieve  $Z_{eq,2} = R_s$ , we require:

$$R_s = \frac{R_p}{1 + (\omega R_p C)^2} \Rightarrow \omega R_p C = \sqrt{\frac{R_p}{R_s} - 1}$$

and


$$\omega L = \omega R_p C \frac{R_p}{1 + (\omega R_p C)^2} = \sqrt{\frac{R_p}{R_s} - 1} R_s$$

OR 
$$\frac{\omega L}{R_s} = \sqrt{\frac{R_p}{R_s} - 1}$$



Defining a "Transformation Q"  $Q_T$
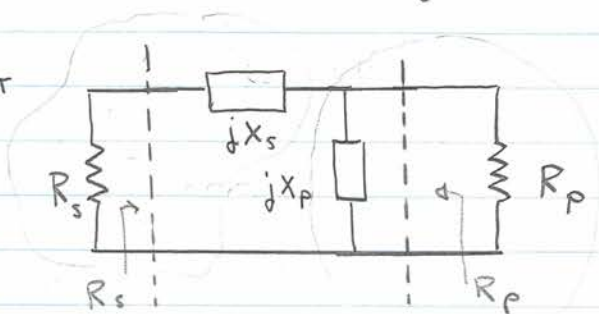
$$Q_T \triangleq \sqrt{\frac{R_P}{R_S} - 1}$$



we need for matching:

$$\frac{X_s}{R_s} = \frac{R_p}{X_p} = Q_T$$



If we implement one element as an inductor (quality factor  $Q_L = \frac{\omega L}{R_{L,ESR}}$ ) and one element as a capacitor (quality factor  $Q_C = \frac{1}{\omega C R_{C,ESR}}$ )

we get a matching network efficiency:  $\eta \approx 1 - \frac{Q_T}{Q_L} - \frac{Q_T}{Q_C}$


\* The larger the transformation ratio, the lower the efficiency!

Also \* Note: the larger the transformation ratio we want, the more narrowband the transformation becomes (high Q)

Result Only:  
Shown in handout

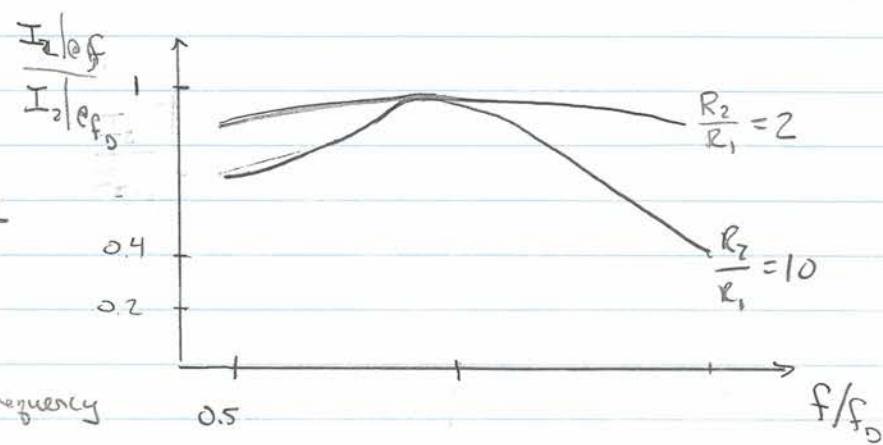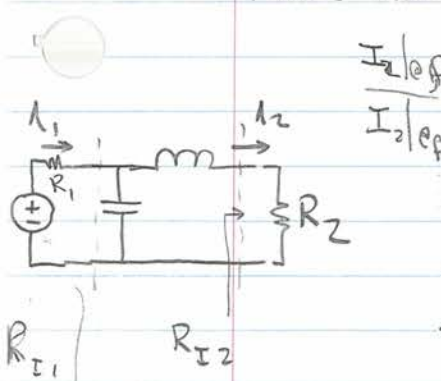

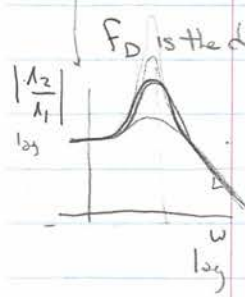
See  
Everitt+Anner  
"Communication  
Engineering" 3<sup>rd</sup> Ed  
P. 412



Moreover, the transformation requires increasingly high Q components to remain efficient.

For limited available size + Q of components, or for wider-band operation, we may choose a multi-stage design, e.g.:

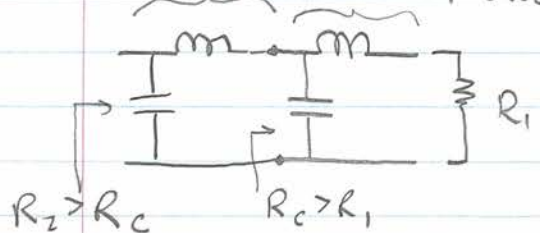Xform  $R_2$  to  $R_c$  / Xform  $R_1$  to  $R_c$




e.g., select  $R_c = \sqrt{R_1 R_2}$

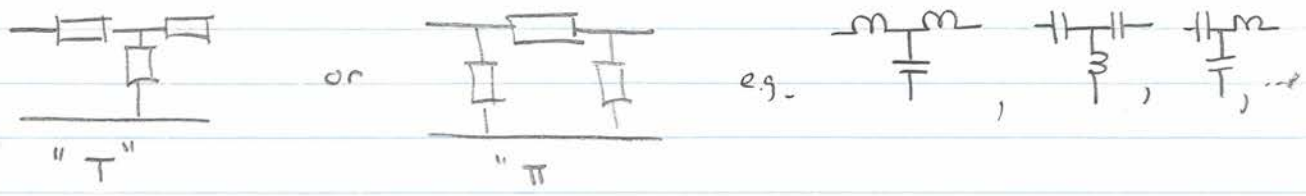
6.334 Lecture

Resonant Converters: Matching Networks

Sometimes other "forms" of matching networks are used



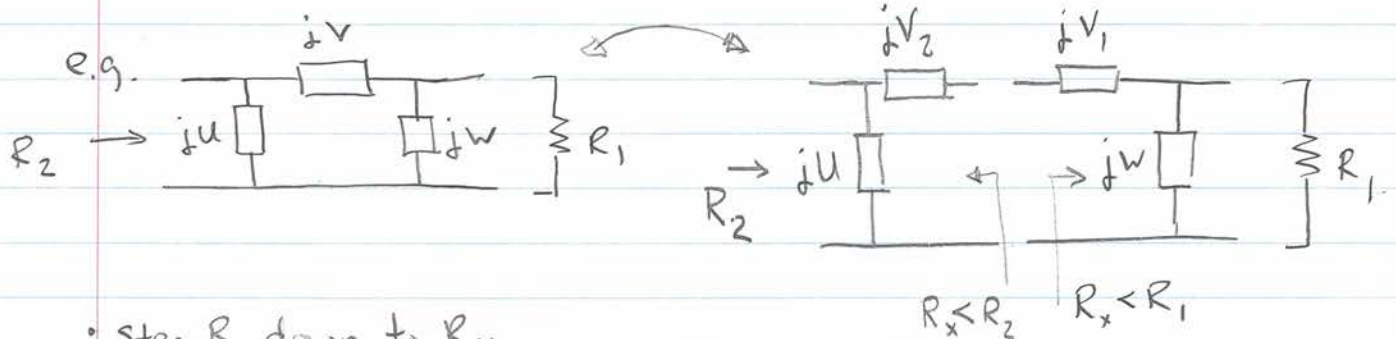These can be thought of as "back-to-back" L-section networks




- Step  $R_1$  down to  $R_x$
- Step  $R_x$  up to  $R_2$

⇒ L-section networks are broader-band and more efficient than T or Pi networks, but are fully determined by the required transformation ratio + frequency

⇒ T + Pi sections allow an additional degree of freedom ( $R_x$ ) which can be used to

- provide narrower bandwidths (selectable)
- use more desirable component values
- control phase shift of waveforms at input + output

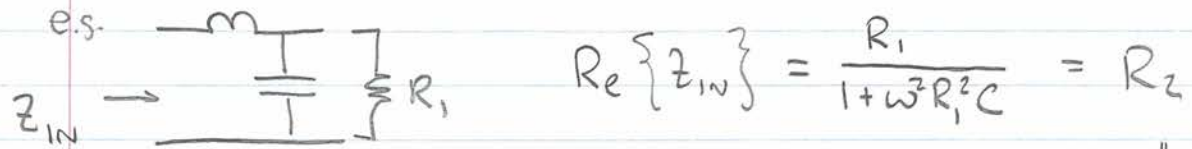It is also useful to note how variations affect our designs



- as  $R_1 \uparrow$   $R_2 \downarrow$  and vice versa "inversion"!
- T + Pi networks double invert, so as  $R_1 \uparrow$ ,  $R_2 \uparrow$  also

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>