

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Electrical Engineering and Computer Science**

6.622 Power Electronics

Issued: April 10, 2023

Problem Set 8

Due: April 19, 2023


Reading: KPVs Chapter 12 through 12.4; KPVs Chapter 13 through 13.1, 13.3

---

**Problem 8.1**

Fig. 1 shows a dc/dc converter. Assume that the converter operates in continuous conduction mode (CCM).

- a. Assuming that the converter is operating in periodic steady state (PSS), find an expression for the dc capacitor voltage  $V_C$  in terms of dc input voltage  $V_1$  and fixed switch duty ratio  $D$ .
- b. Derive the average state-space equations for this converter under duty ratio control. You can use either state space averaging or direct circuit averaging, but express your results as a pair of state-space equations in terms of the local averages of state variables  $i_L$  and  $v_C$  and local averages of inputs  $v_1$  and  $q$ . (The local average of  $q$  is denoted as  $d$ .) You may assume that  $i_L$  and  $v_C$  have small ripple and are slowly varying.
- c. Draw an averaged circuit model for this system. (i.e., draw a circuit that has the same state-space equations as the averaged model of the original system.)
- d. Is the averaged system linear (with respect to the state variables and inputs  $V_1$  and  $d$ )? Justify your answer in three sentences or less.

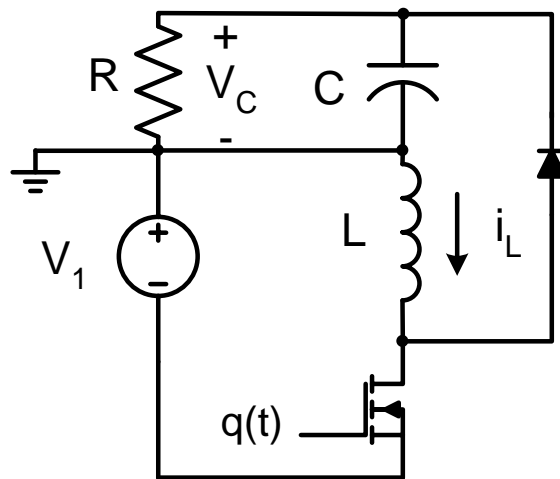

**Figure 1** A dc/dc converter.

### Problem 8.2

Following the approach of KPVS example 12.5, derive the averaged model for a boost converter operating in *discontinuous* conduction mode. Another reference for this approach is P.R.K. Chetty, "Current Injected Equivalent Circuit Approach to Modeling of DC-DC Converters in Discontinuous Inductor Conduction Mode," *IEEE Transactions on Industrial Electronics* **29:230-234**, August, 1982.

### Problem 8.3

Derive the averaged, linearized model for a buck converter in continuous conduction mode. Do this both by direct circuit averaging and state-space averaging. (You must show both the averaged circuit and the averaged state-space description of the system.) Show that the state-space averaged model and the averaged circuit model are equivalent descriptions of the system.

Linearize the state-space averaged model about an operating point (if it is not already linear) and derive the transfer function from perturbation in duty ratio to perturbation in output voltage.

Find the *audio susceptibility* for the buck converter. The audio susceptibility is defined as the transfer function from perturbation of the input voltage to perturbation of the output voltage with duty ratio held constant.

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>