

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

6.622 Power Electronics

Issued: April 19, 2023

Problem Set 9

Due: April 24, 2023

Reading: KPVS Chapter 12 through 12.4; KPVS Chapter 13 through 13.1, 13.3

Note: *Work on the design project!*

Problem 9.1

Consider a continuous conduction mode buck converter to be operated under peak current mode control. The converter parameters are $f_{sw} = 500$ kHz, $L = 6.8$ μ H, $C = 800$ μ F, and $V_{out,ref} = 10$ V. What is the smallest magnitude of compensating ramp that will yield stable dynamics for the ripple instability over an input voltage range of 15 V $< V_{in} < 30$ V?

Note: Models for computing the ripple dynamics will be discussed in class. They can also be found in: H. Hsu, A. Brown, L. Rensink, and R.D. Middlebrook, "Modeling and Analysis of Switching dc-to-dc Converters in Constant-Frequency Current-Programmed Mode," 1979 IEEE Power Electronics Specialists Conference, pp. 284-301, and in R.W. Erickson, Fundamentals of Power Electronics, Boston: Kluwer, 1997, Chapter 11 (Current Programmed Control).

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>