

6.6220 HW9 Solutions*

9.1 Compensating Ramp in Peak Current Control

First, we derive the inductor current change rates ($M_1, -M_2$) for the buck converter.

When the switch is on for DT ,

$$M_1 = \frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

and when the switch is off for $(1-D)T$

$$-M_2 = \frac{di_L}{dt} = \frac{-V_{out}}{L}$$

and for a continuous conduction mode buck converter, $D = \frac{V_{out}}{V_{in}}$.

The inductor current waveform in peak current mode control is shown in Fig. 1, where if the initial current difference for the n th period is ΔI_n , with the compensating ramp, the current difference at the start of the $(n+1)$ th period will be ΔI_{n+1} . From geometric relationships, we have

$$\frac{\Delta I_{n+1}}{\Delta I_n} = -\frac{M_2 - M_c}{M_1 + M_c}$$

where M_1 , M_2 and M_c are all defined to be positive. Hence to achieve ripple stability (no sub-harmonic oscillations), we need

$$\begin{aligned} -\frac{M_2 - M_c}{M_1 + M_c} &< 1 \\ \implies M_c &> \frac{M_2 - M_1}{2} = \frac{2V_{out} - V_{in}}{2L} \end{aligned}$$

Since V_{out} is regulated at $V_{out,ref} = 10\text{ V}$ and V_{in} is in the range of 15 V to 30 V , the smallest M_c that can guarantee stable ripple dynamics occurs across the entire input voltage range is when $V_{in} = 15\text{ V}$. Plugging in numbers, we have

$$M_c > \frac{2 * 10\text{ V} - 15\text{ V}}{2 * 6.8\ \mu\text{H}} = 368\text{ kA/s}$$

Note that the equations imply that if $V_{in} > 2V_{out}$ for a CCM buck converter, then ripple stability is guaranteed and no compensating ramp is needed. The condition, of course, would vary with input voltage specs and circuit topologies.

*Khandoker Nuzhat Rafa Islam 2023, adapted from Yang 2022

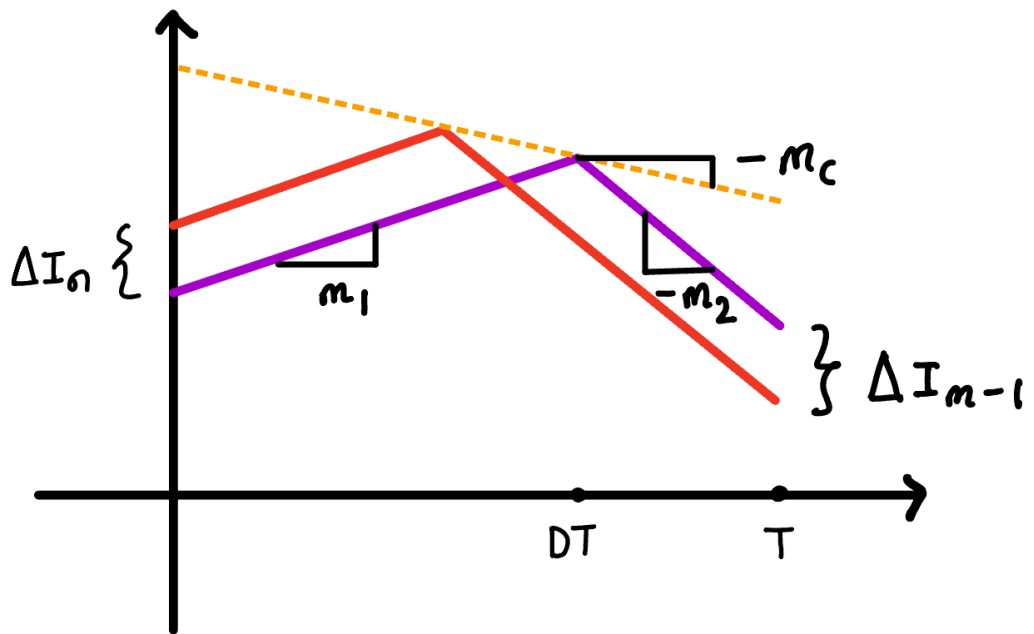


Figure 1: Current Waveforms with Peak Current Mode Control

MIT OpenCourseWare
<https://ocw.mit.edu>

6.622 Power Electronics
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>