

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Electrical Engineering and Computer Science**

6.622 Power Electronics

Issued: May 1, 2023

Problem Set 11

Due: May 8, 2023

---

Reading: KPVS Chapter 6 through Section 6.4; KPVS Section 24.6

Note: *Work on the design project!*

---

**Problem 11.1** KPVS Problem 6.1

**Problem 11.2** KPVS Problem 6.3

**Problem 11.3**

Figure 1 shows the topology, circuit states and operating waveforms of a ZVS resonant transition boost converter that is suitable for use at high- and very-high frequencies. For purposes of this problem, you may ignore device drops and component nonidealities. Please find the range of output voltages  $V_2$  that will guarantee zero-voltage turn on of the MOSFET. That is, find the range of output voltages for which the MOSFET drain voltage ( $v_{\text{drain}} = v_{C1}$ ) will ring down to zero in state 4, as illustrated. State your answer in terms of the input voltage  $V_1$ . *You must provide either a derivation or justification for your answer.*

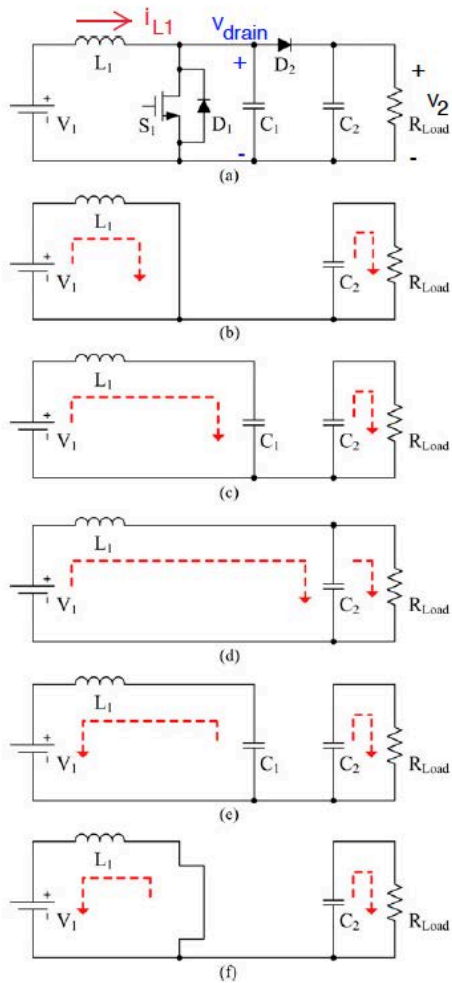


Fig. 2. Proposed VHF resonant boost converter: (a) circuit topology, (b) state 1, (c) state 2, (d) state 3, (e) state 4, and (f) state 5.

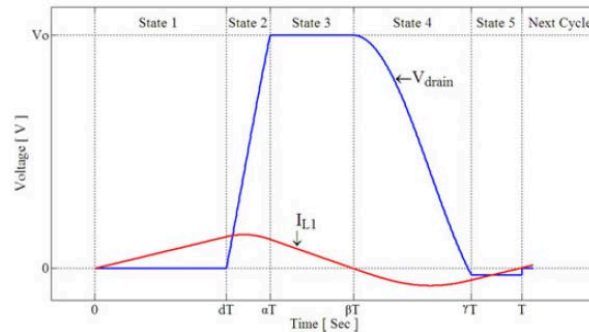


Fig. 3. Drain voltage and inductor current waveforms.

© IEEE. All rights reserved. This content is excluded from our Creative Commons license. For more information, see <https://ocw.mit.edu/help/faq-fair-use/>

**Figure 1** A ZVS resonant-transition boost converter and its operating waveforms. This converter topology is suitable for operation at very high frequencies. Figures adopted from Shamsi, et. al. “Design and Development of Very High Frequency Resonant Boost Converters,” *IEEE Transactions on Power Electronics*, Vol. 27, No. 8, Aug. 2012.

MIT OpenCourseWare  
<https://ocw.mit.edu>

6.622 Power Electronics  
Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>