

# 8.022 (E&M) – Lecture 9

## Topics:


- RC circuits
- Thevenin's theorem

## Last time

- Electromotive force:
  - How does a battery work and its internal resistance
- How to solve simple circuits:
  - Kirchhoff's first rule: at any node, sum of the currents in = sum of the currents out (conservation of charge at nodes)
  - Kirchhoff's second rule: around any closed loops, the sum of EMF and potential drops is 0 (electrostatic field is conservative)
- Power dissipated by a resistor:  $P = VI = RI^2$
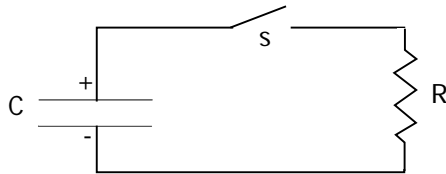
## Capacitors in circuits

- A new way of looking at problems:
  - Until now: charges at rest or constant currents
  - When capacitors present: currents vary over time



- Consider the following situation:
  - A capacitor C with charge  $Q_0 \rightarrow V_0 = Q_0/C$
  - A resistor R in series connected by switch s
- What happens when switch s is closed?


G. Sciolla – MIT

8.022 – Lecture 9

3
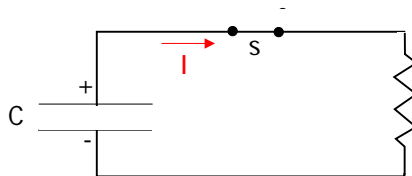
## Discharging capacitors: qualitative

- Before switch s is closed:
  - Difference in potential between C plates:  $V_0$
  - No current circulating in the circuit (open)



- After switch s is closed:
  - Difference in potential between capacitor plates will induce current I
  - As I flows, charge difference on capacitor decreases  $\rightarrow V_C$  decreases  $\rightarrow I$  decreases over time

G. Sciolla – MIT

8.022 – Lecture 9

4

## Discharging capacitors: quantitative

- Apply second Kirchhoff's law:
  - EMF supplied by capacitor C:  $V=Q/C$ 
    - NB: this is true at any moment in time  $\rightarrow Q(t) \rightarrow V(t)$
  - Voltage drop on the resistor:  $-IR$

$$\frac{Q}{C} - IR = 0$$

- Not useful in this form since  $I=I(Q)$ 
  - $I=-dQ/dt$  (- sign because C is losing charge)

$$\frac{Q}{C} + \frac{dQ}{dt} R = 0$$

- Easy integral yields to exponential decay of the charge:

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

## How to integrate RC circuits

To solve  $\frac{Q}{C} + \frac{dQ}{dt} R = 0$ , rewrite as:  $\frac{dQ}{Q} = -\frac{dt}{RC}$

Integrate both sides:

$$\int_{Q_0}^{Q(t)} \frac{dQ}{Q} = -\int_0^t \frac{dt}{RC}$$

$$\ln \frac{Q(t)}{Q_0} = -\frac{t}{RC}$$

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

NB:  $\tau=RC$  is called "decay constant" of the circuit

## Solution of RC circuit

- Solution:  $Q(t) = Q_0 e^{-\frac{t}{RC}}$ 
  - Exponential decay of charge stored in capacitor
  - $\tau = RC$  is called "decay constant" of the circuit
  - After a time  $RC$ , the charge decreased by  $1/e$  w.r.t. original value
  - Units of  $RC$ :
    - cgs:  $[R] = \text{statvolt s /esu}$ ;  $[C] = \text{esu/statvolt} \rightarrow [RC] = \text{s}$
    - SI:  $[R] = \text{V/A}$ ;  $[C] = \text{C/V}$ ;  $\text{A} = \text{C/s} \rightarrow [RC] = \text{s}$
- Derive the current:
$$I(t) = -\frac{dQ}{dt} = -Q_0 \frac{d}{dt} \left( e^{-\frac{t}{RC}} \right) = \frac{Q_0}{RC} e^{-\frac{t}{RC}}$$
  - Same exponential decay as for  $Q(t)$


G. Sciolla – MIT

8.022 – Lecture 9

7
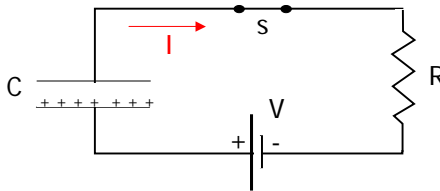
## Charging capacitors

- Now 3 elements in circuit: EMF, capacitor and resistor
  - Capacitor starts uncharged




- What happens when switch  $s$  is closed?
  - When  $s$  is closed, current will suddenly flow and  $C$  will charge
  - As  $C$  charges,  $E$  opposite to EMF builds up and slows down current
  - $I(t)$  stops when  $V_c$  reaches  $V$

G. Sciolla – MIT

8.022 – Lecture 9

8

## Charging capacitor: solve the circuit

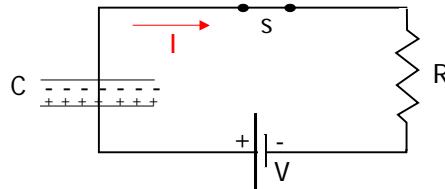

- Solve using Kirchoff's second law:  $V - \frac{Q}{C} - IR = 0$ 
  - $I(t) = +dQ/dt$
  - NB: + because the capacitor is now charging!
- First order differential equation  $\frac{dQ}{dt}R + \frac{Q}{C} - V = 0$
- Solution:  $Q(t) = CV \left( 1 - e^{-\frac{t}{RC}} \right)$

G. Sciolla – MIT

8.022 – Lecture 9

9

## Details of integration

To solve  $\frac{dQ}{dt}R + \frac{Q}{C} - V = 0$ , rewrite as:  $\frac{dQ}{dt} = -\frac{(Q - CV)}{RC}$

Setting:  $Q' = Q - CV$

$$\Rightarrow \frac{dQ'}{Q'} = -\frac{dt}{RC}$$

Integrating between  $t=0$  and  $t$ :

$$\int_{Q=0}^{Q=Q(t)} \frac{dQ'}{Q'} = -\int_{t=0}^{t=t} \frac{dt}{RC} \Rightarrow \ln \frac{Q(t) - CV}{-CV} = -\frac{t}{RC} \Rightarrow \frac{Q(t) - CV}{CV} = -e^{-\frac{t}{RC}}$$


$$Q(t) = CV \left( 1 - e^{-\frac{t}{RC}} \right)$$

G. Sciolla – MIT


8.022 – Lecture 9

10


## Graphical solution

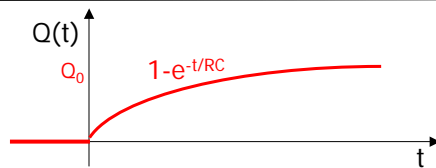
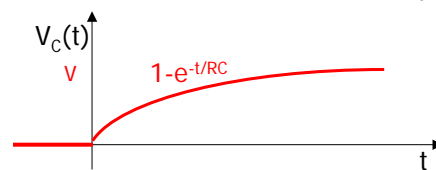
$$Q(t) = CV \left( 1 - e^{-\frac{t}{RC}} \right)$$


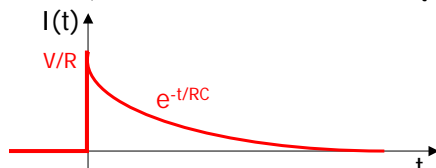
$$V_c(t) = Q(t) / C = V \left( 1 - e^{-\frac{t}{RC}} \right)$$



$$I(t) = \frac{dQ(t)}{dt} = \frac{V}{R} e^{-\frac{t}{RC}}$$

G. Sciolla – MIT

8.022 – Lecture 9

11

## Important comments

- Solution of RC circuit:  $V_c(t) = V \left( 1 - e^{-\frac{t}{RC}} \right)$ ;  $I(t) = \frac{V}{R} e^{-\frac{t}{RC}}$

- Are Kirchhoff's laws valid at any moment in time?

$$V - \frac{Q}{C} - IR = V - V \left( 1 - e^{-\frac{t}{RC}} \right) - R \frac{V}{R} e^{-\frac{t}{RC}} = 0 \quad \text{OK!}$$

- Asymptotic behavior of the capacitor:

- At  $t=0$ :  $I=V/R$  as if  $C$  were a short circuit
- At  $t=\infty$ ,  $I=0$  as if  $C$  were an open circuit

- Conclusion: no need to solve the differential equation!

- Solution is an exponential with time constant  $RC$
- Asymptotic behavior of  $C$  gives initial/final values for  $V(t)$  and  $I(t)$

G. Sciolla – MIT

8.022 – Lecture 9

12



## Time constant of RC circuit (E9)

- Simple RC circuit with

- $V_{EMF} = 3\text{ V}$
- $C = 1.3\text{ F}$
- $R = 11.7\ \Omega$

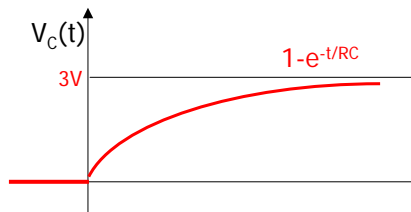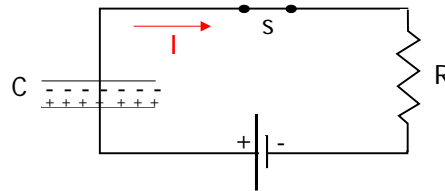- Questions:

- What are  $V_C$  and  $I$ ?
- Verify that time constant is  $RC$



$$V_C(t) = V_{EMF} \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$RC = 15.2\text{ s}$$

If formula is correct  $\Rightarrow$

$$V_C = V_{EMF}(1 - 1/e) = 1.9\text{ V} \text{ when } t = 15.2$$

G. Sciolla – MIT

8.022 – Lecture 9

13




## Verify time constant (E8)

- RC circuit with

- $V_{EMF} =$  squared 5 V pulses
- Variable  $C$  initially =  $0.3\ \mu\text{F}$
- Variable  $R_2$  initially =  $400\ \Omega$
- $R_1 = 100\ \Omega$

- Display on scope  $V_C$  and  $I(R_1)$

- Verify that time constant is  $RC$

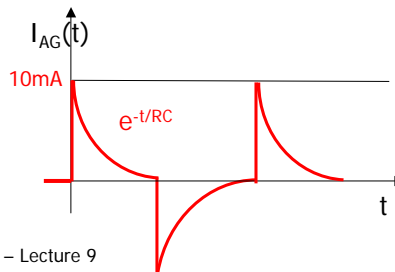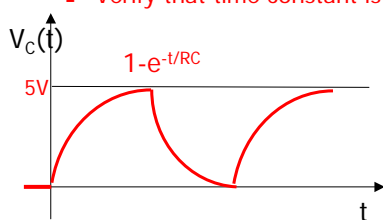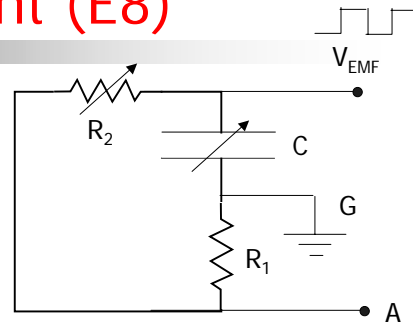


G. Sciolla – MIT

8.022 – Lecture 9

14
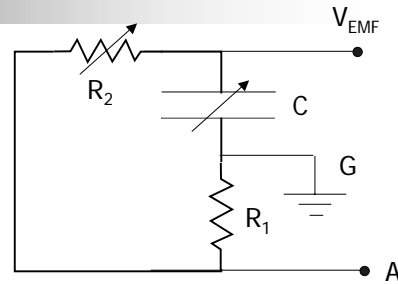
## Verify time constant (E8)

- RC circuit with
  - $V_{EMF}$  = squared 5 V pulses
  - Variable C initially =  $0.3 \mu\text{F}$
  - Variable  $R_2$  initially =  $400 \Omega$
  - $R_1 = 100 \Omega$




Assuming  $\tau = RC \dots$

- What happens when we double C?
  - $\tau_1 = RC' = 2RC = 2\tau_0 \rightarrow V(I_{AG})$  raises (falls) twice as fast
- How should we change  $R_2$  to have the same effect?
  - $R' = 2R = 2(R_1 + R_2) \rightarrow R_2': 400 \rightarrow 900 \Omega$
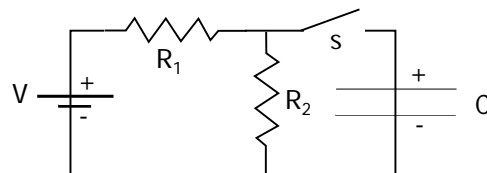
## More complicated RC circuits

- What if the RC circuit is more than just a series of R and C?
- Consider the following circuit:



- Calculate  $Q(t)$  on the capacitor
- Solution:
  - Kirckhoff's laws will solve it: TEDIOUS!
  - Use Thevenin's Theorem




# Thevenin equivalence

## Thevenin's theorem:

Any combination of resistors and EMFs with 2 terminals can be replaced with a series of a battery  $V_{OC}$  and a resistor  $R_T$  where

- $V_{OC}$  is the open circuit voltage
- $R_T = V_{OC}/I_{short}$  where  $I_{short}$  is the current going through the shorted terminals or  $R_T = R_{eq}$  with all the EMF shorted

### In our case:

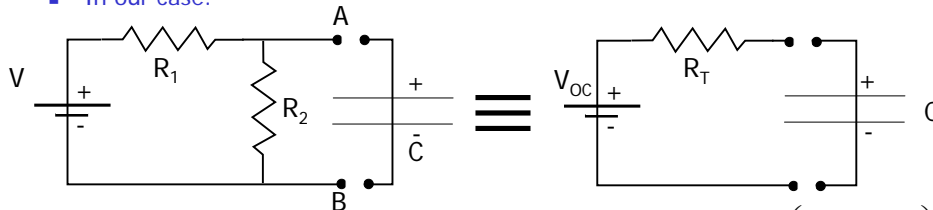

- Once the circuit is reduced, the solution is known:  $Q(t) = CV_{oc} \left( 1 - e^{-\frac{t}{R_T C}} \right)$

G. Sciolla – MIT


8.022 – Lecture 9

17

# Thevenin's demonstration
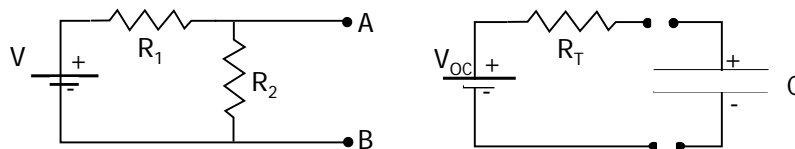
## Prove that $V_{OC}$ is the open circuit voltage

- Since  $Q(t) = CV_{oc} \left( 1 - \exp\left(-\frac{t}{R_T C}\right) \right) \rightarrow V_C(t) = V_{oc} \left( 1 - \exp\left(-\frac{t}{R_T C}\right) \right)$
- So  $V_{OC}$  is the asymptotic V for the capacitor
- Since for  $t \rightarrow \infty$ ,  $C \rightarrow$  open circuit:  $V_{OC} = V$  of the open circuit



## Prove that $R_T = V_{OC}/I_{short}$ with $I_{short}$ = current through shorted terminals

- There is only one current going through the reduced circuit
- At  $t=0$ , C behaves like a short  $\rightarrow$  At  $t=0$   $I_{short} = V_{OC}/R_T$   
 $\rightarrow R_T = V_{OC}/I_{short}$


G. Sciolla – MIT

8.022 – Lecture 9

18
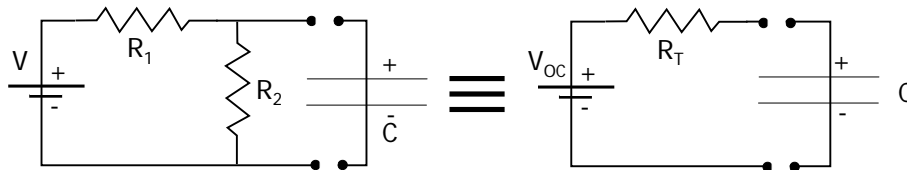
## Solve the actual problem

Calculate  $V_{OC}$  and  $R_T = V_{OC}/I_{short}$  for our problem:



$$V_{OC} = \frac{V}{R_1 + R_2} R_2$$

Shorting  $C$  makes  $R_2$  irrelevant in the circuit:  $I_{short} = \frac{V}{R_1} \Rightarrow Q(t) = C \frac{V R_2}{R_1 + R_2} \left( 1 - e^{-\frac{t(R_1 + R_2)}{C R_1 R_2}} \right)$

$$R_{Thevenin} = \frac{V_{OC}}{I_{short}} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow I(t) = \frac{V}{R_1} e^{-\frac{t(R_1 + R_2)}{C R_1 R_2}}$$

NB: This is  $R_1 // R_2$ , same resistance we would get if we shorted EMF!

G. Sciolla – MIT


8.022 – Lecture 9

19
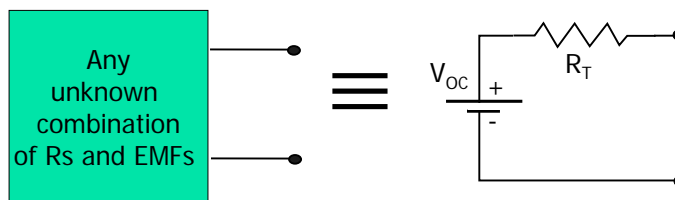
## Thoughts on Thevenin

The importance of Thevenin:

- When we have a messy system of resistors and EMFs, we can reduce it to a simple  $R + EMF$  in series just measuring  $I_{short}$  and  $V_{open}$ :



Careful:

- Thevenin works only when the elements in the box follow Ohm's law, i.e. linear relation between  $V$  and  $I$

G. Sciolla – MIT


8.022 – Lecture 9

20
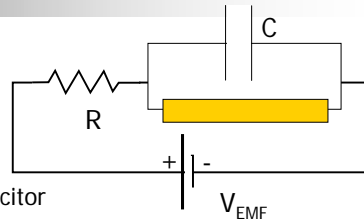
## Oscillating circuit (E13)

- RC circuit with:

- $V_{EMF} = 1 \text{ kV}$
- $C = 0.1 \text{ } \mu\text{F}$
- $R = 2.5 \text{ M}\Omega$
- Fluorescent light in parallel with capacitor  
( $R_{FL} \ll R$  when current flows;  $\sim$  infinite otherwise)




- Why is light flashing at  $\nu \sim 1 \text{ Hz}$ ?

- Initially the capacitor will start charging (no current through the lamp)
- When  $V_C >$  certain value  $\sim 1 \text{ kV} \rightarrow$  current flows through fluorescent light discharging the capacitor very quickly
- The process will start again
- $\nu \sim 1/\tau = 1/RC = 4 \text{ Hz}$
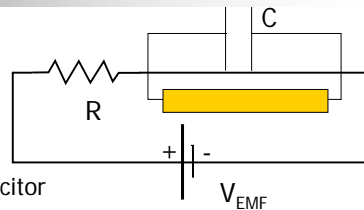
## Oscillating circuit (E13)

- RC circuit with:

- $V_{EMF} = 1 \text{ kV}$
- $C = 0.1 \text{ } \mu\text{F}$
- $R = 2.5 \text{ M}\Omega$
- Fluorescent light in parallel with capacitor  
( $R_{FL} \ll R$  when current flows;  $\sim$  infinite otherwise)




- NB: charging and discharging time constants are very different!**

- Charging:** fluorescent light is  $\sim$  open circuit:  $\tau_{\text{charge}} = RC$
- Discharge:** fluorescent light has a (very small) resistance  $R_{FL}$ 
  - Thevenin:  $R_T = R // R_{FL} \sim R_{FL}$
  - $\tau_{\text{discharge}} = R_T C \sim R_{FL} C \ll RC$
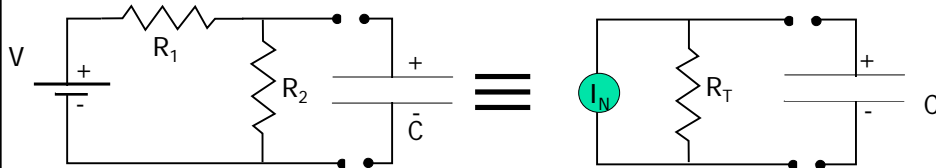
# Norton's theorem

Any combination of resistors and EMFs with 2 terminals can be replaced with a parallel of a current generator  $I_N$  and a resistor  $R_T$  where

- $R_T$  is the equivalent resistance of the circuit with all the EMF shorted and all the current sources open (same as Thevenin!)
- $I_N = V_{OC}/R_T$



$$\begin{cases} R_T = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} \\ I_N = \frac{V_{OC}}{R_T} = \frac{V R_2 / (R_1 + R_2)}{R_1 // R_2} = \frac{V}{R_1} \end{cases}$$

# Summary and Outlook

- Today:
  - RC circuits
  - Thevenin's theorem
- Next time:
  - Magnetism
- Remember: don't miss office hours
  - Bring your problems and let's find solutions together!