

8.022 (E&M) – Lecture 16

Topics:

- Inductors in circuits
 - RL circuits
 - LC circuits
 - RCL circuits


Last time

Our second lecture on electromagnetic induction

- 3 ways of creating emf using Faraday's law:
 - Change area of circuit $S(t)$
 - Change angle between B and $S \rightarrow$ AC generators
 - Change B magnitude
- Self and mutual inductance
 - Energy stored in inductor
 - Applications: transformers

Today is our 3rd lecture on inductance: inductors in circuits

RL circuits: intuitive description

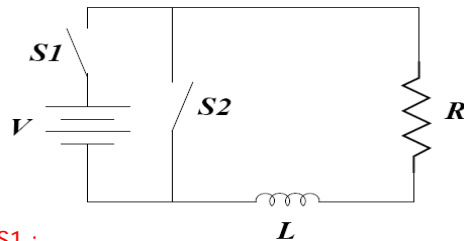


- At $t=0$, close $S1$:
 - Lenz's law opposes change in Φ_B through L
 - Since $\Phi_B(t=0) = 0$, L will impede current flow $\rightarrow I(0)=0$
 - As time passes, I will start flowing saturating at $I=V/R$
- After a long time, simultaneously open $S1$ and close $S2$:
 - Lenz's law opposes change in Φ_B through L
 - Back emf will keep current flowing for a while
 - R dissipates power \rightarrow the current will die exponentially

G. Sciolla – MIT

8.022 – Lecture 16

3

RL circuits: quantitative description

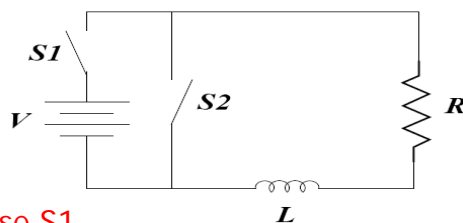

- At $t=0$: close $S1$
 - Kirchoff's rule #2: $V - IR - L \frac{dI}{dt} = 0$

$$\text{Rewrite as: } -I + \frac{V}{R} = \frac{L}{R} \frac{dI}{dt} \Rightarrow \frac{dI}{I - \frac{V}{R}} = -\frac{R}{L} dt$$

$$\Rightarrow \ln \frac{I - V/R}{-V/R} = -\frac{R}{L} t \Rightarrow I - \frac{V}{R} = -\frac{V}{R} e^{-\frac{R}{L} t} \Rightarrow \boxed{I = \frac{V}{R} (1 - e^{-\frac{R}{L} t})}$$

G. Sciolla – MIT

8.022 – Lecture 16

4

RL circuits: quantitative description(2)


- At $t=t'$: open S1 and close S2

- Kirchoff's rule #2: $-IR - L \frac{dI}{dt} = 0$


Rewrite as: $-I = \frac{L}{R} \frac{dI}{dt} \Rightarrow \int_{I=I_0}^{I=I(t)} \frac{dI}{I} = - \int_{t=0}^t \frac{R}{L} dt$

$\Rightarrow \ln \frac{I}{I_0} = -\frac{R}{L} t \Rightarrow I = \frac{V}{R} e^{-\frac{R}{L} t}$

- Graphically:

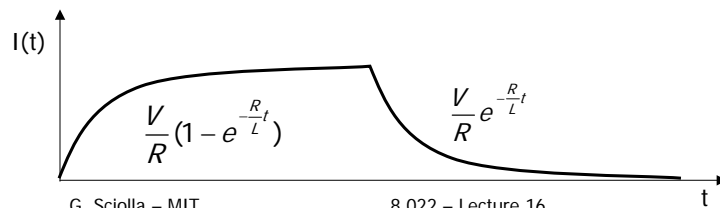


RL circuits: interpretation of results

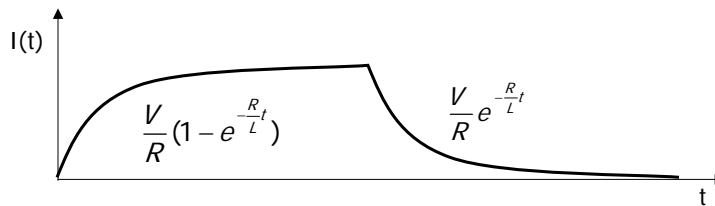

- How do we interpret these results?
 - Inductors cause currents to have an "inertia"
 - If no current flowing: L forces I to build up gradually
 - If current is flowing: L will do what it takes to make it continue (back-emf)
 - Asymptotic behavior when "charging" L
 - At $t=0$, $I=0$, as if L were an open circuit
 - At $t=\infty$, $I=V/R$, as if L did not exist
- $\left. \begin{array}{l} t=0: L \rightarrow \text{open circuit} \\ t=\infty: L \rightarrow \text{short circuit} \end{array} \right\}$

RL circuits: time constant

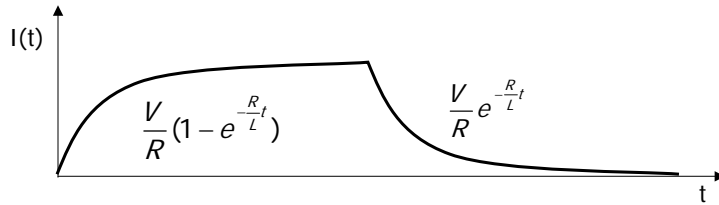

- Results of RL circuit are exponentials, as in RC circuits
 - RC circuit: time constant $\tau=RC$
 - RL circuits: time constant $\tau=L/R$
- NB: time constant is the time it takes the exponential function to decrease (increase) to $1/e$ ($1-1/e$) of its original (final) value
- Check units
 - cgs: $[L]/[R]=(\text{sec}^2/\text{cm})/(\text{sec}/\text{cm})=\text{sec}$
 - SI: $[L]/[R]=\text{H}/\Omega=(\text{V sec}/\text{A})/(\text{V}/\text{A})=\text{sec}$


G. Sciolla – MIT

8.022 – Lecture 16

7


LR time constant

- Consider the following circuit

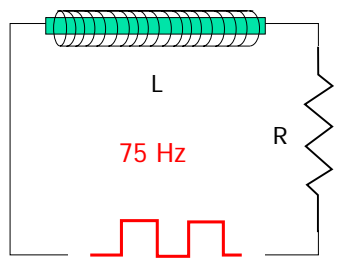

$$V_L = L \, di/dt$$

- On the oscilloscope:

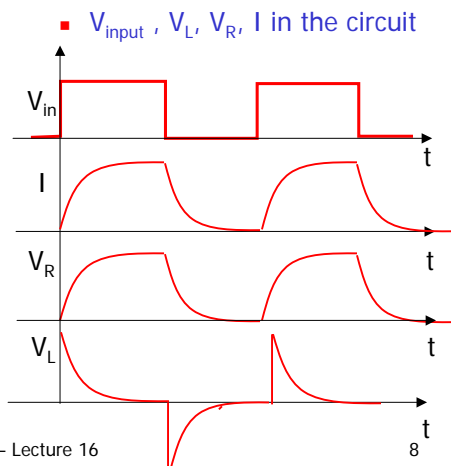


G. Sciolla – MIT

8.022 – Lecture 16

8

LC circuits

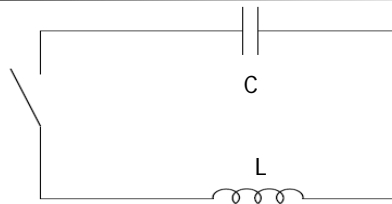

- Start with charged capacitor and close switch at $t=0$:

- Kirchoff's second rule: $\frac{Q}{C} - L \frac{dI}{dt} = 0$

Since $I = -\frac{dQ}{dt}$: $\frac{d^2Q}{dt^2} + \frac{Q}{LC} = 0$

- How to solve this? Educated guess: $Q(t) = A \cos \omega_0 t + B \sin \omega_0 t$

$$\Rightarrow \frac{d^2Q}{dt^2} = -\omega_0^2 A \cos \omega_0 t - \omega_0^2 B \sin \omega_0 t = -\omega_0^2 Q(t) \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

G. Sciolla – MIT

8.022 – Lecture 16

9

LC circuits: solution

- Plug this in the differential equation:

$$\frac{d^2Q(t)}{dt^2} = -\frac{1}{LC} Q(t) \Rightarrow -\omega_0^2 Q(t) = -\frac{1}{LC} Q(t) \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

- Determine constants A and B from initial conditions:

- $Q(t=0) = Q_0 = A \cos(0) + B \sin(0) \rightarrow A = Q_0$

- $I(t=0) = 0 = -\omega_0 A \sin(0) + \omega_0 B \cos(0) \rightarrow B = 0$

- Complete solution:

$$Q(t) = Q_0 \cos \omega_0 t \Rightarrow V_c(t) = \frac{Q(t)}{C} = \frac{Q_0}{C} \cos \omega_0 t$$

$$I(t) = -\frac{dQ}{dt} = \frac{Q_0}{\sqrt{LC}} \sin \omega_0 t$$

- NB: current and voltages are off by 90 degrees


G. Sciolla – MIT

8.022 – Lecture 16

10

LC circuits: solution

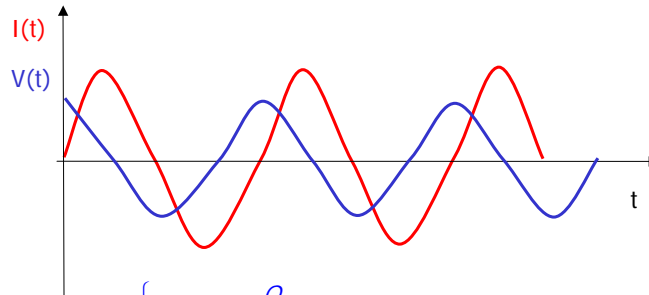Graphical representation of the solution:



$$\begin{cases} V_c(t) = \frac{Q_0}{C} \cos \omega_0 t \\ I(t) = \frac{Q_0}{\sqrt{LC}} \sin \omega_0 t \end{cases}$$

NB: Q and I have a phase of 90 deg

Energy conservation

- Energy stored in the capacitor over time:

$$U_c(t) = \frac{Q^2(t)}{2C} = \frac{Q_0^2(t)}{2C} \cos^2 \omega_0 t$$

- Energy stored in the inductor:

$$U_L(t) = \frac{1}{2} L I(t)^2 = \frac{1}{2} L \frac{Q_0^2}{LC} \sin^2 \omega_0 t = \frac{Q_0^2}{2C} \sin^2 \omega_0 t$$

- Total energy:


$$U(t) = U_L(t) + U_c(t) = \frac{Q_0^2}{2C} (\sin^2 \omega_0 t + \cos^2 \omega_0 t) = \frac{Q_0^2}{2C}$$

- What is happening over time?

- Energy swings back and forth between C and L but at any moment in time the total energy is equal to the energy initially stored in the capacitor:
Energy is conserved!

RCL circuits

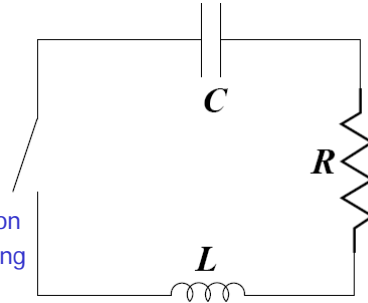- LC circuits don't belong to this world:
 - R is never exactly 0!
- So let's concentrate on RCLs
 - Start with a charged C
- Intuitively:
 - LC → oscillatory part: sin and cos solution
 - R → dissipative part: exponential damping
- Rigorous solution:



Use Kirchoff: $\frac{Q}{C} - IR - L \frac{dI}{dt} = 0$

Since $I(t) = -\frac{dQ}{dt} \Rightarrow \frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$

G. Sciolla – MIT

8.022 – Lecture 16

13

RCL circuits: solution

- How to solve this equation? $\frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$
- Educated guess!
 - Intuition tells us that the solution must have an oscillatory term and a damping term
 - Strategy #1: exponential * sin/cos functions:

$$Q(t) = e^{-t/\tau} (A \cos \omega_0 t + B \sin \omega_0 t)$$
 Very heavy on algebra!!!
 - Strategy #2: complex exponentials
 - Idea: the solution is the real part of a complex solution

$$\tilde{Q}(t) = A e^{i\phi_0} e^{i\alpha t} \Rightarrow Q(t) = \text{Re}[\tilde{Q}(t)]$$
 Much easier algebra!!!
 - NB: a can be complex!

G. Sciolla – MIT


8.022 – Lecture 16

14

Complex number notation

- Complex number: number with both a real and an imaginary part
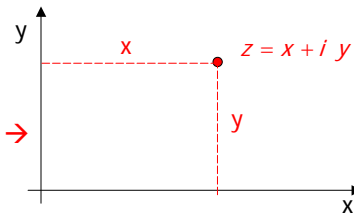
$$z = x + i y \quad \text{with } i = \sqrt{-1}$$



- Complex plane representation $z = (x, y) \rightarrow$

- Another useful representation

Set magnitude $r = \sqrt{x^2 + y^2}$ and phase $\theta = \arctg \frac{y}{x} \Rightarrow z = r(\cos \theta + i \sin \theta)$

- Given Euler's relation: $e^{i\theta} = \cos \theta + i \sin \theta$

- Prove it using Maclaurin expansion (see handout)

$$\Rightarrow z = r e^{i\theta} \quad (\text{Phasor representation})$$

RCL circuits: solution (cont)

Plug expected solution $\tilde{Q}(t) = e^{i\phi_0} e^{i\alpha t}$ into the differential equation

$$\frac{d^2 \tilde{Q}}{dt^2} + \frac{R}{L} \frac{d\tilde{Q}}{dt} + \frac{1}{LC} \tilde{Q} = 0$$

$$\frac{d\tilde{Q}}{dt} = i\alpha \tilde{Q}; \quad \frac{d^2 \tilde{Q}}{dt^2} = -\alpha^2 \tilde{Q} \Rightarrow \tilde{Q} \left(-\alpha^2 + i\alpha \frac{R}{L} + \frac{1}{LC} \right) = 0$$

Simple quadratic equation: $-\alpha^2 + i\alpha \frac{R}{L} + \frac{1}{LC} = 0 \Rightarrow \alpha = i \frac{R}{2L} \pm \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$

This gives us 2 complex solutions for $\tilde{Q}(t)$:

$$\begin{cases} \tilde{Q}_+(t) = A e^{i\phi_0} e^{\frac{R}{2L}t} e^{i\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t} \\ \tilde{Q}_-(t) = A e^{i\phi_0} e^{\frac{R}{2L}t} e^{-i\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t} \end{cases}$$

\Rightarrow real part: $Q(t) = A e^{\frac{R}{2L}t} \cos(\pm \omega t + \phi_0)$ with $\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$

The weak damping limit

Weak damping limit: small $R \rightarrow$ the damping is small \rightarrow several oscillations occur before amplitude start decreasing in sizable way

$$I(t) = -\frac{dQ}{dt} = Q_0 e^{-\frac{R}{2L}t} \left[\omega \sin(\omega t + \phi_0) + \frac{R}{2L} \cos(\omega t + \phi_0) \right]$$

When $\omega \gg R/(2L)$ (damping limit), the second term can be ignored and

$$I(t) \sim A e^{-\frac{R}{2L}t} \omega \sin(\omega t) \text{ with } \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \sim \frac{1}{\sqrt{LC}} = \omega_0$$


$$\Rightarrow \text{final solution for "weak damping": } \begin{cases} Q(t) \sim Q_0 e^{-\frac{R}{2L}t} \cos(\omega_0 t + \phi_0) \\ I(t) \sim \omega_0 Q_0 e^{-\frac{R}{2L}t} \sin(\omega_0 t + \phi_0) \\ \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$$

RCL in weak damping limit

- Initial conditions: $Q(0) = Q_0 = A \cos(\phi_0)$ and $I(0) = 0 = A \omega_0 \sin \phi_0 \Rightarrow A = Q_0; \phi_0 = 0$

$$\Rightarrow \begin{cases} Q(t) \sim Q_0 e^{-\frac{R}{2L}t} \cos(\omega_0 t) \\ I(t) \sim \omega_0 Q_0 e^{-\frac{R}{2L}t} \sin(\omega_0 t) \end{cases}$$

- Graphical representation of solution:

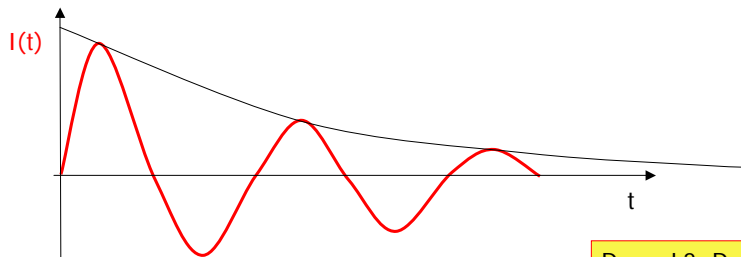

Summary and outlook

- Today:

What happens when we put L in circuits?

- RL circuits: exponential solutions



- LC circuits: oscillatory solution



- RCL circuits: damped oscillation



- Next Tuesday:

- Quiz # 2: good luck!!!