

*Massachusetts Institute of Technology*

*Spring Term 2005*

**8.02X Electricity and Magnetism**

**Practice Quiz #2b**

**Problem 1 (30 points)**



In lecture, you saw a demo with a parallel plate capacitor with capacitance  $C_0$ . The capacitor was connected to an ideal power supply with an output voltage  $\Delta V$  and charged to a charge  $Q$ . The capacitor was disconnected from the power supply, still carrying the same charge  $Q$ . Then the distance between the plates was increased by a factor of 2.

- (a) How big is the potential difference between the capacitor plates after they have been moved apart?
  
- (b) How big is the stored electrical energy in the capacitor after the plates have been moved apart?
  
- (c) Explain how energy was conserved when moving the plates apart (1 sentence).
  
- (d) Suppose we had not disconnected the power supply before moving the plates apart. How big would the stored energy be after the plates have been moved apart in this case?

**Problem 2 (20 points)**

Shown below is the cross-section of a parallel plate capacitor with distance  $2d$  between the plates. The capacitor is given a charge  $Q$  using a power supply and then disconnected from the power supply. Then a dielectric with thickness  $d$  and dielectric constant  $K=2$  is inserted between the plates.

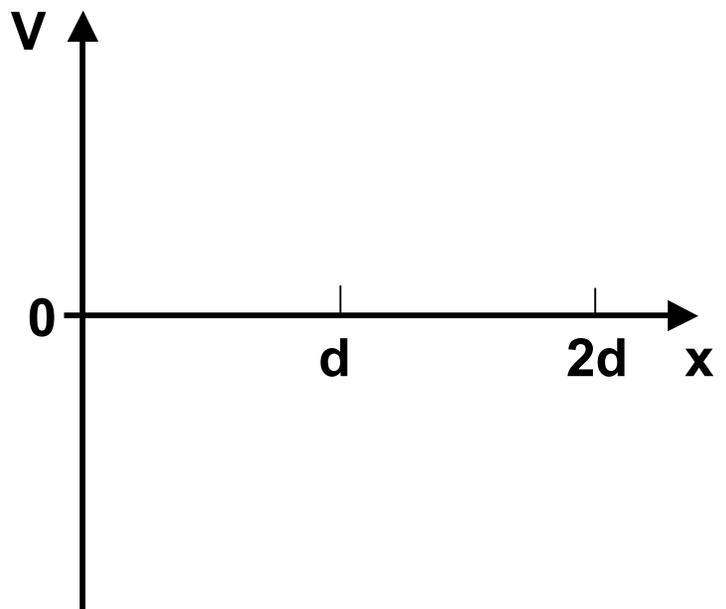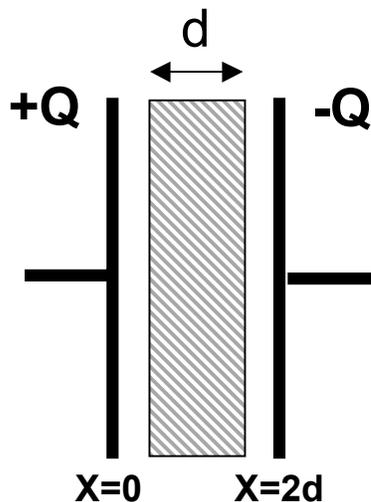
- (a) Does the stored energy increase, decrease or stay the same when the dielectric is inserted?
- (b) On the graph below, draw a qualitative sketch of the electric potential between the capacitor plates as a function of  $x$  between  $x=0$  and  $x=2d$ . At which value of  $x$  did you choose to set  $V=0$ ?


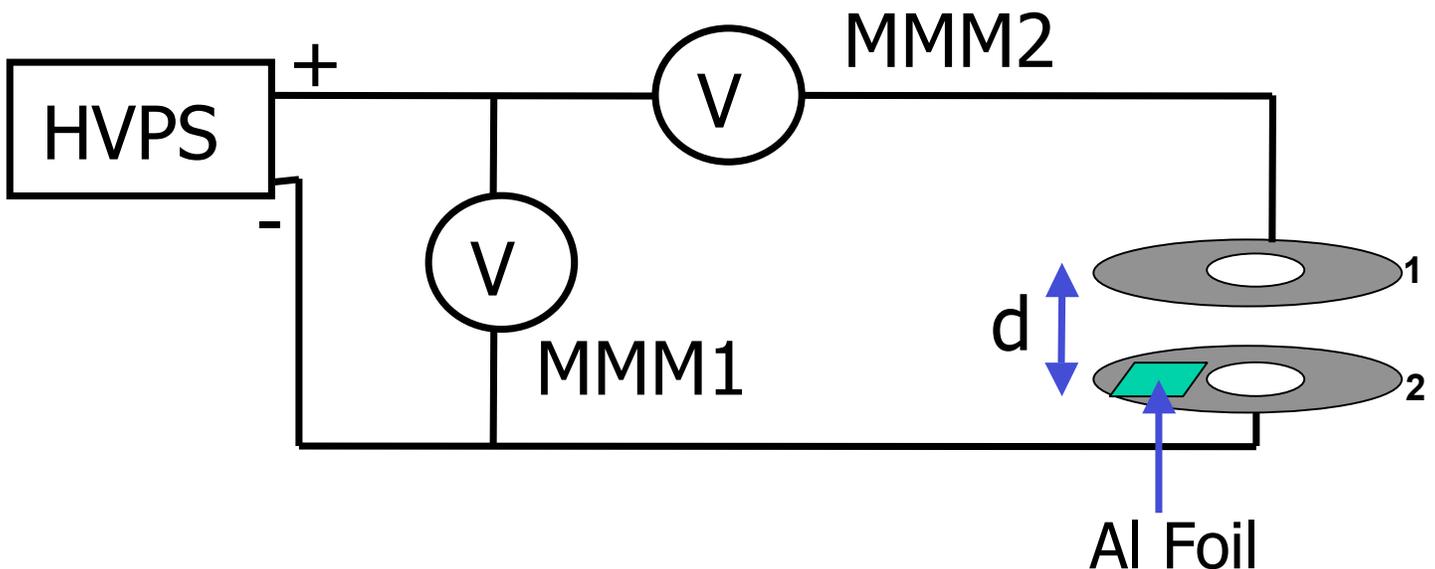
### Problem 3 (30 points)

Shown below is the schematic setup of the EF experiment, including the HVPS and the two multimeters. The multimeters have a resistance of  $20\text{M}\Omega$ . Suppose MMM1 measures  $400\text{V}$  just before the foil jumps. We define the negative terminal of the HVPS to be at a potential of  $0\text{V}$ .

- What is the potential of washer 1 before the foil jumps and connects the two washers?
- What is the reading of MMM2 before the foil jumps?
- After the foil jumps, the reading of MMM1 drops to  $380\text{V}$ . What is the potential of washer 1 now?
- What is the reading of MMM2, after the foil has jumped?
- Explain why the reading of MMM1 dropped after the foil jumped.
- Assume the experiment was repeated with the distance between the washers doubled to  $2*d$ . At which reading of MMM1 would the foil jump in this case? Explain your answer.





**Problem 4 (20 points)**

**Shown below is a simple circuit consisting of a pair of light bulbs, connected in series to an ideal power supply providing a constant 'voltage'  $\Delta V = 12V$ .**

- (a) Assume bulb 1 is rated as a 36W bulb at 12V, i.e. it will consume 36W of electrical power if connected to a 12V power supply. What is its resistance?**
- (b) Assume bulbs 1 and 2 are identical. In the circuit below, which one would burn brighter or would they show the same brightness?**
- (c) Assume bulb 1 is rated as a 36W bulb and bulb 2 as a 72W bulb. Which one would burn brighter (i.e. consume more power) in the circuit below, or would they both show the same brightness? Explain your answer.**

